

**PHOTOSTAT AND BOOK CENTER ADDRESS**

NEAR MADE EASY F-21A, LADO SARAI, NEW DELHI-30

(PHOTOSTAT, BOOK CENTER)

F-53 BER SARAI, NEW DELHI-110016 (PHOTOSTAT)

SHOP NO. 5/123-A, SADULAZAB MARKET, IGNOU ROAD,  
SAKET, NEW DELHI-30 (PHOTOSTAT, BOOK CENTER)

**PHONE NO.**

**ANUPAM SHUKLA**

**9311989030, 8130782342**

**9560163471**

**9654353111, 8595382884**

# **HIND PHOTOSTAT AND HIND BOOK CENTER**

NAME:-.....

SUBJECT:-.....

INSTITUTE:-.....

**NETWORK THEORY**

**PLEASE CONTACT FOR:-**

- PHOTOSTAT (LASER DIGITAL)
- PRINT OUT FROM COMPUTER
- SPIRAL BINDING, HARD BINDING
- TEST PAPER FOR PSU, GATE, IES
- ALL NOTES AVAILABLE
- ALL BOOK AVAILABLE

Network Theory :-

1. Basics
2. Steady state A.C circuits (Resonance)
3. Theorems
4. Transients
5. Two-port
6. Magnetic coupled circuits and Graph theory
7. Filters
8. Synthesis → IES

Books :-

→ Fundamentals of electric circuits

By Alexander Sadiku

→ Engg. Circuit analysis

By Hayt and Kemmerly

→ Networks and systems

By B. Roy Choudhury

→ Network Analysis

By Van Valkenburg

PHOTOSTAT  
All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contd.

PHOTOSTAT  
All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contd.

-PHOTOSTAT-

## Lecture - I


HIND PHOTOSTAT  
F-21-A, LADOSARAI, NEW DELHI-30  
8130782342

### Charge :-

- The basic quantity in the electric circuit is charge
- The charge on the electron is given ( $-1.6 \times 10^{-19} C$ )
- The flow of e's is called as current

OR

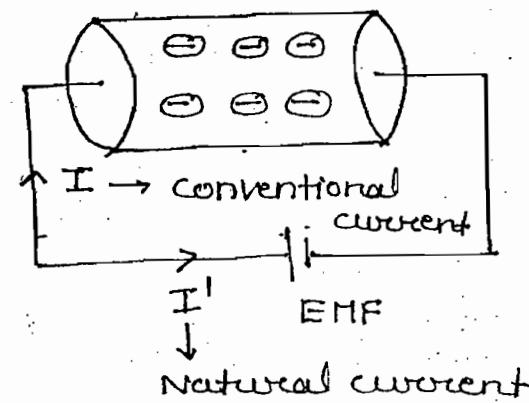The time rate of charge is also called as current.



$$I = \frac{dq}{dt}$$

C/S or A

- By using conventional current direction KVL and KCL equations are developed
- To move the e from one point to other point in particular direction external force is required. In electric ckt external force is provided by EMF and it is given by

$$V = \frac{dw}{dq}$$

J/C or Volts

- The time rate of energy is called as power

$$P = \frac{dw}{dt}$$



J/S or Watts

$$P = \frac{dw}{dt} \cdot \frac{dq}{dt}$$


$$P = V \cdot I$$

HIND PHOTOSTAT  
F-21-A, LADOSARAI, NEW DELHI-30  
8130782342

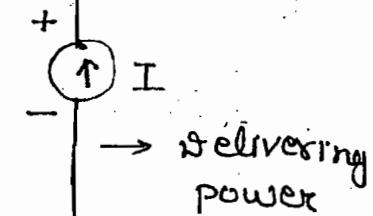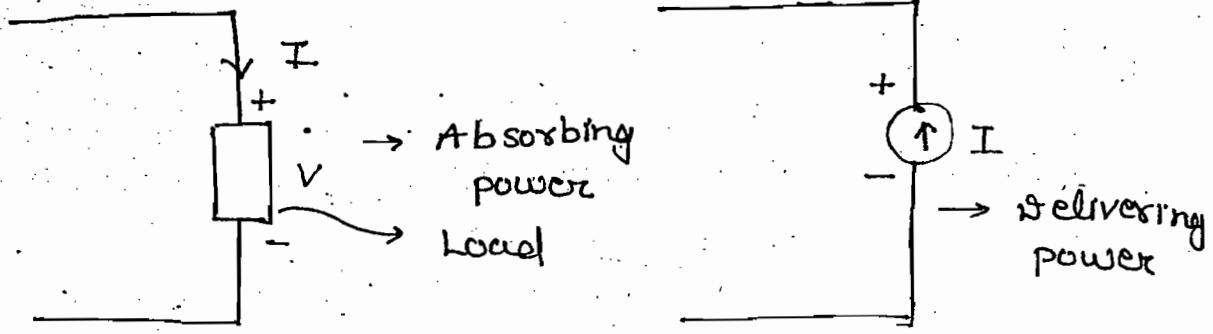HIND PHOTOSTAT  
(All Study Material Available)  
Lado Sarai, New Delhi  
Cont: 9716132273



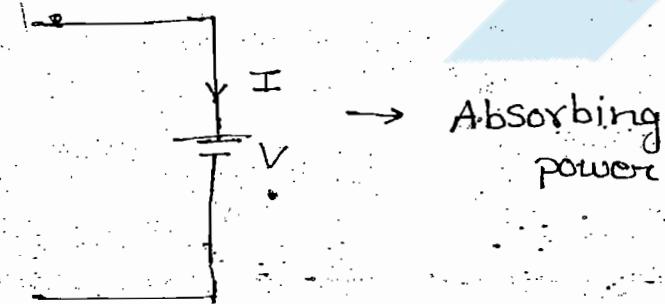
**PHOTOSTAT**  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont: 9, 12342578


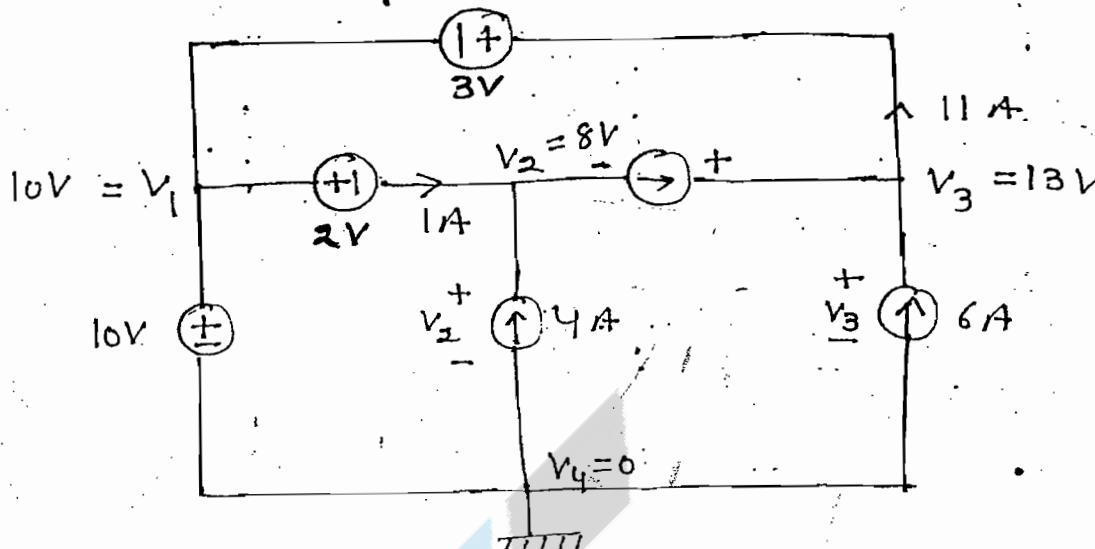
### Note:-

- When current is entering into the terminal element, it's absorbing power
- When current is leaving from the terminal element, it's delivering power

Cues! :- Find power of each element of the circuit shown



$$\text{Soln: } - V_1 - V_2 = 2 \Rightarrow V_2 = 8V$$

$$V_3 - V_1 = 3 \Rightarrow V_3 = 13V$$

$$P_4 = 4 \times 8 = 32W \text{ (Delivering Power)}$$

$$P_6 = 13 \times 6 = 78W \text{ ( " " )}$$

$$P_5 = 5 \times 5 = 25W \text{ ( " " )}$$

$$P_{10} = 10 \times 10 = 100W \text{ ( Absorbing Power )}$$

$$P_3 = 3 \times 11 = 33W \text{ ( " " )}$$

$$P_2 = 1 \times 2 = 2W \text{ ( " " )}$$


$$(P_T)_{\text{Absorbing}} = (P_T)_{\text{Delivering}}$$

$$\Rightarrow 135W = 185W$$

PHOTOSTAT  
(All Study Material Available  
Lado Sarai, New Delhi  
Call: 9810000000)

HIND PHOTOSTAT  
F-21-A, LADOSARAI, NEW DELHI-30  
8130782342

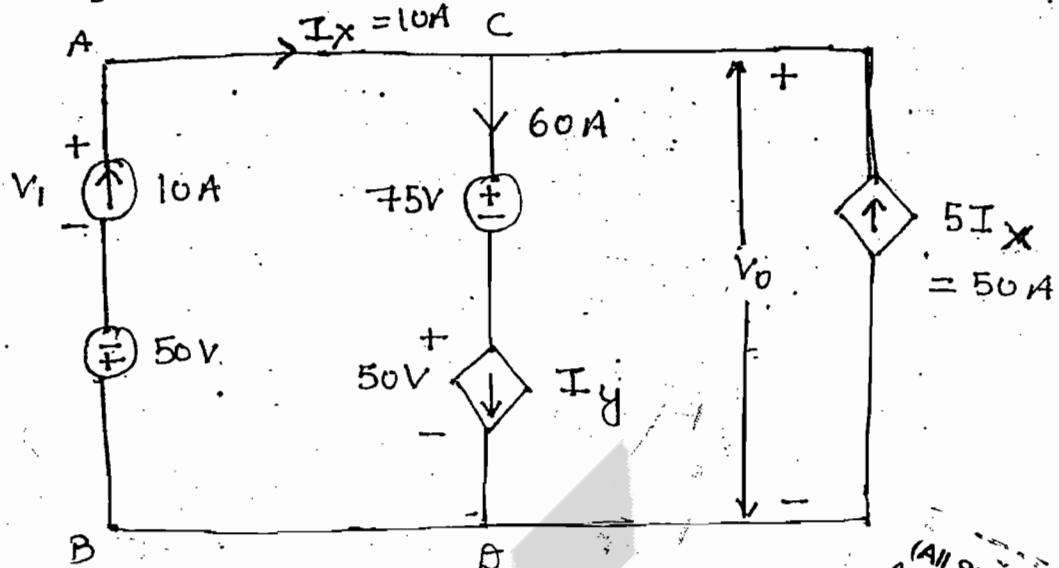ques!:- Find power developed in a ckt when  $V_o = 125 V$



PHOTOSTAT  
(All Study Material Available  
Lado Sarai, New Delhi  
Contd.)

$$\text{Soln: } V_{AB} = V_i - 50$$

$$\Rightarrow 125 = V_i - 50 \Rightarrow V_i = 175$$

$$P_{5I_x} = 125 \times 50 = 6250 \text{ W}$$

$$P_{10} = 175 \times 10 = 1750 \text{ W}$$

$$P_T = 6250 + 1750 = 8000 \text{ W}$$

### Classification of elements :-

- (1) Active and Passive
- (ii) Linear and Non-linear
- (iii) Uni-direction and Bi-direction
- (iv) Time variant and invariant
- (v) Lumped and Distributed

### Active & Passive Element!:-


#### Active Element!:-

When the element is capable of delivering energy for long time (approximately  $\propto$  time)  $\rightarrow$  A.E

OR When the element is having property of internal amplification then the element is called as active element
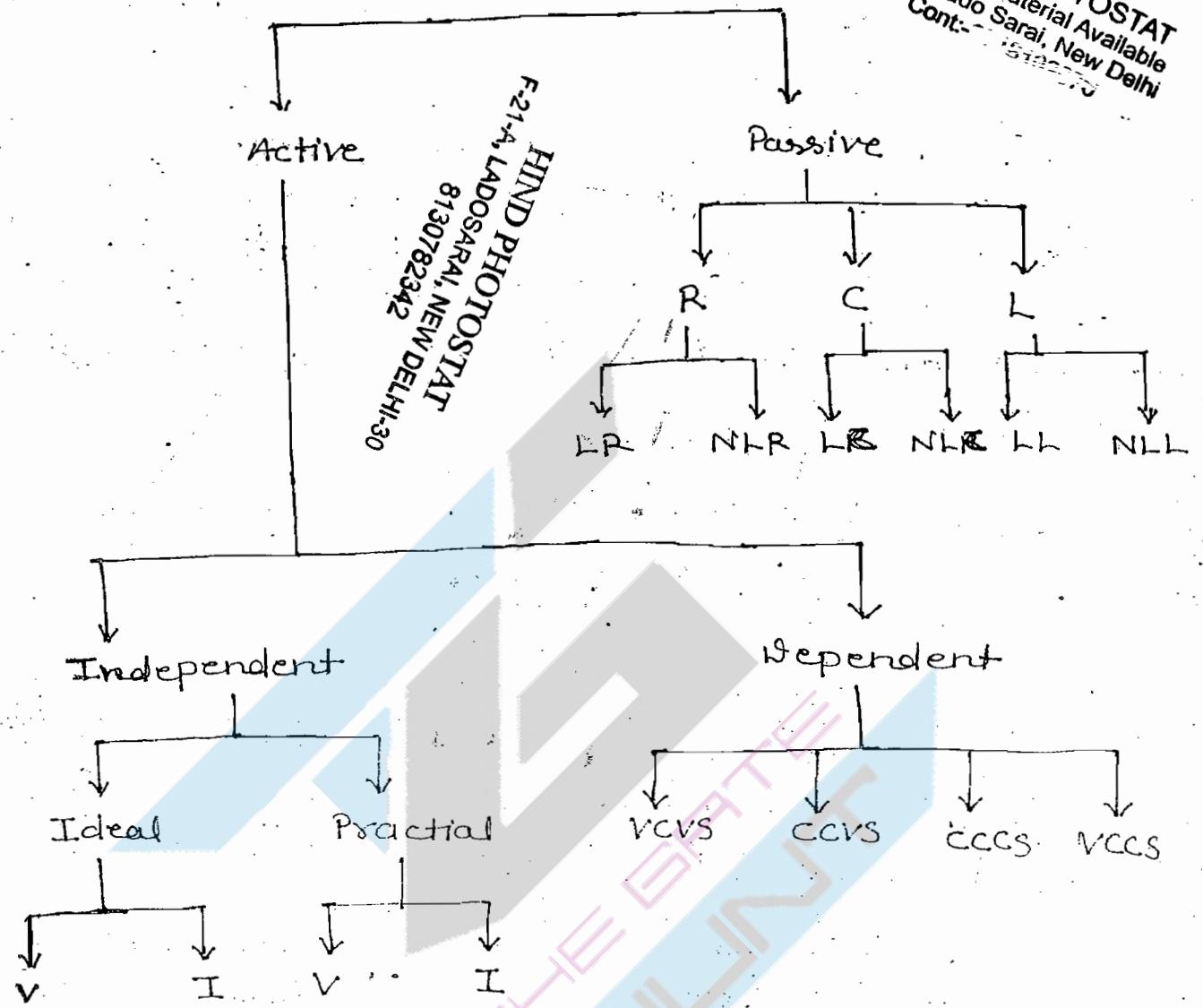
## Elements

PHOTOSTAT  
 (All Study Material Available  
 Lado Sarai, New Delhi  
 Cont. -)



Voltage source, current source → Independent

Transient, op-amp → Dependent

→ Swinging discharging capacitor (inductor) can deliver energy independently for a short time and capacitor (inductor) is not having property of internal amplification

### Passive Elements:-


When the element is not capable of delivering energy independently then the element is called as passive element.

eg:- Resistor, bulb, transformer

↓  
It can't step-up or  
down power

Resistor :-

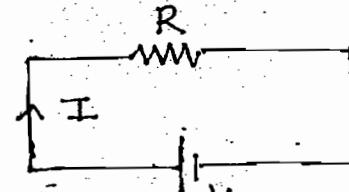- Resistance is a property of resistor.. It always opposes the current. By doing so it converts electric energy to heat & energy
- Resistance is nothing but a friction to flow of e's




$$P = I^2 R$$

$$W = I^2 R t$$

↓  
Heat

$$R = \rho \frac{l}{a} \quad \Omega$$

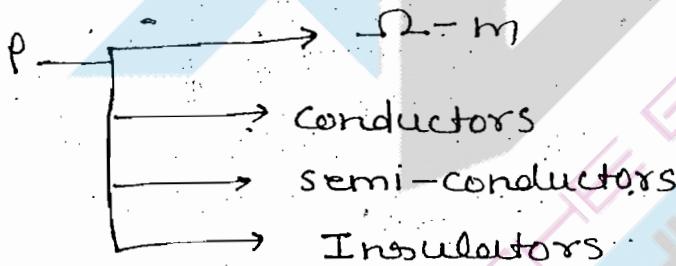

PHOTOSTAT  
(All Study Material Available  
A-1 Lado Sarai, New Delhi  
Co.)

Super conductor

$$\rho = 0.$$

eg:- Mercury  
at 4.15 K

$$R_t = R_0 (1 + \alpha_0 t)$$


where

$R_0$  = Resistance at  $0^\circ C$

$t$  = Change in temp.
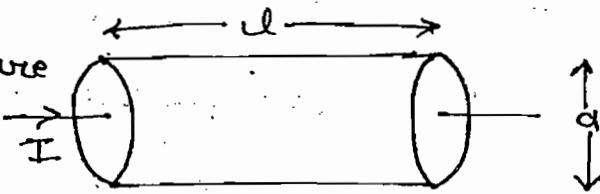
## Ohm's Law:-

→ At constant temperature current density is directly proportional to electric field intensity



→ At constant temp. potential diff. across the element is directly proportional to current flowing into element.

$$J = \frac{I}{a} \text{ A/m}^2$$

$$\underline{E} = \frac{V}{l} \text{ Volts/m}$$

$$\rho = \frac{l}{A} \text{ mho/m}$$

$$R = \rho \frac{l}{a}$$

$$J \propto E$$

$$\Rightarrow J = \rho E$$

$$\Rightarrow \frac{E}{a} = \frac{1}{\rho l} V$$


$$\Rightarrow \boxed{\frac{V}{l} = \frac{\rho l}{a} = R}$$

$$V \propto I$$

$$V = RI$$

$$\boxed{R = \frac{V}{I} = \text{constant}}$$

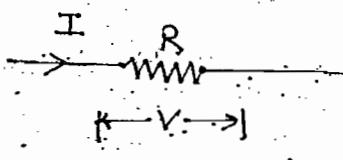HIND PHOTOSTAT  
F-21-A, LADOSARAI, NEW DELHI-30  
8130782342



HIND PHOTOSTAT  
(All Study Material Available  
At Lado Sarai, New Delhi  
Contd.)

## Different forms of Ohm's law:-

$$J = \sigma E \quad \text{--- (I)}$$


$$V = RI \quad \text{--- (II)}$$

$$I = GV \quad \text{--- (III)}$$

$$G = \frac{1}{R} \quad \text{mh6}$$

$$V = R \frac{d\phi}{dt} \quad \text{--- (IV)}$$

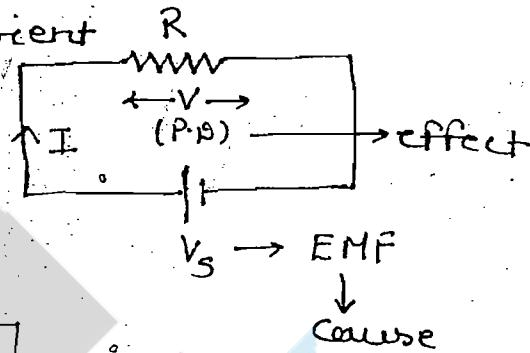→ EMF is independent on current and resistance magnitude



→ Potential difference depends on current and resistance magnitude


$$I \propto V_s$$

↓  
EMF

$$V \propto I$$

↓  
P.D / Voltage drop

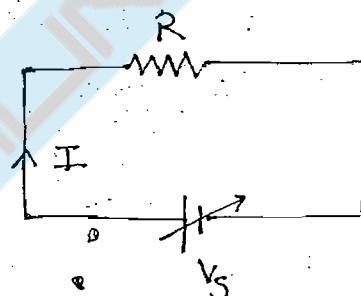→ When element properties and characteristics independent on the direction of current then the element is called as bidirectional element (bilateral)






→ When element obeys ohm's law then the element is called as linear resistor  
→ Every linear element should obey the bidirectional properties but not vice-versa

$$I \uparrow 10\%, V \uparrow 10\%$$

$$I \uparrow 90\%, V \uparrow 10\%$$

$$R = \frac{V}{I} = \text{constant}$$

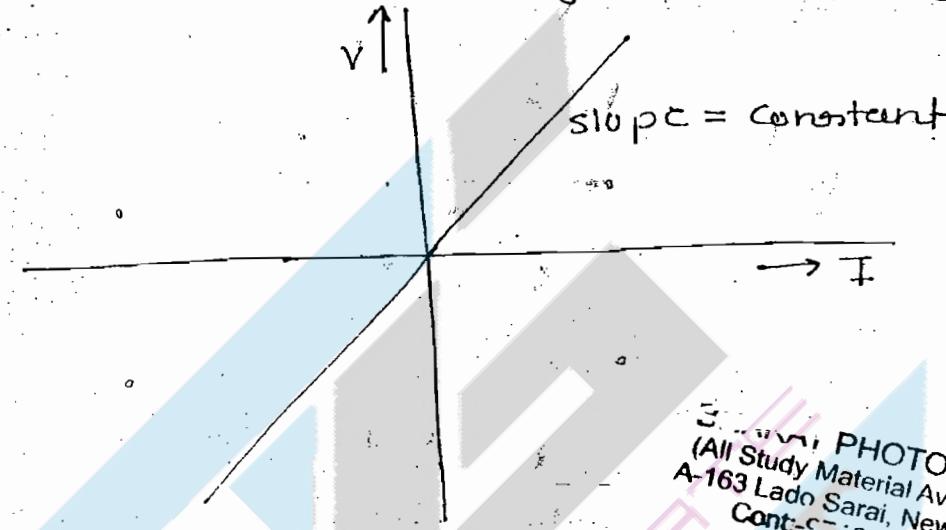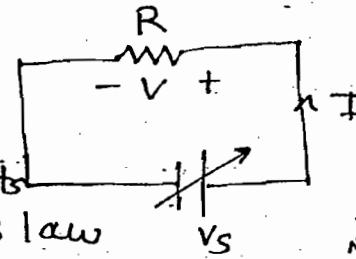
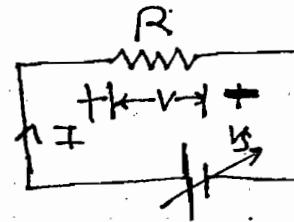
$\frac{V}{I} = \text{constant}$  then elements obey ohm's law



F-21-A, LABOSARAI, NEW DELHI-30  
HIND PHOTOSTAT  
8130782342

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9810000000

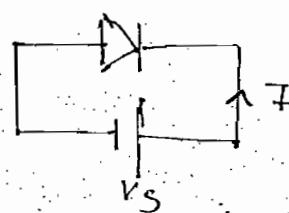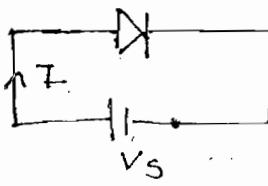- When element properties and characteristics depends on the direction of current then element is called as unidirectional element
- When element does not obey the ohm's law then the element is called as non-linear resistor




$$|I| \neq |I'|$$

Note:-




$$\frac{V}{I} = +ve$$

then element is passive

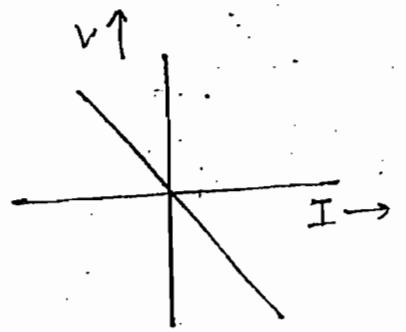


- Linear
- Bi-directional
- Active

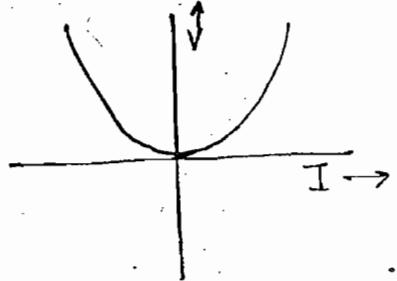


- Non-linear
- Uni-directional
- Active

Note :-

- If in any of the quadrant  $\frac{V}{I} = +ve$  then the element is active
- Every linear element should obey the bidirectional property but not vice-versa
- If  $\frac{V}{I} = +ve$  in both coordinates then the element is passive. → (I)
- In the above
- If  $\frac{V}{I} = -ve$  either in any of the coordinates or both the coordinates then the element is active → (II)
- In the above two cases waveform should pass through origin

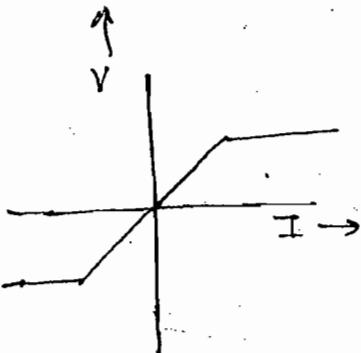


- Non-Linear
- Bi-directional
- Passive

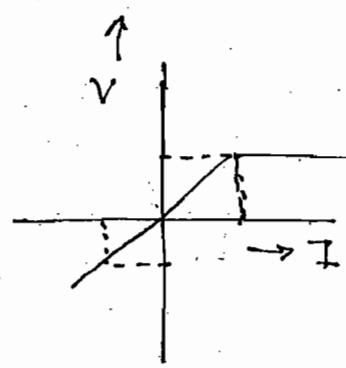

- Non-linear
- Unidirectional
- Passive

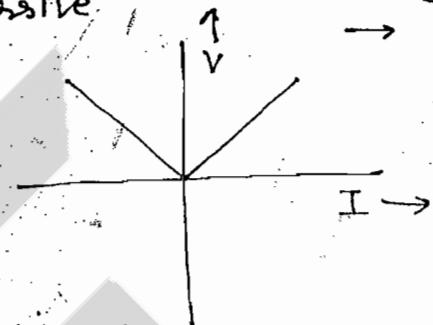
E-I T PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9



- Non-linear
- Uni-directional
- Active

→ When the element obeys the bi-directional property characteristic should be identical in the opposite coordinates but not in the adjacent coordinates

### Inductor (L) :-

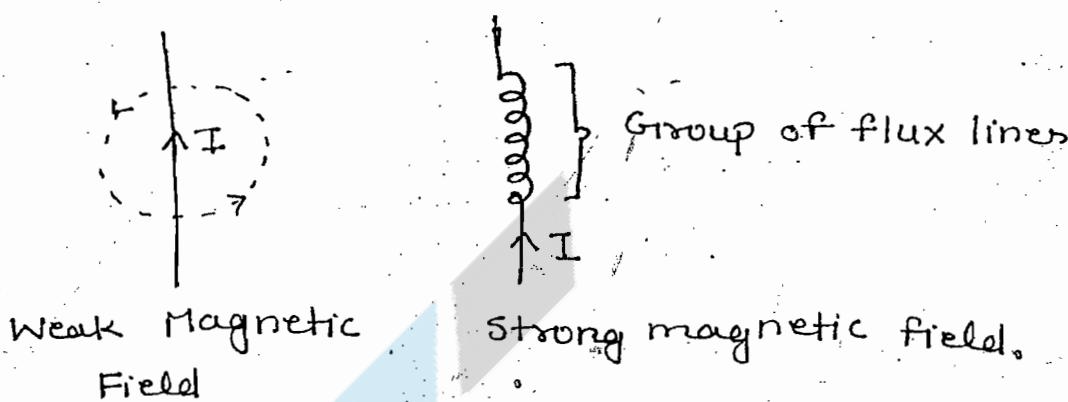

PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Cont: 9719122310

HIND PHOTOSTAT  
F-214A, LADOSARAI, NEW DELHI-30  
8130782342

### Faraday's Laws :-

#### 1st law:-

When conductor cuts a magnetic lines of force an emf induced in the conductor

#### Second law:-

An emf induced in the conductor is directly proportional to rate of change of flux

$$e = Bld \sin \phi, e \propto \frac{d\phi}{dt}$$

where


$B$  = flux density

$l$  = length of conductor




$v$  = velocity of conductor

$\phi$  = Phase displacement b/w conductor & magnetic field

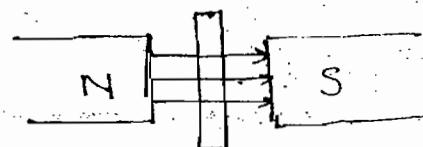$e$  = dynamically induced emf (eg:- generator)



## Inductor (L) :-

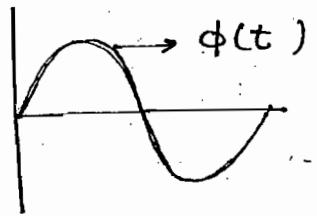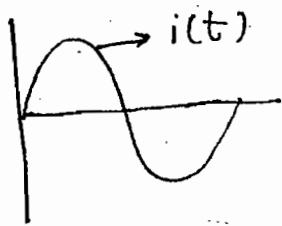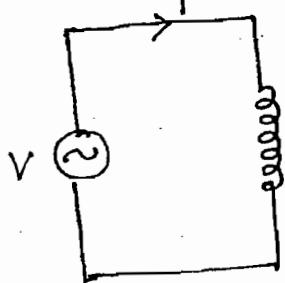

L  
PHOTOSTAT  
(All Study Material Available  
At Lado Sarai, New Delhi  
Contd...)

$$e \propto \frac{d\phi}{dt}$$

$$\Rightarrow e = -N \frac{d\phi}{dt} \rightarrow \text{Lenz's Law}$$

$$\rightarrow V, i, \phi, e \Rightarrow V = N \frac{d\phi}{dt}$$

Lenz's Law

$$\rightarrow \Psi = N\phi$$

(Flux linkage)

$$V = \frac{d\Psi}{dt}$$

$$\Psi \propto \phi$$

$$\Psi \propto i$$

$$\Psi \propto I$$

$$\boxed{\Psi = LI}$$

$$\boxed{V = L \frac{di}{dt}}$$

$$\Rightarrow L = \frac{V}{\frac{di}{dt}}$$

$$\Psi = N\phi$$

$$\Psi = Li$$


$$\boxed{L = \frac{N\phi}{i}}$$

Henry

$$L = \frac{N\phi}{i} = \text{constant}$$


$$i \uparrow 10\%, \phi \uparrow 10\%$$

$$i \uparrow 90\%, \phi \uparrow 90\%$$

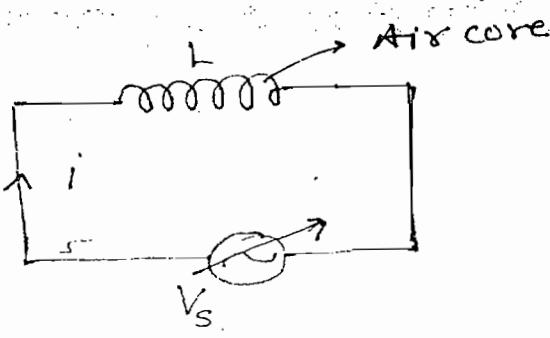



$$V = L \frac{di}{dt}$$
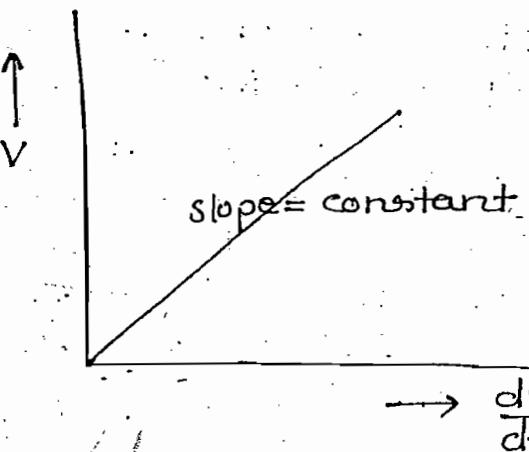
$$\Rightarrow L = \frac{V}{\frac{di}{dt}}$$



HIND PHOTOSTAT  
(All Study Material Available)  
A-103 Lado Sarai, New Delhi  
Cont-0718102076

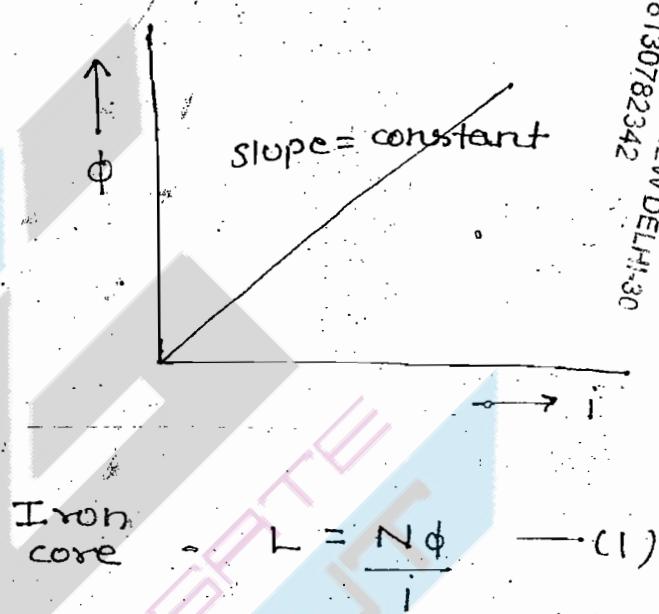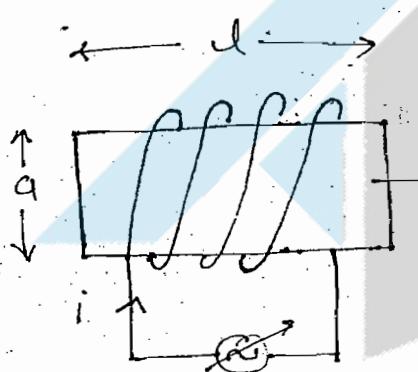
HIND PHOTOSTAT  
F-21-A, LADOSARAI,  
NEW DELHI-110042  
8130782342




If  $i \uparrow 10\%$ ,  $\phi \uparrow 10\%$

If  $i \uparrow 60\%$ ,  $\phi \uparrow 60\%$

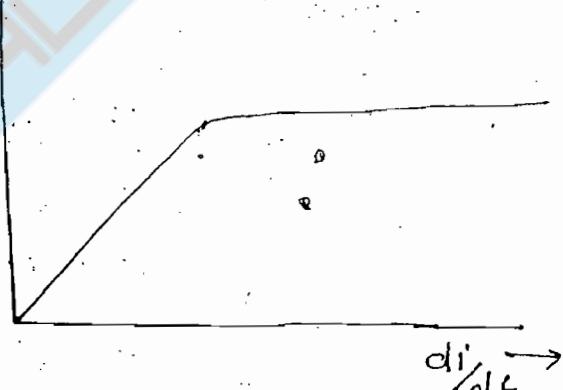If  $i \uparrow 90\%$ ,  $\boxed{\phi = \text{constant}}$   
(saturation)



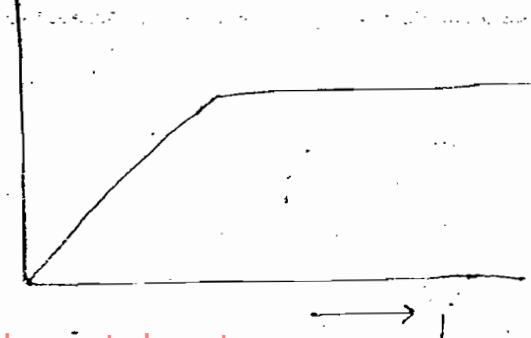→ The flux linked with iron-core is upto a certain limit.



→ When inductance of a inductor is independent on the current magnitude then inductor is called as linear inductor  
 eg:- Air core inductor

→ When inductance of a inductor depends on current magnitude then inductor is called as non-linear inductor

eg:- iron core inductor

Electric circuit


$$1. i = \frac{EMF}{R}$$

$$2. i = \frac{EMF}{\mu_0 \frac{l}{a}}$$

Magnetic circuit

$$\phi = \frac{MMF}{S(\text{Reluctance})}$$
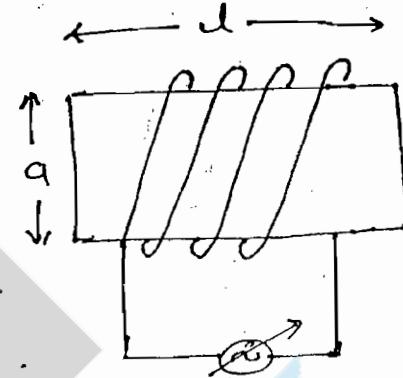
$$\phi = \frac{NI}{\frac{l}{\mu_0 M_r}} \quad \rightarrow (\text{II})$$



Substitute eq-(II) in eq-(I)

$$* L = \frac{N^2 \mu_0 M_r a}{l}$$

PHOTOSTAT  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont.-9

where,  $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$

$M_r$  = Relative permeability

$a$  = Area of cross-section of core

$$L = \frac{N^2}{\frac{l}{\mu_0 M_r}} \Rightarrow L = \frac{N^2}{S}$$

$$L = \frac{N^2}{S}$$

$$\rightarrow V = L \frac{di}{dt}$$

$\Rightarrow$

$$i = \frac{1}{L} \int_{-\infty}^t V dt$$

→ The above formula is only applicable for linear inductor.

$$P = Vi$$

$$P = L \frac{di}{dt} i$$

→ Instantaneous Power

$$W = \int P dt$$

$$\Rightarrow W = \int L \frac{di}{dt} i \cdot dt = \frac{1}{2} L i^2$$

→ Power dissipation in ideal inductor is zero since internal resistance is zero.

→ Inductor stores energy in the form of magnetic field (K.E.)

→ Due to energy storage property inductor is also called as dynamic element

### Conclusion :-

Under steady state condition, for a dc source inductor  $V_s$  behave as a short circuit

$$V = L \frac{di}{dt}$$

For dc,  $\frac{di}{dt} = 0$




$$V = 0$$

↓  
S.C.



L

$$\frac{di}{dt} = 0$$

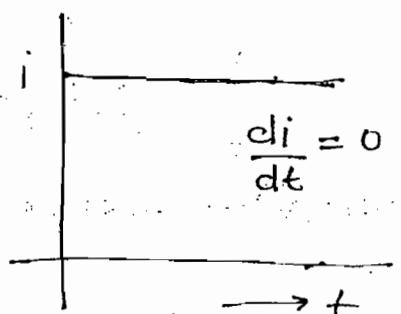

HIND PHOTOSTAT  
F-21, A, LADOSARAI, NEW DELHI-110030  
6130782342

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont:- 9891111111

2 Inductor does not allow sudden change of current since

(a) For sudden change of current infinite voltage is required but practically it is not possible

(b) Practical inductive circuit having finite value of time constant i.e.  $\tau = \frac{L}{R}$

$$V = L \frac{di}{dt}$$

$$dt \rightarrow 0 \Rightarrow V = \infty$$



3  $r = 0$

Ideal

Practical

$$r \approx m\Omega$$

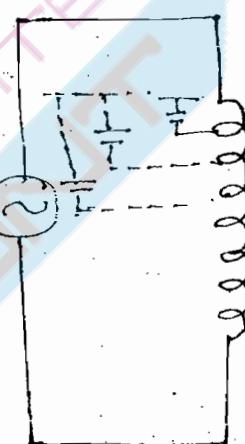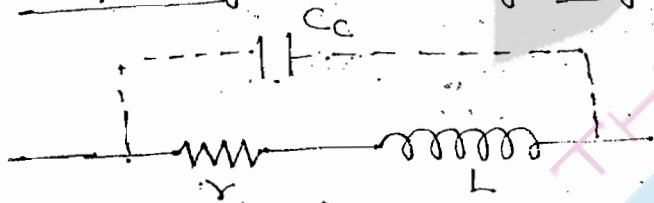Inter-turn capacitance is present when inductor is operated at either at very high frequency or very high voltage




where  $c_c$  = inter-turn capacitance

or Transmission

• self capacitance

$$X_L = 2\pi f L$$

$$X_C = \frac{1}{2\pi f C}$$

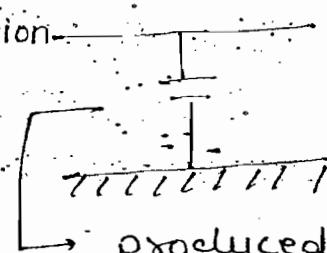

→ produced due to high potential diff.


## Capacitor:-

$$\theta \propto V$$

$$\Rightarrow \theta = CV$$

$$\Rightarrow C = \frac{\theta}{V}$$

$C/V$  or F

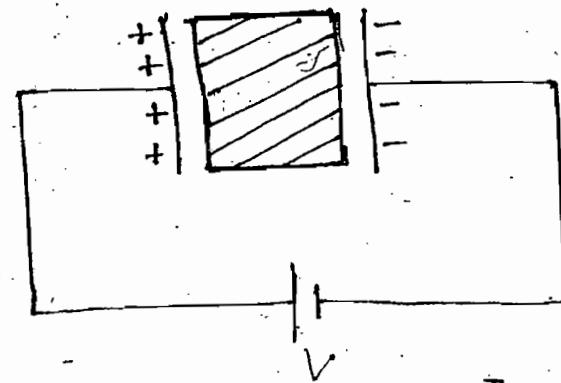

$$\text{Again } \theta = CV$$

$$\Rightarrow \frac{d\theta}{dt} = C \frac{dV}{dt}$$

$$\Rightarrow i = C \frac{dV}{dt}$$

$$\Rightarrow C = \frac{i}{\frac{dV}{dt}}$$

→ Capacitor opposes rate of change of voltage

$$i = C \frac{dV}{dt}$$

→ Ohm's law  
7th form

$$V = \frac{1}{C} \int_{-\infty}^t i dt$$

→ Ohm's law  
8th form

$$P = VI$$

$$\Rightarrow P = VC \frac{dV}{dt}$$

→ Instantaneous power

$$W = \int P dt$$


$$W = \int V C \frac{dV}{dt} dt$$

$$\Rightarrow W = \frac{1}{2} CV^2$$

→ Potential Energy

HIND PHOTOSTAT  
F-21-A, LADOSARAI, NEW DELHI-30  
A-163 Lado Sarai, New Delhi  
Cont.-9, 22333333  
All Study Material Available  
8130782342


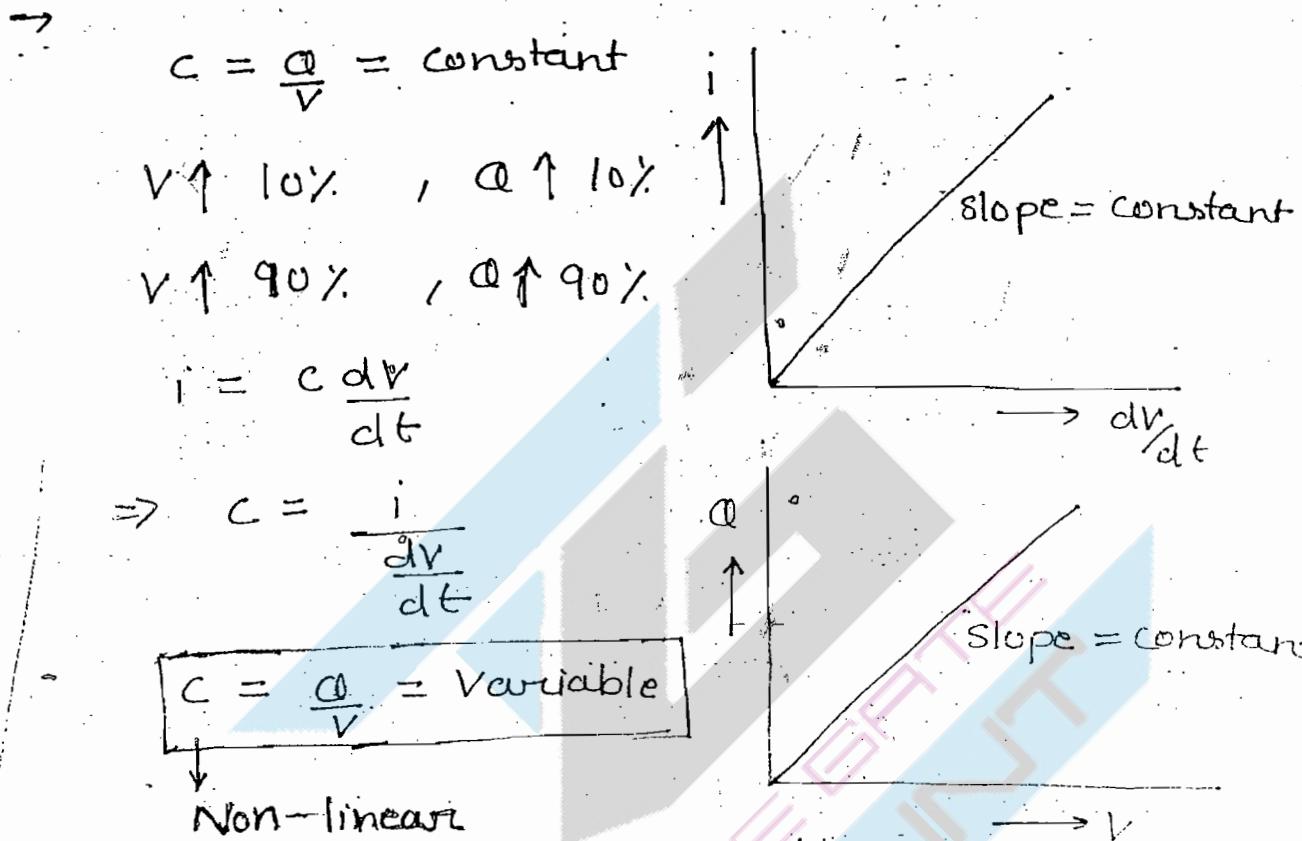
- Power dissipation in ideal capacitor = 0.
- Capacitor stores energy in the form of electric field (Potential Energy).
- Due to energy storage property capacitor is also called as dynamic element.



- When capacitance of a capacitor is independent on the voltage magnitude then the capacitor is called as linear capacitor.
- When capacitance of a capacitor depends on the voltage magnitude then capacitor is called as non-linear capacitor.  
eg:- Varactor diode
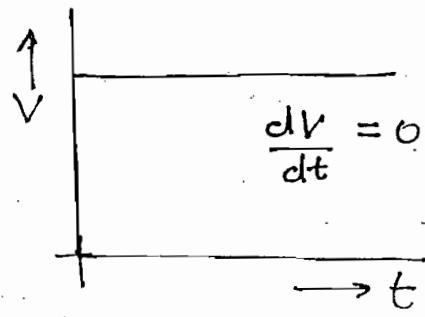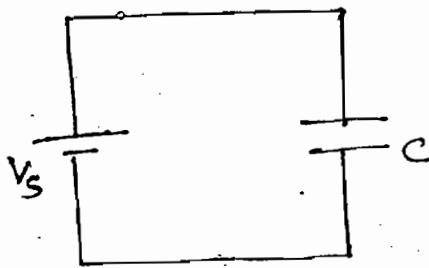
### Conclusion:-

- Under steady state condition for a dc source capacitor behaves as an open circuit



$$i = C \frac{dV}{dt}$$

$$\frac{dV}{dt} = 0 \rightarrow i = 0 \Rightarrow 0 \cdot C$$

E-21-A, HIND PHOTOSTAT  
 8130762342, LADO SARAI, NEW DELHI-30

2. Capacitor does not allow sudden change of voltages. Since

(a) For sudden change of voltages, infinite current is required but practically it is not possible

(b) Practical capacitive circuit has finite value of time constant

$$(a) i = C \frac{dV}{dt} = \infty \quad dt \rightarrow 0$$


$$(b) T = RC$$

3. For ideal capacitor :-

$$\boxed{R_1 = 0 \\ R_2 = \infty}$$




(Ideal)

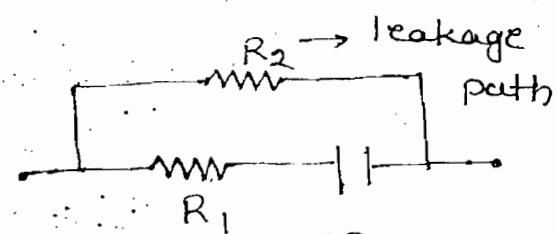


Dielectric loss (Power loss) (Practical)
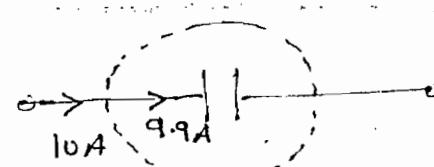
$$\boxed{R_1 \approx \text{Very less} \\ R_2 \approx \text{Very High}}$$



$R_2$  = leakage path


### Ideal Voltage Source

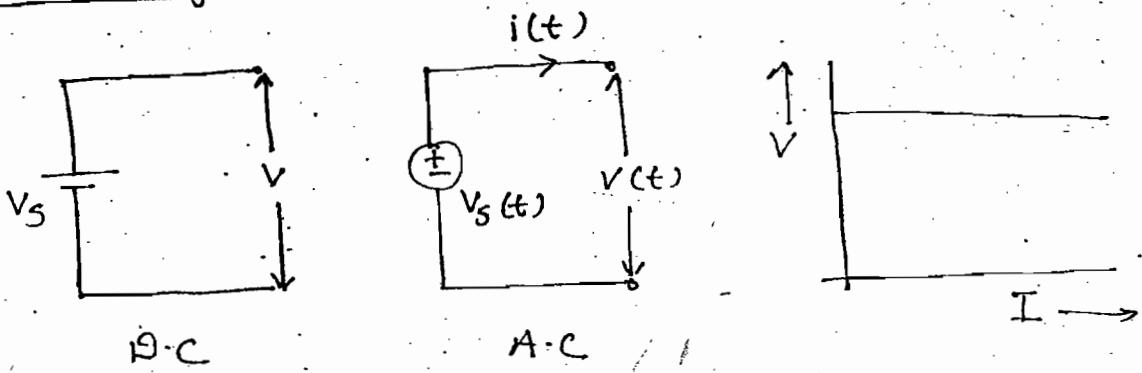

$$\rightarrow R_s = 0$$

$\rightarrow V_s(t) \rightarrow$  either AC or DC if  $t \rightarrow$  specify  
then AC

### Practical Voltage Source

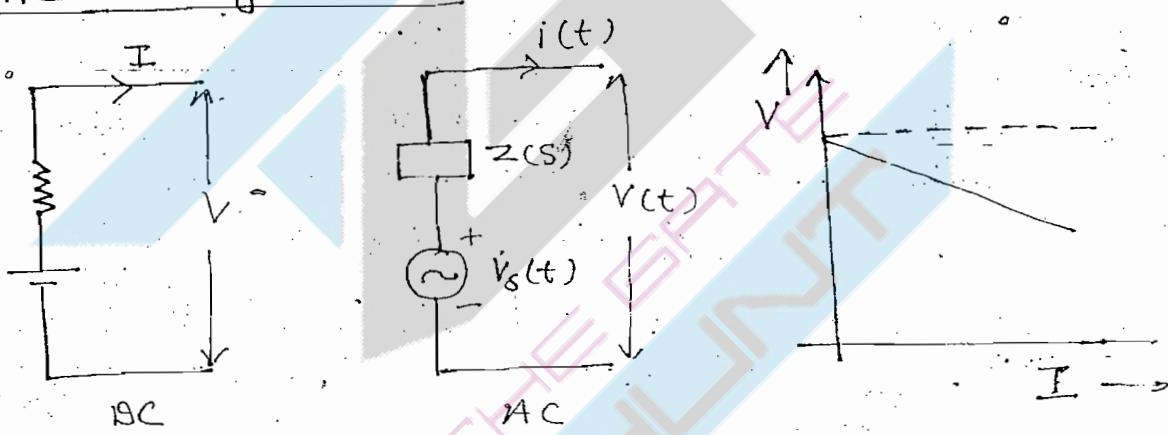

$$V_s = V + I R_s$$







$$V = V_s - I R_s$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont-97181 0





- Ideal voltage source delivers energy at specified voltage ( $V$ ) it is independent on current delivered by the source
- Internal resistance of ideal voltage source is zero
- Practical voltage source delivers energy at specified voltage ( $V$ ) which depends on current delivered by the source.

- Linear, → characteristic passes through origin and inc. linearly
- Independent voltage source does not obey the Ohm's law. Since V-I characteristic is non-linear.

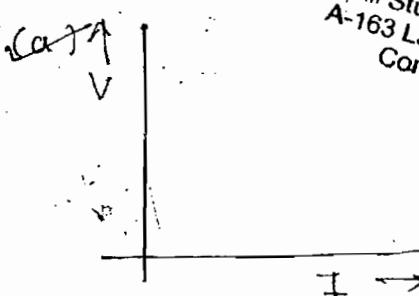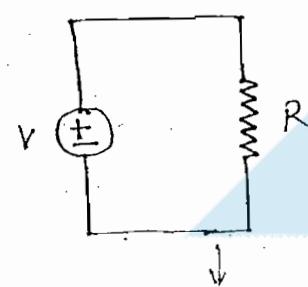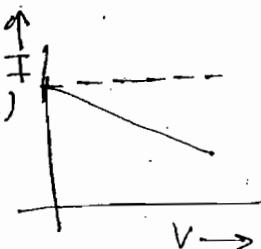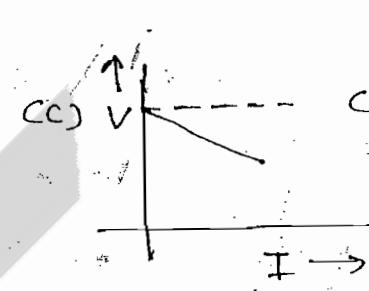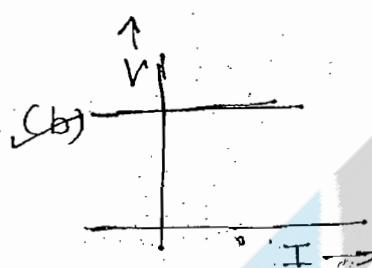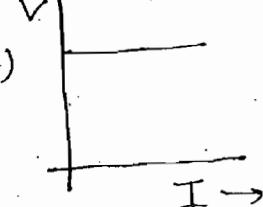Ques:- Identify V-I characteristic of ideal voltage source




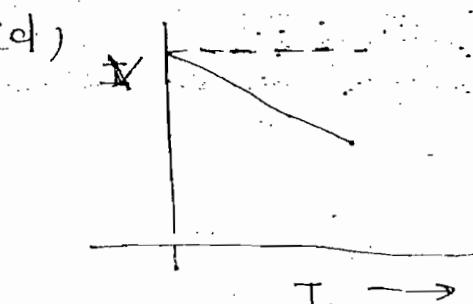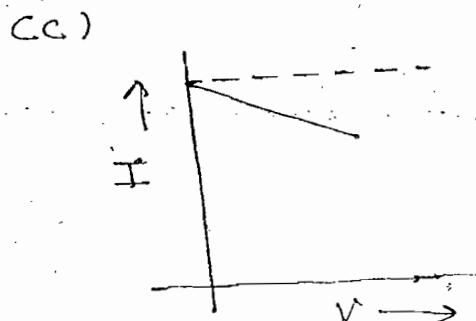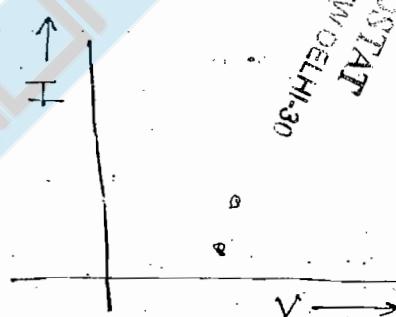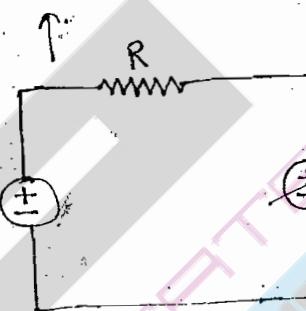**PHOTOSTAT**  
(All Study Material Available  
A-163 Lado Sarai, New Delhi)  
Cont: 9711222070




Note :-


(I)

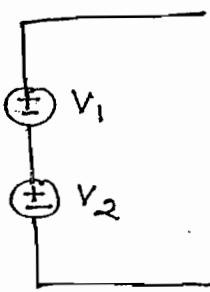



?

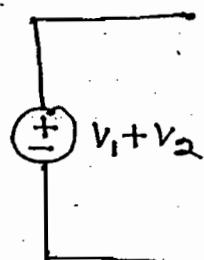

(II)

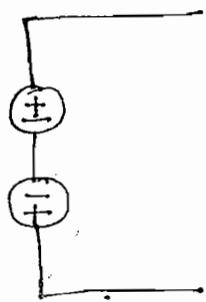


?

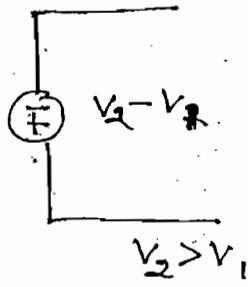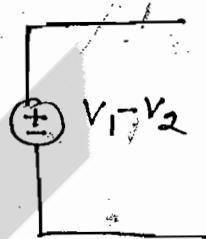


$$V_2 > V_1$$


(III)

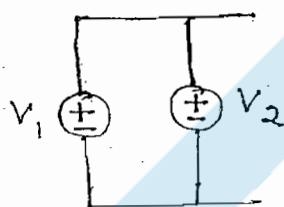


?

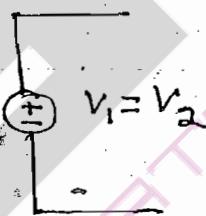


(IV)

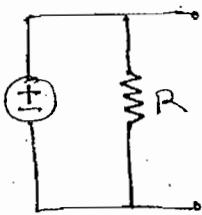


?

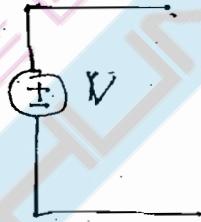

(V)

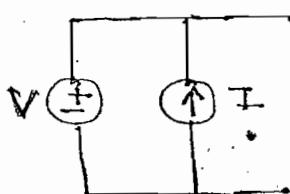

?

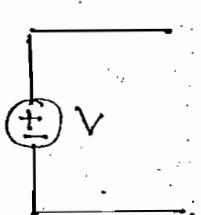


PHOTOSTAT  
Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. No. 9899000000


Ques:- Find current in the  $2\Omega$  resistor

(a) 5A (b) 10A

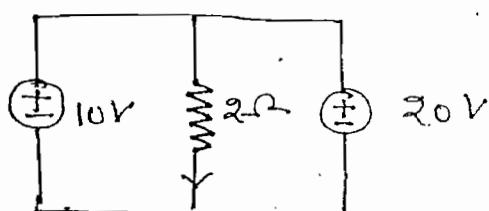(c) 15A (d) None or  
Not satisfying  
KVL




Note:-

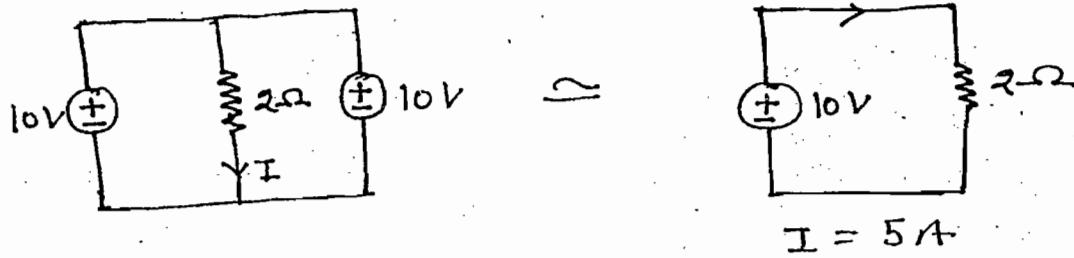


By using superposition theorem

Case - I

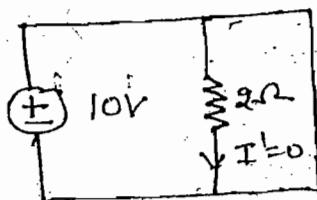


Case - II

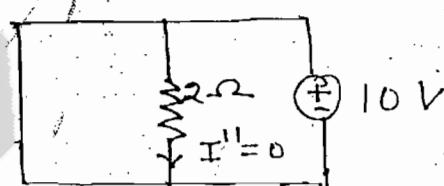

$$I = I' + I'' = 0$$

→ For the above circuit superposition theorem can't be applied since case-(I) & case-(II) circuits are not satisfying KVL.

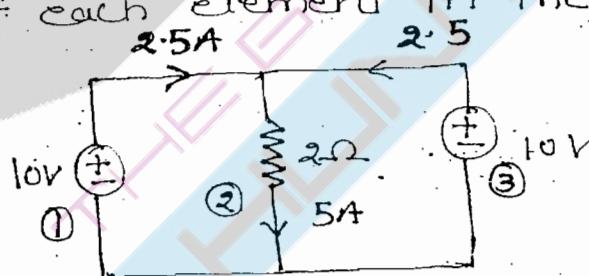Ques:- Find power of each element in the circuit given below.



Soln:-

$$P_1 = 10 \times 2.5 = 25W \text{ (Delivering)}$$

$$P_3 = 10 \times 2.5 = 25W \text{ (Del.)}$$


$$P_2 = I^2 R = 5^2 \times 2 = 50W \text{ (Absorbing)}$$

Note:-

$$I_S = 10 + 2 = 12A$$


$$P_S = 20 \times 12 = 240W$$

20V

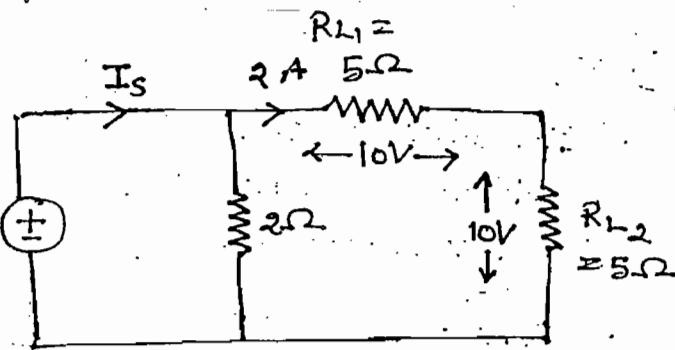

$$I_S' = 2A$$

$$P_S' = 20 \times 2 = 40W$$

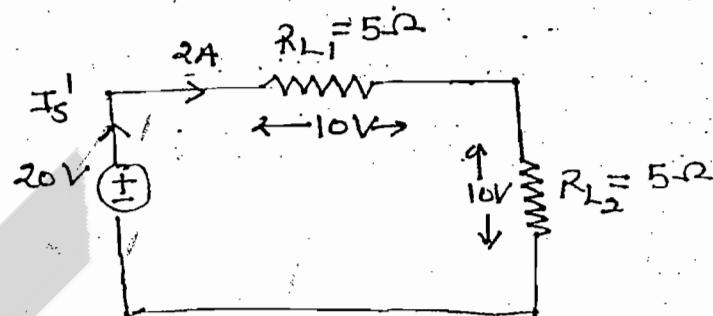


- In the above circuit  $2\Omega$  resistance can be neglected while calculating either load current or load voltages
- In the above circuit  $2\Omega$  resistance can't be neglected while calculating either source current or source power

$$I_S + 0.5 = 2$$


$$\Rightarrow I_S = 1.5A$$

$$P_S = 20 \times 1.5 \\ = 30W$$

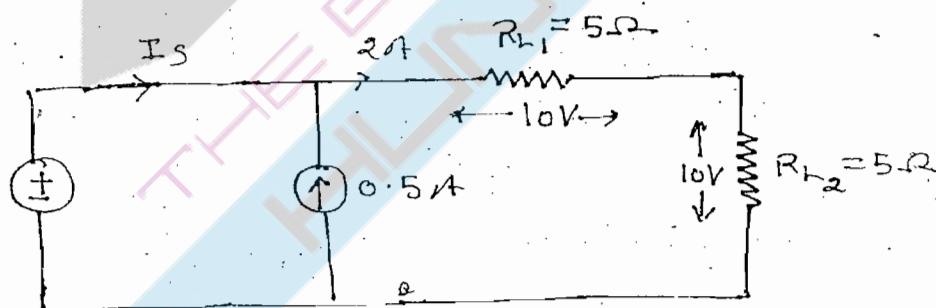

$$I_S' = 2A$$

$$P_S' = 20 \times 2 \\ = 40W$$

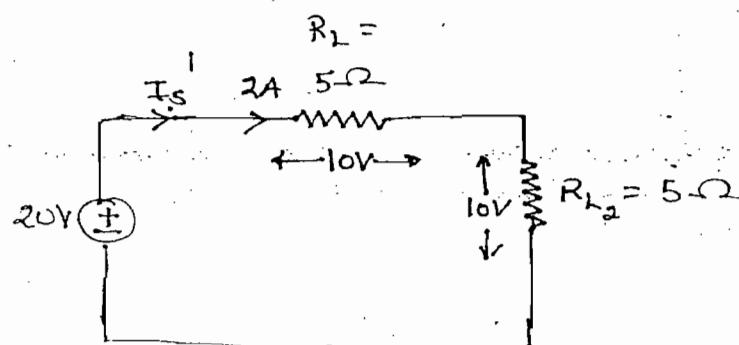


Note:-


- In the above circuit current source can be neglected while calculating either load current or load voltage.
- In the above circuit current source can't be neglected while calculating either voltage source current or voltage source power.

RIBBON PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9499020711

Current (I) :-

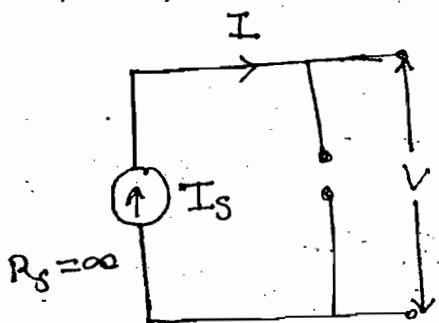


Ideal DC  
current source

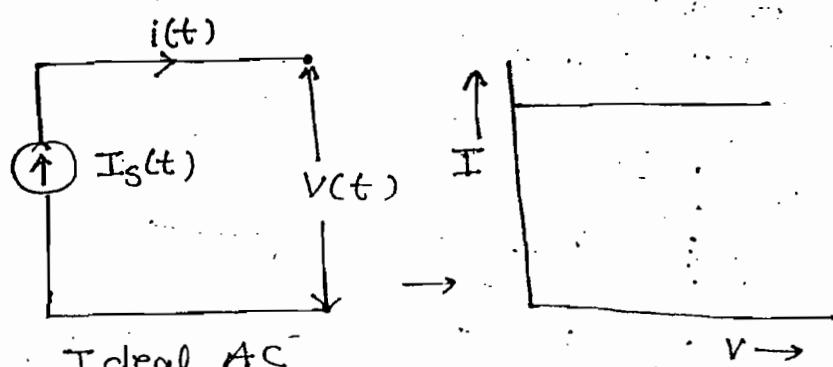

Ideal AC  
current source

Practical current source:-

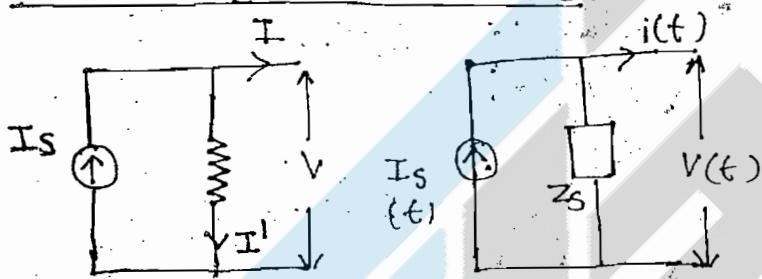


$$I_S = I + I'$$

$$I = I_S - I'$$









$$I = I_S - \frac{V}{R_S}$$

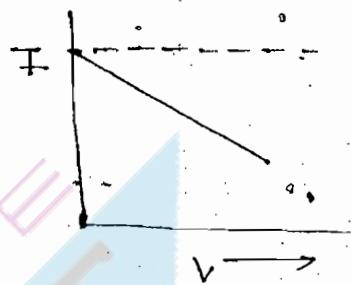SHARAT PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contact: 9718102070





- Ideal current source deliver energy at specified current (I) which is independent on voltage across source
- Internal resistance of ideal current source =  $\infty$
- Practical current source deliver energy at specified current (I) which depends on voltage across source
- Independent current source doesn't obey the ohm's law since V-I characteristics are non-linear

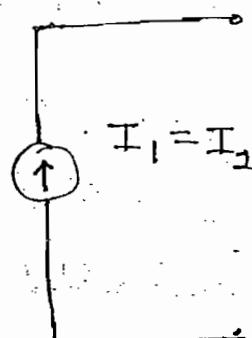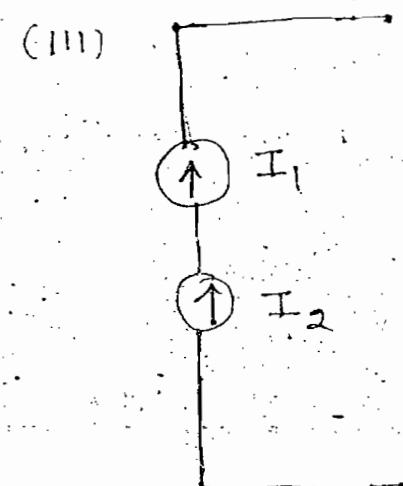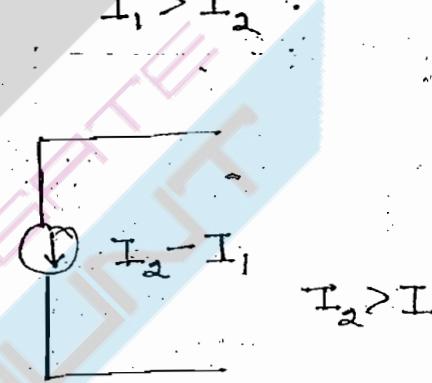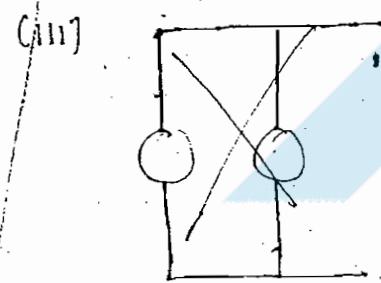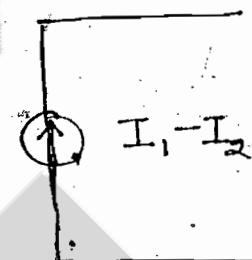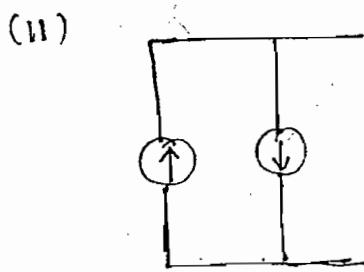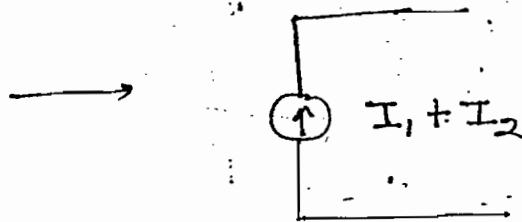
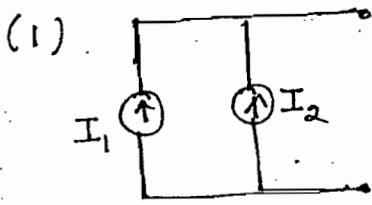
→ In the practical system no independent current source exist but dependent current source are exist.




(IV)

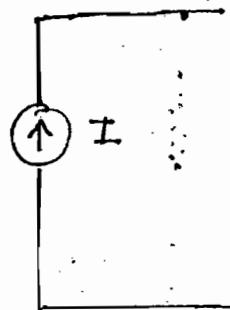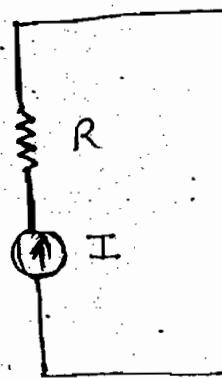

(V)

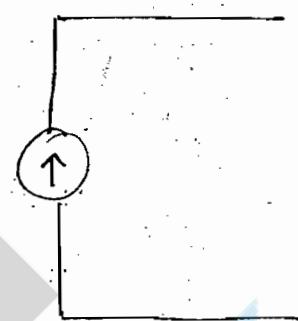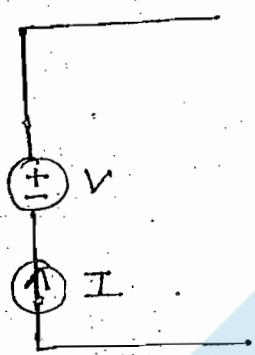

Ques:-

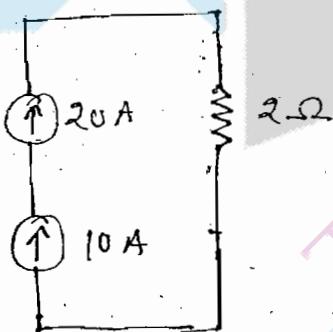

(a) 10 A

(b) 20 A


(c) 30 A

(d) None of these  
OR Not satisfied  
KCL

Note:-


With respect to KCL current flowing through all the series element should be equal

Ans:-

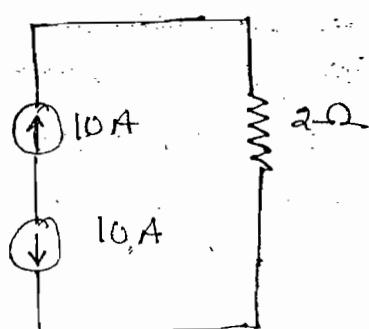

What is the current through 2 ohm resistor?

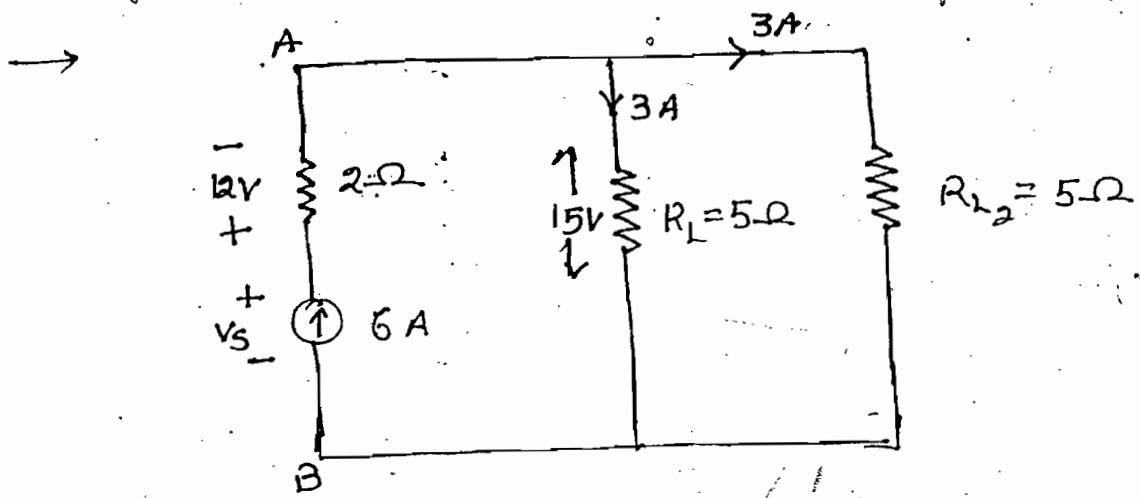SOLN:- Not satisfied KCL  
bec. polarities are  
opposite.




$$V_{AB} = V_s - 12$$

$$\Rightarrow 15 = V_s - 12$$

$$\Rightarrow V_s = 27$$

$$\therefore P_s = 27 \times 6 = 162\text{ W}$$

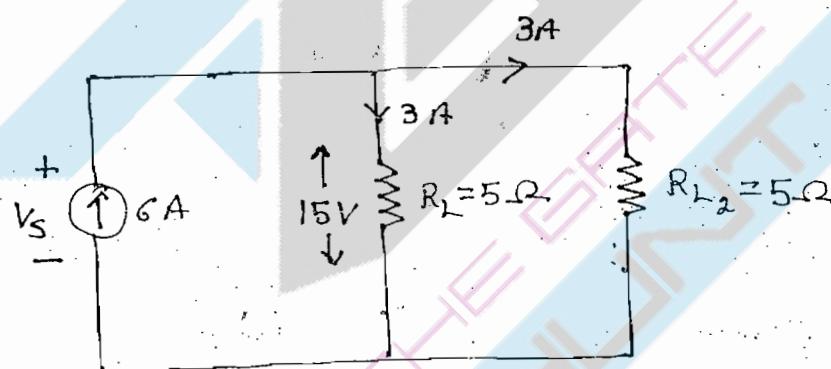PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont:-)



$$V_s' = 15\text{ V} \quad P_s' = 15 \times 6 = 90\text{ W}$$

Note:-

- In the above circuit  $2\Omega$  resistance can be neglected either by calculating load current or load voltage.
- In the above circuit  $2\Omega$  resistance can't be neglected by calculating either voltage across current source or power of the current source.



### Note:-

- In above circuit voltage source can be neglected by calculating either load current or load voltage
- In the above circuit voltage source cannot be neglected by either calculating voltage across current source or power of the current source


### KCL:-

- Based on law of conservation of charge

$$I_1 + I_3 + I_6 = I_2 + I_4 + I_5$$

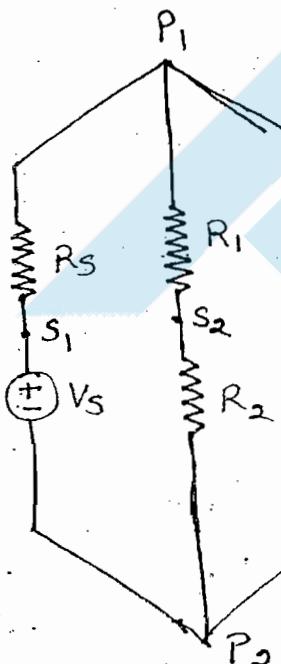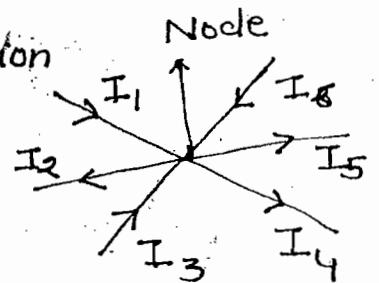

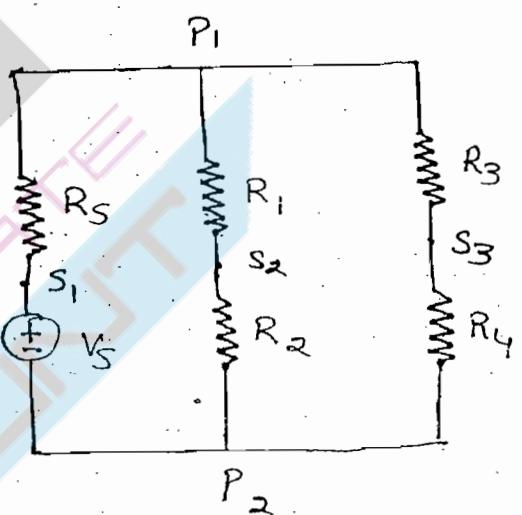OTOSTAT  
All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contact:



- KCL states that algebraic sum of currents meeting at a point is equal to zero.

- When two elements are connected together then common point is called as simple node
- When more than two elements are connected together then common point is called as principal node.

## Current division technique:-

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



$$I_1 = I \frac{R_2}{R_1 + R_2}$$

$$I_2 = I \frac{R_1}{R_1 + R_2}$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

$$I_1 = I \frac{L_2}{L_1 + L_2}$$


$$I_2 = I \frac{L_1}{L_1 + L_2}$$

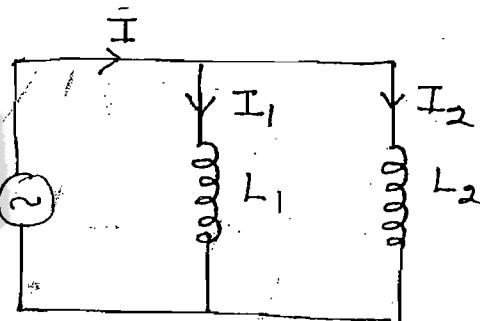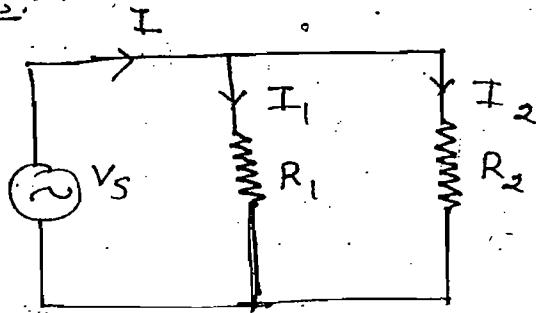


$$C_{eq} = C_1 + C_2$$

$$I_1 = I \frac{C_1}{C_1 + C_2}$$

$$I_2 = I \frac{C_2}{C_1 + C_2}$$

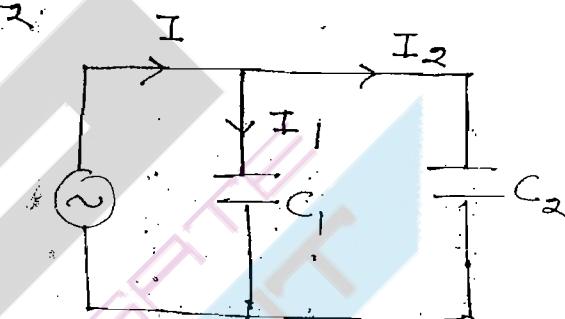

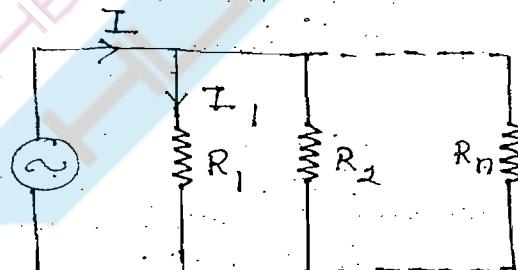
$$I_1 = I \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$



## KVL :-


→ KVL works based on the principle of law of conservation of energy

$$V_1 + V_2 + V_3 - V_S = 0$$

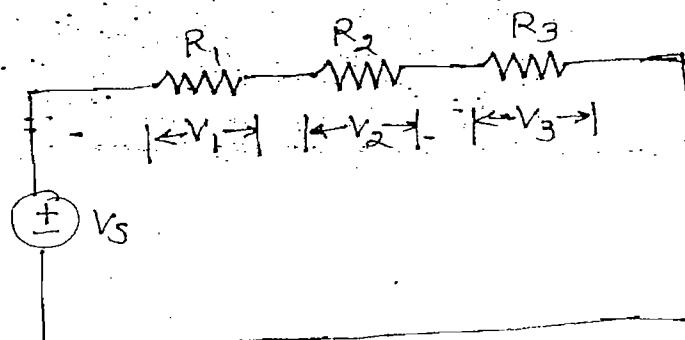


$$V_{S_1} - V_1 - V_{S_3} + V_2 = 0$$

$$V_{S_1} + V_2 = V_1 + V_{S_3}$$

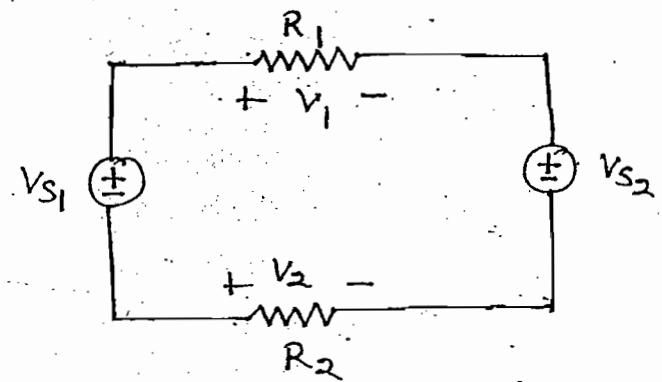

→ KVL states that algebraic sum of voltages in a closed loop is equal to zero

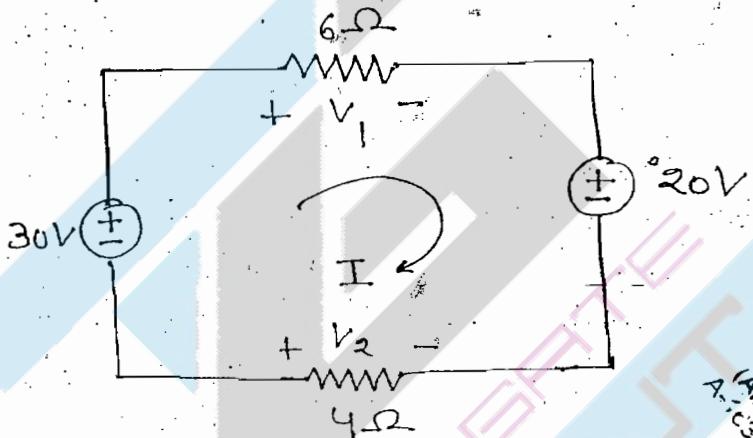Ques:- Find  $V_1$  &  $V_2$  of the circuit shown



Soln:-

$$V_1 = 6I$$

$$V_2 = -4I$$

$$30 - V_1 + 20 - V_2 = 0$$

$$\Rightarrow -30 + 6I + 20 - (-4I) = 0$$

$$\Rightarrow I = 1A$$

$$V_1 = 6V \quad \& \quad V_2 = -4V$$


PHOTO COPY  
IIT JEE Study Material Available  
A/C 3 Lado Sarai, New Delhi  
Contd.../1

## Voltage Division Technique:-

$$R_{eq} = R_1 + R_2$$

$$V_1 = V_s \frac{R_1}{R_1 + R_2}$$

$$V_2 = V_s \frac{R_2}{R_1 + R_2}$$

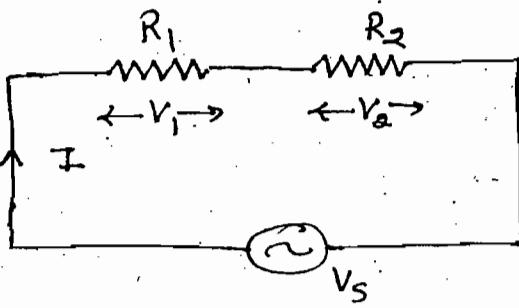

$$L_{eq} = L_1 + L_2$$



$$V_1 = V_s \frac{L_1}{L_1 + L_2}$$

$$V_2 = V_s \frac{L_2}{L_1 + L_2}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$V_1 = V_s \frac{C_2}{C_1 + C_2}$$

$$V_2 = V_s \frac{C_1}{C_1 + C_2}$$

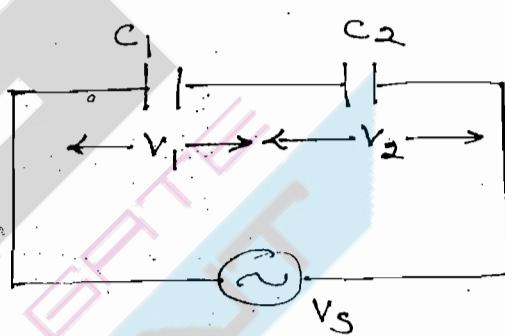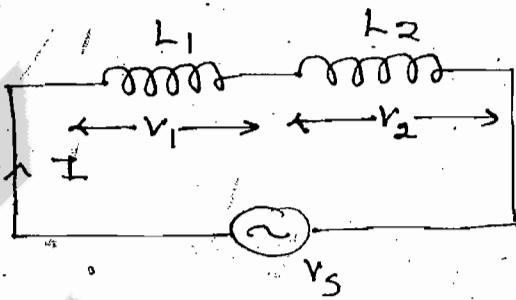

PHOTOSTAT  
All Study Material Available  
A-110 Lado Sarai, New Delhi  
Contd. 9810000000

Downloaded from www.thegatehunt.com

## Conclusions:-

Field Theory —



→ Low frequency

→ High frequency


Network Theory → low frequency

- Field theory can be applied for low or high frequency application
- In field theory accurate results are obtained but developing mathematical equation is complex
- Network theory is applied only for low frequency applications
- In the network theory approximate results are obtained and developing mathematical equation is simple
- KVL and KCL fails for high frequencies application.

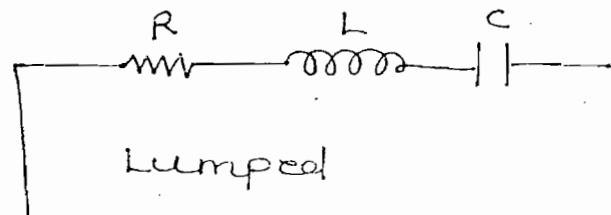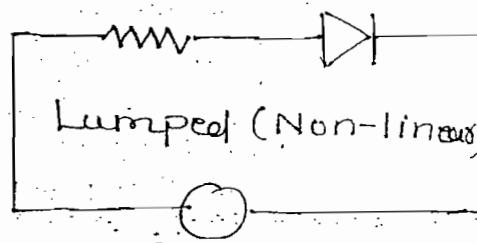EE-EE PHOTOSTAT  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont: 9899999999



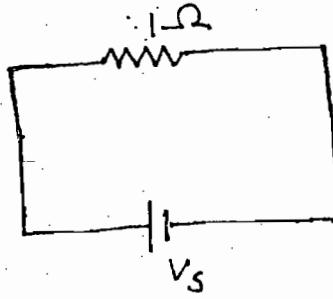
$$V_s = iR + L \frac{di}{dt} + \frac{1}{C} \int idt$$



Lumped  
(Linear)


$$J = -E$$

(Ohm's Law)

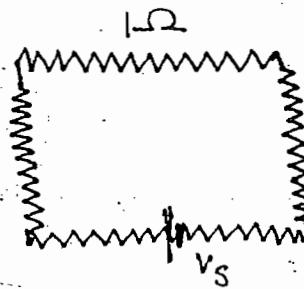

Distributed

Transmission Line.

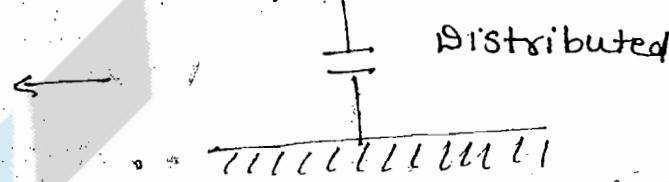

Distributed


- Ohm's law can be applied lumped (linear) and distributed parameters

- KVL and KCL fails for distributed parameters since in the distributed parameters electrically, it is not possible to separate resistance, inductance, and capacitance effects

- KVL and KCL are applied for lumped parameters (Linear, non-linear, uni-directional, bi-directional, time variant and invariant elements)


Cues! :-

$$L_{eq} = ?$$

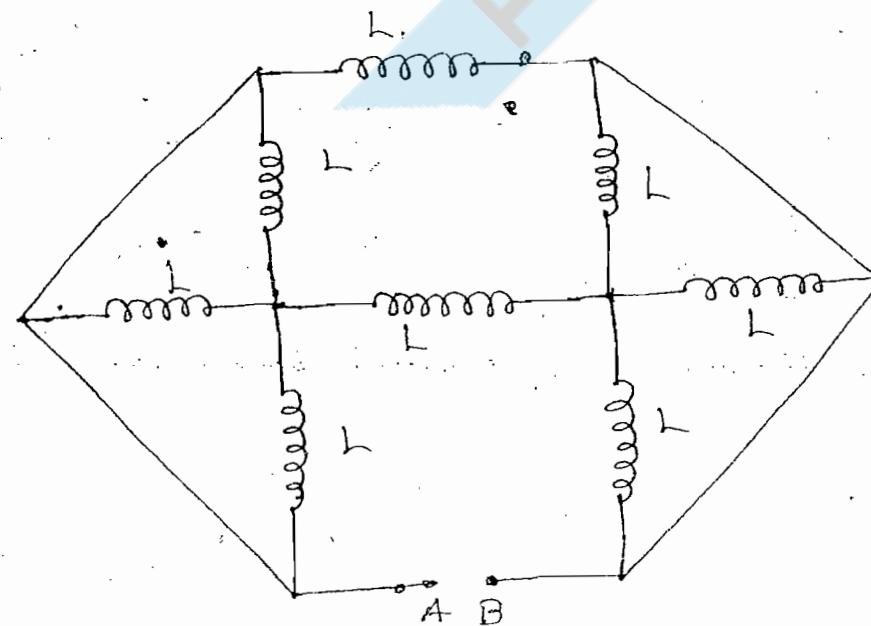


Note!—

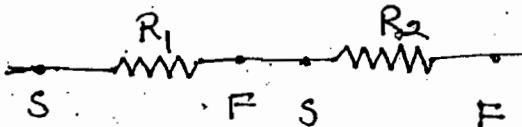
- (I) one joint
- (II)  $I \rightarrow$  same



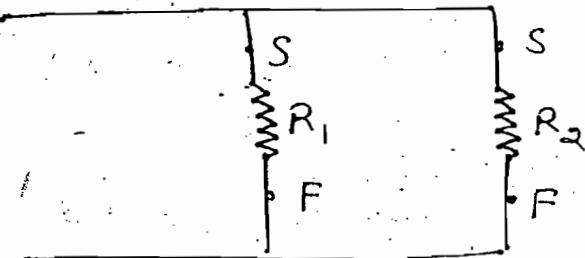
- (I) Twice
- (II)  $V \rightarrow$  same



Soln!—

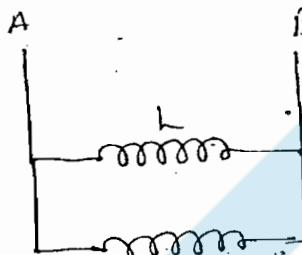
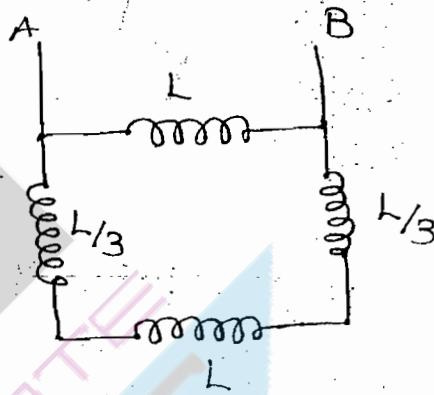
$$\frac{L}{3} + L + \frac{L}{3} = \frac{5L}{3}$$





$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2} = \frac{5L}{8}, \text{ Ans}$$

Ques!— Find equivalent capacitance w.r.t A & B


Soln!—
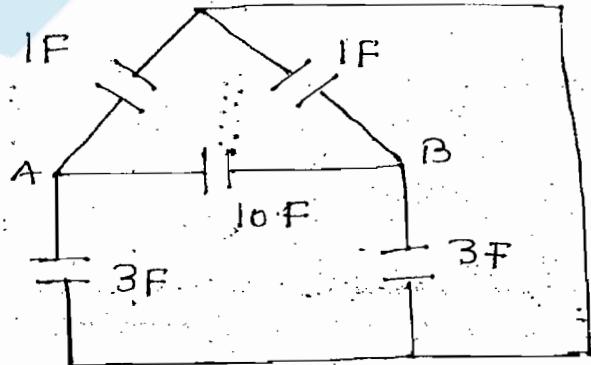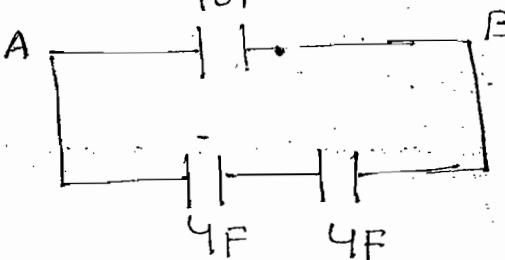
$$Q_{eq} = \frac{1}{4} + \frac{1}{4} + \frac{1}{10} = 10F$$



$$C_{eq} = 10 + 2 = 12F$$

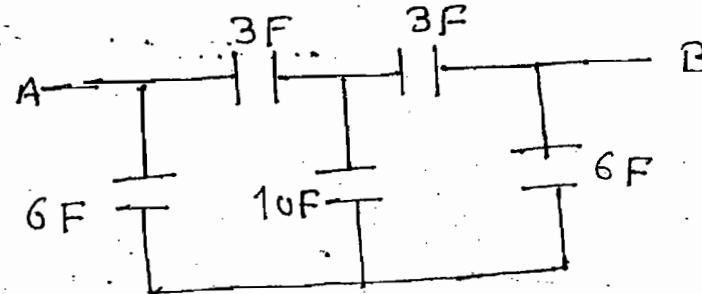
Ques:- Find equivalent capacitance w.r.t A & B.




Soln:-

Balanced bridge


$$z_1 z_4 = z_2 z_3$$

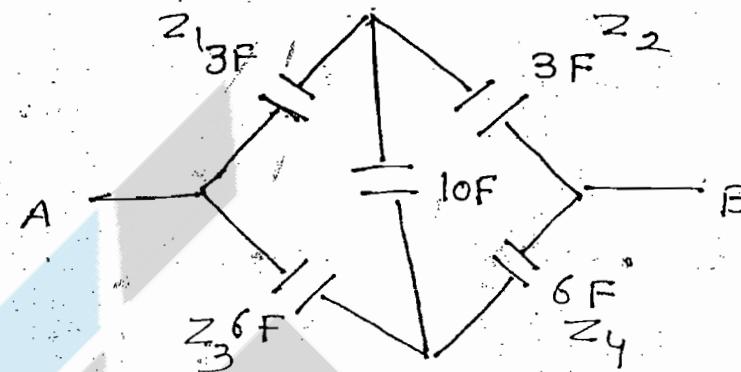
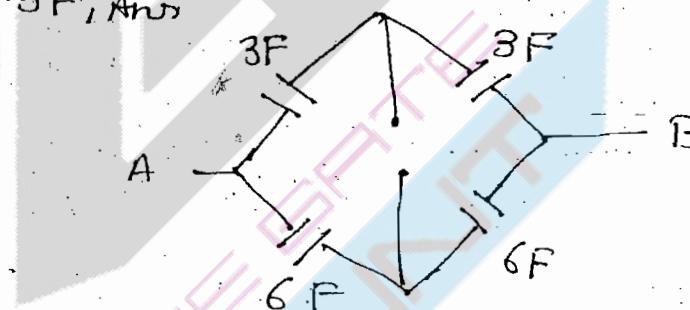
$$C_{eq} = 3 + 1.5 = 4.5 F, \text{ Ans}$$




Ques:- Find I of the circuit shown

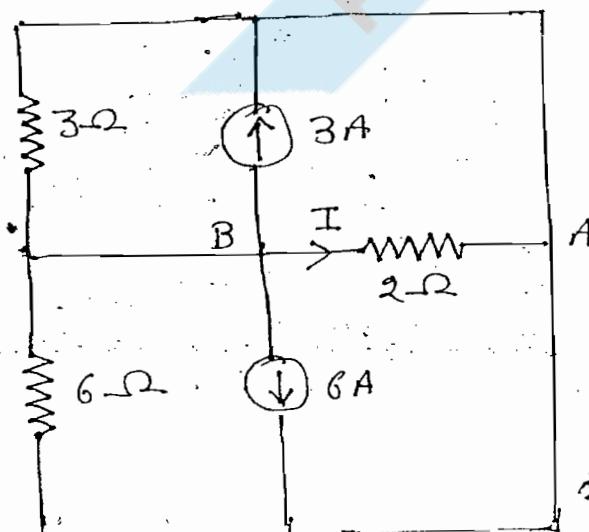


24/7  
(All Study Material Available  
PHOTOSTAT  
Cont'd  
A-163 Lado Sarai, New Delhi


Soln:-

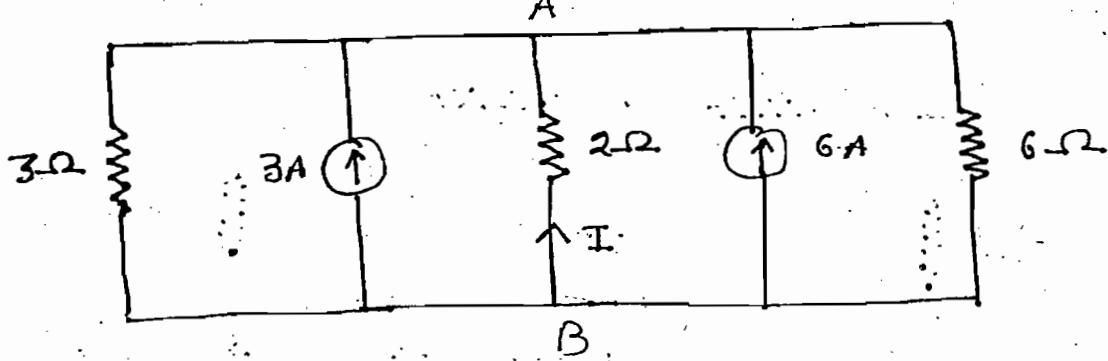

$$I = -4.5 \text{ A}$$

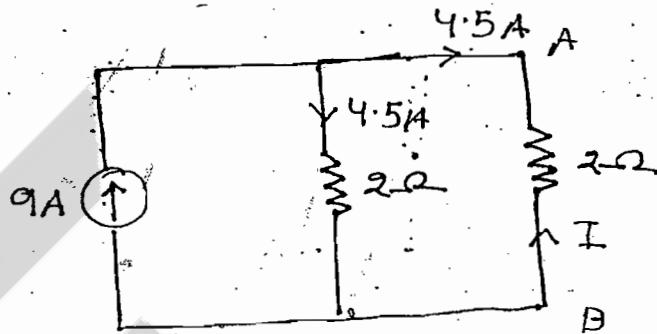

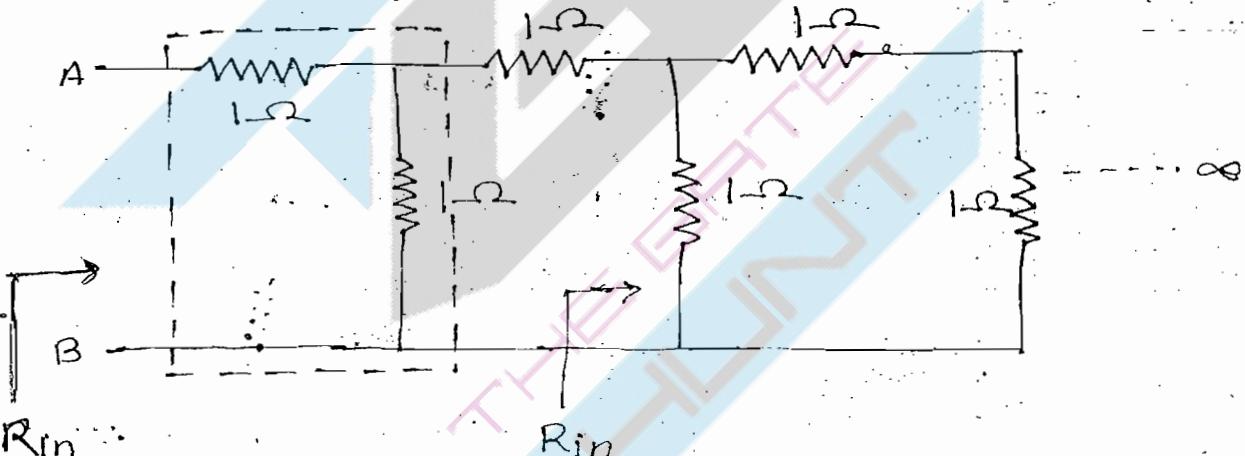Ques:- Find the equivalent resistance w.r.t A & B




Soln:-

$$R_{in} = 1 + \frac{1 \times R_{in}}{1 + R_{in}}$$

$$\therefore R_{in} = \frac{1 + R_{in} + R_{in}}{1 + R_{in}}$$

$$\Rightarrow R_{in}^2 - R_{in} - 1 = 0$$


$$R_{in} = \frac{1 + \sqrt{5}}{2}$$

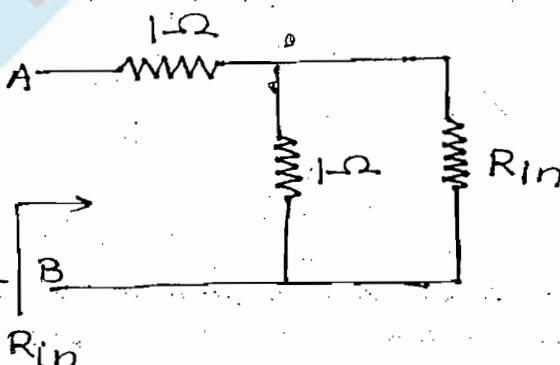

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contd. 987007070)

Ans

Ques!— Find I of the circuit shown

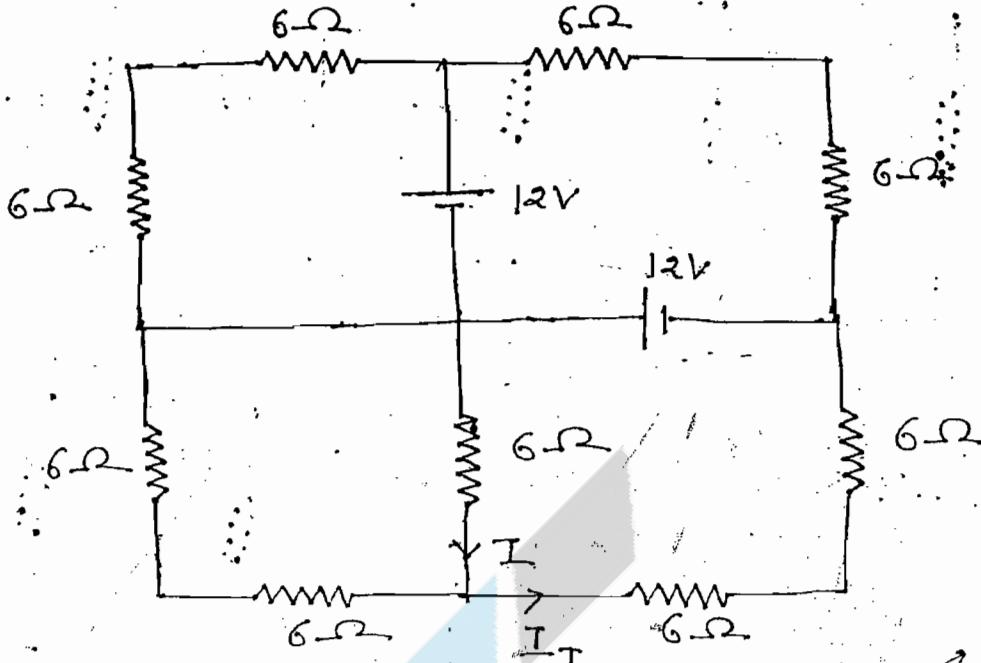

Not effect

in cal:  $I_T$

( $\because V \rightarrow$  ideal)

8 Hrs  
in parallel  
(II)

6 ohm  
6 ohm

6 ohm  
6 ohm


Soln:-

$$I_T = \frac{12}{4+12}$$

$$I = I_T \cdot \frac{12}{12+6}$$

$$= \frac{12}{16} \times \frac{12}{18} = 0.5A$$

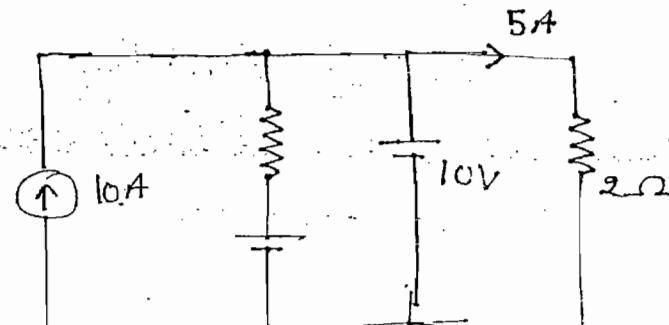CLEARPHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9712622776




Ques:- When two capacitance 40F & 20F are connected in series with a source voltage 90V

When two capacitor charged fully then they are connected in parallel. Find voltage across capacitor in parallel branch.

- (a) 40V (b) 60V (c) 45V (d) 30V

Soln:-

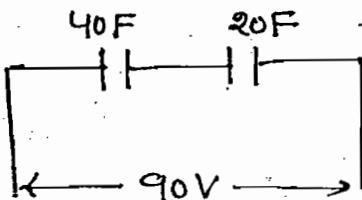

$$C_{eq} = \frac{40 \times 20}{40+20} = \frac{40}{3}$$


$$Q = C_{eq}V = \frac{40}{3} \times 90 \\ = 1200C$$

$$Q_T = 1200 + 1200 = 2400C$$

$$Q_T = 2400$$

$$C_{eq} = \frac{40+20}{60} = 60$$

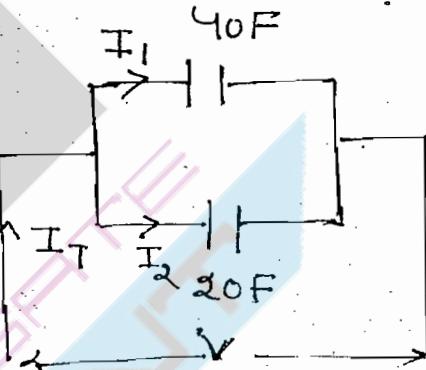
$$V = \frac{Q_T}{C_{eq}} = \frac{2400}{60} \\ = 40V, Ans$$




Note:-



Note:-

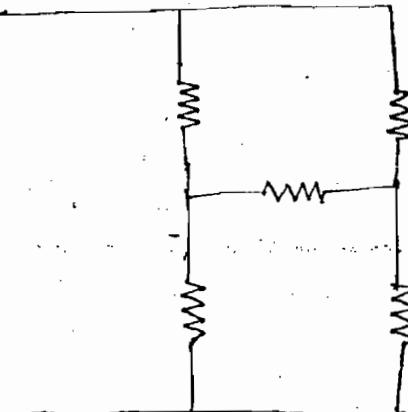When elements are connected not in series nor in parallel network is reduced by Star-delta transformation




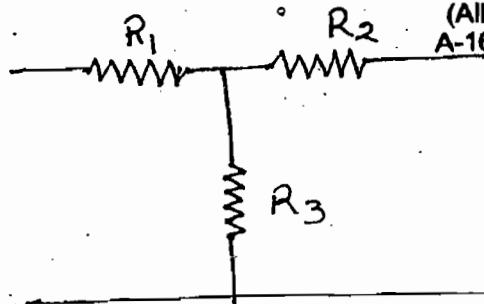


T

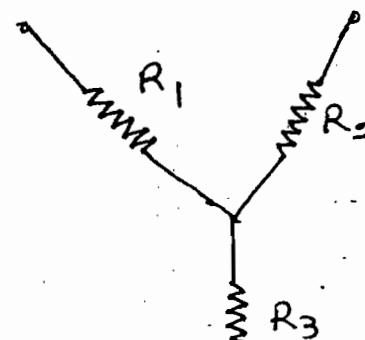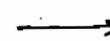


Y OR  
star

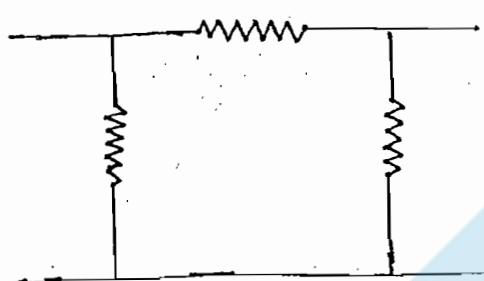

Δ

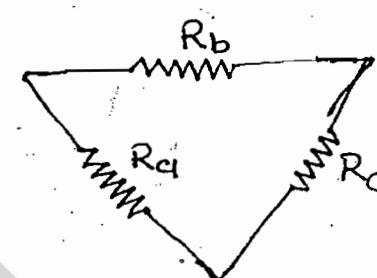

Delta or Mesh

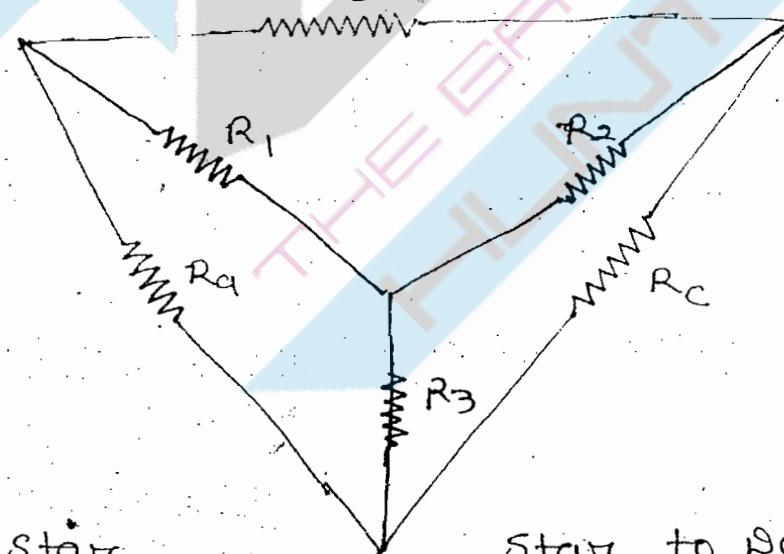

Delta to Star

$$R_1 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_c}{R_a + R_b + R_c}$$


Star to Delta

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

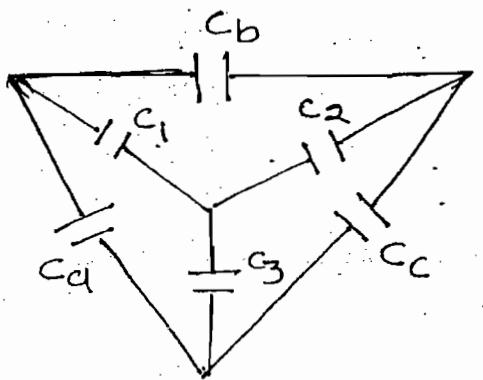→ The procedure of transformation either from delta to star or star to delta for the resistor, inductor and impedance is same



Delta to Star :-

$$\frac{1}{c_1} = \frac{\frac{1}{c_a} \cdot \frac{1}{c_b}}{\frac{1}{c_a} + \frac{1}{c_b} + \frac{1}{c_c}}$$

$$\frac{1}{c_2} = \frac{\frac{1}{c_b} \cdot \frac{1}{c_c}}{\frac{1}{c_a} + \frac{1}{c_b} + \frac{1}{c_c}}$$

$$\frac{1}{c_3} = \frac{\frac{1}{c_a} \cdot \frac{1}{c_c}}{\frac{1}{c_a} + \frac{1}{c_b} + \frac{1}{c_c}}$$

Star to Delta :-

$$\frac{1}{c_a} = \underbrace{\frac{1}{c_1} \frac{1}{c_2} + \frac{1}{c_2} \frac{1}{c_3} + \frac{1}{c_3} \frac{1}{c_1}}_{\frac{1}{c_2}}$$


$$\frac{1}{c_b} = \underbrace{\frac{1}{c_1} \frac{1}{c_2} + \frac{1}{c_2} \frac{1}{c_3} + \frac{1}{c_3} \frac{1}{c_1}}_{\frac{1}{c_3}}$$

$$\frac{1}{c_c} = \underbrace{\frac{1}{c_1} \frac{1}{c_2} + \frac{1}{c_2} \frac{1}{c_3} + \frac{1}{c_3} \frac{1}{c_1}}_{\frac{1}{c_1}}$$
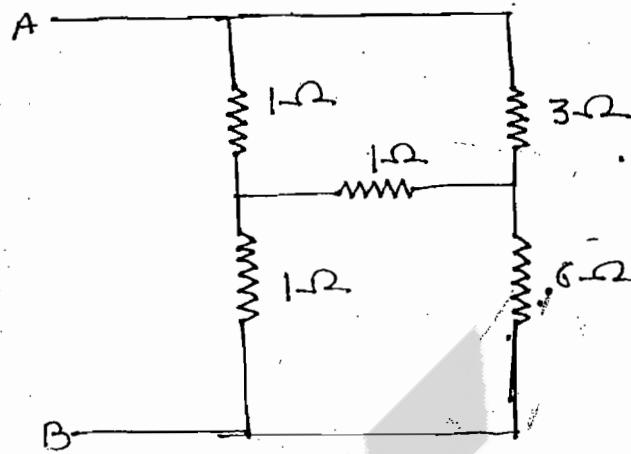
## Lecture - 3

PHOTOSTAT  
 (A Photostatic Copying Machine Available  
 At 10% Discount Price), New Delhi  
 1997

Ques:- Find equivalent resistance w.r.t A & B






Soln:-

$$R_a = \frac{(1 \times 1) + (1 \times 1) + (1 \times 1)}{1} = 3\Omega$$

$$R_b = 3$$

$$R_c = 3$$

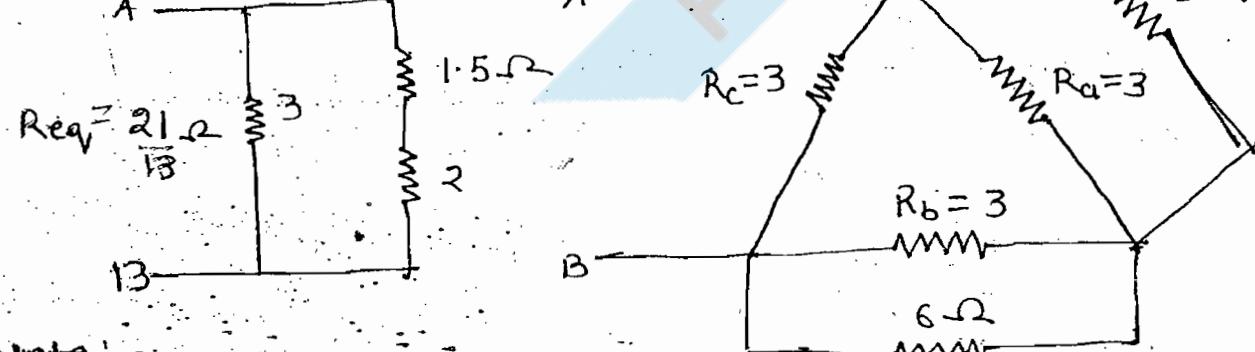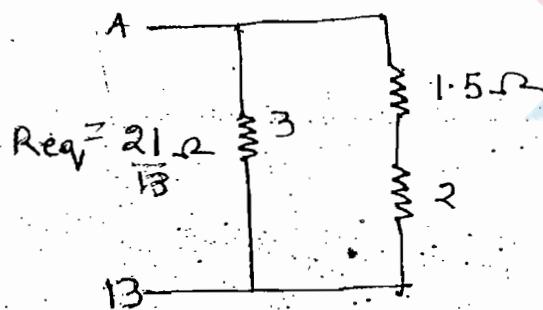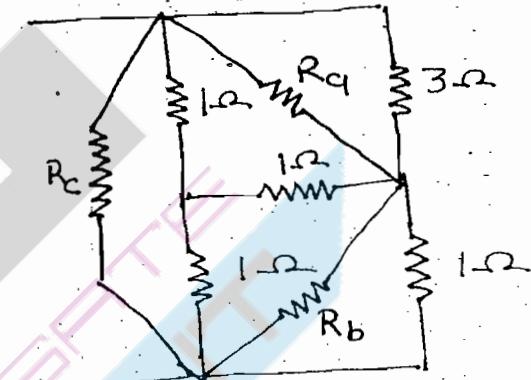


Note:-

When resistor of equal value transfer from star to delta resistance inc. by 3 times.

When capacitance of equal value transform from star to delta capacitance dec. by 3 times

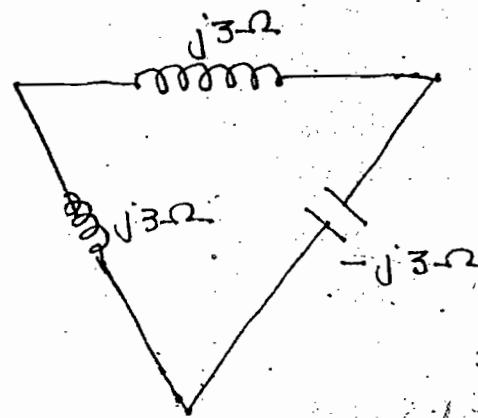ques:- Obtain equivalent star connection of the circuit shown



Soln:-  $jX_L, -jX_C$

$$Z_1 = \frac{(j3)(j3)}{j3 + j3 - j3}$$


$$\boxed{Z_1 = j3}$$

$$Z_2 = \frac{(j3)(-j3)}{j3}$$



$$\Rightarrow \boxed{Z_2 = -j3}$$

$$Z_3 = \frac{(j3)(-j3)}{j3}$$

$$\Rightarrow \boxed{Z_3 = -j3}$$

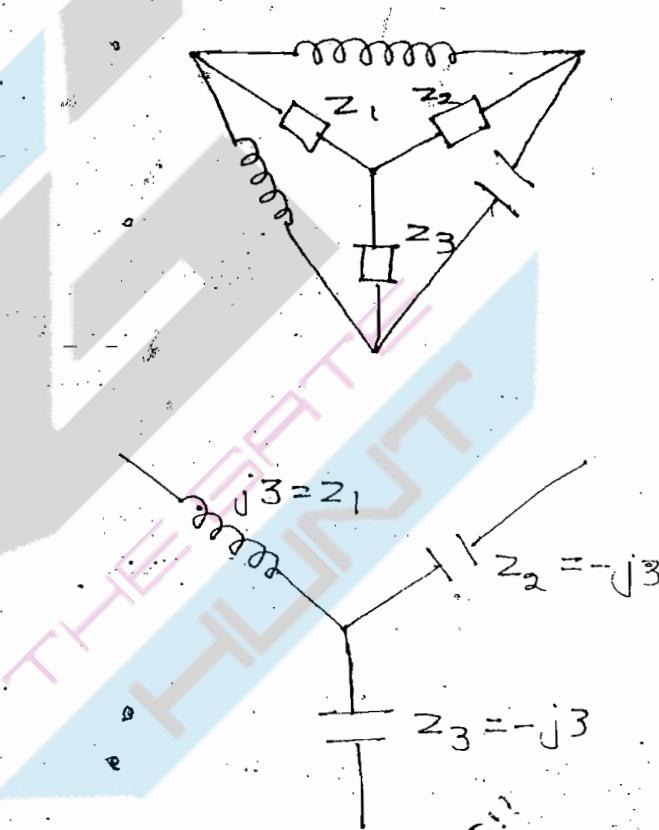

Source Transformation:-

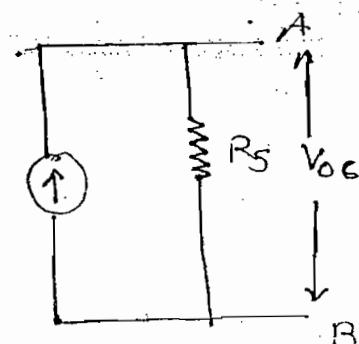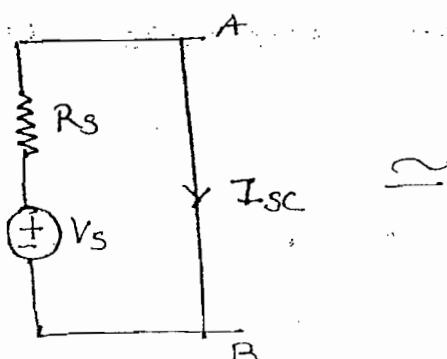

PHOTOSTAT  
All Study Material Available  
A-163 Lado Sarai, New Delhi  
Control


$$I_S = I_{Sc} = \frac{V_S}{R_S}$$

$$V_S = V_{oc} = I_S R_S$$


$$\Rightarrow R_S = R_S$$

$$R_S = R_S$$

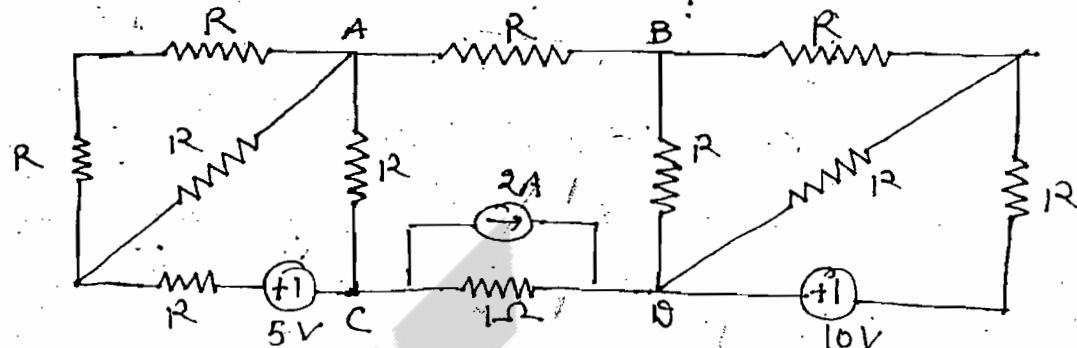ques:- In a circuit shown with  $V_A - V_B = 6$  then find  $V_C - V_D$




Soln:-

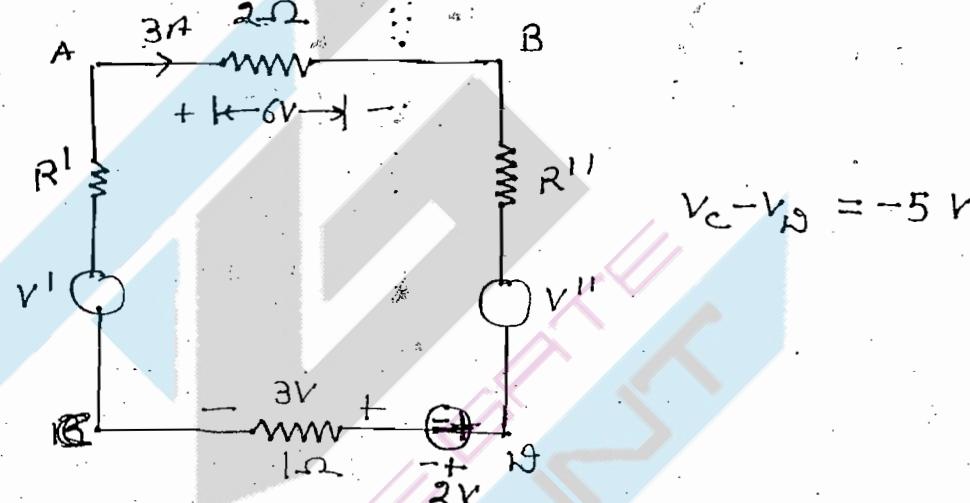

ques:- Find current flown through ideal diode of the circuit



Soln!-

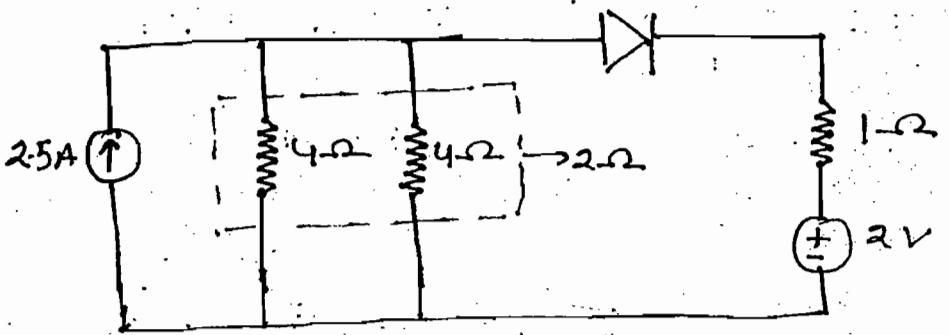

$$V_{S_1} = 2.5 \times 2 = 5V$$


$$i = \frac{V_{eq}}{R_{eq}}$$

$$\Rightarrow i = \frac{5-2}{2+1}$$

$$i = 1A$$



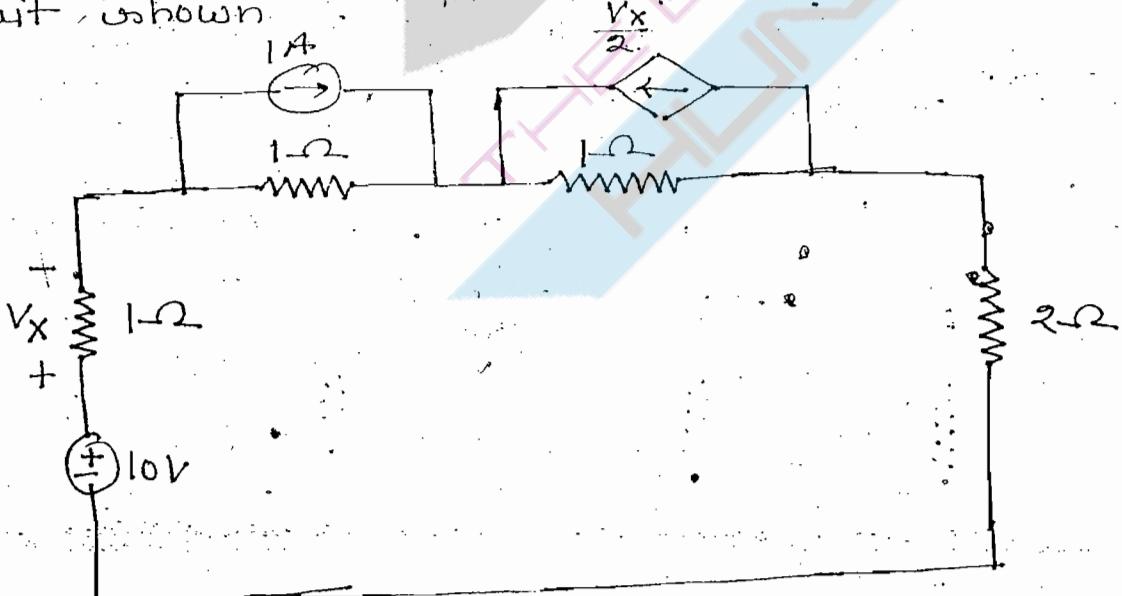
Ques:- Find current in  $2\Omega$  resistor for the circuit shown.



Note!-

While applying source transformation for dependent source wherever dependent source magnitude depends without disturbing an element transformation can be applied

Soln:-

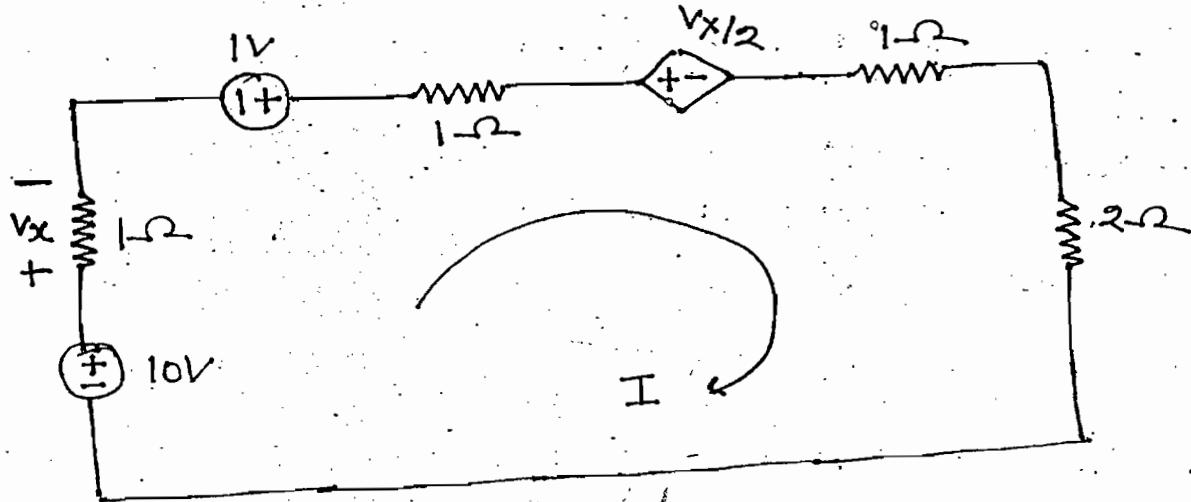

$$-10 + 5I - 1 + \frac{V_x}{2} = 0 \quad \text{---(1)}$$

$$V_x = 1 \times I = I \quad \text{---(2)}$$

From (1) & (2)


$$I = 2 \text{ A}$$

Ans.




PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont.

### Mesh Analysis:

Planar

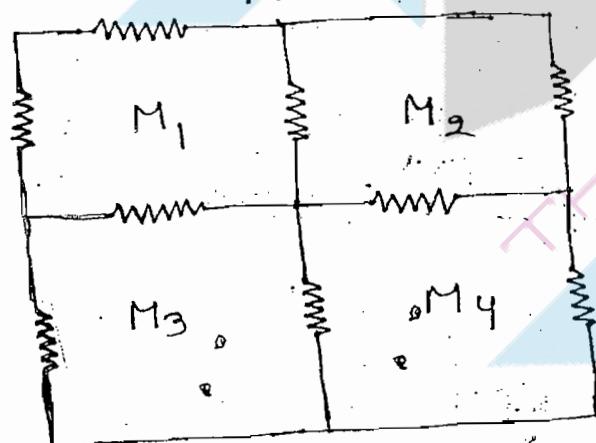

Planar

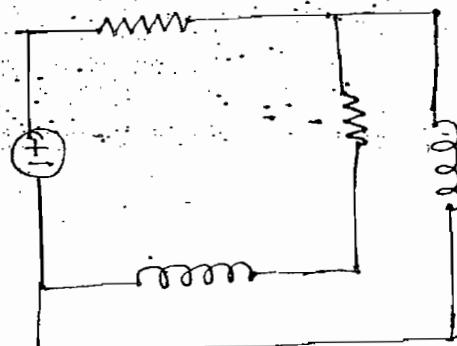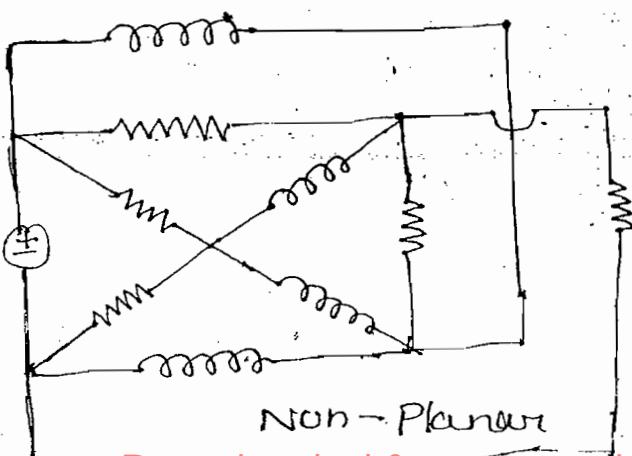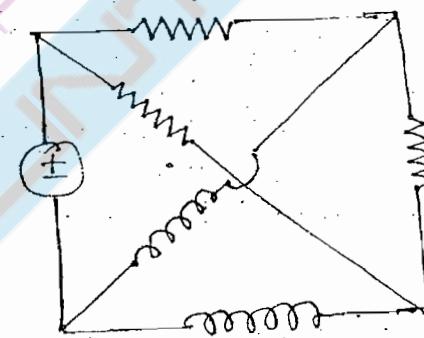


Non-Planar

- Mesh is a loop which does not consist of any loop
- When the network is drawn on plane without any crossover then the network is called as planar network

### Procedure of Mesh Analysis:-

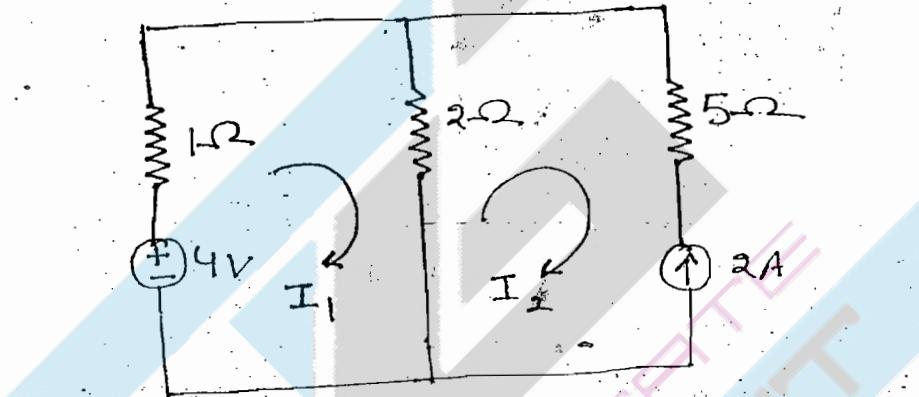1. Identify total no. of meshes in the given network
2. Assign the current direction for each mesh
3. Develop KVL equation for each mesh
4. By solving KVL equations find loop currents



$$\begin{aligned} -4 + 3I_1 - 2I_2 &= 0 \\ -4 + (1 \times I_1) + 2(I_1 - I_2) &= 0 \end{aligned} \quad \rightarrow (I) \text{ (same)} \quad (II)$$

$$I_2 = -2 \quad \text{From (I) \& (II)}$$

$$\boxed{I_1 = 0}$$

Note:-

e = Mesh No      b = total no. of branches

N = total no. of nodes

\*  $\boxed{e = b - (N-1)}$

In above ques

$$e = ?$$

$$b = ?$$

$$N = ?$$


$$e = 3 - (2-1)$$

$$\boxed{e = 2}$$

$$\cancel{e = 3 - 2}$$

→ In above network to find loop current minimum one equation required.

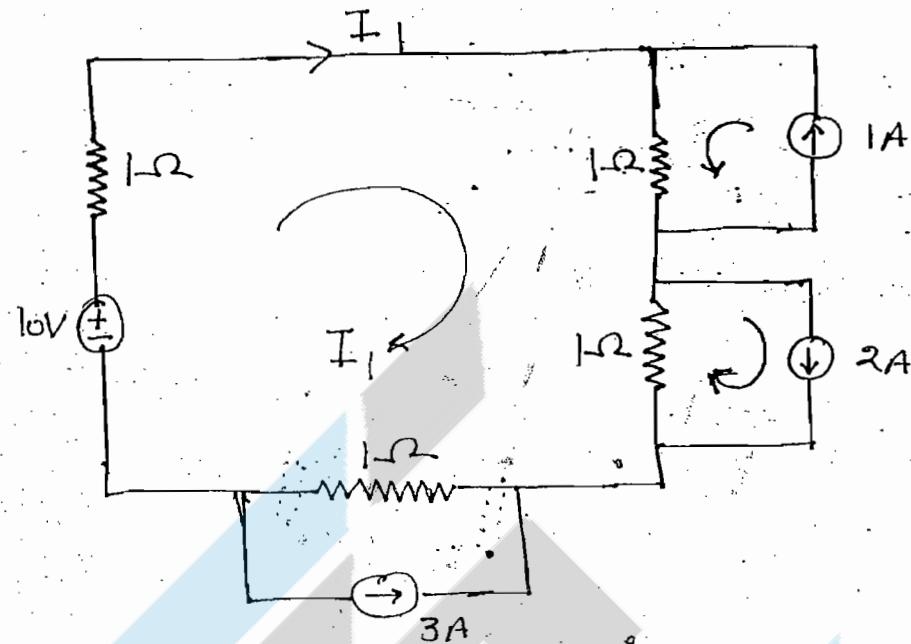
ques:- Find  $I_1$  of the circuit shown.



Soln:-

$$-10 + 4I + (1 \times 1) - (2 \times 1) + 3(1) = 0$$
$$\Rightarrow I = 2A \quad \& \quad I_1 = I$$

ques:- Find  $I_0$ .

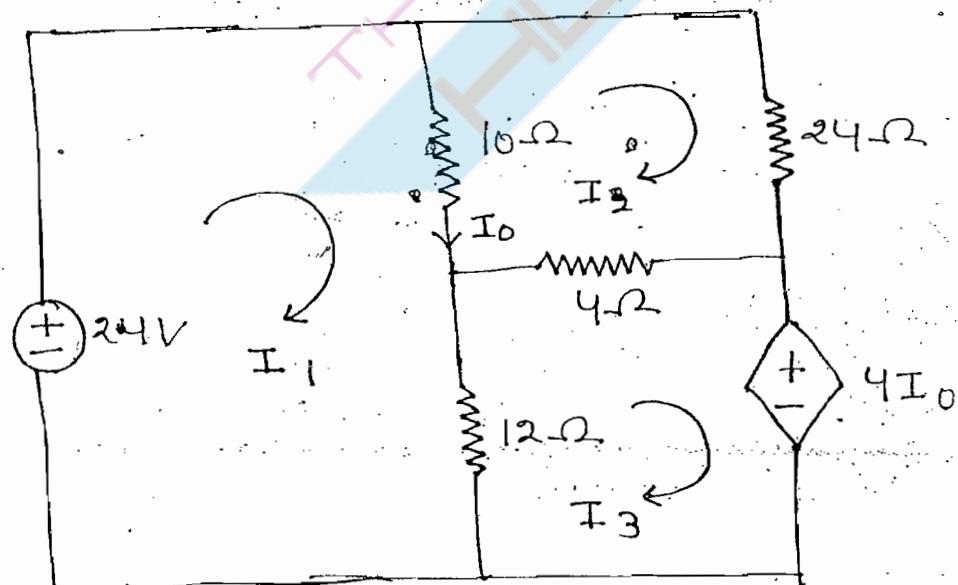

Soln:-

$$24 = 22I_1 - 10I_2 - 12I_3 \quad (I)$$


$$0 = -10I_1 + 38I_2 - 4I_3 \quad (II)$$

$$-4I_0 = -12I_1 - 4I_2 + 16I_3 \quad (III)$$

$$I_0 = I_1 - I_2$$

$$I_0 = 1.5A$$

Ques:- Find i of the ckt unknown

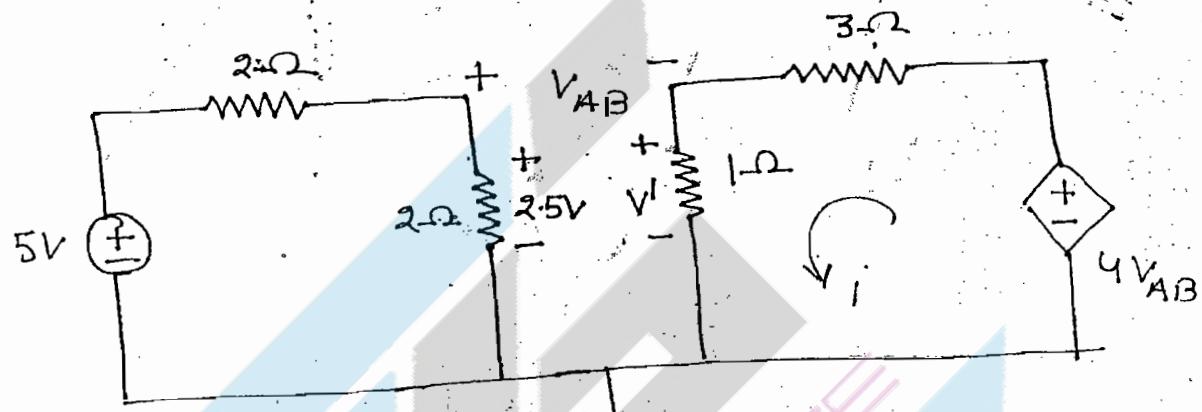

Soln:-

$$i = \frac{4V_{AB}}{3+1} = V_{AB}$$

$$V^1 = i \times 1 = i$$

$$-2.5 + V_{AB} + V^1 = 0$$


$$\Rightarrow i = 2.5A \quad \text{Ans}$$

Ques:- Find  $C_{eq}$  w.r.t A & B

Soln:-

$$V_S = 2I_1 + \frac{1}{50} \int (I_1 + 49I_1) dt$$
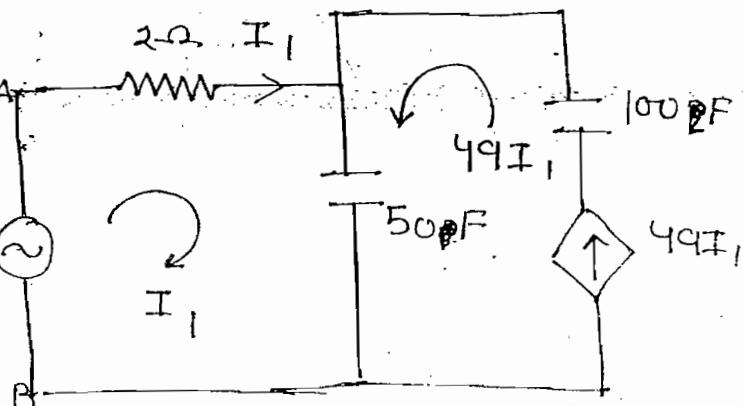
$$\Rightarrow V_S = 2I_1 + \frac{50}{50} \int I_1 dt \quad (1)$$



$$V_s = RI_1 + \frac{1}{C_{eq}} \int I_1 dt - (II)$$


Compare (I) & (II)

$$C_{eq} = 1$$

Ans

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9711022020

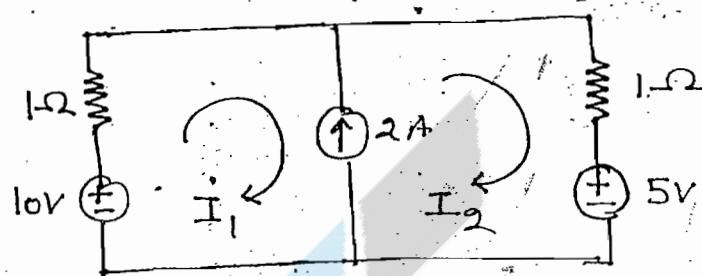Ques:- Find  $I_1$  and  $I_2$  of the circuit shown



Note:-

When current source branch is common for two meshes it is possible to find solution using supermesh technique.

$$KVL \rightarrow -10 + (1 \times I_1) + (1 \times I_2) + 5 = 0 \rightarrow (I)$$


$$KCL \rightarrow I_2 - I_1 = 2 \rightarrow (II)$$

Mesh  $\rightarrow$  KVL + Ohm's law


Super Mesh  $\rightarrow$  KVL + KCL + Ohm's law

$$\Rightarrow I_1 = 1.5 \quad I_2 = 3.5, \text{ Ans}$$

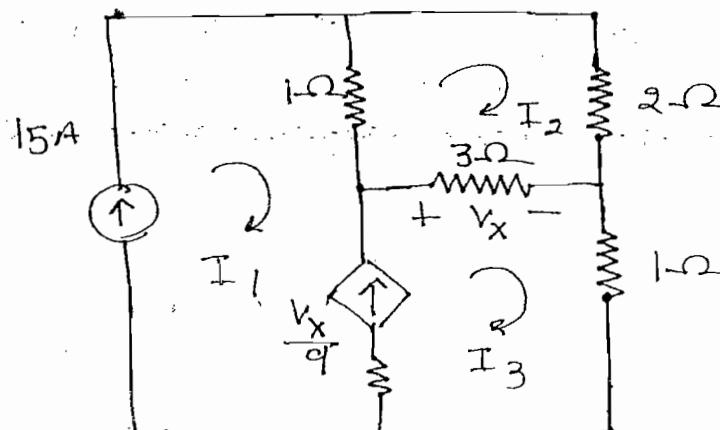Ques:- Find loop currents of the circuit shown!-



Ques:-

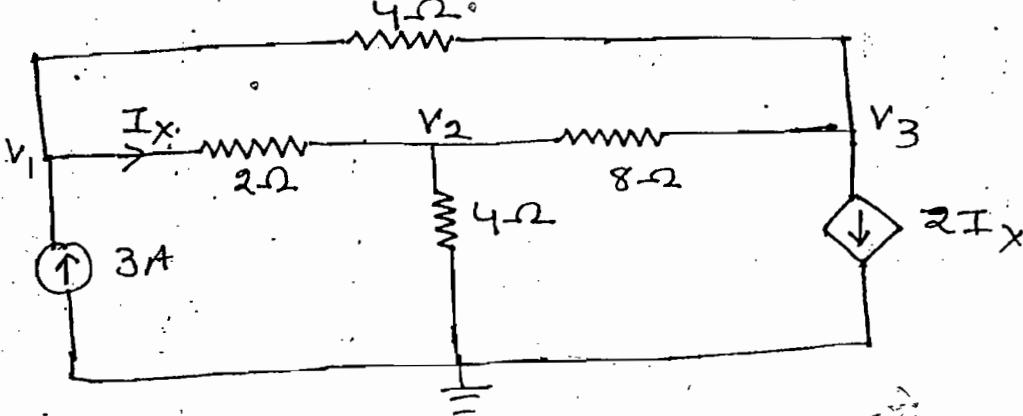

Find  $V_1$ ,  $V_2$  &  $V_3$

$$\text{Solt}:- \quad \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{4} = 3 \quad \text{--- (I)}$$

$$\frac{V_2}{4} + \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{8} = 0 \quad \text{--- (II)}$$


$$\frac{V_3 - V_1}{4} + \frac{V_3 - V_2}{8} + 2I_x = 0 \quad \text{--- (III)}$$

$$I_x = \frac{V_1 - V_2}{2} \quad \text{--- (IV)}$$

$$V_1 = 4.8, \quad V_2 = 2.4, \quad V_3 = -2.4, \quad \text{Ans}$$

Ques:-

Find  $V_1$  &  $V_2$

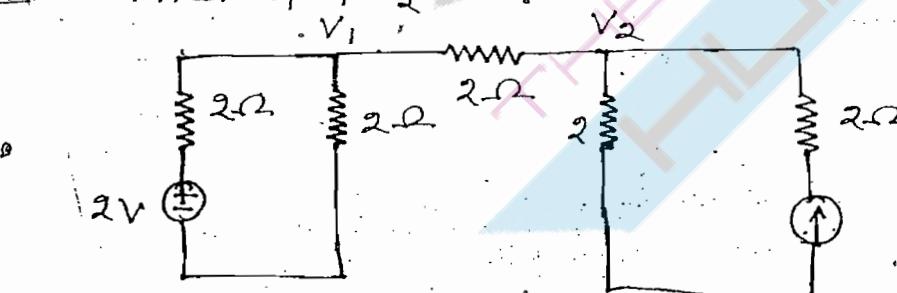


Solt:


$$\frac{V_1 - 2}{2} + \frac{V_1}{2} + \frac{V_1 - V_2}{2} = 0 \quad \text{--- (I)}$$

$$\frac{V_2}{2} + \frac{V_2 - V_1}{2} = 2 \quad \text{--- (II)}$$
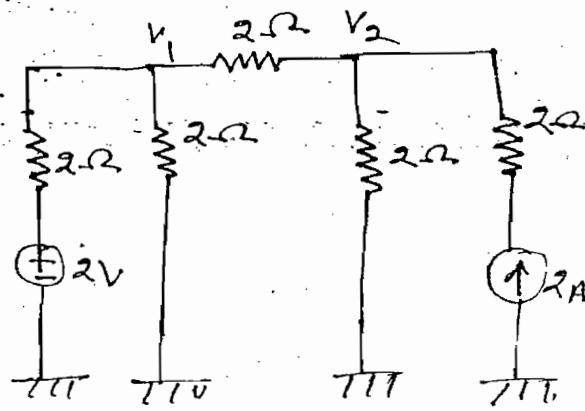
$$\boxed{V_1 = 1.6V \\ V_2 = 2.8V} \quad \text{Ans}$$



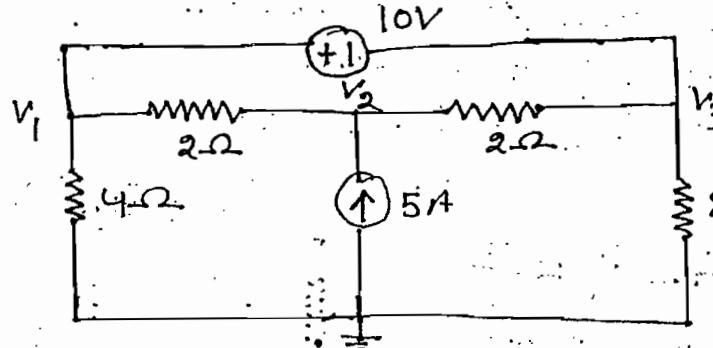Ques!- Find node voltages of the circuit shown.



Note!-

When ideal voltage source is connected b/w two non-reference node it is possible to find solution by using supernode technique.

Soln:-

$$\frac{V_1}{4} + \frac{V_1 - V_2}{2} + \frac{V_3}{8} + \frac{V_3 - V_2}{2} = 0 \quad \rightarrow (I) \rightarrow KCL$$

$$V_1 - V_3 = 10 \quad \rightarrow (II) \rightarrow KVL$$

$$-5 = \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{2} \quad \rightarrow (III)$$


$$V_1 = 16.67V \quad V_2 = 16.67V \quad V_3 = 6.67V, \text{ Ans}$$

Note!-

Nodal  $\rightarrow$  KCL + ohm's law

Super Node  $\rightarrow$ , KCL + KVL + ohm's law

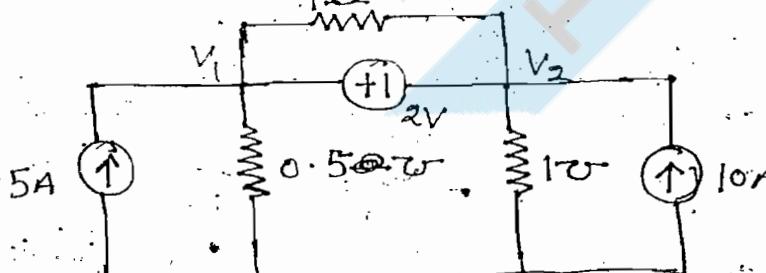Ques!- Find  $V_1$  and  $V_2$  of the circuit shown



Soln!- Resistance connected in parallel with voltage source does not influence

$$10 + 5 = (V_1 \times 0.5) + (V_2 \times 1) \rightarrow KCL$$

$$V_1 - V_2 = 2 \rightarrow KVL$$

ques:- The practical source of 3V and internal resistance  $2\Omega$  connected to non-linear resistor. The characteristic of non-linear resistor is given by  $V_{NL} = I_{NL}^2$ . Find power dissipation in the non-linear resistor.

Soln:-

$$-3 + 2I_{NL} + V_{NL} = 0$$


$$-3 + 2I_{NL} + I_{NL}^2 = 0$$

$$I_{NL}^2 + 2I_{NL} - 3 = 0$$

$$I_{NL} = 1$$

$$V_{NL} = I_{NL}^2 = (1)^2 = 1$$

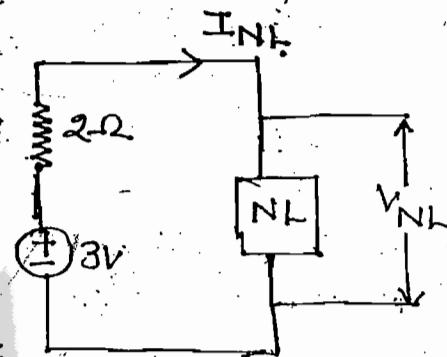
$$P_{NL} = V_{NL} I_{NL} = 1 \times 1 = 1W$$



PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9811000000

ques:- A fully charged mobile phone is good for 10min talktime. During talktime battery delivers a constant current of 2A. The voltage characteristics of battery is as shown in figure. Find energy of battery during talk time

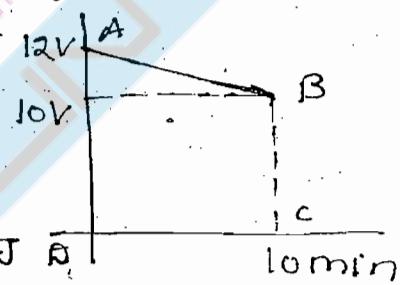Soln:-  $t = 10\text{min} = 10 \times 60 = 600\text{s}$




$$V \times t = 6600$$

$$W = Vit = 6600 \times 2 = 13.2 \text{ kJ}$$

Note:-

$$40W \rightarrow R_1$$

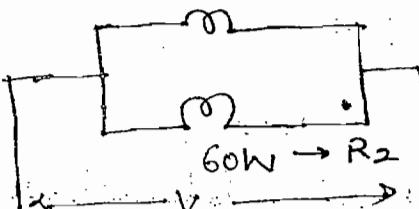

$$R_2 > R_1$$

$$R_1 > R_2$$


$$P_1 = \frac{V^2}{R_1}$$

$$P_2 = \frac{V^2}{R_2}$$

$$P_1 < P_2$$

↓  
More brightness

$$40 \quad 60W$$

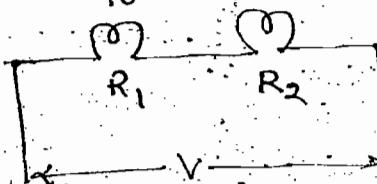

$$P_1 = I^2 R_1$$

$$P_2 = I^2 R_2$$

$$P = \frac{V^2}{R}$$

$$R_1 > R_2$$

$$P_1 > P_2$$

↓  
More brightness


- When the bulbs are connected in series low rating bulb uses more brightness
- When the bulbs are connected in parallel high rating bulb uses more brightness
- In the above two cases voltage reading of bulb are equal

Ques:- In the given connection which bulb glow brightly

$$SOLN:- R = \frac{V^2}{P}$$

$$R_1 = \frac{(100)^2}{40} \quad R_2 = \frac{(200)^2}{60}$$

$$R_2 > R_1$$

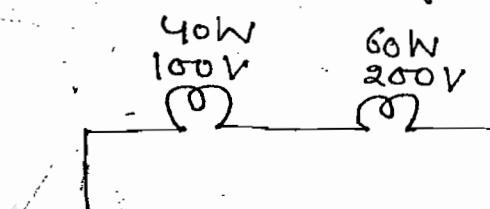

$$R = \frac{V^2}{P}$$

- 60W bulb having more brightness

### Steady State AC Circuits :-

$$V(t) = V_m \sin \omega t$$

$V_m$  = Peak or Max value

$\omega$  = Angular frequency

→ rad/sec

$\omega t$  = Argument - rad



$$\omega T = 2\pi$$

$$\Rightarrow T = \frac{2\pi}{\omega} \text{ sec.}$$


$$f = \frac{1}{T}$$

$$f = \frac{\omega}{2\pi}$$

Hz or cycles/sec.

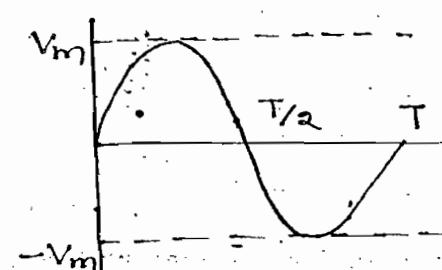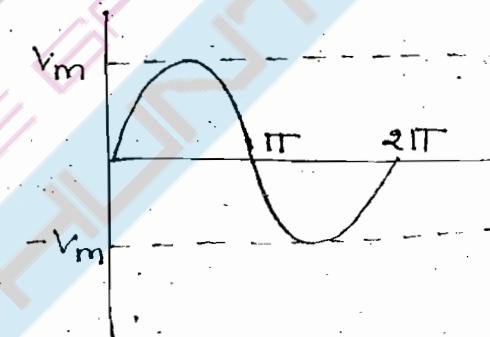


$$V(t) = V_m \sin \omega t$$

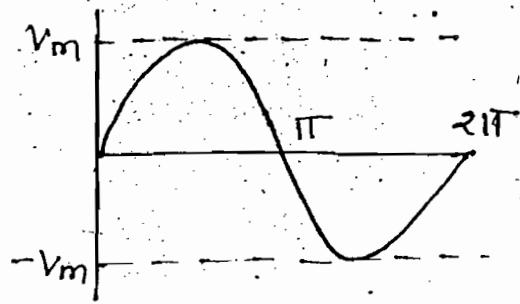

**PHOTOSTAT**  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contd)


$$V(t) = V_m \sin(\omega t + \theta)$$

→ Leading

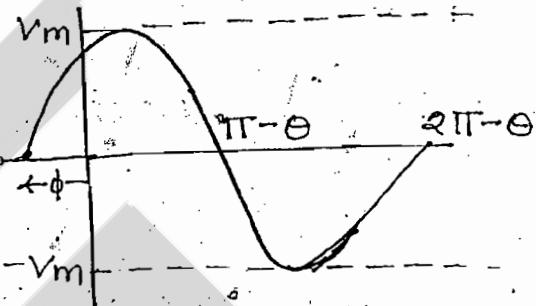


$$V(t) = V_m \sin(\omega t - \theta)$$

→ Lagging

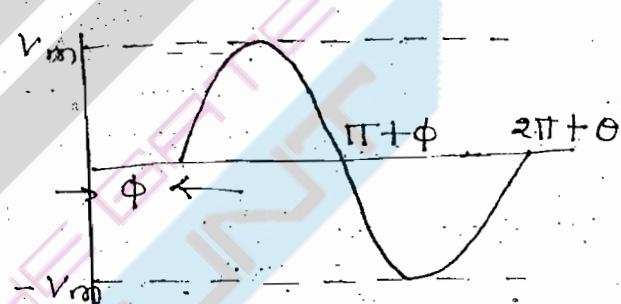

RMS Value :-

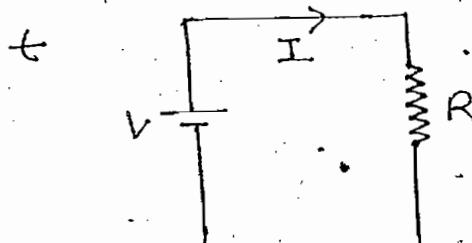


$$P = I^2 R$$

$$W = I^2 R t$$

↓ DC

Heat

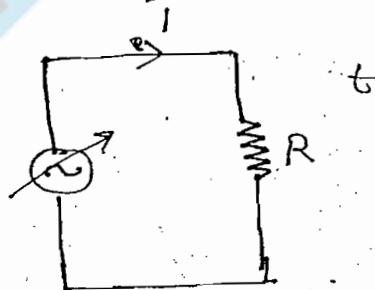

$$P = I^2 R$$

$$W = I^2 R t$$

↓ AC

Heat

$$W_{AC} = W_{DC}$$

- RMS value is defined based on heating effect of the waveform.
- The voltage at which heat dissipation in A.C circuit is equal to heat dissipation in DC circuit is called as  $V_{RMS}$  provided both AC and DC circuit having equal value of resistance and operated for same time.

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2 dt}$$


$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T V^2 dt}$$

### Lecture - 4

PHOTOSTAT  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont: 9811310221

ques:- Find RMS value of following waveforms

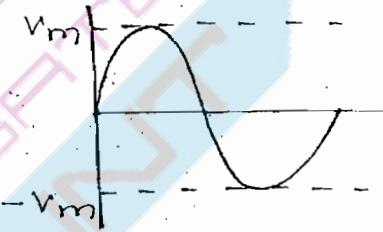
$$(I) V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2 dt}$$



$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \omega t)^2 dt}$$

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \left(\frac{1-\cos 2\omega t}{2}\right) dt}$$
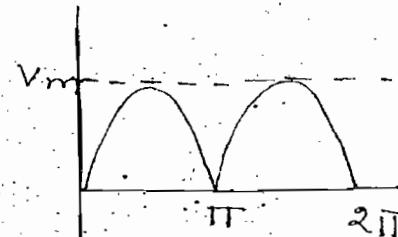
$$\Rightarrow V_{RMS} = \frac{V_m}{\sqrt{2}}$$




$$(II) V_{RMS} = \frac{V_m}{\sqrt{2}}$$

PHOTOSTAT  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont: 9811310221




$$V_{RMS} = \frac{V_m}{2}$$

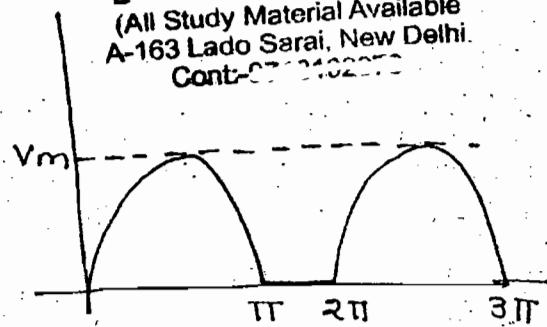

$$V_{RMS} = \frac{V_m}{\sqrt{2}}$$

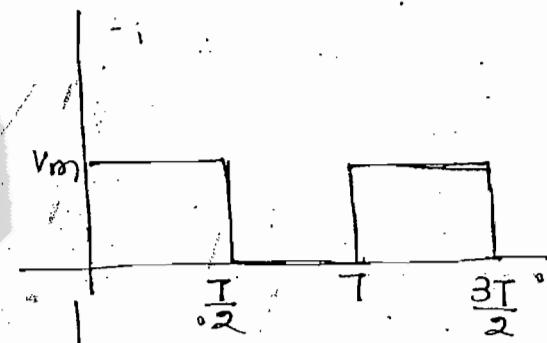
$$V_{RMS} = \sqrt{\frac{1}{T} \left[ \int_0^{\frac{T}{2}} V_m^2 dt + \int_{\frac{T}{2}}^T 0 dt \right]}$$



$$V_{RMS} = \frac{V_m}{\sqrt{2}}$$

Note: RMS value is independent on the position of waveform.


But it depends on the shape of Waveform

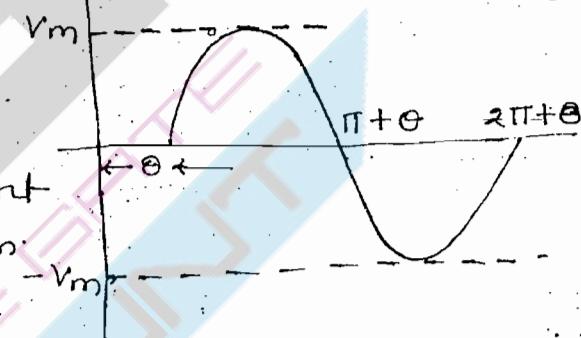


$$V_{RMS} = \frac{V_m}{\sqrt{3}}$$

$$0 < t < T \quad y = mct$$

$$\Rightarrow V = \frac{V_m}{T} t$$

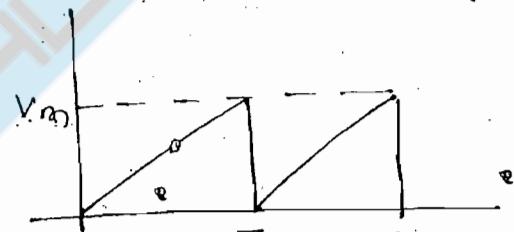

$$V_{RMS} = V_m$$

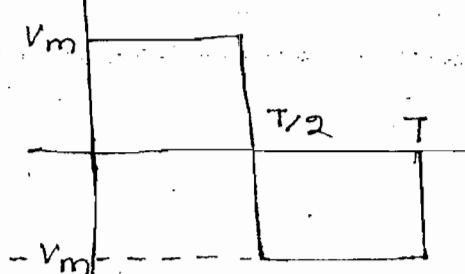


$$\rightarrow V_{RMS} = \sqrt{\frac{1}{T} \int_0^T V^2 dt}$$

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{V_m t}{T}\right)^2 dt}$$

$$\Rightarrow V_{RMS} = \frac{V_m}{\sqrt{3}}$$

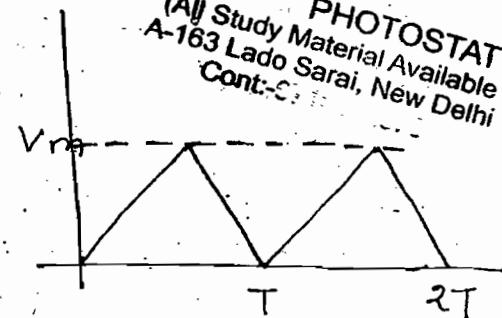PHOTOSTAT  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Contd...).




$$\rightarrow 0 < t < 2$$

$$y = m x c$$

$$m = \frac{y_2 - y_1}{x_2 - x_1} = \frac{10 - 0}{2 - 0} \\ = 5$$

$$V = 5t$$

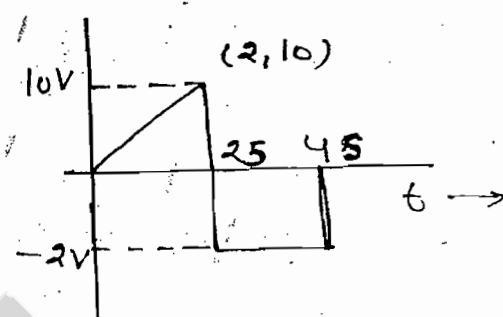


$$V_{RMS} = \sqrt{\frac{1}{4} \left[ \int_0^2 (5t)^2 dt + \int_2^4 (-2)^2 dt \right]}$$

$$\Rightarrow V_{RMS} = \sqrt{\frac{1}{4} [25(t^{3/2})_0^4 + (4t)_2^4]}$$

$$\Rightarrow V_{RMS} = 4$$

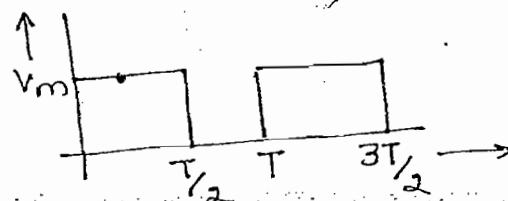ques: Find power dissipation in the resistor for the given voltage waveform



$$(a) P_{av} = \frac{P_{peak}}{\sqrt{2}}$$

$$(b) P_{av} = \frac{P_{peak}}{2}$$

$$(c) P_{av} = P_{peak}$$

$$(d) P_{av} = \frac{P_{peak}}{\sqrt{3}}$$

Soln:- B.  $P_{peak} = \frac{V_m^2}{R}$

$$P_{av} = \frac{V_{RMS}^2}{R} = \frac{(V_m/\sqrt{2})^2}{R} = \frac{V_m^2}{2R} = \frac{P_{peak}}{2}$$

M

Note:-

$$\rightarrow P_{RMS} = \frac{V_{RMS}^2}{R}$$

\*\*

→

$$\frac{P_{AC}}{P_{RMS}} = \frac{I_{av}^2 R}{\frac{I^2_{RMS} R}{2}}$$

ques:- Find RMS value for the following function

$$V(t) = 3 + \sin 3t + \cos t$$

Soln:-


$$V_{RMS} = \sqrt{V_{RMS_1}^2 + V_{RMS_2}^2 + V_{RMS_3}^2 + \dots + V_{RMS_n}^2}$$

[Used when different waves present]

$$\Rightarrow V_{RMS} = \sqrt{(3)^2 + \left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2}$$


$$\Rightarrow V_{RMS} = \sqrt{10}$$

Average Value:-

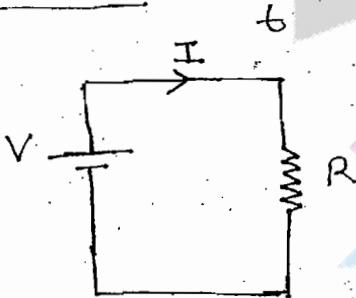

$$I = \frac{V}{R}$$

$$Q = It \rightarrow DC$$

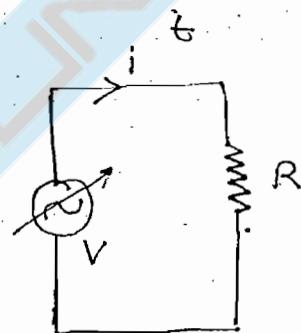

$$i = \frac{V}{R}$$


$$Q = it \rightarrow AC$$

$$Q_{AC} = Q_{DC}$$

PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Cont.

- Average value is defined based on charge transfer in the circuit
- The voltage at which charge transfer in AC circuit is equal to charge transfer in DC circuit is called as  $V_{avg}$ . provided both AC and DC circuit having equal value of resistance and operated for same time.

Symmetrical Wave :-

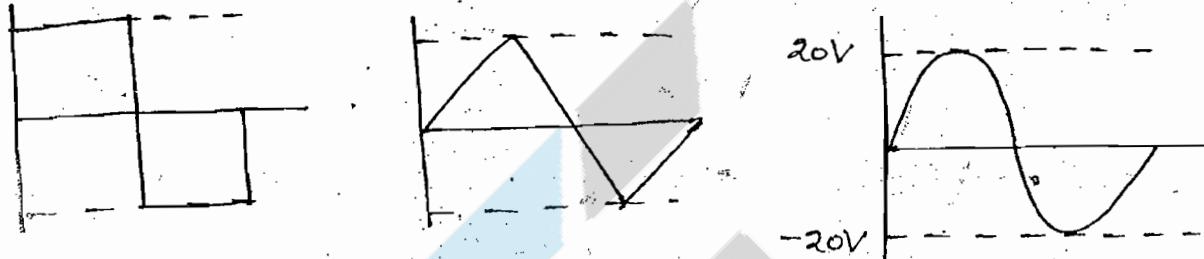

$$\text{Form factor} = \frac{V_{RMS}}{V_{av}}$$


- Avg. Value for complete unsymmetrical wave = 0
- Hence we can find Average value only for half cycles for symmetrical waveform

$$V_{av} = \frac{1}{\pi} \int_0^{\pi} V dt$$

[For current and voltage waveform]

Unsymmetrical Wave :-

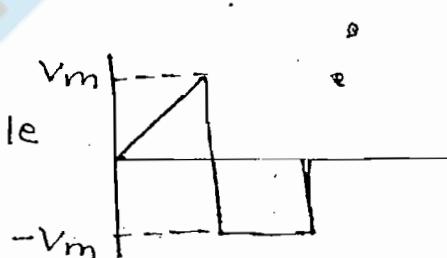- Finding average value of  $V_m$  unsymmetrical wave angle of complete cycle is considered



$$V_{av} = \frac{1}{2\pi} \left[ \int_0^{\pi} V dt + \int_{\pi}^{2\pi} V dt \right]$$


PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. 9810651870

ques:- Find Avg. value of following waveforms


$$\rightarrow V_{av} = \frac{1}{\pi} \int_0^{\pi} v dt$$

$$V_{av} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t dt$$
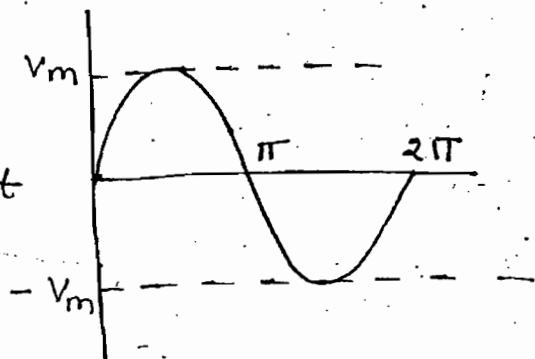
$$\Rightarrow V_{av} = \boxed{\frac{2V_m}{\pi}}$$




$$\rightarrow V_{av} = \frac{V_m}{2}$$

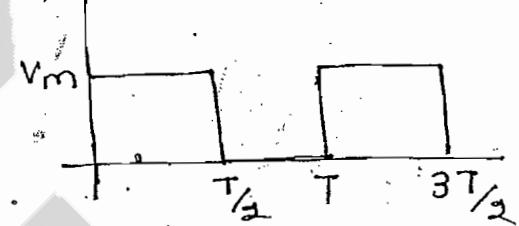


$$\rightarrow V_{av} = \frac{2V_m}{\pi}$$

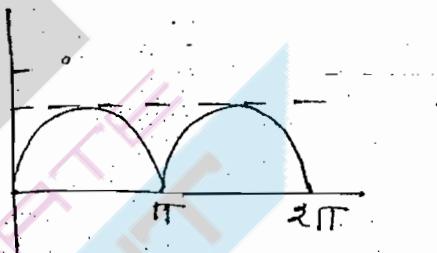
PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Cont: 9876543210



$$\rightarrow V_{av} = \frac{V_m}{\pi}$$

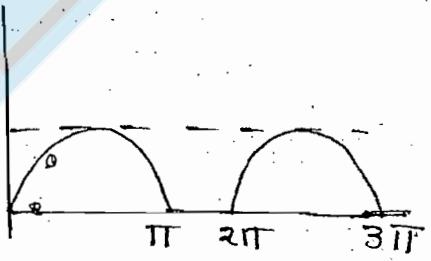


$$\rightarrow V_{rms} = V_{av} = V_m$$

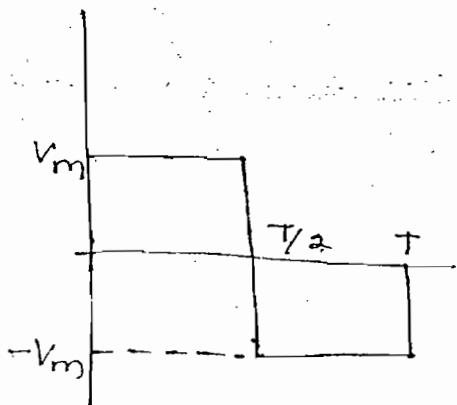


$$\rightarrow V_{av} = \frac{1}{4} \left[ \int_0^2 10dt + \int_2^4 20dt \right] = 20V$$


$$V_{av} = 15$$

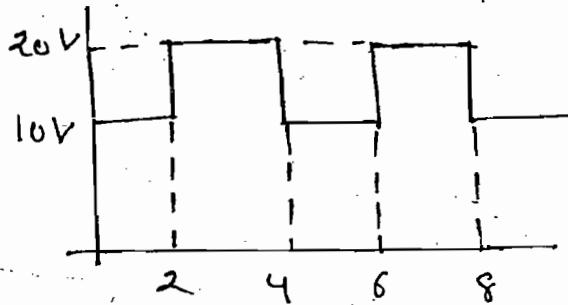


$$\rightarrow V_{av} = \frac{V_m}{2}$$

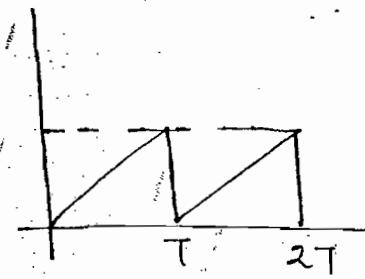

$$\rightarrow V_{av} = \frac{V_m}{2}$$

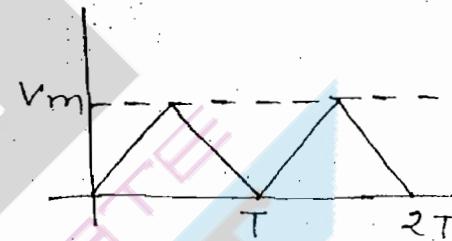

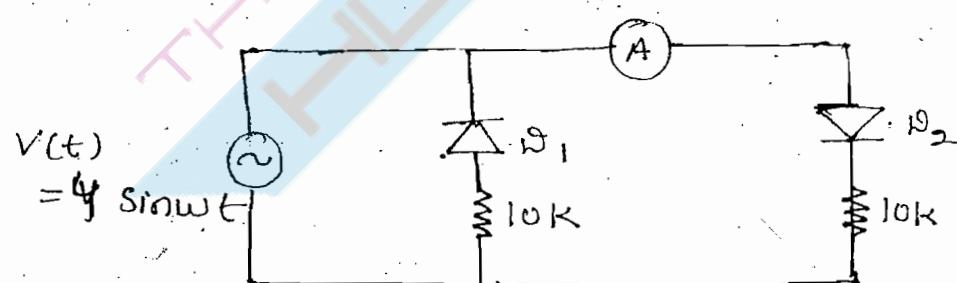ques - When the circuit is having ideal diodes and avg. value of indicating ammeter. Find reading of ammeter



$$\text{Soln: } V_{av} = \frac{V_m}{\pi} = \frac{4}{\pi}$$

$$I_{av} = \frac{V_{av}}{10 \times 10^3} = \frac{4/\pi}{10 \times 10^3}$$

$$\Rightarrow I_{av} = \frac{0.4}{\pi} \text{ mA}$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. 9899999999

Note:-

For sine wave

$$\text{Form factor} = \frac{V_{\text{RMS}}}{V_{\text{av}}} = \frac{\frac{V_m}{\sqrt{2}}}{\frac{2V_m}{\pi}} = 1.11$$




$$\text{Peak factor} = \frac{V_m}{V_{\text{RMS}}} = \frac{V_m}{\frac{V_m}{\sqrt{2}}} = \sqrt{2}$$

### Power System :-

[11 kV, 33 kV, 66 kV, 132 kV, 220 kV] → basis of form factor

→ To justify above shape of waveform form factor and peak factor concepts are introduced

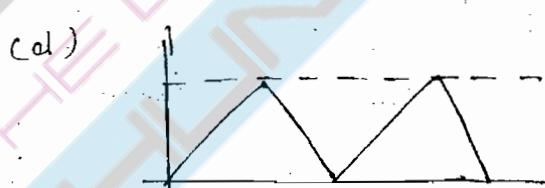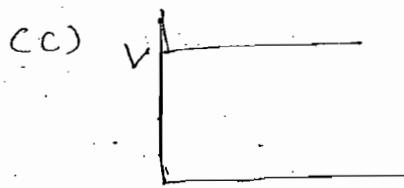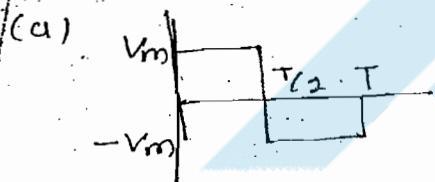Ques:- Which of the following waveforms have  
form factor = peak factor?



Soln:- (a)  $V_{\text{RMS}} = V_{\text{av}} = V_m$

Form factor = 1

Peak factor = 1

$$(b) V_{\text{RMS}} = \frac{V_m}{\sqrt{2}}, \quad V_{\text{av}} = \frac{V_m}{2}$$

$$\text{Form factor} = \frac{V_{\text{RMS}}}{V_{\text{av}}} = \sqrt{2}$$

$$\text{Peak factor} = \frac{V_m}{V_{\text{RMS}}} = \sqrt{2}$$

$$(c) V_{\text{RMS}} = V_m = V_{\text{av}}$$

$$= V$$

Form factor = 1

Peak factor = 1

$$(d) V_{\text{RMS}} = \frac{V_m}{\sqrt{3}}$$

$$V_{\text{av}} = V_m/2$$

$$\text{Form factor} = 2/\sqrt{3}$$

$$\text{Peak factor} = \sqrt{3}$$

## AC Source Across Resistor:-

$$i(t) = \frac{V(t)}{R}$$

$$i(t) = \frac{V_m}{R} \sin \omega t$$

$$\Rightarrow i(t) = I_m \sin \omega t$$

$$P(t) = V(t) i(t)$$

$$P(t) = V_m \sin \omega t I_m \sin \omega t$$

$$P(t) = \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} P(t) d\omega t$$

$$\Rightarrow P_{av} = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} = V_{RMS} I_{RMS}$$

e.g. —  $f = 50 \text{ Hz}$  or  $\text{c/sec}$

$\Rightarrow f_p = 100 \text{ Hz}$  (Power of frequency)

→ When voltage or current completes one cycle then power completes two cycle.


## AC Source across Inductor:-

$$V = L \frac{di}{dt}$$


$$\therefore V(t) = L \frac{d}{dt} (I_m \sin \omega t)$$

$$V(t) = \omega L I_m \cos \omega t \quad (X_L = \omega L)$$

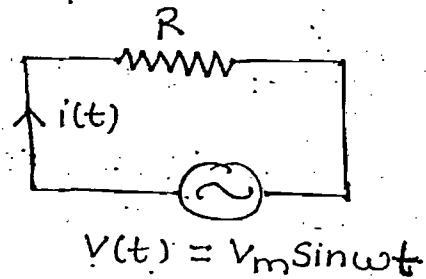
$$V(t) = V_m \sin (\omega t + 90^\circ)$$



$$V(t) = V_m \sin \omega t$$

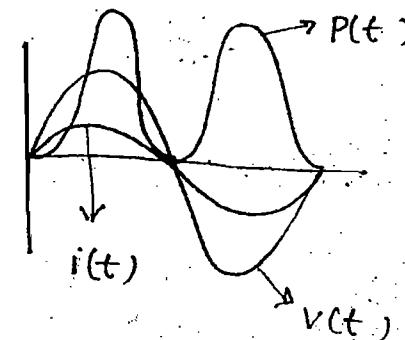

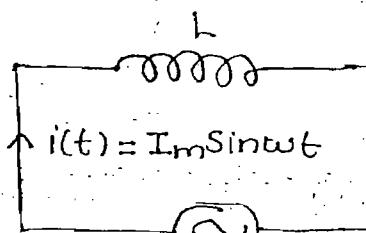BEST PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9810000072



$$i(t) = I_m \sin \omega t$$

$$V(t)$$

$$\begin{aligned}
 P &= I^2 R = VI \cos \theta \\
 Q_L &= I^2 X_L = VI \sin \theta \\
 S &= I^2 Z = VI^* \rightarrow \text{conjugate}
 \end{aligned}$$

eg:-  $V = 10 \angle 40^\circ$        $i = 5 \angle 15^\circ$

$$S = Vi$$

$$\Rightarrow S = 10 \angle 40^\circ \cdot 5 \angle 15^\circ$$

$$\Rightarrow S = 50 \angle 55^\circ$$


Wrong

$$S = Vi^*$$

$$\Rightarrow S = 10 \angle 40^\circ \cdot 5 \angle -15^\circ$$

$$\Rightarrow S = 50 \angle -25^\circ$$

Correct

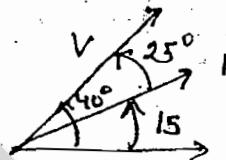


### R-C Series Circuit :-

By KVL


$$V = V_R \angle 0^\circ + V_C \angle -90^\circ$$

$$\Rightarrow IZ = IR - jIX_C$$

$$\Rightarrow Z = R - jX_C$$

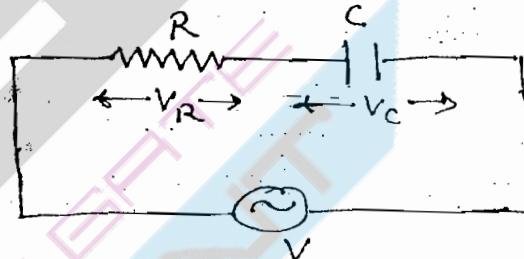


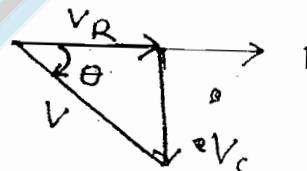PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contt. 242110)




$$V = \sqrt{V_R^2 + V_C^2}$$
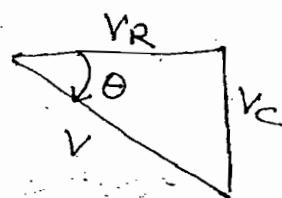
$$\theta = \tan^{-1} \left( \frac{-V_C}{V_R} \right)$$



$$Z = \sqrt{R^2 + X_C^2}$$

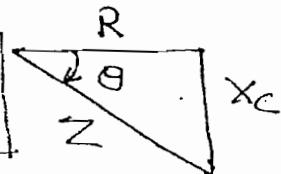
$$\theta = \tan^{-1} \left( \frac{-X_C}{R} \right)$$



$$S = \sqrt{P^2 + Q^2}$$

$$\theta = \tan^{-1} \left( -\frac{Q_c}{P} \right)$$

$$I^2 R = P$$

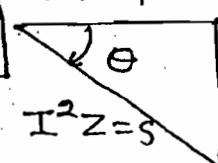


$$Q_c = I^2 X_C$$

Power Factor :-

$$\text{Power Factor} = \cos \theta = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S} \rightarrow \text{leading}$$

ques:- Find voltage across inductor

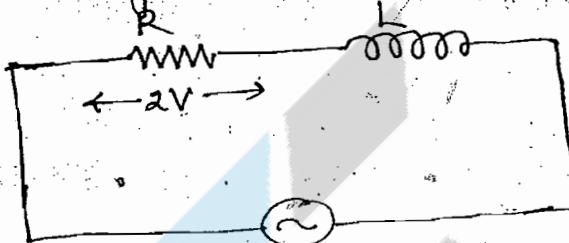

PHOTOSTAT  
All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont-S... E...


Soln:-

$$V_m = 10$$

$$V_{RMS} = \frac{10}{\sqrt{2}} = V$$

$$V = \sqrt{V_R^2 + V_L^2}$$
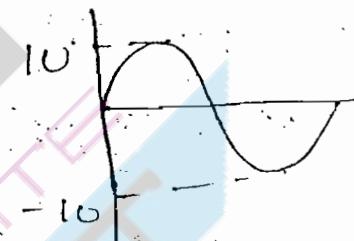
$$\Rightarrow \frac{10}{\sqrt{2}} = \sqrt{2^2 + V_L^2} \Rightarrow V_L = \sqrt{46} V$$



ques:- Find circuit element for given voltage and current equations



$$V(t) = 9 \sin(t + 45^\circ)$$

$$i(t) = 3 \sin(t - 45^\circ)$$

Soln:-

$$X_L = \frac{V}{i}$$

$$X_L = \frac{9/\sqrt{2}}{3/\sqrt{2}}$$

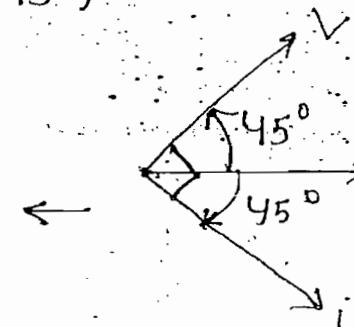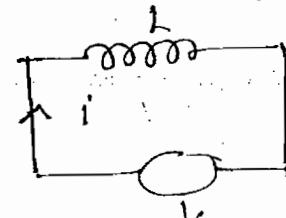

$$\Rightarrow X_L = 3 = \omega L \Rightarrow L = 3 \quad (\because \omega = 1)$$

Ques:- Find circuit element for given voltage and current equations

$$V(t) = 9 \sin(t + 30^\circ)$$

$$i(t) = 3 \sin(2t + 60^\circ)$$

Note:-

By using above equations it is not possible to design the network since frequency of voltage and current are unequal.

Ques:- Find active power, reactive power and apparent power by using following equations:-

$$V(t) = 9 \sin(t + 30^\circ)$$


$$i(t) = 3 \sin(t + 60^\circ)$$

Soln:-

$$P = VI \cos\theta$$

$$\Rightarrow P = \frac{9}{\sqrt{2}} \cdot \frac{3}{\sqrt{2}} \cos 30^\circ$$
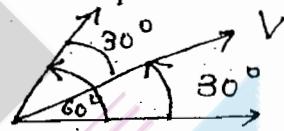
$$\Rightarrow P = 27 \times \frac{\sqrt{3}}{2}$$



→ R-C Circuit (I leading)

$$\alpha_c = VI \sin\theta$$

$$\Rightarrow \alpha_c = \frac{9}{\sqrt{2}} \frac{3}{\sqrt{2}} \sin 30^\circ$$

$$\Rightarrow \alpha_c = \frac{27}{4}$$

$$S = \sqrt{P^2 + \alpha_c^2} =$$

Alternate Way:-

$$Z = \frac{V}{I}$$

$$Z = \frac{9/\sqrt{2}}{3/\sqrt{2}}$$

$$Z = 3$$

$$\cos\theta = \frac{R}{Z}$$

$$\Rightarrow \cos 30^\circ = R/3 \Rightarrow R = 3 \cos 30^\circ$$

$$X_C = \sqrt{Z^2 - R^2}$$


$$P = I^2 R = (3/\sqrt{2})^2 R$$

$$\alpha_c = I^2 X_C = (3/\sqrt{2})^2 X_C$$

Ques - Find ammeter reading and power factor of the ckt shown

$$V_1(t) = 10 \sin t$$

$$V_2(t) = 10\sqrt{5} \sin 2t$$

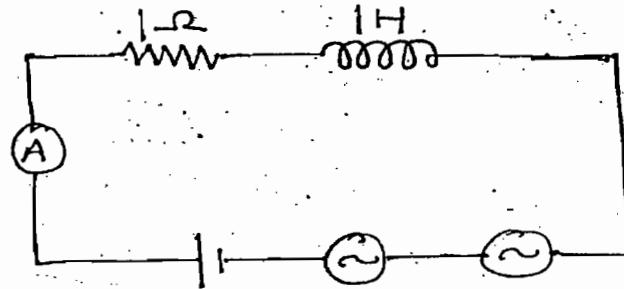

Soln - When multiple sources are present then at one time only one source is activated.

For  $V_1$        $X_{L1} = \omega_1 L = 1$

$$Z_1 = \sqrt{R^2 + X_{L1}^2} = \sqrt{1^2 + 1^2} = \sqrt{2}$$

$$I_1 = \frac{V_1}{Z_1} = \frac{10/\sqrt{2}}{\sqrt{2}} = 5$$

For  $V_2$        $X_{L2} = \omega_2 L = 2$

$$Z_2 = \sqrt{R^2 + X_{L2}^2} = \sqrt{5}$$

$$I_2 = \frac{V_2}{Z_2} = \frac{10\sqrt{5}/\sqrt{2}}{\sqrt{5}} = \frac{10}{\sqrt{2}}$$

For  $V_3$        $19C \rightarrow \omega = 6$

$$I_3 = \frac{V_3}{R} = \frac{5}{1} \Rightarrow I_3 = 5$$


When assume frequency are present then directly add them But above question different frequency are present Hence use general formula  $(i = \sqrt{i_1^2 + i_2^2 + i_3^2} = 10A)$  Ans

For power factor use power triangle not impedance triangle (same reason)

$$P.F = \cos \theta = P/S \Rightarrow \cos \theta = IR/V_i = \frac{IR}{V} = 0.55$$

$$V = \sqrt{V_1^2 + V_2^2 + V_3^2} = \sqrt{\left(\frac{10}{\sqrt{2}}\right)^2 + \left(\frac{10\sqrt{5}}{\sqrt{2}}\right)^2 + 5^2}$$

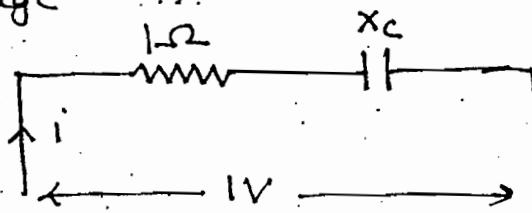Cause:- In the circuit shown power dissipation in the resistor is 500 mW. Find angle of current w.r.t. source voltage.



$$\text{SOLN: } P = i^2 R \Rightarrow P = \left(\frac{V}{Z}\right)^2 R$$

$$\Rightarrow P = \frac{V^2}{R^2 + X_c^2} R$$

$$\Rightarrow \frac{500}{1000} = \frac{I^2}{I^2 + X_c^2} \quad (1) \Rightarrow X_c = 1$$

$$Z = R - jX_c$$

$$Z = 1 - j1 \Rightarrow \theta = \tan^{-1}(-\frac{1}{1}) = -45^\circ$$

$$i = \frac{V \angle 0^\circ}{Z \angle -45^\circ} = \frac{V \angle 45^\circ}{Z} \Rightarrow \theta = 45^\circ \text{ Ans}$$


R-L-C Series Circuit:-

By KVL

$$V = V_R \angle 0^\circ + V_L \angle 90^\circ + V_C \angle -90^\circ$$



$$\Rightarrow IZ = IR + jIX_L - jX_C$$

$$\Rightarrow Z = R + j(X_L - X_C)$$

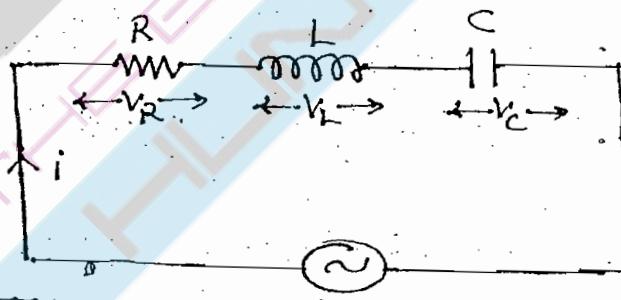

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

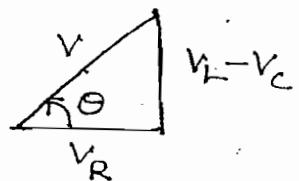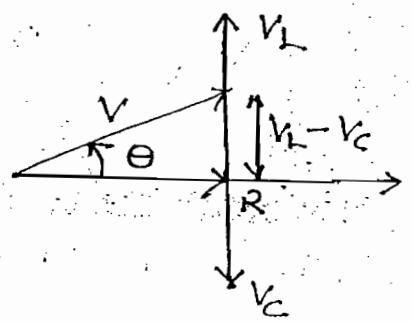
$$\theta = \tan^{-1} \left( \frac{V_L - V_C}{V_R} \right)$$



DIGITAL PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Cont: 9710222223

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$
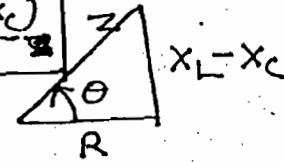
$$\theta = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$



$$S = \sqrt{P^2 + (Q_L - Q_C)^2}$$

$$\theta = \tan^{-1} \left( \frac{Q_L - Q_C}{P} \right) \Rightarrow Z = \sqrt{I^2 R^2 + (Q_L - Q_C)^2}$$


Power factor :-

$$\cos \theta = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S}$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 0713122270

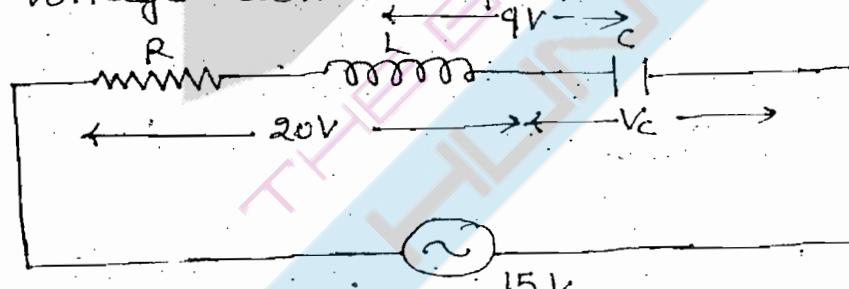- (i) If  $V_L > V_C \rightarrow$  lagging power factor
- (ii) If  $V_L < V_C \rightarrow$  leading power factor
- (iii) If  $V_L = V_C \rightarrow$  unity power factor

Ques:- Find voltage across capacitor of circuit shown



- (a) 7 (b) 25 (c) 7 or 25 (d) 20

Soln:-  $V_L - V_C = 9V$

$V = 15V$


$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\Rightarrow 15^2 = V_R^2 + 9^2$$

$$V_R = \sqrt{225 - 81} = 12V$$

$$20 = \sqrt{V_R^2 + V_L^2} = \sqrt{12^2 + V_L^2} \Rightarrow V_L = 16$$
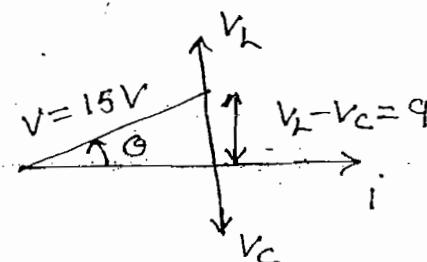
$$V_L - V_C = 9 \Rightarrow V_C = 7V, Ans$$



## Lecture - 5

PHOTOSTAT  
 (All Study Material Available)  
 A-163 Lado Sarai, New Delhi  
 Cont: 9711020276

### R-L Parallel Circuit:-

By KCL



$$I = I_R \angle 0^\circ + I_L \angle 90^\circ$$

$$\Rightarrow \frac{V}{Z} = \frac{V}{R} - j \frac{V}{X_L}$$

$$\Rightarrow VY = VG_1 - jVB_L$$

$$Y = G_1 - jB_L$$

mho      mho      mho

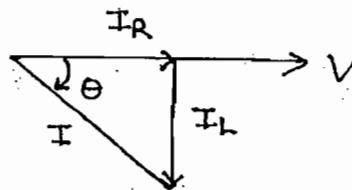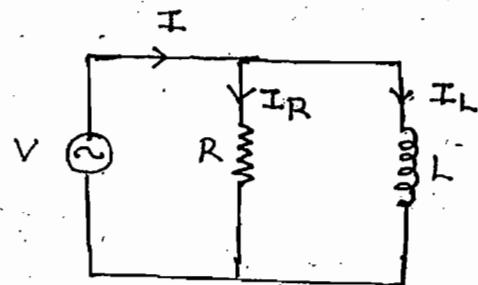

$$I = \sqrt{I_R^2 + I_L^2}$$

$$\theta = \tan^{-1} \left( \frac{-I_L}{I_R} \right)$$

$$I_R = VG_1$$

$$I_L = VB_L$$

$$Y = \sqrt{G_1^2 + B_L^2}$$

$$\theta = \tan^{-1} \left( \frac{-B_L}{G_1} \right)$$



$$S = \sqrt{P^2 + Q_L^2}$$

$$\theta = \tan^{-1} \left( \frac{-Q_L}{P} \right)$$

$$G_1 V^2 G_1 = P$$

$$S = V^2 Y \quad B_L V^2 = Q_L$$

### Power factor:-


$$\cos \theta = \frac{I_R}{I} = \frac{G_1}{Y} = \frac{P}{S} = \text{Lagging}$$

### R-C Parallel circuit:-

By KCL

$$I = I_R \angle 0^\circ + I_C \angle 90^\circ$$
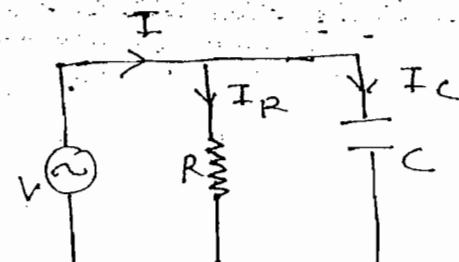
$$\Rightarrow \frac{V}{Z} = \frac{V}{R} + j \frac{V}{X_C}$$




PHOTOSTAT  
 (All Study Material Available)  
 A-163 Lado Sarai, New Delhi  
 Cont: 9711020276

$$\Rightarrow VY = VG_I + jVB_C$$

$$\Rightarrow Y = G_I + jB_C$$


↓      ↓      ↓  
Mho   Mho   Mho

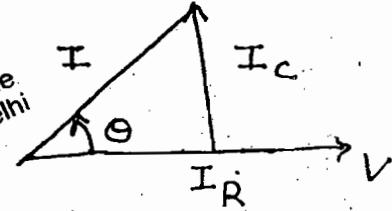EASY T PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 011-26111111




$$I = \sqrt{I_R^2 + I_C^2}$$
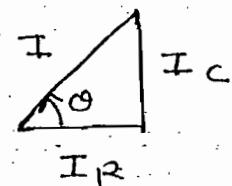
$$\theta = \tan^{-1} \left( \frac{I_C}{I_R} \right)$$




$$Y = \sqrt{G_I^2 + B_C^2}$$
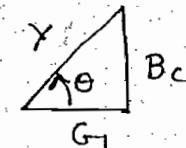
$$\theta = \tan^{-1} \left( \frac{B_C}{G_I} \right)$$



$$S = \sqrt{P^2 + Q_C^2}$$
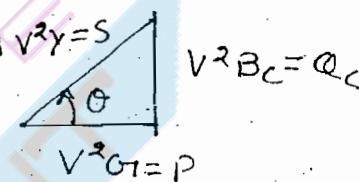
$$\theta = \tan^{-1} \left( \frac{Q_C}{P} \right)$$



Power Factor  $\Rightarrow$

$$\cos \theta = \frac{I_R}{I} = \frac{G_I}{Y} = \frac{P}{S} = \text{leading}$$

RLC Parallel Circuit:



By KCL

$$I = I_R \angle 0^\circ + I_L \angle -90^\circ + I_C \angle +90^\circ$$

$$\Rightarrow \frac{V}{Z} = \frac{V}{R} - j \frac{V}{X_L} + j \frac{V}{X_C}$$


$$\Rightarrow VY = V [G_I + j(B_C - B_L)]$$

$$\Rightarrow Y = G_I + j(B_C - B_L)$$

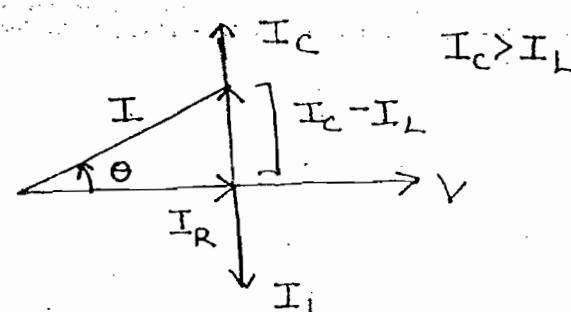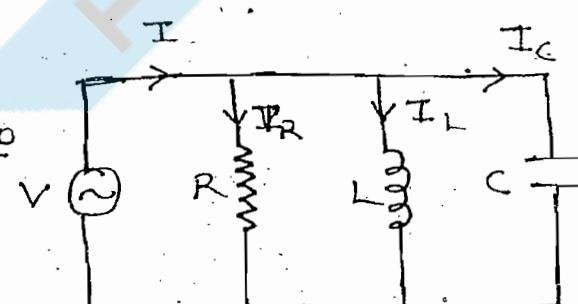


$$I = \sqrt{I_R^2 + (I_C - I_L)^2}$$
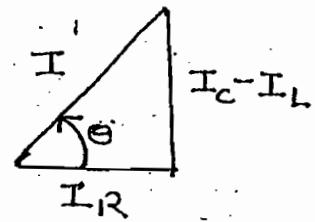
$$\theta = \tan^{-1} \left( \frac{I_C - I_L}{I_R} \right)$$



$$Y = \sqrt{G^2 + (B_C - B_L)^2}$$
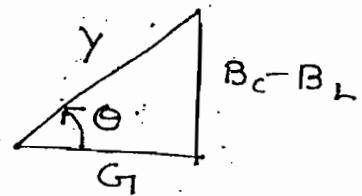
$$\theta = \tan^{-1} \left( \frac{B_C - B_L}{G} \right)$$



$$\text{Power Factor} = \cos\theta = \frac{I_R}{I} = \frac{G}{Y} = \frac{P}{S}$$

(I)  $I_C > I_L \rightarrow$  leading

(II)  $I_C < I_L \rightarrow$  lagging

(IV)  $I_C = I_L \rightarrow$  Unity Power factor


Note:-

When combinational elements are present then we can't directly find conductance, admittance etc. Then following procedure is used

$$I_1 = \left( \frac{V}{R_1 + jX_L} \right) \left( \frac{R_1 - jX_L}{R_1 + jX_L} \right)$$

$$\Rightarrow \frac{V_1}{Z_1} = V \left[ \frac{R_1}{R_1^2 + X_L^2} - j \frac{X_L}{R_1^2 + X_L^2} \right]$$

$$\Rightarrow Y_1 = G_1 - jB_L$$

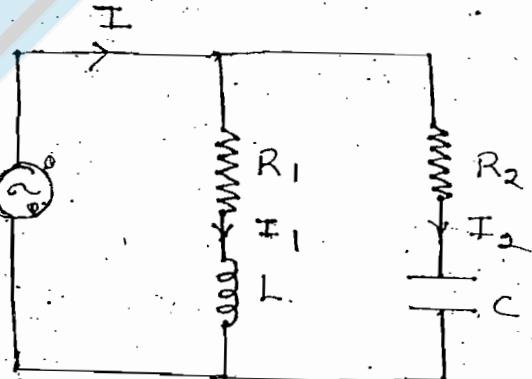

$$I_2 = \frac{V}{R_2 - jX_C} \frac{R_2 + jX_C}{R_2 - jX_C}$$

$$\Rightarrow \frac{V}{Z_2} = V \left[ \frac{R_2}{R_2^2 + X_C^2} + j \frac{X_C}{R_2^2 + X_C^2} \right]$$

ELECTRICAL PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. 9899900000

$$Y_2 = G_{12} + jB_C$$

$$I = I_1 + I_2$$


$$\Rightarrow VY_{eq} = VY_1 + VY_2$$

$$\Rightarrow Y_{eq} = Y_1 + Y_2$$

$$\Rightarrow Y_{eq} = (G_1 + G_{12}) + j(B_C - B_L)$$

PHOTOSTAT  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont: 9899999999

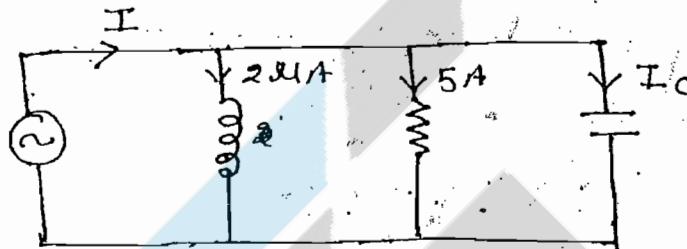Ques: — Find  $I_c$  and  $I$  of the circuit shown



Soln:-

$$I_3 = \sqrt{5^2 + I_c^2} \Rightarrow I_c = 12A$$

$$I = \sqrt{I_R^2 + (I_c - I_L)^2}$$

$$\Rightarrow I = \sqrt{5^2 + (12 - 2\text{mA})^2} = 13 A$$

Note:-

A.C  $\rightarrow$  (KVL, KCL)  $\rightarrow$  Phasor sum

D.C  $\rightarrow$  (KVL, KCL)  $\rightarrow$  Arithmetic sum

Ques: — Find capacitance of

the capacitor when power factor of the circuit


is -0.8 lagging

$$V(t) = 5\sin t$$

Soln:- For Branch-1

$$X_L = \omega L = 1$$
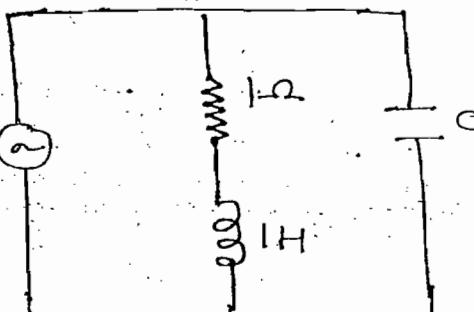
$$G_1 = \frac{R_1}{R_1^2 + X_L^2} = \frac{1}{1^2 + 1^2} = \frac{1}{2}$$



$$B_L = \frac{X_L}{R^2 + X_L^2} = \frac{1}{1^2 + 1^2} = \frac{1}{2}$$

$$Y_1 = G_1 - jB_L$$

$$\Rightarrow Y = \frac{1}{2} - j\frac{1}{2}$$

For Branch-2

$$Y_2 = +jB_C$$

$$Y_2 = j \frac{1}{X_C} = j\omega C \Rightarrow Y_2 = \omega C$$

$$Y_{eq} = Y_1 + Y_2$$

$$\Rightarrow Y_{eq} = \frac{1}{2} + j\left(C - \frac{1}{2}\right)$$

$$\cos \theta = \frac{G_1}{\sqrt{G^2 + (B_C - B_L)^2}}$$

$$\Rightarrow 0.8 = \frac{\frac{1}{2}}{\sqrt{(Y_2)^2 + (C - \frac{1}{2})^2}}$$

$$\Rightarrow C = \frac{7}{8} \text{ or } \frac{1}{8}$$


Since  $B_L > B_C$

$$\frac{1}{2} > C$$

Hence,  $C = \frac{1}{8}$  Ans

Ques Find voltage across A and B of the circuit shown (a) 55 (b) 56 (c) 60 (d) 65

Soln:-

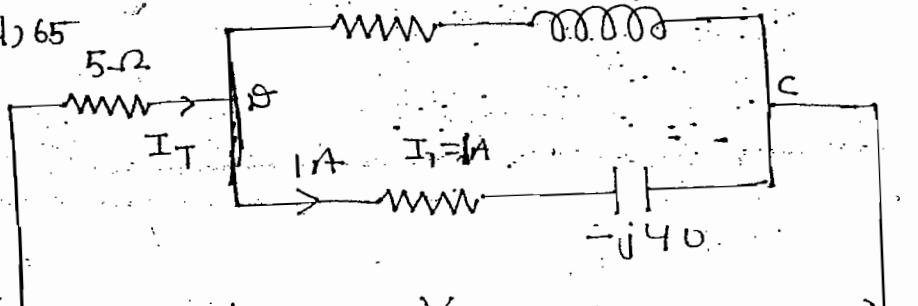

Apply current division technique.

$$I_1 = I_T \frac{30 + j40}{30 + j40 + 30 - j40} =$$

PHOTOSTAT  
 (All Study Material Available)  
 Cont...  
 A-163 Lado Sarai, New Delhi

$$\Rightarrow I = I_T \cdot \frac{50 \lfloor \tan^{-1}(4/3) \rfloor}{60}$$

$$\Rightarrow I_T = \frac{60}{50 \lfloor \tan^{-1}(4/3) \rfloor} = 1.2 \lfloor \tan^{-1}(-4/3) \rfloor$$

$$V_{AB} = I_T \times 5$$

$$\Rightarrow V_{AB} = (1.2 \times 5) \lfloor \tan^{-1}(-4/3) \rfloor$$

$$\Rightarrow V_{AB} = 6 \lfloor \tan^{-1}4/3 \rfloor$$

$$V_{BC} = (30 - j40) \text{ } \Omega$$

$$V_{BC} = 50 \lfloor \tan^{-1}(-4/3) \rfloor$$

Angles are same hence they can be added

$$V_{AB} = V_{AC} = \cancel{V_{AB}} + V_{BC}$$

$$\Rightarrow V_{AB} = 56 \lfloor \tan^{-1}(-4/3) \rfloor \text{ Ans}$$

Locus Diagram :-

$$X_L = 2\pi f L$$

$$X_L = 0$$



$$Z = R \Rightarrow I = \frac{V}{R}$$

$$\Rightarrow \theta = 0$$

$$X_L \uparrow \quad Z \uparrow \quad I \downarrow$$

$$\theta = \tan^{-1}\left(\frac{X_L}{R}\right)$$
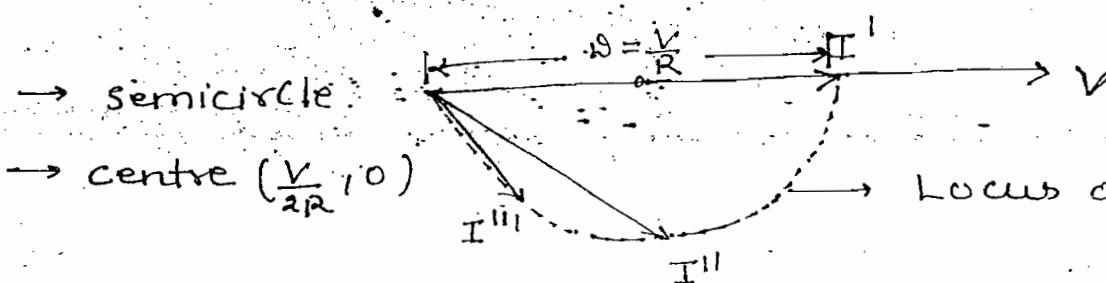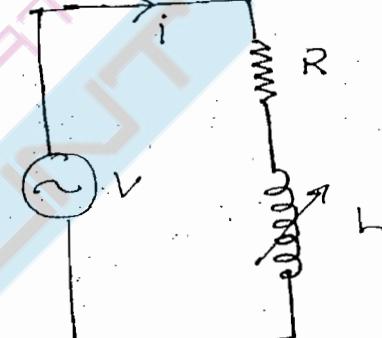
$$X_L \approx \infty \quad Z \approx \infty \quad I = 0$$



→ Locus diagram are useful for analysis and designing of the circuit. e.g.: filters

→ With respect to practical application it is possible to develop the following locus diagram

(i) Current locus diagram

(ii) Voltage locus diagram

(iii) Impedance locus diagram

(iv) Admittance locus diagram

→ The path traced by terminous of current vectors by varying either any of the circuit elements or by varying source frequency is called as current locus.

→ In the above circuit by keeping all the elements constant and by varying source frequency also same shape of the current locus diagram is obtained.

→ Develop current

$$R=0$$

$$Z=X_L$$

$$I = \frac{V}{X_L}$$

$$\theta = 90^\circ$$



$$R \uparrow$$

$$Z \uparrow$$

$$I \downarrow$$

$$\theta = \tan^{-1} \left( \frac{X_L}{R} \right)$$

Locus of the circuit shown

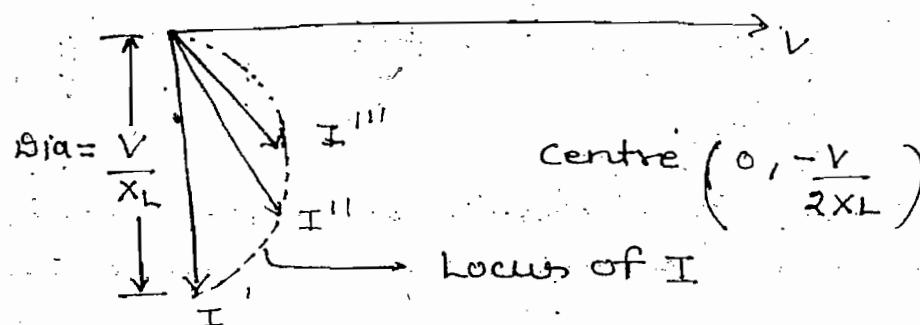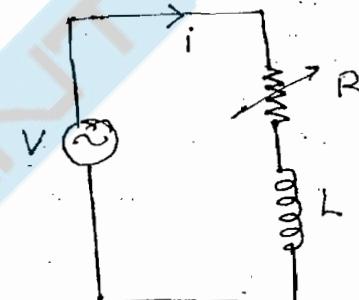

→ Diameter is always due to constant element

Ques:- Develop current locus of  $I_1$  and  $I$  of the circuit shown:-


Soln:-  $R_1 \approx 0.1\Omega$

$$I_1 = \frac{V}{R_1}$$

$$\theta_1 = 0$$

$$I = I_1 + I_2$$


$R_1 \uparrow$	$R_1 \approx \infty$
$I_1 \downarrow$	$I_1 = 0$
$\theta_1 = 0$	$I_2 = I$
$I_2 = \text{constant}$	
$I \downarrow$	

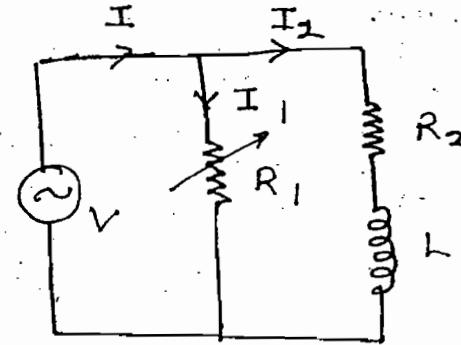

$$I_2 = \frac{V}{R_2 + jX_L}$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont:-)

Note:-

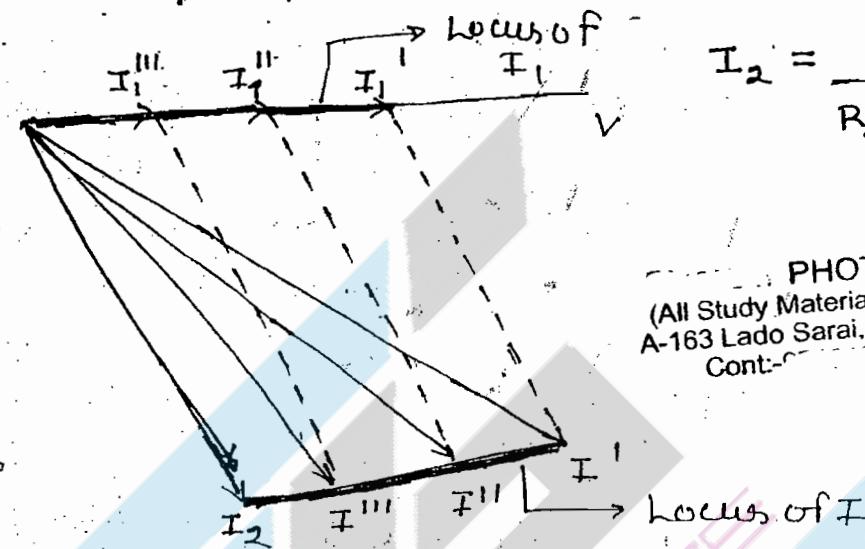

→ When power factor angle is variable the shape of current locus is semi-circle

→ When power factor angle is constant the shape of the current locus diagram is straight line.

Ques:- Develop current locus of  $I_1$  and  $I$  of the circuit shown

Soln:-  $X_C = \frac{1}{2\pi f C}$


$$X_C \approx 0$$

$$I_1 = \frac{V}{R_1}$$

$$\theta_1 = 0$$


$$I = I_1 + I_2$$

$X_C \uparrow$	$X_C \approx \infty$
$Z_1 = \sqrt{R_1^2 + X_C^2} \uparrow$	$I_1 = 0$
$I_1 \downarrow$	$I = I_2$
$\theta_1 = \tan^{-1} \left( -\frac{X_C}{R_1} \right) \uparrow$	
$I_2 = \text{constant}$	
$I_1 \downarrow$	

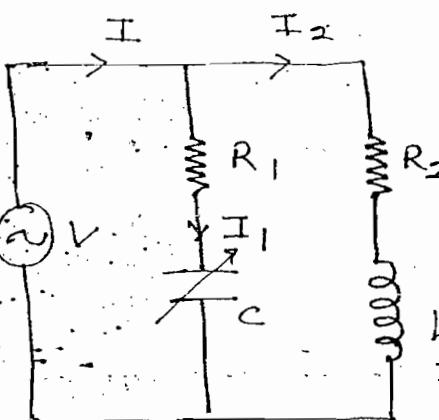


$$I_2 = \frac{V}{R_2 + jX_L}$$

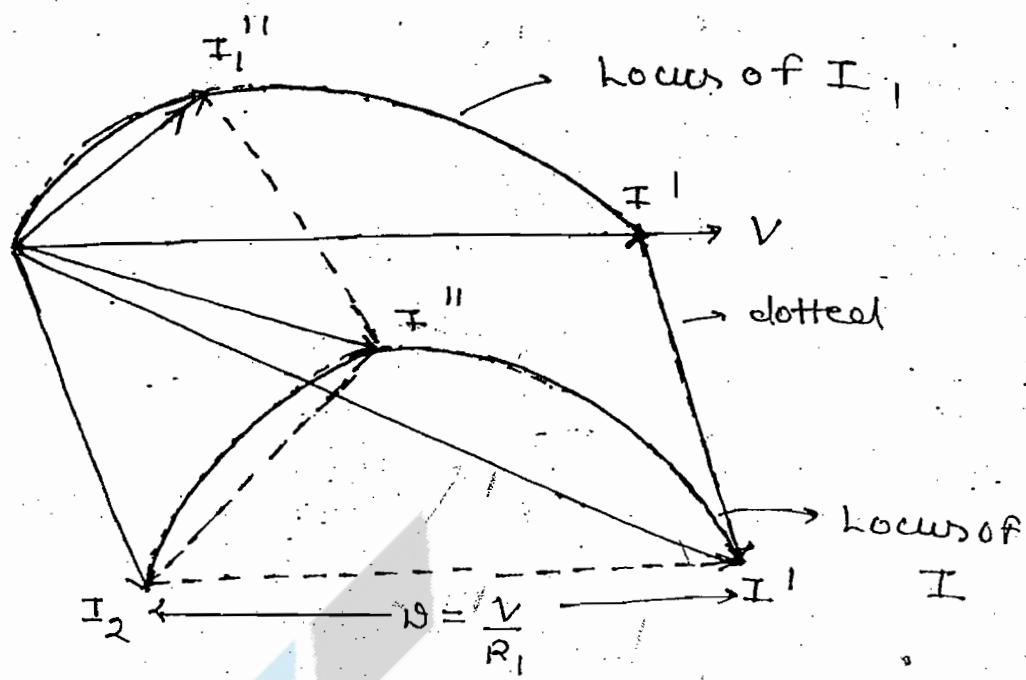Focus only angles not signs but focus on magnitude





ques:- Design a N/w for given current locus diagram

Sol<sup>n</sup>:

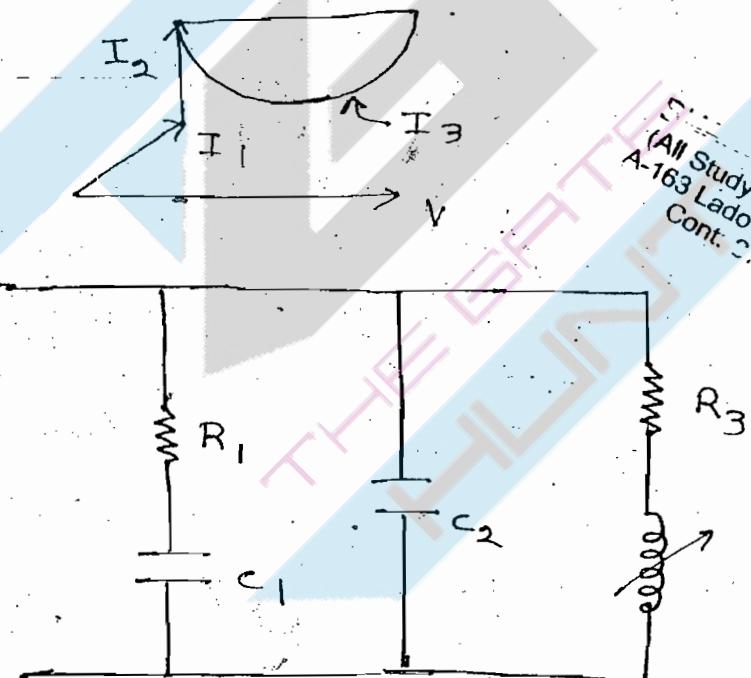

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. 2713-1343

Resonance:-

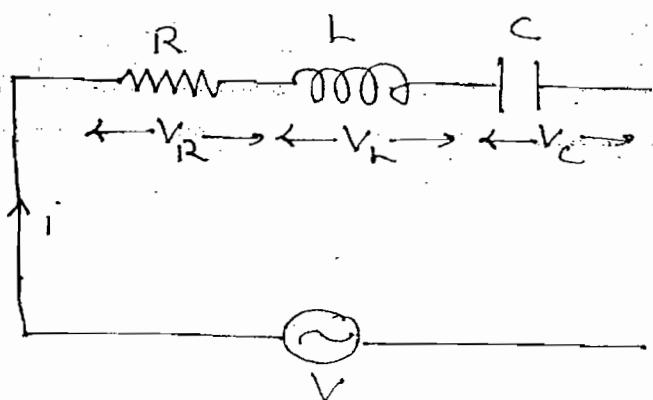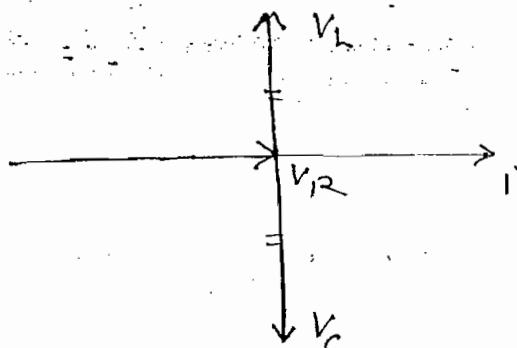

By KVL,  $V = V_R \angle 0^\circ + V_L \angle 90^\circ + V_C \angle -90^\circ$

At resonance,

$$V_L = V_C$$

$$IX_L = IX_C$$

$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

$$\Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

→ For occurrence of resonance in any circuit two energies are required. In RLC circuit inductor is having energy in the form of magnetic field capacitor is having energy in the form of electric field. When these two energies are present at particular frequency wide variations are present in the system is called as resonance.

- The circuit is said to be resonance when source current is in phase with source voltage
- The frequency at which  $X_C = X_L$  is called as resonant frequency
- The resonant frequency indicates rate at which energy transformation is done b/w inductor and capacitor

$$1 \rightarrow Z = R + j(X_L - X_C) \\ = 0$$

$$Z_{min} = R$$

$$2 \rightarrow I_{max} = \frac{V}{Z_{min}} = \frac{V}{R}$$

$$3 \rightarrow \cos \theta = 1$$

$$4 \rightarrow V_R = V$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Corrigendum

5. Net Reactive.
6. Voltage across inductor or voltage across capacitor greater than source. This phenomenon is called as voltage magnification.

Application:-

- Oscillators
- Filters (BP, BE)
- Tuning circuits
- Induction heating

Series RLC circuit

Variation of voltage across inductor and voltage across capacitor w.r.t frequency:-


$$V_C = I X_C$$

$$X_L = 2\pi f L, \quad X_C = \frac{1}{2\pi f C}$$

$$\rightarrow f=0, \quad X_L=0, \quad X_C=\infty$$

$$\rightarrow X = |X_L - X_C| = \infty$$
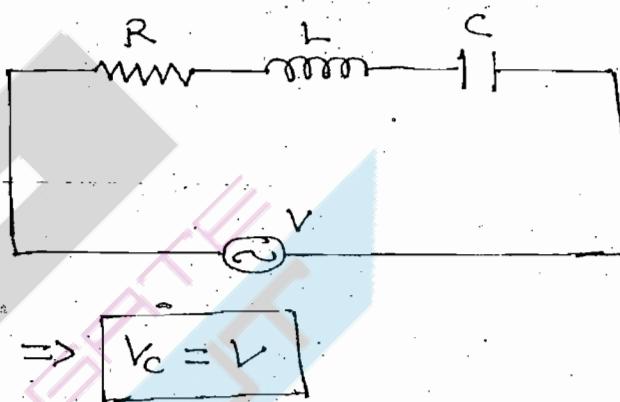
$$\Rightarrow Z = \infty \quad \& \quad I = 0$$



$$\Rightarrow V_C = V$$

For Inductor:-

$$\rightarrow f \uparrow \quad X_L \uparrow \quad X_C \downarrow \quad X = |X_L - X_C| \downarrow \downarrow \quad Z \downarrow \downarrow \quad I \uparrow \uparrow \quad V_C \uparrow$$

(10Ω)      (100Ω)      (90Ω)

$$\rightarrow f \uparrow \uparrow \quad X_L \uparrow \uparrow \quad X_C \downarrow \downarrow \quad Z = R + j(X_L - X_C) \uparrow \uparrow \uparrow \quad I \downarrow \downarrow \downarrow$$

(Very low)

$V_C \downarrow$

$$\rightarrow V_C = \frac{V X_C}{\sqrt{R^2 + (X_L - X_C)^2}} \Rightarrow V_C = \frac{V \frac{1}{\omega C}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad (1)$$

Differentiate eq-(1) w.r.t  $\omega$  and equal to zero we get

$$f_C = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \left(\frac{R^2}{2L}\right)^2}$$

For Inductor :-

$$\rightarrow V_L = I X_L$$

$$\rightarrow X_L = 2\pi f L \quad \& \quad X_C = \frac{1}{2\pi f C}$$

$$\rightarrow f = 0, \quad X_L = 0, \quad X_C = \infty \quad Z = |X_L - X_C| = \infty$$

$$Z = \infty, \quad I = 0,$$

$$V_L = 0$$

$$\rightarrow f \uparrow \quad X_L \uparrow \quad X_C \downarrow \quad Z = |X_L - X_C| \downarrow \downarrow \quad Z \downarrow \downarrow$$

$$(10\Omega) \quad (100\Omega)$$

$$I \uparrow \uparrow \quad V_L \uparrow$$

$$\rightarrow f \uparrow \uparrow \quad X_L \uparrow \uparrow \quad X_C \downarrow \downarrow$$


(Very low)

$$Z = R + j(X_L - X_C) \uparrow \uparrow \quad I_C \downarrow \downarrow \downarrow \quad V_L \downarrow$$

$$\rightarrow V_L = \frac{V X_L}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{V \omega L}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad \text{--- (ii)}$$

Differentiate eq-(ii) w.r.t  $\omega$  and equal to zero
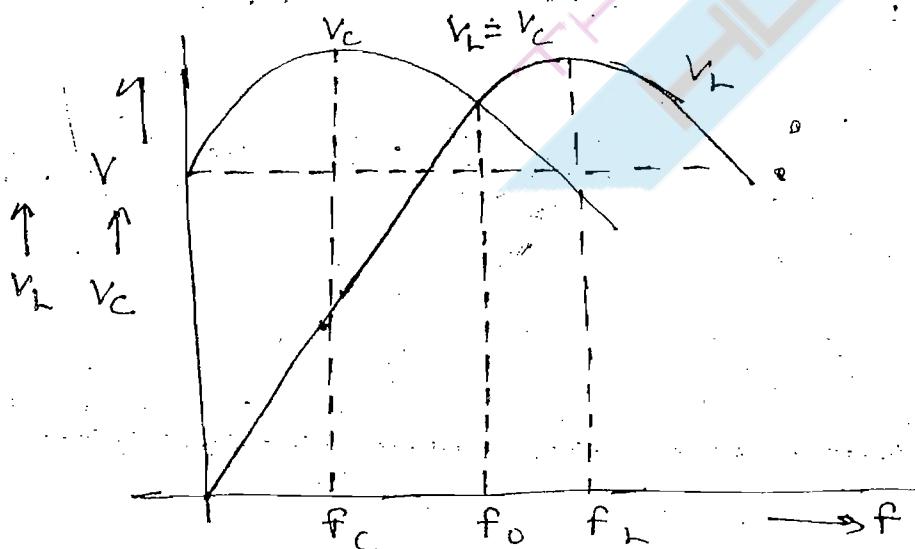
$$f_L = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{1}{1 - \left(\frac{R^2 C}{2L}\right)}}$$



Digitized by PHOTOSTAT  
(All Study Material Available)  
N-163 Lado Sarai, New Delhi  
Cont: 9711111111

## Quality factor :-

→ Q-factor is a ratio of max. energy stored in the circuit to power dissipation per cycle

$$Q =$$

$$i(t) = I_m \sin \omega t \quad \text{--- (i)}$$

$$V_c(t) = \frac{1}{C} \int i(t) dt = \frac{1}{C} \int I_m \sin \omega t dt$$

$$\Rightarrow V_c(t) = -\frac{I_m}{\omega C} \cos \omega t \quad \text{--- (ii)}$$

$$w_g = \frac{1}{2} L I_m^2 + \frac{1}{2} C V_c^2$$

$$\Rightarrow w_g = \frac{1}{2} L (I_m \sin \omega t)^2 + \frac{1}{2} C \left( -\frac{I_m}{\omega C} \cos \omega t \right)^2$$

$$\Rightarrow w_g = \frac{1}{2} L I_m^2 \sin^2 \omega t + \frac{1}{2} C \frac{I_m^2}{\omega^2 C^2} \cos^2 \omega t$$

$$\Rightarrow w_g = \frac{1}{2} L I_m^2 \sin^2 \omega t + \frac{1}{2} L I_m^2 \cos^2 \omega t$$

$$\Rightarrow w_g = \frac{1}{2} L I_m^2$$

$$w_g = \frac{1}{2} C V_{cm}^2$$

$$\begin{aligned} \omega^2 &= \frac{1}{LC} \\ L &= \frac{1}{\omega^2 C} \end{aligned}$$

$$\left( \therefore V_{cm} = \frac{I_m}{\omega C} \right)$$

$$Q = \frac{\frac{1}{2} L I_m^2}{\left( \frac{I_m}{\sqrt{C}} \right)^2 R \frac{1}{\omega}}$$

$$I^2 R = \left( \frac{I_m}{\sqrt{C}} \right)^2 R$$

$$\Rightarrow Q = \frac{\omega L}{R}$$

$$\left( \omega = \frac{1}{\sqrt{C}} \right)$$

$$\Rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q = \frac{\omega L}{R} = \frac{I X_L}{I R} = \frac{V_L}{V_R} = \frac{V_L}{V} \quad (V_R = V)$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont.

$$Q = \frac{V_L \text{ or } V_C}{V}$$

( $\because V_L = V_C$ )

$$Q = \frac{I^2 X_L}{I^2 R} = \frac{Q_L}{P}$$

$$Q = \frac{X_L \text{ or } X_C}{R}$$

( $\because X_L = X_C$ )

$$Q = \frac{X_C}{R} = \frac{1}{\omega R C}$$

$$\rightarrow Q > 1, X_L > R, X_C > R$$

$$\rightarrow Q \propto \frac{1}{\text{Power loss } (I^2 R = P)}$$


$$\rightarrow Q \propto \frac{1}{\text{BW}}$$

Note:-

- To obtain high efficiency circuit is designed with high Q-factor
- To obtain wide BW circuit is designed with low Q-factor

Bandwidth:-

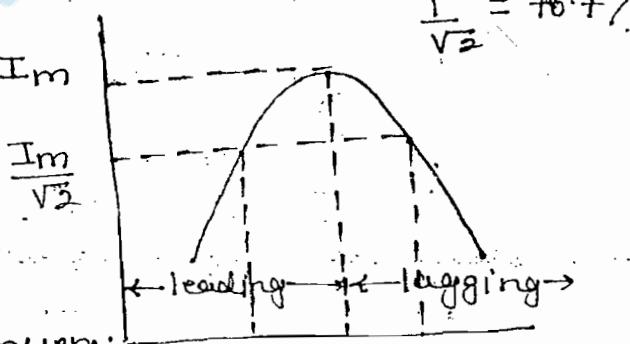- When the curve is Im developed b/w current and frequency then curve is called as resonance curve



- BW is the range of frequencies on either side of the resonant frequencies where the current falls from max. value to 70.7% of the max. value and it is given by

$$BW = f_2 - f_1$$

where  $f_2$  = upper cut-off frequency

$f_1$  = lower " "

$f_1, f_2$  = 3dB points or half power frequencies

1.  $f_0 \rightarrow Im \quad z=R$

$$f_1, f_2 \rightarrow \frac{Im}{\sqrt{2}} \Rightarrow z = \sqrt{2}R$$

2.  $f_0 \rightarrow \cos\theta = 1$

$$f_1, f_2 \rightarrow z = R \pm jx$$

$$z = \sqrt{R^2 + x^2} = \sqrt{2}R$$

$$\Rightarrow x = R$$

w.r.t  $f_1 \rightarrow z = R - jx \quad x=R$

$$\text{Impedance Angle} = \tan^{-1}\left(\frac{-x}{R}\right)$$

$$= -45^\circ$$

$$I = \frac{V_0}{Z \angle -45^\circ} = \frac{V}{Z} \angle +45^\circ$$

Power factor angle = ~~-45~~ 45

$$\Rightarrow \text{Power factor} = \cos 45^\circ = \frac{1}{\sqrt{2}} \rightarrow \text{leading}$$

w.r.t  $f_2$ :

$$f_2 \rightarrow z = R + jx \quad x=R$$

$$\text{Impedance angle} = \theta = \tan^{-1}\left(\frac{x}{R}\right) = +45^\circ$$

$$\text{Power factor angle} = -45^\circ$$

$$\text{Power factor} = \cos(-45^\circ) = \frac{1}{\sqrt{2}} \rightarrow \text{lagging}$$

3.  $f_1 \rightarrow x_c > x_L \quad x=R$

$$\frac{1}{\omega_C} - \omega_L = R \rightarrow (1)$$

BRIARES PHOTOSTAT  
All Study Material Available  
A-163 Lajpat Singh Sarai, New Delhi  
Contd-9718102070

$$f_2 \rightarrow X_L > X_C \quad x=R$$

$$\omega_2 L - \frac{1}{\omega_2 C} = R \rightarrow (II)$$

From (I) & (II)

$$\omega_1 \omega_2 = \frac{1}{LC} \rightarrow (III)$$

$$\Rightarrow \omega_0^2 = \frac{1}{LC} \rightarrow (IV)$$

From (III) & (IV)

$$\omega_0^2 = \omega_1 \omega_2$$

$$\Rightarrow \omega_0 = \sqrt{\omega_1 \omega_2}$$

$$f_0 = \sqrt{f_1 f_2}$$

Add eq (I) & (II)

$$\frac{1}{C} \left[ \frac{1}{\omega_1} - \frac{1}{\omega_2} \right] + L [\omega_2 - \omega_1] = 2R$$

$$\Rightarrow \frac{1}{C} \left[ \frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right] + L [\omega_2 - \omega_1] = 2R$$

$$\Rightarrow L [\omega_2 - \omega_1] + L [\omega_2 - \omega_1] = 2R$$

$$\text{BW} = \omega_2 - \omega_1 = \frac{R}{L} \text{ rad/sec}$$

$$\text{BW} = f_2 - f_1 = \frac{R}{2\pi L} \text{ Hz}$$

$$Q = \frac{\omega_0 L}{R} \Rightarrow Q' = \frac{\omega_0}{R/L}$$

$$\Rightarrow Q = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{f_0}{f_2 - f_1}$$

## Lecture-6

**BHARAT PHOTOSTAT**  
 All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont: 9718102070

By KVL

$$V = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

Diffr w.r.t t.

$$V' = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C}$$

Dividing both sides of L

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = \frac{V'}{L}$$

$$\left( \omega^2 + \frac{R}{L} \omega + \frac{1}{LC} \right) i = 0$$

$$\omega^2 + 2\zeta\omega_n + \omega_n^2 = 0$$

$$2\zeta\omega_n = \frac{R}{L}$$


$$2\zeta \frac{1}{\sqrt{LC}} = \frac{R}{L}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{L}{C}}$$


$$\text{Damping ratio} = \delta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$\boxed{s = \frac{1}{2\zeta}}$$

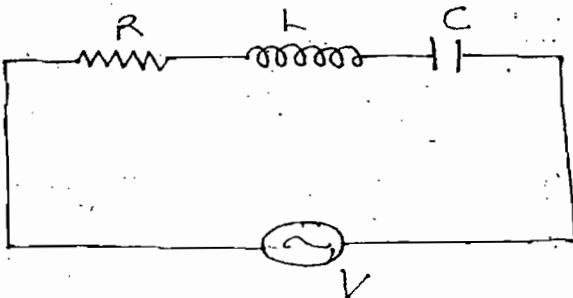Ques: Find  $f_0$ ,  $\zeta$ ,  $s$ , BW,  $f_1, f_2$ , I at  $f_0$



**BHARAT PHOTOSTAT - 9718102070**

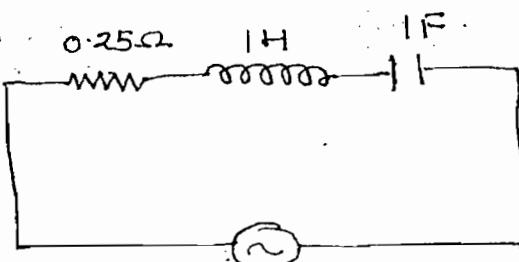

**BHARAT PHOTOSTAT**  
 All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont: 9718102070

$$\text{Soln:- (i) } f_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi}$$

$$(ii) Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{0.25} \sqrt{\frac{1}{1}} = 4$$

$$(iii) S = \frac{1}{2Q} = \frac{1}{8}$$

$$(iv) \text{ BW} = \frac{f_0}{Q} = \frac{1/2\pi}{4} = \frac{1}{8\pi} \text{ Hz}$$

$$(v) f_2 - f_1 = \frac{1}{8\pi}$$

$$f_1 f_2 = f_0^2 = \left(\frac{1}{2\pi}\right)^2$$

$$(f_2 + f_1)^2 - (f_2 - f_1)^2 = 4f_1 f_2$$

$$f_1 =$$


$$f_2 =$$

$$(vi) I = \frac{V}{Z} = \frac{V}{R}, \quad (\text{At Resonance})$$

$$I = \frac{10/\sqrt{2}}{0.25}$$

$$I = \frac{40}{\sqrt{2}}, \text{ Ans.}$$

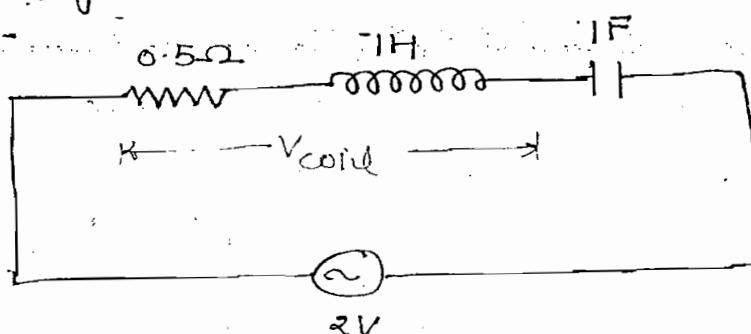ques:- Find voltage across the coil under resonance condition.



Soln:-

$$V_R = V = 2$$

[When nothing is given take it  
as RMS]

$$\textcircled{1} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$\textcircled{2} = \frac{1}{0.5} \sqrt{\frac{1}{1}} = 2$$

$$\textcircled{3} = \frac{V_L}{V}$$

$$\Rightarrow 2 = \frac{V_L}{2}$$

$$\Rightarrow V_L = 4$$

$$V_{\text{coil}} = \sqrt{V_R^2 + V_L^2}$$

$$\begin{aligned}\Rightarrow V_{\text{coil}} &= \sqrt{2^2 + 4^2} \\ &= \sqrt{20}, \text{ Ans.}\end{aligned}$$

PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Cont: 9718102070

PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Cont: 9718102070

## Parallel Resonance :-

Case - (I) :-

$$I_C = I_L$$



$$\frac{V}{X_C} = \frac{V}{X_L} \quad X_L = X_C$$

$$\Rightarrow B_C = B_L$$

$$\omega_C = \frac{1}{\omega_L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec.}$$
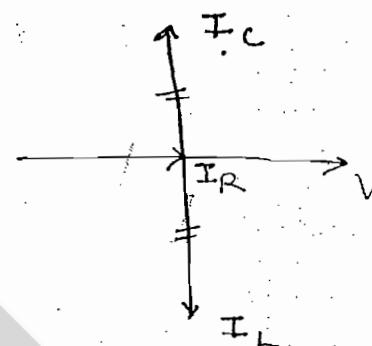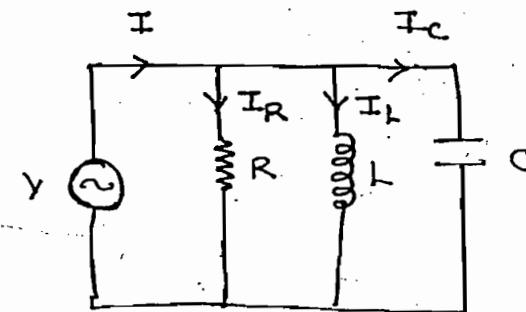
$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$



$$(I) \quad Y = G_T + j \left( B_C - B_L \right)$$

$$Y_{\min} = G_T$$

$$(II) \quad Z_{\max} = \frac{1}{Y_{\min}}$$

$$(III) \quad I_{\min} = \frac{V}{Z_{\max}}$$

$$(IV) \quad \text{case} = 1$$

$$(V) \quad I_R = I$$

$$(VI) \quad \text{Net Reactive current} = 0$$

(VII) Current in inductor or current in capacitor is greater than total current. This phenomena is called as current magnification.

HOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. ~ ~ ~ ~ ~

viii) Parallel Resonance circuit is also called as Anti-Resonance circuit.

Cause-(II):-

$$AB = I_1 \cos\theta_1$$

$$AF = BC = I_1 \sin\theta_1$$

$$AB = I_2 \cos\theta_2$$

$$AK = BF = I_2 \sin\theta_2$$

$$BL = BC$$

$$\frac{X_L}{R_1^2 + X_L^2} = \frac{X_C}{R_2^2 + X_C^2}$$

$$\frac{\omega L}{R_1^2 + (\omega L)^2} = \frac{\omega C}{R_2^2 + (\frac{1}{\omega C})^2}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \sqrt{\frac{R_1^2 - \frac{L}{C}}{R_2^2 - \frac{1}{L/C}}}$$

$$I = VY$$

$$\Rightarrow I = V [ (G_1 + G_2) + j(B_C - B_L) ]$$

$$\Rightarrow I = V \left[ \frac{R_1}{R_1^2 + X_L^2} + \frac{R_2}{R_2^2 + X_C^2} \right]$$




Ans:-  
Cause-(III):-

$$AB = I_1 \cos\theta_1$$

$$AF = BC = I_1 \sin\theta_1$$


$$\cos\theta_1 = \frac{R_1}{Z_1}$$

$$\sin\theta_1 = \frac{X_L}{Z_1}$$

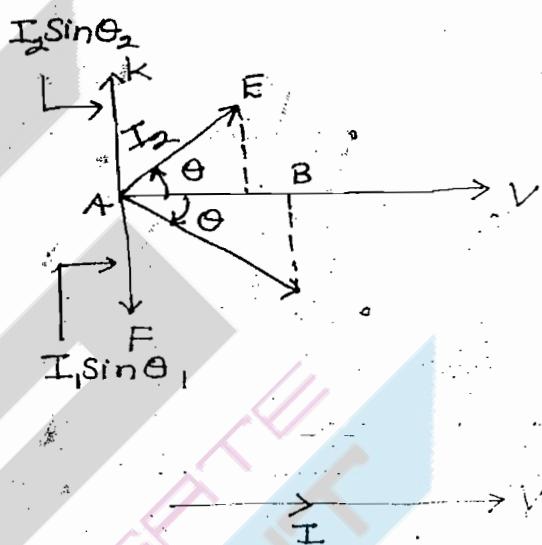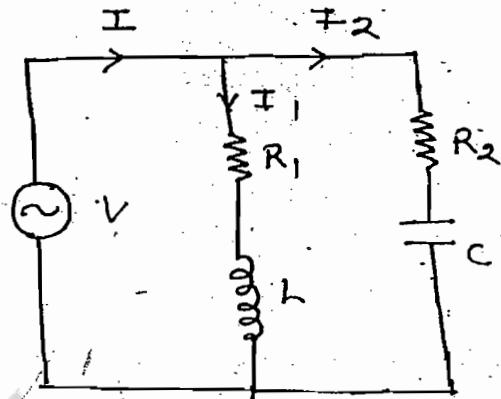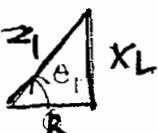

$$I = I_1 \cos\theta_1 + I_2 \cos\theta_2$$

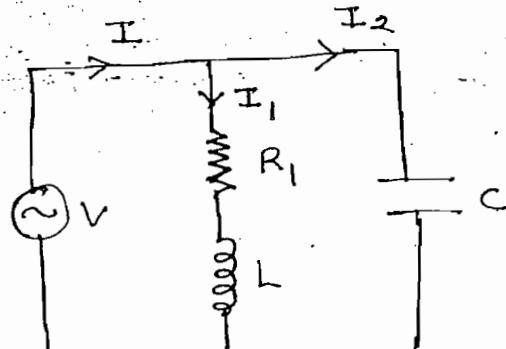PHOTOSTAT  
All Study Material Available  
A-163 Lado Sarai, New Delhi  
Call: 011-26516000



Tank Ckt

$$I_2 = I_1 \sin \theta_1$$

$$\frac{V}{X_L} = \frac{V}{Z_1} \cdot \frac{X_L}{Z_1}$$

$$\Rightarrow Z_1^2 = X_L Z_1$$

$$\Rightarrow Z_1^2 = \frac{V^2 L}{V^2 C}$$

$$\Rightarrow Z_1^2 = \frac{L}{C}$$

$$\Rightarrow Z_1 = \sqrt{\frac{L}{C}}$$

$$\rightarrow B_L = B_C$$

$$Z_1^2 = R_1^2 + X_L^2$$

$$\frac{L}{C} = R_1^2 + (\omega 2\pi f_0 L)^2$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R_1^2}{L^2}}$$

$$\rightarrow I = I_1 \cos \theta_1$$

$$\Rightarrow I = \frac{V}{Z_1} \cdot \frac{R_1}{Z_1}$$

$$\Rightarrow I = \frac{VR_1}{Z_1^2} \quad \Rightarrow \quad I = \frac{VR_1}{L/C}$$


$$\Rightarrow I = \frac{V}{\frac{L}{R/C}}$$

$$\Rightarrow Z_{DyN} = \frac{1}{R/C}$$

Ideal Tank Circuit :-


$$Z_{DyN} = \frac{L}{R/C} = \infty$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

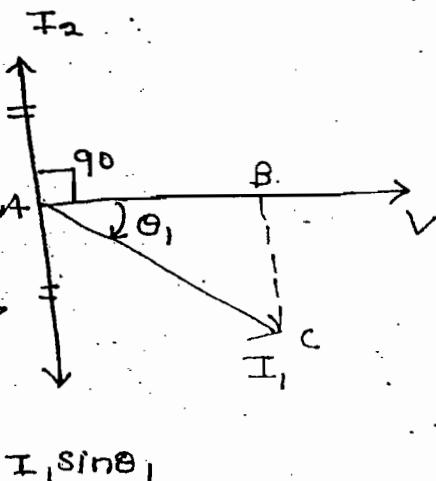

$$I = I_1 \cos \theta_1$$

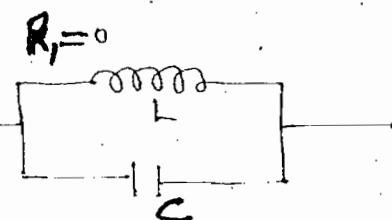PHOTOSTAT  
A-163 Lado Sarai, New Delhi  
(All Study Material Available)




Q-Factor :-

$$Q = \frac{V_L \text{ or } V_C}{V}$$

Series

$$Q = \frac{I_L \text{ or } I_C}{I}$$

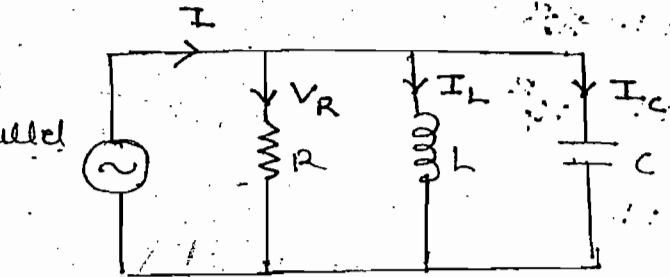

$$Q = \frac{I_L}{I} = \frac{I_L}{I_R} = \frac{\text{Reactive component of current}}{\text{Active component of current}}$$

This combination is valid for any combination of parallel circuit

$$Q = \frac{I_L}{I_R} = \frac{V/X_L}{V/R} = \frac{R}{X_L} = \frac{R}{\omega L}$$

$$(\omega = \sqrt{\frac{1}{LC}})$$

$$Q = \frac{X_L}{R} = \frac{B_L \text{ or } B_C}{G}$$

$$(B_L = B_C)$$

$$Q = R \sqrt{\frac{C}{L}}$$

$$Q = \frac{I_C}{I} = \frac{I_C}{I_R} = \frac{V/X_C}{V/R} = \frac{R}{X_C} = R\omega C$$

For


$$Q > 1, R > X_L, R > X_C$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cor)

Tank Circuit :-

$$Q = \frac{\text{Reactive component of current}}{\text{Active comp. of current}}$$

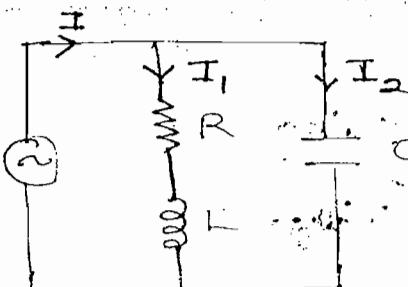
$$Q = \frac{I_1 \sin \theta, \text{ or } I_2}{I}$$




$$\alpha = \frac{I_2}{I} = \frac{\frac{V/X_C}{V}}{\frac{1}{L/RC}} = \frac{\frac{1}{X_C}}{\frac{1}{L/RC}} = \frac{\omega_L}{R} = \frac{XL}{R}$$

For  $\alpha > 1$ ,  $X_L > R$

$$B.W = f_2 - f_1$$

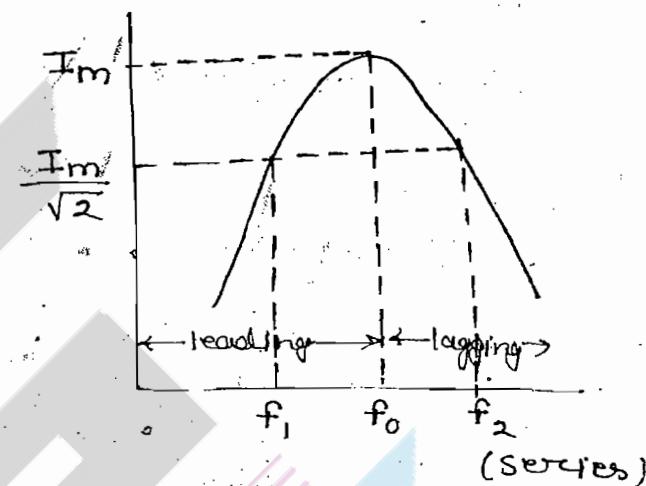


$$B.W = f_2 - f_1$$

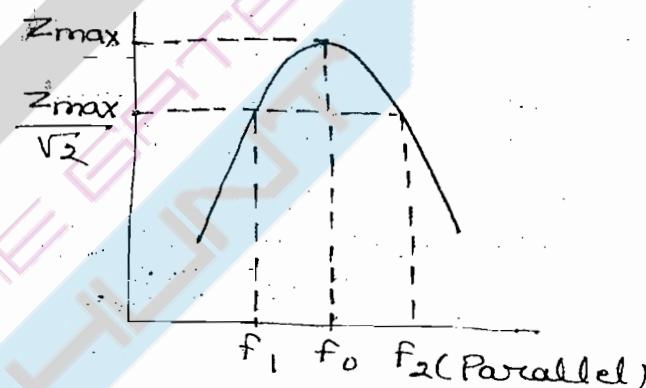

$$B.W = f_2 - f_1$$

$$B_L = \frac{1}{2\pi f L}$$

$$B_C = 2\pi f C$$

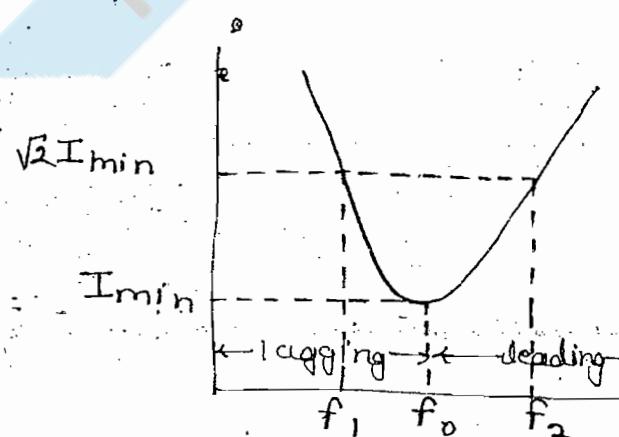

For parallel circuit we concentrate on the value of  $B_L$  and  $B_C$  (Parallel)

By KCL

$$I = \frac{V}{R} + C \frac{dV}{dt} + \frac{1}{L} \int V dt$$

Difff. w.r.t t

$$I' = \frac{1}{R} \frac{dV}{dt} + C \frac{d^2V}{dt^2} + \frac{V}{L}$$

Dividing both sides by C, we get

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{V}{LC} = \frac{I'}{C}$$

$$\theta = \frac{dV}{dt}$$

$$\left( \theta^2 + \frac{1}{RC} \theta + \frac{1}{LC} \right) V = 0$$

Compare with  $s^2 + 2\zeta\omega_n s + \omega_n^2 = 0$  we get

$$2\zeta\omega_n = \frac{1}{RC}, \quad \omega_n^2 = \frac{1}{LC}$$


$$2\zeta \frac{1}{\sqrt{LC}} = \frac{1}{RC}, \quad \omega_n = \frac{1}{\sqrt{LC}}$$

$$\alpha = R \sqrt{\frac{C}{L}}$$

$$\text{Damping Ratio} = \zeta = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

$$\zeta = \frac{1}{2\alpha}$$

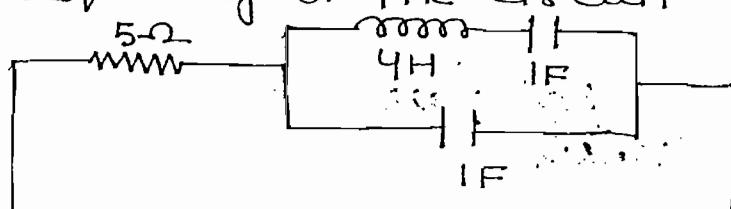Ques:- Find resonant frequency of the circuit shown



Soln:- At resonance in any of the case if  $\text{Imag. part} = 0$ .

Note:-

To find resonant frequency for any combination of the network

(I) Find  $Z_{eq}$

(II) Equate imag. part of  $Z = 0$

$$Z_1 = j(x_L - x_C) = j(\omega L - \frac{1}{\omega C}) = j(4\omega - \frac{1}{\omega})$$

$$Z_2 = -jx_C = -\frac{j}{\omega C} = -j\frac{1}{\omega}$$

$$Z_{eq}' = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$\Rightarrow Z_{eq}' = \frac{j(4\omega - \frac{1}{\omega})(-j/\omega)}{j(4\omega - \frac{1}{\omega}) - j/\omega}$$

$$\Rightarrow Z_{eq}' = \frac{(4\omega - \frac{1}{\omega})(+\frac{1}{\omega})}{j(4\omega - \frac{1}{\omega}) - j/\omega} \times \frac{j}{j}$$

$$\text{Im } Z_{eq}' = 0$$


$$(4\omega - \frac{1}{\omega}) \frac{1}{\omega} = 0$$

$$\Rightarrow \boxed{\omega = 0.5 \text{ rad/sec}}$$


HOTOSTAT  
Study Material Available  
A-163 Lado Sarai, New Delhi  
Contd.

Ques:- Find resonant frequency of the circuit shown

Ans:-  $\omega_0 = 3 \text{ rad/sec}$

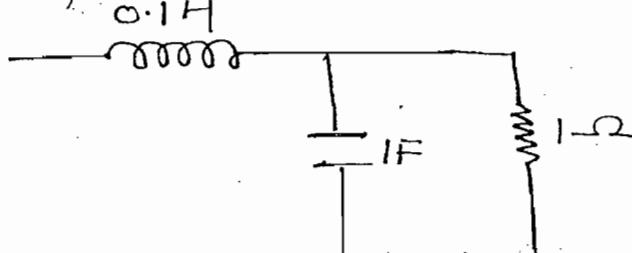


ques1- Find  $V_o$  under resonance condition

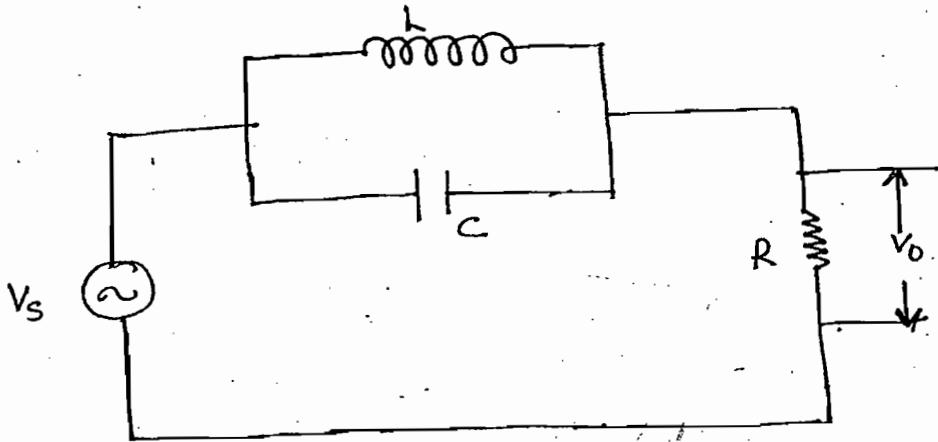


Soln1-

Ideal tank circuit,  $Z_{syn} = \infty$

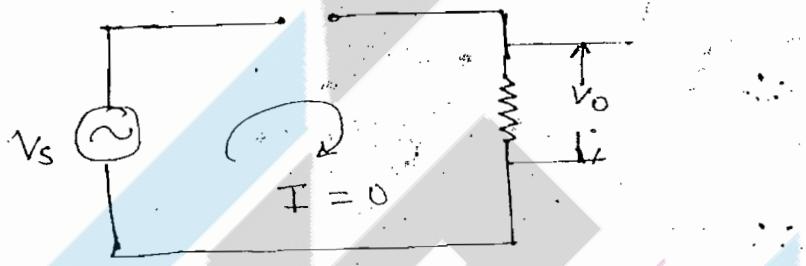


Note:-

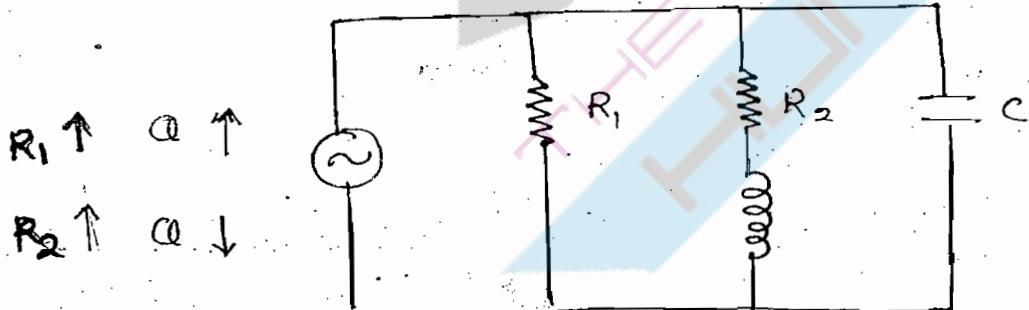
PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai New Delhi  
Contd...)



$$\therefore Q = \frac{R_1}{\omega L}$$

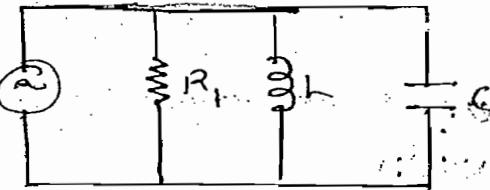

$$Q = \frac{\omega L}{R_2}$$

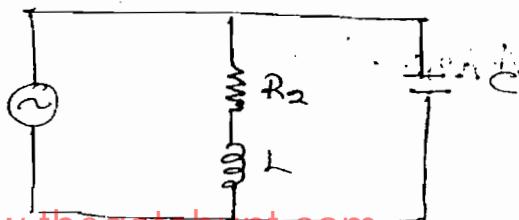

## THEOREMS :-

When the N/W is having more no. of nodes and more no. of meshes, the response in any one of the branches can be easily obtained by using theorem

### Superposition theorem:-



In any linear bidirectional circuit having more than one independent source the response in any of the branches is equal to algebraic sum of the responses caused by individual sources while rest of the sources are replaced by its internal resistances.

Ques:- Find the value of  $I$  by using superposition theorem

Soln:- Cause-(I) :-

Due to 18V


$$I^1 = \frac{18}{6+3} \\ = 2A$$

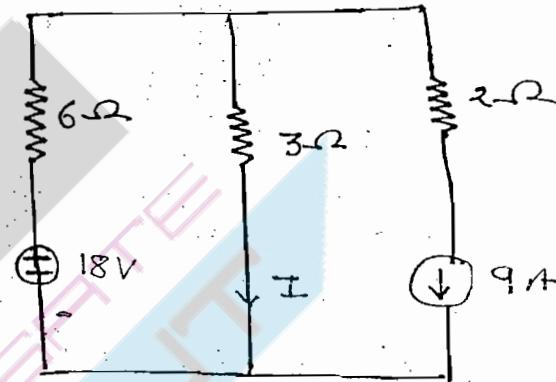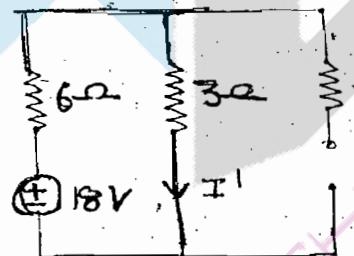


Cause-(II) :-

$$I'' = -9 \cdot \frac{6}{6+3} = -6A$$
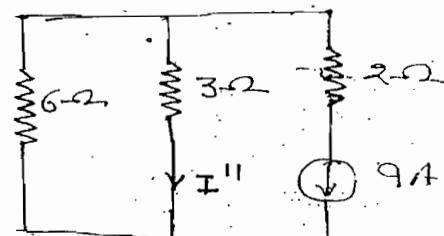
$$I = I^1 + I'' = 2 - 6 = -4, \text{ Ans.}$$



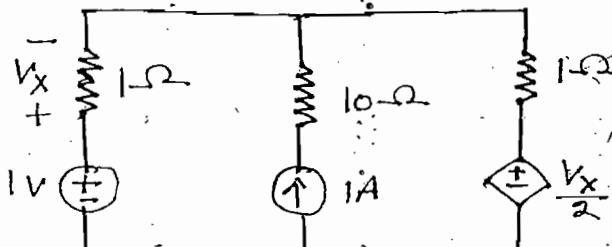Ques:- Find  $V_x$  by using superposition theorem



**PHOTOSTAT**  
(All Study Material Available  
A-163 Lado Sarai New Delhi  
Com.)

Note:-


In the above circuit while applying superposition theorem dependent sources neither are replaced by open circuit nor s.c & it remains as original ckt.

Soln:- Case-(I) :-

$$I = \frac{1 - V_x'}{\frac{2}{1+1}}$$

$$V_x' = 1 \times I = I$$

$$V_x' = \frac{2}{5}$$

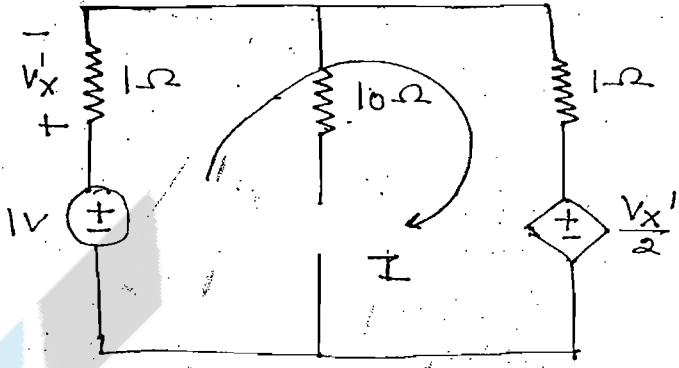


Case-(II) :-

$$V_a = -V_x''$$

$$\frac{V_a}{1} + \frac{V_a - V_x''}{\frac{2}{1}} = 1$$


$$V_x'' = -\frac{2}{5}$$
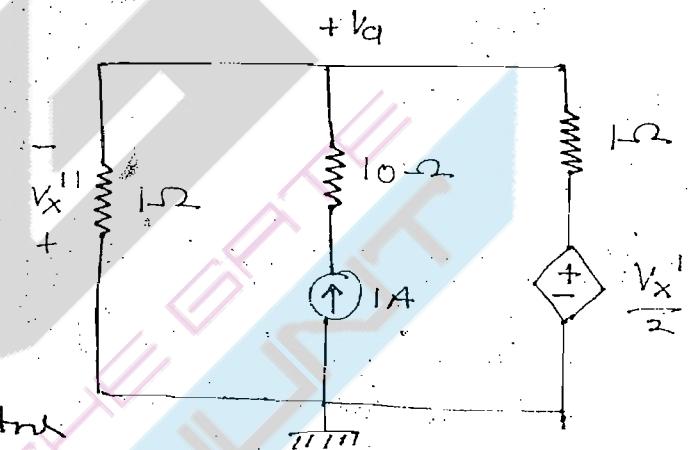
$$V_x = V_x' + V_x'' \neq 0, \text{ And}$$



Ques:- In the circuit shown power dissipation in 1Ω resistor is 576W when voltage source is acting along and power dissipation in 1Ω is resistor is 1W when current source is acting along. Find total power dissipation in 1 ohm resistor

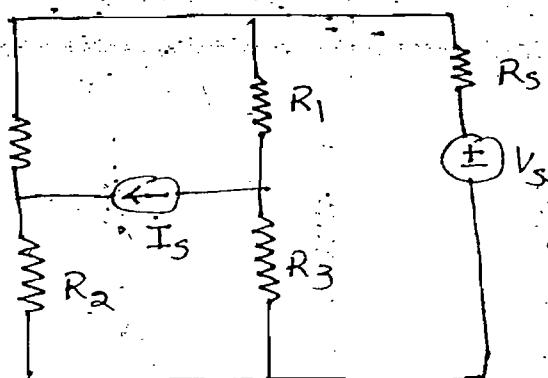PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Call



Soln:-

$$I = \pm I' \pm I'' \quad \checkmark$$

$$V = \pm V' \pm V'' \quad \checkmark$$

$$P = \pm P' \pm P'' \quad \times$$

$$P = I^2 R$$

$$P' = I'^2 R$$

$$I' = \sqrt{\frac{P'}{R}}$$

$$I'' = \sqrt{\frac{P''}{R}}$$

$$I = \pm I' \pm I''$$

$$\Rightarrow I = \pm \sqrt{\frac{P'}{R}} \pm \sqrt{\frac{P''}{R}}$$

$$P = I^2 R$$


$$\Rightarrow P = \left( \pm \sqrt{\frac{P'}{R}} \pm \sqrt{\frac{P''}{R}} \right)^2 R$$

$$\Rightarrow P = \boxed{\left( \pm \sqrt{P'} \pm \sqrt{P''} \right)^2}$$

$$P = \left( +\sqrt{P'} - \sqrt{P''} \right)^2$$

$$= (+\sqrt{576} - \sqrt{1})^2 = 529 \text{ W, Ans.}$$

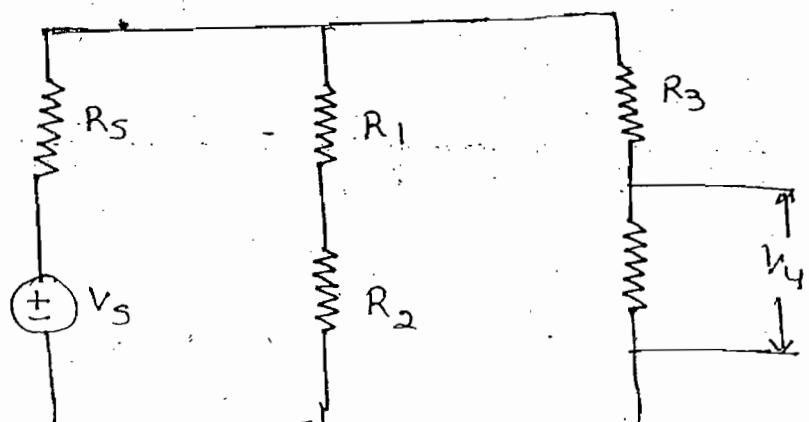Ques:- In the circuit shown if the source voltage is increased by 10% then find variation of the power in the  $R_4$  resistor.



Soln:-

$$P_4 = \frac{V_4^2}{R_4}$$

$$P'_4 = \frac{(1.1 V_4)^2}{R_4} = 1.21 \frac{V_4^2}{R_4} = 1.21 P_4$$


Inc by 21%.

Note:-

When the N/W is having linear bidirectional element if excitation is particularly constant K the response of each element also multiplied by constant K (Homogeneity Principle)

ques:- In the circuit shown, find I when  $V_1 = 10V$  &

$$V_2 = -12V$$

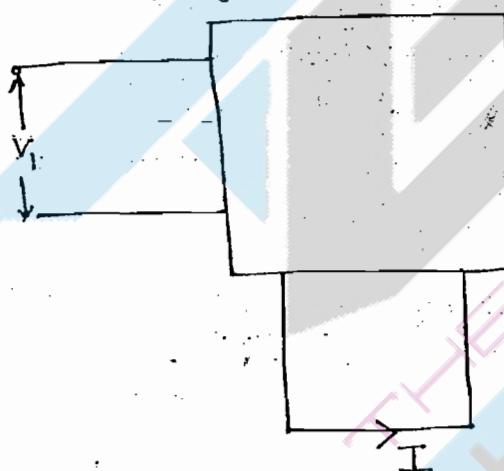

$V_L$	$V_R$	I
2	0	3A
0	3V	-4A

Soln:-  $V_1 = 2$        $I = 3A$

$$V_1 = 10 \text{ then } I' = 5 \times 3 = 15A$$

(2x5)

5 times ↑

$$V_2 = 3V \quad I = -4$$

$$V_2 = -12V \text{ then } I'' = (-4)(-4) \\ (-4 \times 3) = 16$$



$$I = I' + I''$$

$$I = 15 + 16 = 31A, \text{ Ans.}$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Call

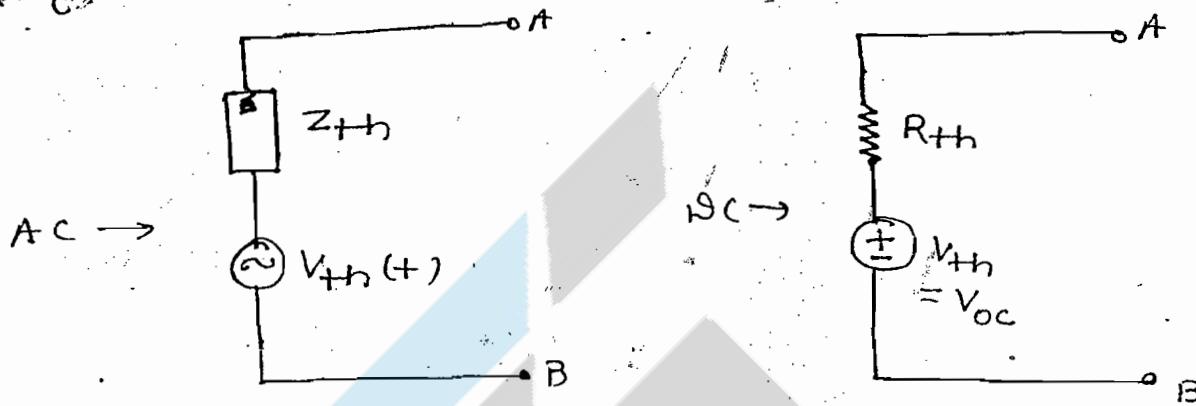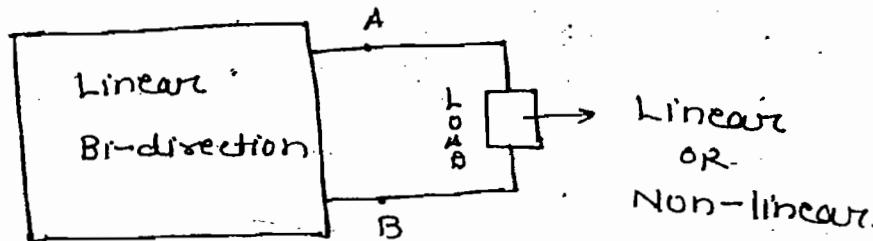
## Thevenin's Theorem:-

URGENT  
 (All Study material Available)  
 C-163 Lado Sarai, New Delhi  
 C-163 Lado Sarai, New Delhi  
 C-163 Lado Sarai, New Delhi



When N/w is having linear bidirectional elements and more no. of active and passive elements, it can be replaced by single equivalent circuit consisting of equivalent voltage source ( $V_{th}$ ) in series with equivalent resistance ( $R_{th}$ )

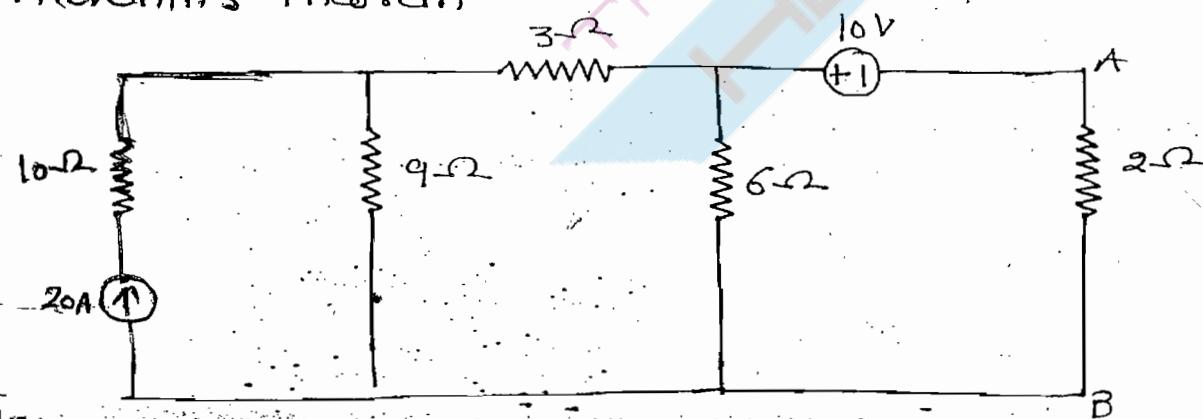
Ques:- Find current in the  $2\Omega$  resistor by using Thvenin's theorem



Soln:-

Case - (1)  $\rightarrow (V_{th})$  :-

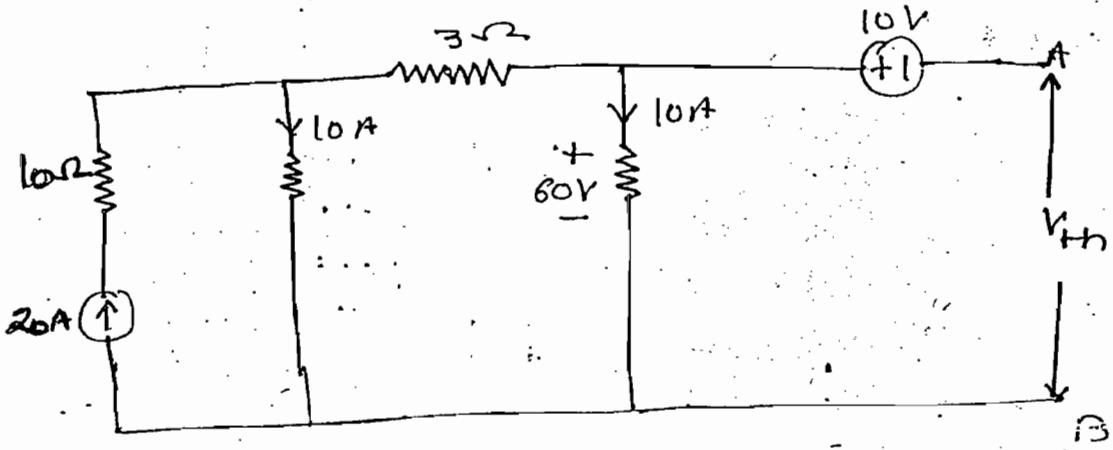Disconnect the load resistor and o.c voltage across the load terminals




$$-60 + 10 + V_{th} = 0$$

$$\Rightarrow V_{th} = 50V$$


Cause - (ii)  $\rightarrow (R_{th})$  :-

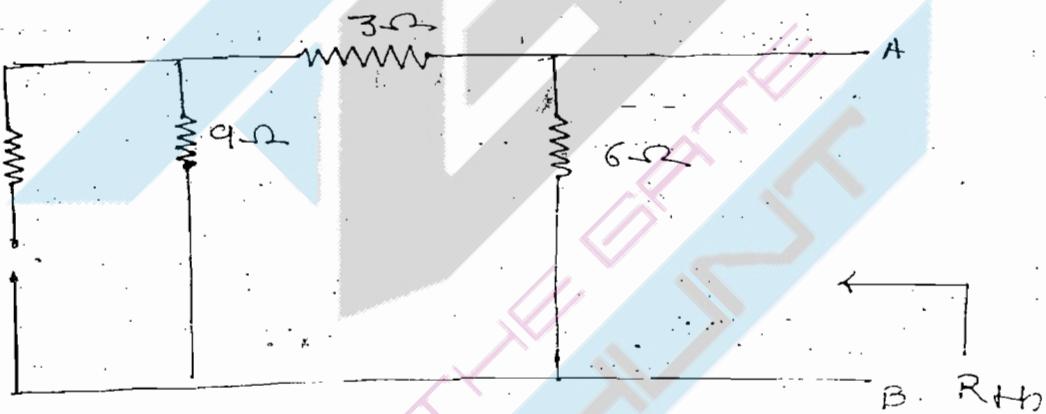Deactivate all the independent sources and find eq. resistance w.r.t. load terminals




$$R_{th} = \frac{12 \times 6}{12 + 6} = 4\Omega$$

$$I = \frac{V_{th}}{R_{th} + R_L}$$

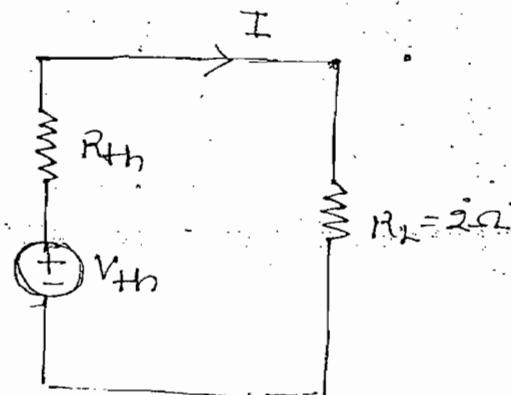


ques:- When a battery charger connected to  $1\Omega$  resistor, current in the resistor is  $5A$ . When same battery charger is connected for charging of ideal  $2V$  battery at  $7A$  rate. Find  $V_{th}$  &  $R_{th}$

solt-

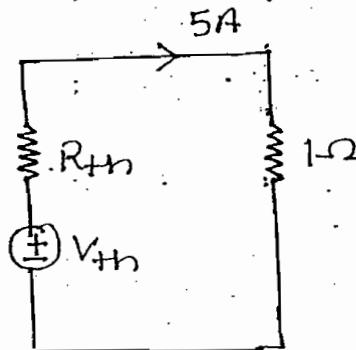
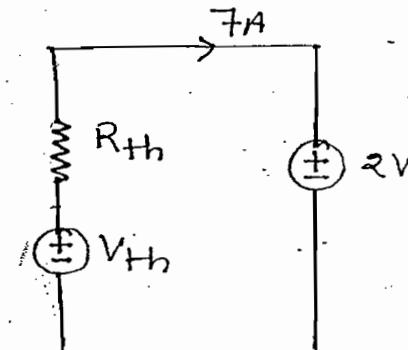
$$5 = \frac{V_{th}}{R_{th} + 1} \quad (1)$$




$$7 = \frac{V_{th} - 2}{R_{th}} \quad (2)$$

$$\Rightarrow V_{th} = 12.5 \text{ and } R_{th} = 1.5$$

ques:- Find  $V_{th}$  w.r.t A and B

Note:-

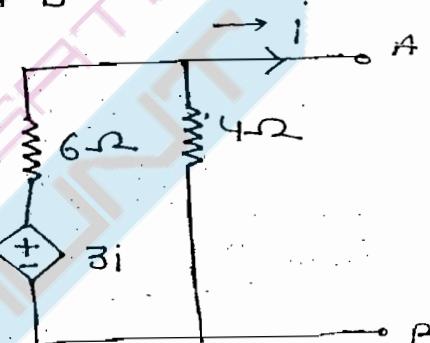In above N/W no independent source is present  
Therefore  $V_{th} = 0$




ques:- Find  $V_{th}$  w.r.t A and B.

- (a) 0    (b) 4    (c) 6

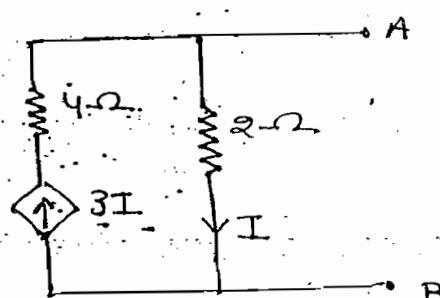(d) None

Note:-


In the above ckt, it's not possible to find O.C Voltage since it is not satisfying KCL



Ques:- Find  $R_{th}$  w.r.t A and B

Note:-

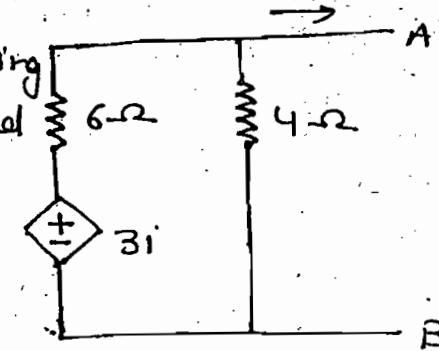In above N/W while finding  $R_{th}$  dependent source is replaced by neither OC nor short ckt and it remains same as original ckt.



Soln:-

$$\frac{V_A - 3i}{6} + \frac{V_A}{4} = 1$$

$$\Rightarrow i = -1$$

$$V_A = 1.2$$

$$V_{AB} = V_A - V_B$$

$$= 1.2 - 0 = 1.2$$

$$R_{th} = \frac{V_{AB}}{I_s} = \frac{1.2}{1} = 1.2 \Omega, \text{ Ans}$$

In parallel consider current source for simple calculation.

Ques:- Find  $R_{th}$  w.r.t A and B



Soln:- In series consider voltage source

$$\frac{V_1 - 3i}{6} + \frac{V_1}{4} + \frac{V_1 - 1}{1} = 0$$

$$i = \frac{V_1 - 1}{1} \Rightarrow V_1 = 6$$

$$= -\frac{5}{11}$$

$$\therefore V_1 = \frac{6}{11}$$

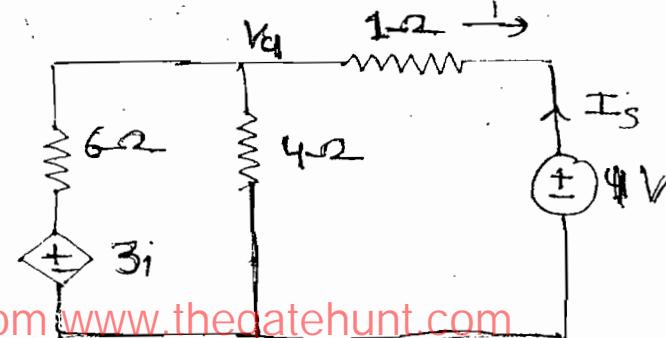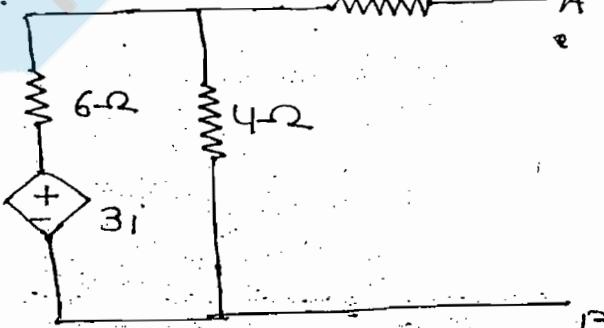


$$I_s = -i = -\left(-\frac{5}{11}\right) = \frac{5}{11}$$

$$R_{th} = \frac{V_s}{I_s} = \frac{1}{\frac{5}{11}} = \frac{11}{5} \Omega, \text{ Ans}$$

$$= 2.2 \Omega, \text{ Ans.}$$

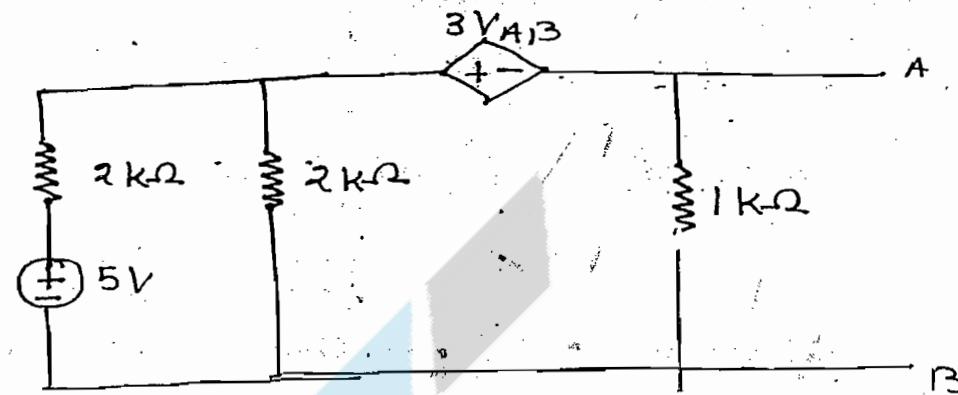Ques:- Find  $V_{th}$  and  $R_{th}$  w.r.t. A and B.



Soln:-

Case-(I):-

$$\frac{V-5}{2 \times 10^3} + \frac{V_1}{2 \times 10^3} + \frac{V_2}{1 \times 10^3} = 0$$

→ (I)


$$V_1 - V_2 = 3V_{th} \quad \text{--- (II)}$$

$$V_2 = V_{th}$$

$$V_1 = 4V_{th}$$

~~4V~~ 
$$V_{th} = 0.5V$$

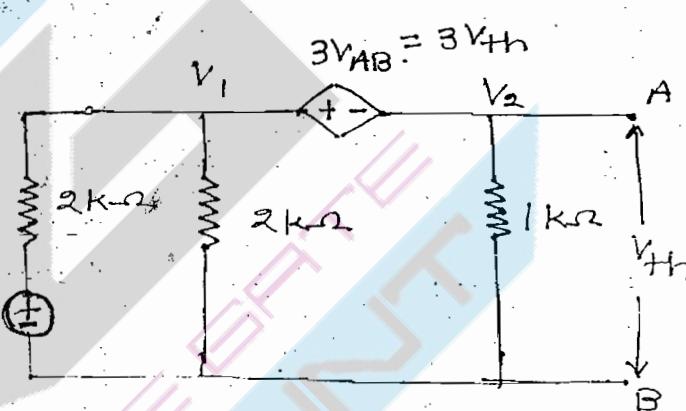PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Col.)





Case-(II):- For  $R_{th}$

$$\frac{V_A + 3V_{AB}}{10^3} + \frac{V_A}{1 \times 10^3} = 1$$

$$V_{AB} = V_A - V_B = V_A$$

$$V_{AB} = 200$$
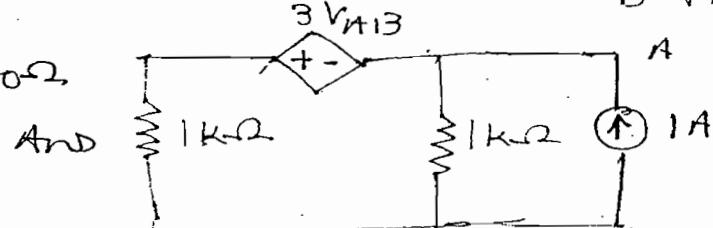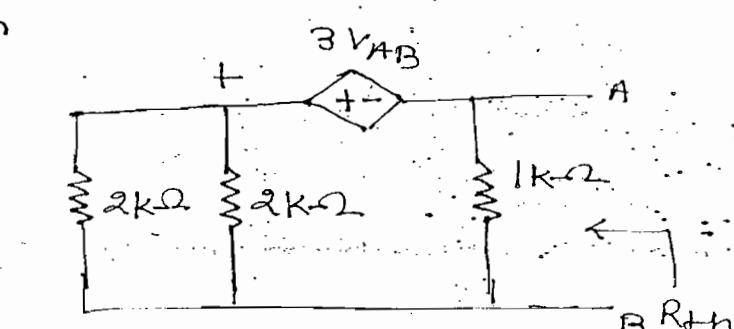
$$R_{th} = \frac{V_{AB}}{I_s} = \frac{200}{1} = 200 \Omega$$



## Verification:-

$$I_{SC} = \frac{V_{OC}}{R_{Th}}$$

$$R_{Th} = \frac{V_{OC}}{I_{SC}}$$





For this method atleast one independent source should be present

$$I_{SC} = \frac{5}{2 \times 10^3}$$


$$R_{Th} = \frac{V_{OC}}{I_{SC}} = \frac{0.5}{\frac{5}{2 \times 10^3}} = 200 \Omega$$
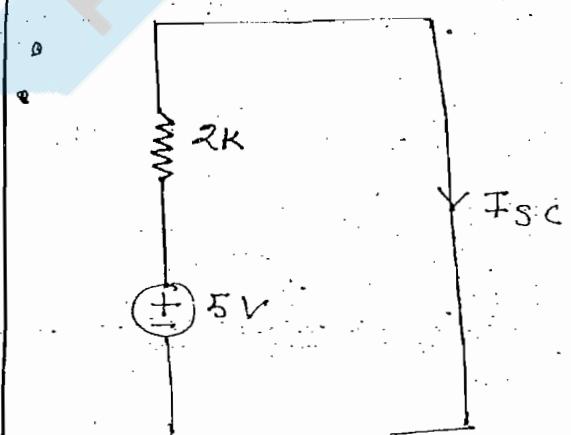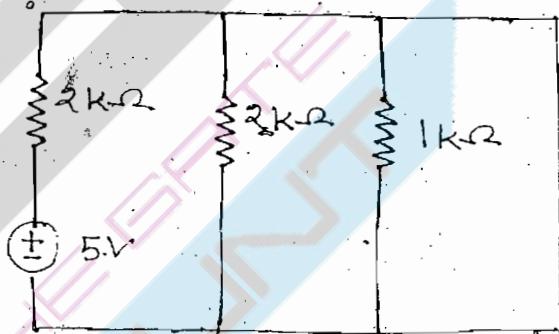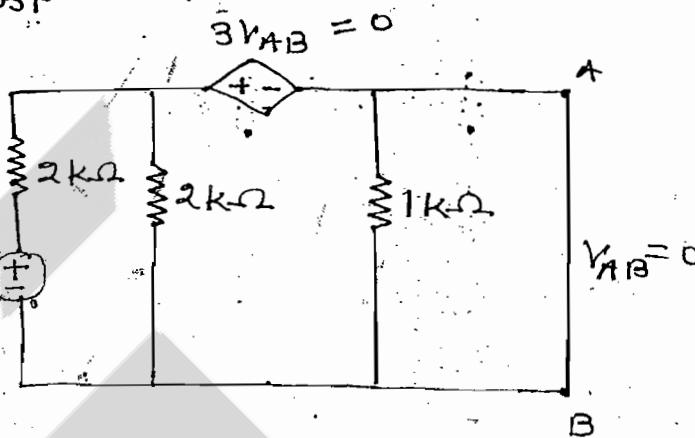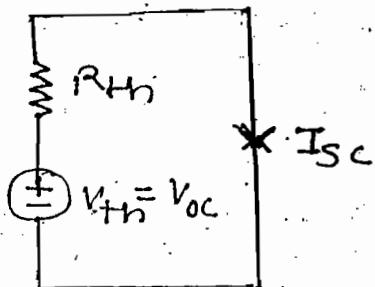
### Note:-

The above method of  $R_{Th}$  calculation can be done provided original N/W should consist of atleast one independent source.




Case - 2 ( $R_{Th}$ ):

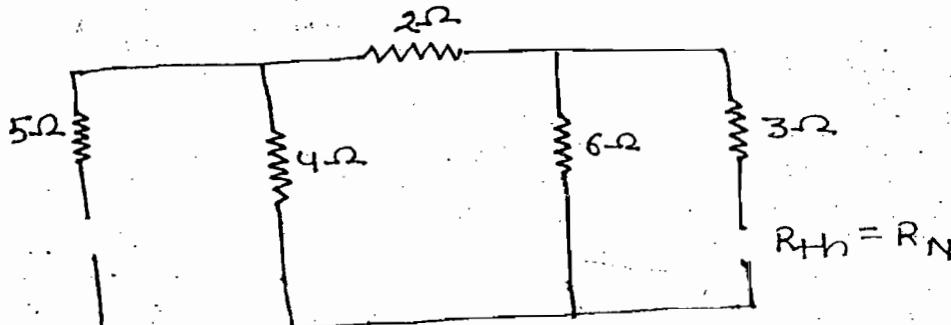


$$R_{Th} = R_N = 6\Omega$$
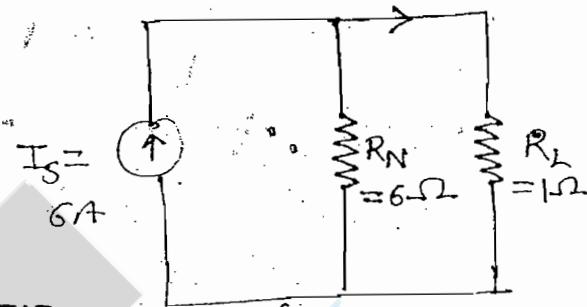
$$\begin{aligned} I_L &= 6 \times \frac{6}{6+1} \\ &= \frac{36}{7} \text{ A, Ans.} \end{aligned}$$





**PHOTOSTAT**  
(All Study Material Available  
A-163, Lado Sarai, New Delhi  
Contact: 9891111111)

Ques!:- Find s.c. current w.r.t A and B

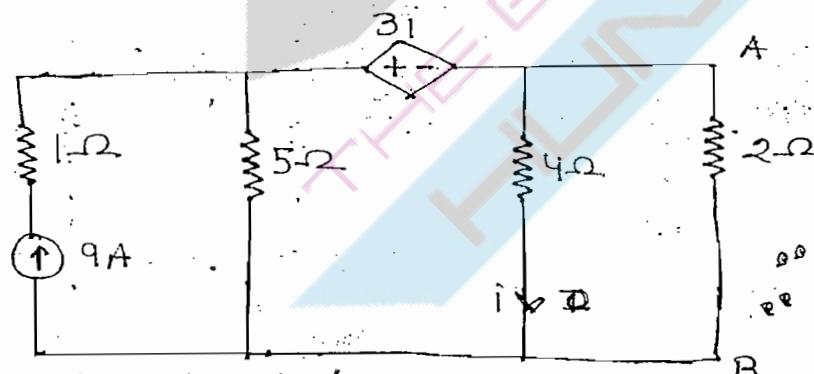

Sol'n:-

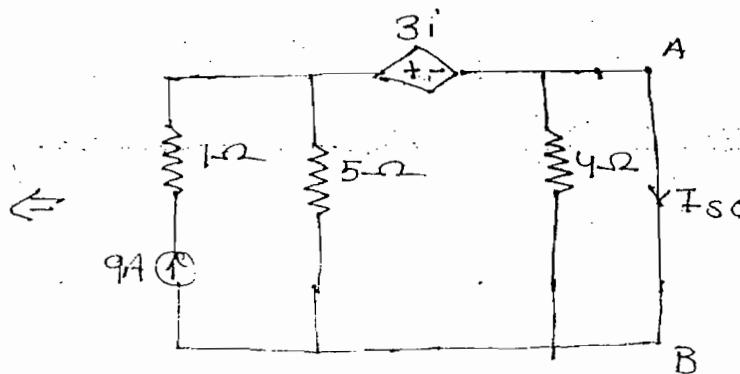
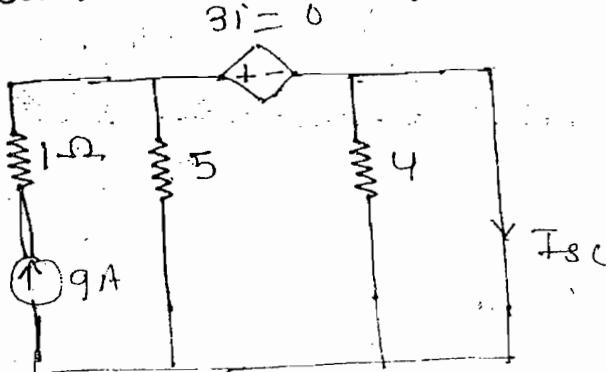


## Lecture - 7


PROTOSTAT  
Available  
A-163 Lado Sarai, New Delhi  
Con.
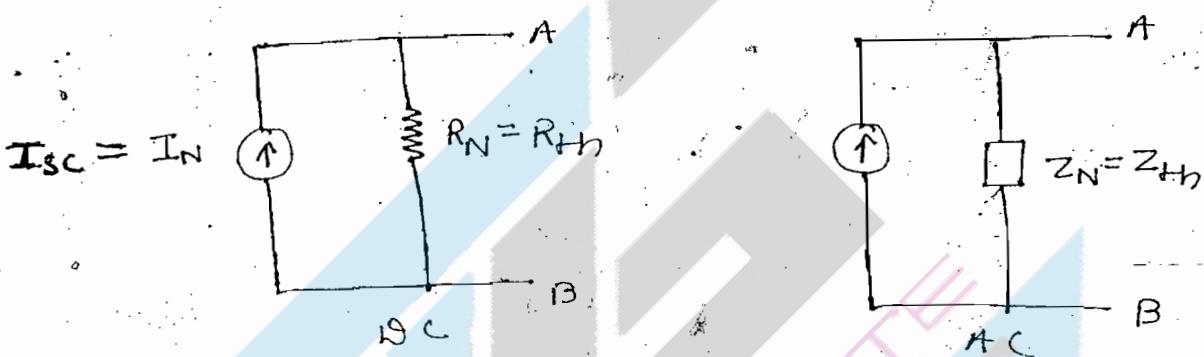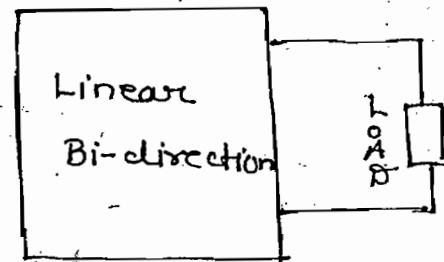
### Norton's theorem:-

In any linear bidirectional circuit having more no. of active and passive element, it can be replaced by single equivalent ckt consisting of equivalent current source ( $I_N$ ) in parallel with equivalent resistance ( $R_N$ )



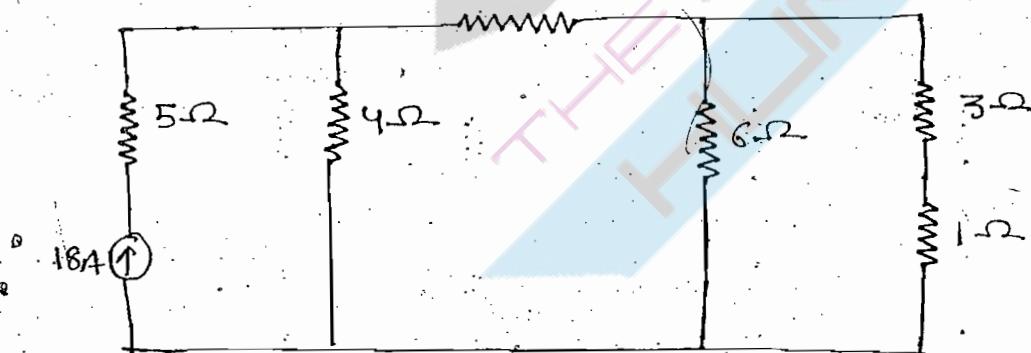Ques:- Find current in  $1\Omega$  resistor using Norton's theorem





Soln:-

Case - (i) :-

Replace the load resistor by S.C and find SC current
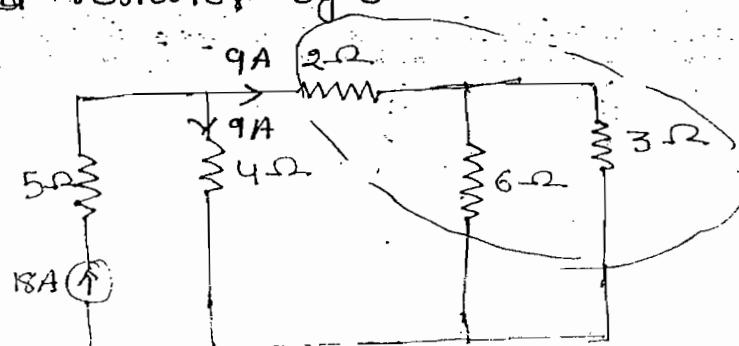
$$I_{SC} = 9 \times \frac{6}{6+3} \\ = 6A$$



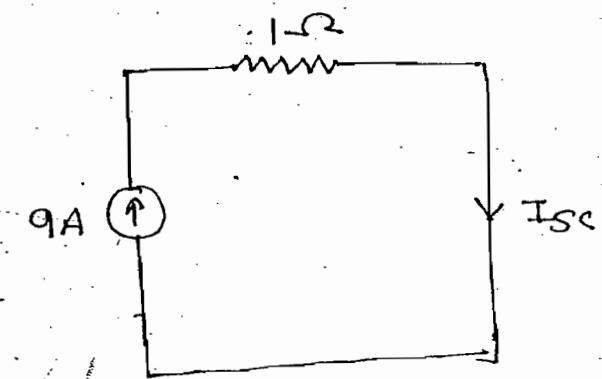


$$I_{sc} = 9A, \text{ Ans.}$$

**ENIAC PHOTOSTAT**  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Contact: 9891111111

Ques:- Find o.c. voltage and sc current w.r.t A & B


Soln:-

$$V_{oc} = 10V$$

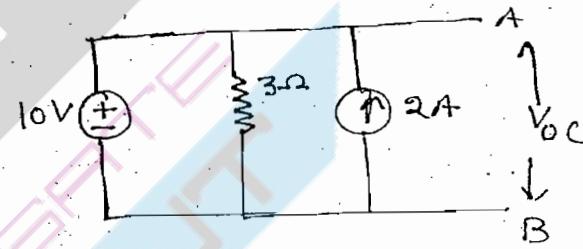

For I\_sc:-


$$I_{sc} = \text{not possible}$$


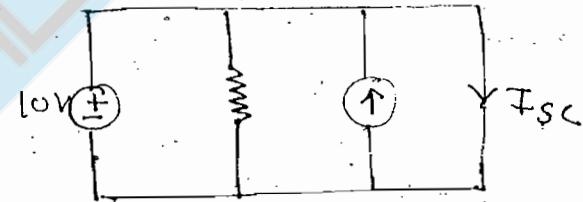


Note:-

In the above circuit it is not possible to find  $I_{sc}$  since it is not satisfying KVL.

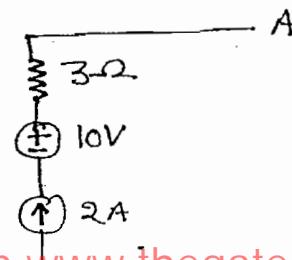Ques:- Find  $V_{oc}$  and  $I_{sc}$  w.r.t A and B



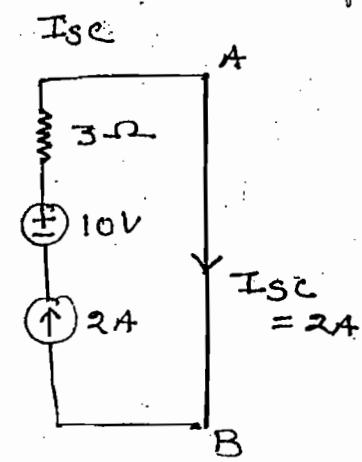
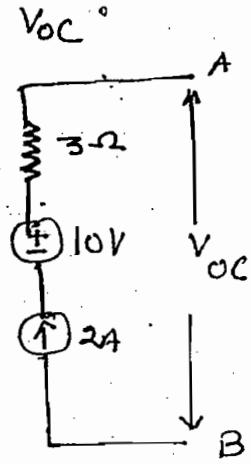


Note:-

In above circuit it is not possible to find O.C voltage since it is not satisfying KCL

ques:- Find Isc w.r.t. A and B

Soln:-

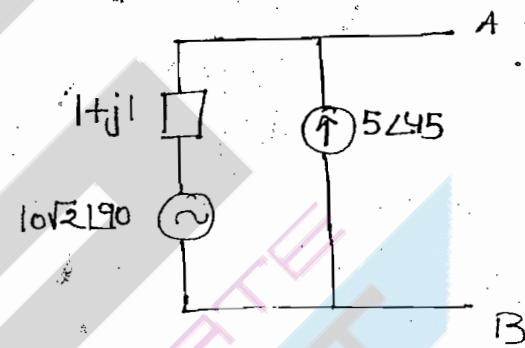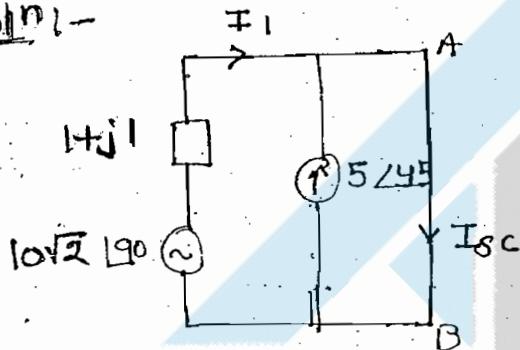

$$I_1 = \frac{10\sqrt{2} \angle 190^\circ}{\sqrt{2} \angle 45^\circ} = 10 \angle 45^\circ$$

$$I_1 + 5 \angle 45^\circ = I_{sc}$$

$$10 \angle 45^\circ + 5 \angle 45^\circ = I_{sc}$$

$$\Rightarrow I_{sc} = 15 \angle 45^\circ$$

HOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Contd... 09810070070


ques:- Find current in 4Ω resistor using the following data:

Soln:-  $V_{oc} = 60$

$$I_{sc} = 10A$$


$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{60}{10} = 6\Omega$$

V	60	0
I	0	10A

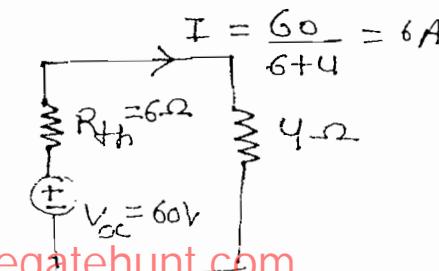

## Reciprocity theorem:

Case-(I) :-

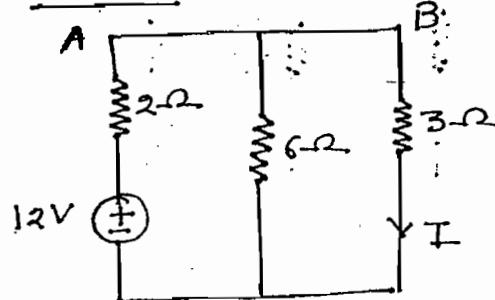


$$R_{eq} = 2 + \frac{6 \times 3}{6+3} = 4$$

$$I_T = \frac{12}{4} = 3A$$

$$I = 3 \cdot \frac{6}{6+3} = 2A$$

$$\frac{\text{Response}}{\text{Excitation}} = \frac{2}{12} = \frac{1}{6}$$

Case-(II) :-

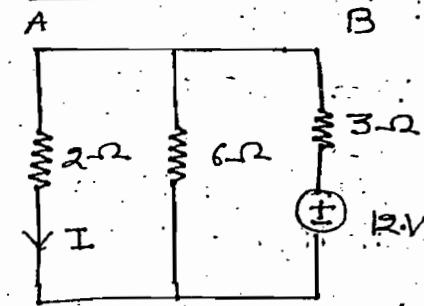

$$R_{eq} = 3 + \frac{6 \times 2}{6+2} = 4$$


$$I_T = \frac{12}{4} = 3A$$

$$I = I_T \cdot \frac{6}{6+2} = 2A$$

$$\frac{\text{Response}}{\text{Excitation}} = \frac{2}{12} = \frac{1}{6}$$

In above N/W after interchanging position of response and excitation the ratio of response to excitation is constant. Hence given N/W satisfy the reciprocity (Linear bi-directional element)

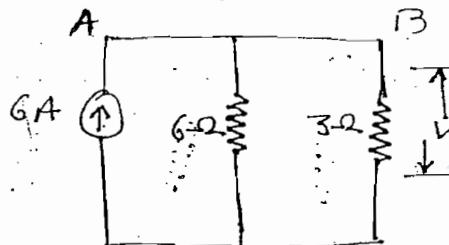Ques:- Verify Reciprocity theorem of the circuit shown



Soln:-


Case-(I) :-

$$I = 6 \times \frac{6}{6+3} = 4A$$

$$V = 3 \times 4 = 12$$

$$\frac{\text{Response}}{\text{Excitation}} = \frac{12}{6} = 2$$

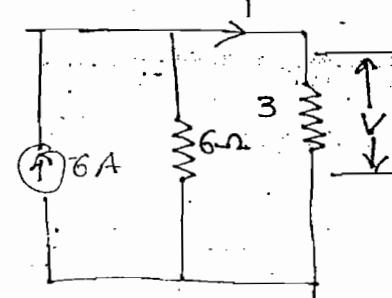HOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9899900004




Case-(ii) :-

$$i_1 = 6 \frac{3}{3+6} = 2A$$


$$V = 6 \times 2 = 12$$

$$\frac{\text{Response}}{\text{Excitation}} = \frac{12}{6} = 2$$

→ Satisfy Reciprocity

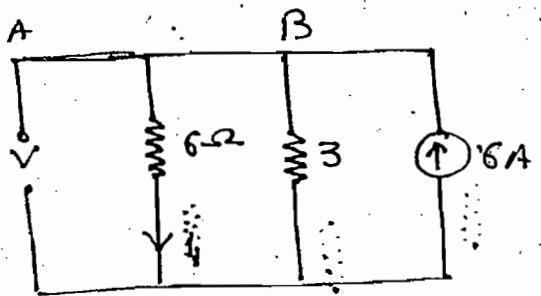

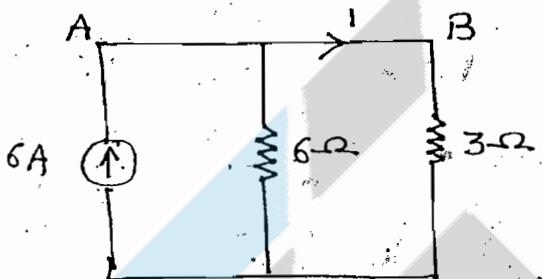
ques:- Verify Reciprocity theorem of the ckt shown:-



Soln:-


Case-(i)

$$I = 6 \frac{6}{6+3} = 4A$$

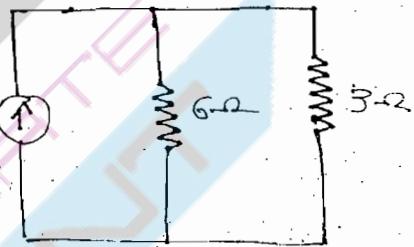

Case-(ii)

$$I = 0$$

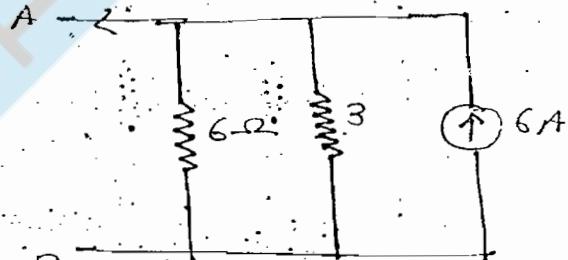

Note:- For above problem

$$(i) \frac{\text{Response}}{\text{Excitation}} = \frac{I}{V_S} \quad (iii) \frac{\text{Response}}{\text{Excitation}} = \frac{i}{I_S}$$

$$(ii) \frac{\text{Response}}{\text{Excitation}} = \frac{V}{I_S} \rightarrow \Omega \quad (iv) \frac{\text{Response}}{\text{Excitation}} = \frac{V}{V_S}$$

No units


Note:-

For the above N/W Reciprocity theorem can't be applied since unit of response to excitation should be neither mho or  $\Omega$

Note:-

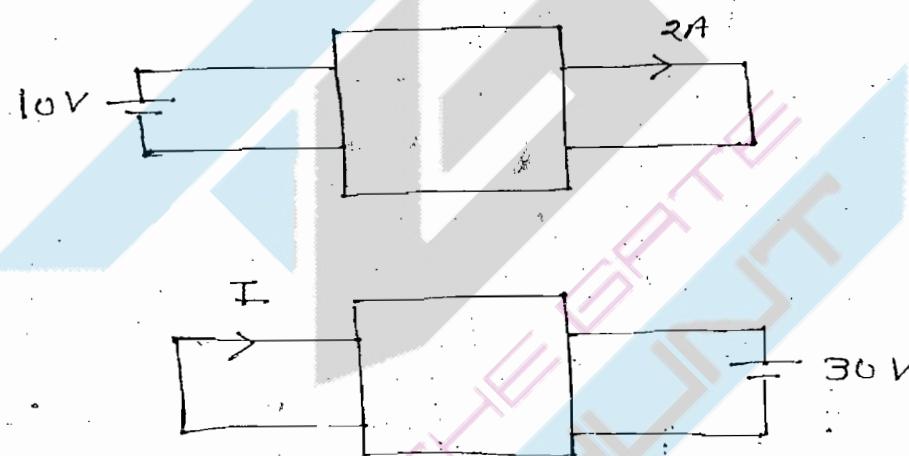1. To apply Reciprocity theorem unit of Res/Exc. should be either mho or ohm
2. While applying reciprocity theorem N/W should consist of only one independent source
3. While applying reciprocity theorem N/W should not consist of any dependent sources


ques:- When given N/W doesn't satisfy the Reciprocity then find the value of I



Soln:-

$$\frac{\text{Response}}{\text{Excitation}} = \frac{2}{10} = -\frac{I}{30} \Rightarrow I = -6A$$

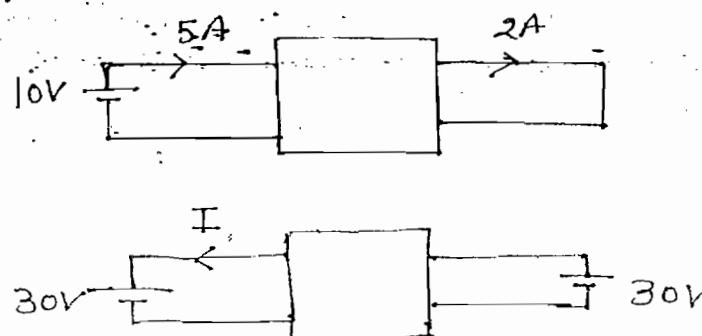ques:- When given N/W doesn't satisfy the Reciprocity then find the value of I




Soln:- Soln by using Superposition & Reciprocity

( $\because$  more than one independent sources are present)

Case-(I) (30V) :-

$$\frac{\text{Response}}{\text{Excitation}} = \frac{I^1}{30} = \frac{2}{10}$$


$$\Rightarrow I^1 = 6A$$

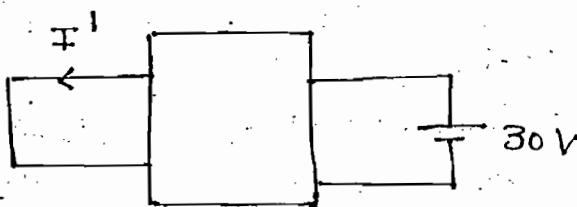

Case-(II) (30V) :-

$$\frac{\text{Response}}{\text{Excitation}} = \frac{-I''}{30} = \frac{5}{10}$$

$$\Rightarrow I'' = -15$$

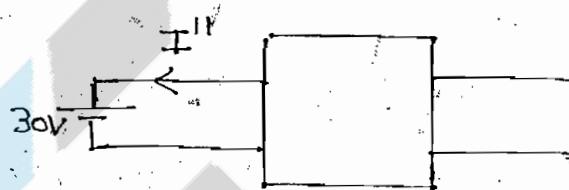

$$I = I^1 + I'' = 6 - 15 = -9A$$

Ques:- When given N/W satisfy the Reciprocity find the value of I



Soln:- Case-(I) (I<sub>SC</sub>) :- (Norton's theorem)


$$\frac{\text{Response}}{\text{Excitation}} = \frac{I_{SC}}{30} = \frac{2}{10}$$

$$I_{SC} = 6A$$




Case 2 ( $R_{Th}$ ):


$$R_{Th} = \frac{10}{5} = 2\Omega$$

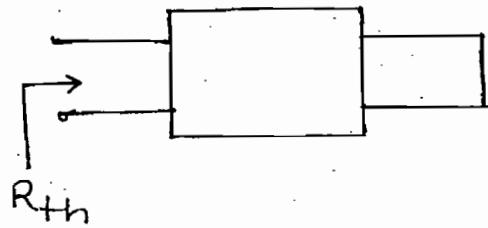

$$I = 6 \times \frac{2}{2+4} = 2A$$

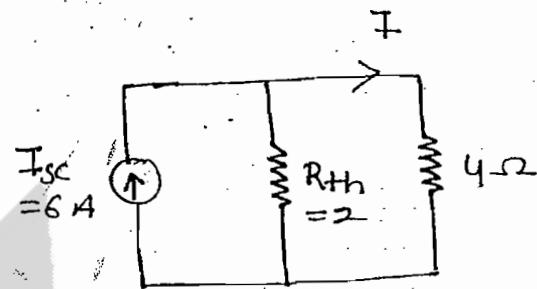

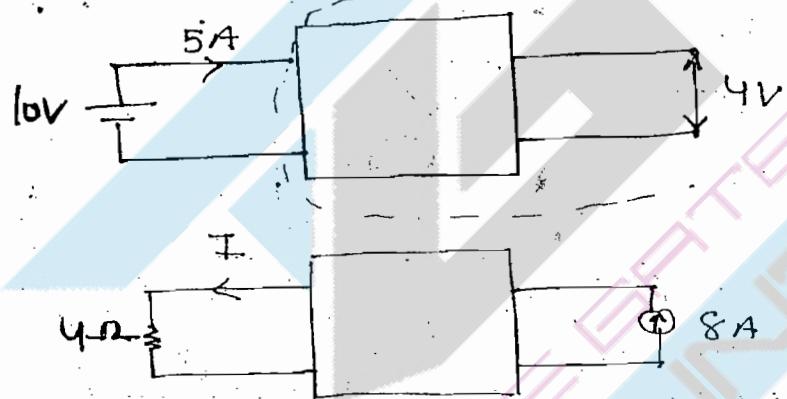
Ques: When given N/w satisfy the Reciprocity. Find the value of I.



Soln:- Case (i) ( $V_{Th}$ ):


$$\frac{\text{Response}}{\text{Excitation}} = \frac{V_{Th}}{8} = \frac{4}{5}$$

$$\Rightarrow V_{Th} = \frac{32}{5}$$

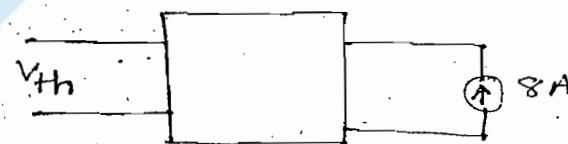


Case (ii) ( $R_{Th}$ ):

$$R_{Th} = \frac{10}{5} = 2\Omega$$

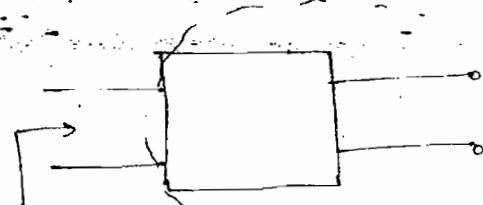
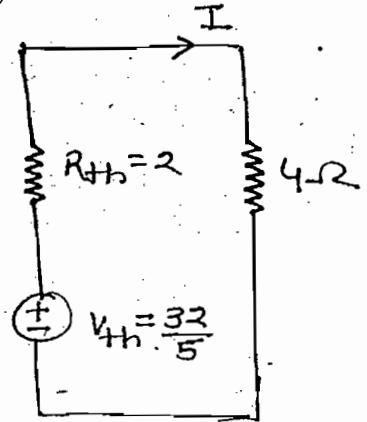
$$I = \frac{32/5}{2+4} = \frac{32}{5} \times \frac{1}{6} = \frac{16}{15} A$$



Maximum Power Transfer theorem: — ✓ (variable = constant)

$$I = \frac{V_S}{R_S + R_L}$$

$$P_L = I^2 R_L$$

$$\Rightarrow P_L = \left( \frac{V_S}{R_S + R_L} \right)^2 R_L \quad (1)$$

If eq-(1) w.r.t  $R_L$  and equated to zero, we get

$$R_L = R_S$$


$$P_{max} = \frac{V_S^2}{(R_L + R_S)^2} R_L$$

$$P_{max} = \frac{V_S^2}{4R_S}$$


$$\eta = \frac{O/P}{I/P} \times 100$$

$$\eta = \frac{I^2 R_L}{I^2 (R_L + R_S)} \times 100 \Rightarrow \eta = \frac{R_L}{R_L + R_S} \times 100$$

$$\Rightarrow \eta = 50\%$$

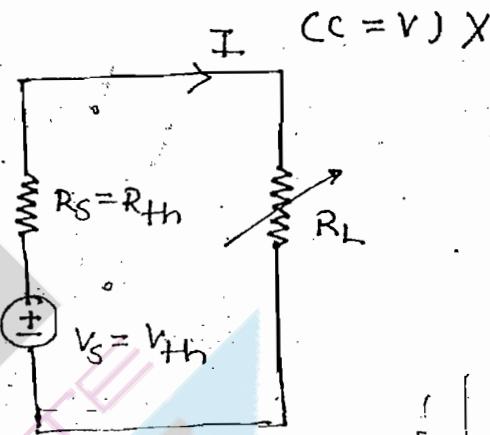

∴  $\eta = 50\%$  (at  $R_L = R_S$ )

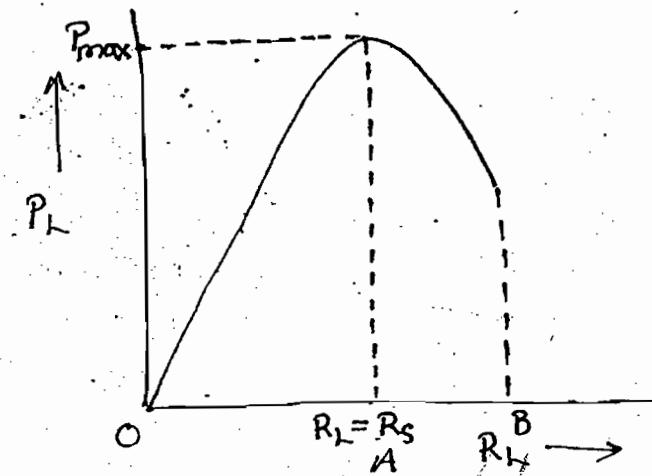

Case - (I) :-

$$OA \Rightarrow R_S > R_L$$

$\eta < 50\%$

Case - (II) :-

$$\text{At point } A \Rightarrow RL = R_S$$


$\eta = 50\%$

Case - (III) :-


$$AB \Rightarrow R_L > R_S$$

$\eta > 50\%$

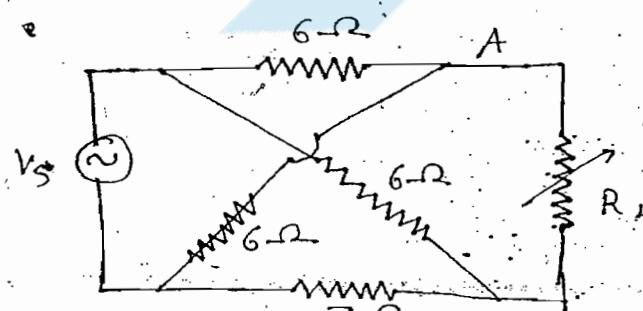ques:- Find  $R_L$  to obtain max. power from source to load




Soln:-

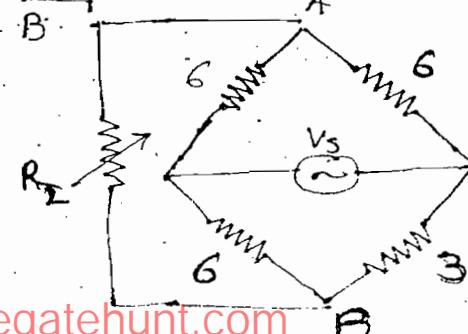


$R_{Th}$ :

$$R_{Th} = 5\Omega$$


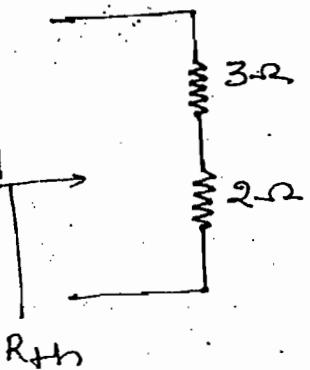


$$R_L = R_{Th} = 5\Omega$$

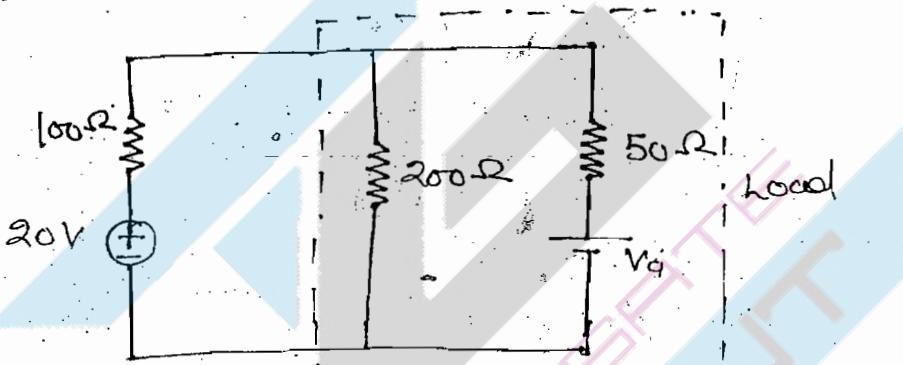ques:- Find  $V_a$  to obtain max power from source to load.



Note:-

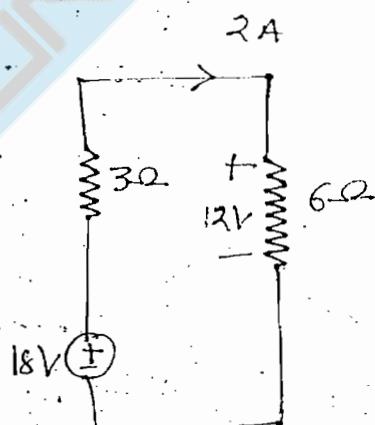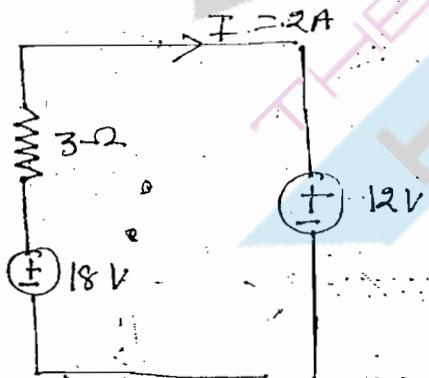


Sol'n:-

$$(Req)_L = R_s = 100$$

$$(Req)_L = \frac{200(50+R)}{200+50+R}$$

$$\Rightarrow 100 = \frac{200(50+R)}{250+R}$$

$$\Rightarrow R = 150\Omega$$

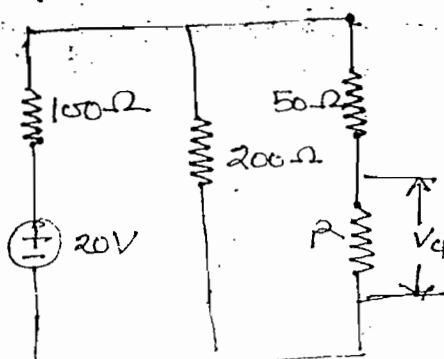


$$I_T = \frac{20}{R_S + (R_{\text{req}})_L}$$

$$I_T = \frac{20}{100+100} = \frac{1}{10} \text{ A}$$

$$V_a = \frac{I_T R}{2} = 7.5 \text{ Volts, Ans}$$

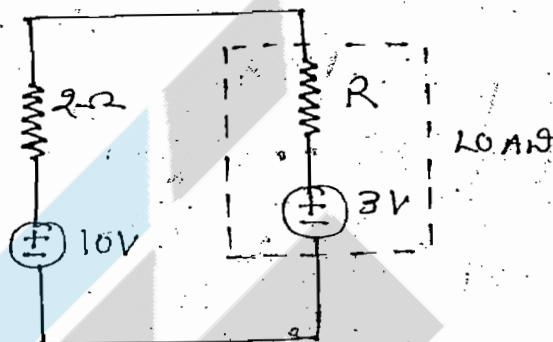ques:- Find resistance  $R$  to obtain maximum power from source to load




$$\text{soln}:- (R_{\text{req}})_L = R_S = 2\Omega$$

$$I_T = \frac{10}{R_S + (R_{\text{req}})_L}$$


$$I_T = \frac{10}{2+2} = 2.5 \text{ A}$$

$$I_T = \frac{10-3}{2+R} = 2.5 \Rightarrow R = 0.8 \Omega \quad \text{Ans}$$

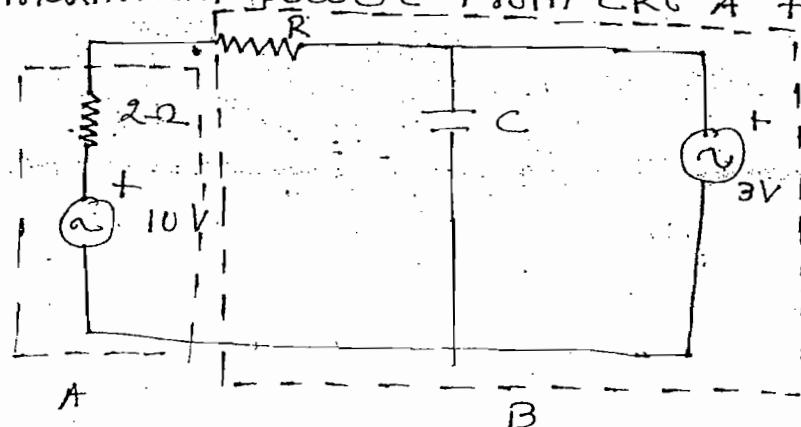ques:- In the figure shown find resistance  $R$  to obtain maximum power from ckt A to ckt B



Note:-

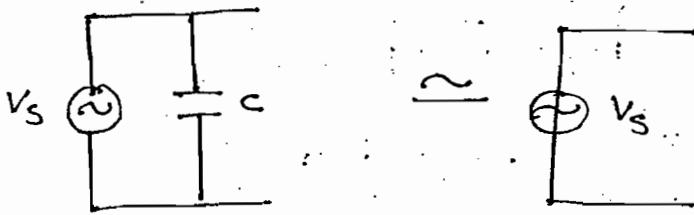

Sol'n:-

$$R = 0.8\Omega$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9899999999)

Maximum Power Transfer theorem (For AC) :-


$$i = \frac{V_{th}}{(R_L + R_{th}) + j(X_L + X_{th})}$$

$$i = \frac{V_{th}}{\sqrt{(R_L + R_{th})^2 + (X_L + X_{th})^2}}$$

$$P_L = i^2 R_L$$

$$P_L = \frac{V_{th}^2 R_L}{(R_L + R_{th})^2 + (X_L + X_{th})^2}$$

(1)

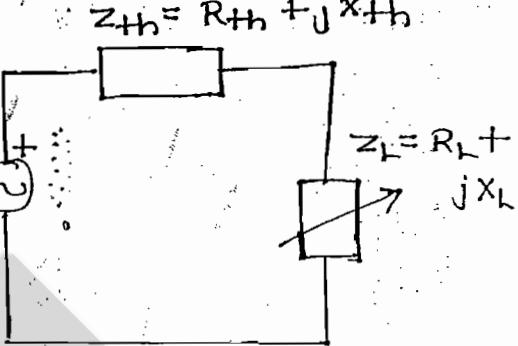

→ Max Power transfer is applicable only for active power

Case (I) :-

Both  $R_L$  &  $X_L$  are variable

- (i) Diff. eq - (1) w.r.t  $R_L$  and equated to zero
  - (ii) Diff. eq - (1) w.r.t  $X_L$  and equated to zero
- we get

$$R_L + jX_L = R_{th} - jX_{th}$$

$$\therefore Z_L = Z_{th}^*$$

Putting these values in eq - (1), we get

$$P_{max} = \frac{V_{th}^2}{4R_L}$$

$$n = 50\%$$

### Case (II) :-

Only  $R_L$  is variable  $\therefore (X_L = \text{constant})$   
 $\rightarrow$  Diff. eq-(I) w.r.t  $R_L$  and equated to zero

$$R_L = |Z_{th} + jX_L| = R_{th} + j(X_{th} + X_L)$$

$$R_L = \sqrt{R_{th}^2 + (X_L + X_{th})^2}$$

$$\eta = \frac{R_L}{R_L + R_{th}} \times 100$$

$$\boxed{\eta \geq 50\%}$$

### Case (III) :-

Load impedance is only resistive ( $X_L = 0$ )

$$P_L = \frac{V_{th}^2 R_L}{(R_L + R_{th})^2 + X_{th}^2} \quad \text{--- (II)}$$

Diff. eq-(II) w.r.t  $R_L$  and equated to zero, we get

$$R_L = \sqrt{R_{th}^2 + X_{th}^2}$$

$$R_L = |Z_{th}|$$

$$R_L > R_{th}$$

$$\boxed{\eta > 50\%}$$

### Case-(IV) :-

Both  $R_L$  &  $X_L \rightarrow$  Variable But load


impedance  $\rightarrow$  constant angle

$$Z_L = R_L + jX_L$$

load impedance  $= \theta_L = \tan^{-1}\left(\frac{X_L}{R_L}\right) = \text{constant}$   
 angle

$$R_L = Z_L \cos \theta_L$$

$$X_L = Z_L \sin \theta_L$$

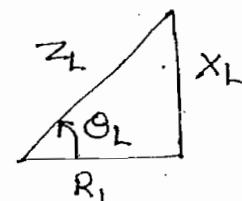


$$P_L = \frac{V_{th}^2 Z_L \cos \theta_L}{(Z_L \cos \theta_L + R_{th})^2 + (Z_L \sin \theta_L + X_{th})^2} \quad (III)$$

Diffr. eq-(III) w.r.t  $Z_L$  and equated to zero, we get

$$Z_L = Z_{th}$$

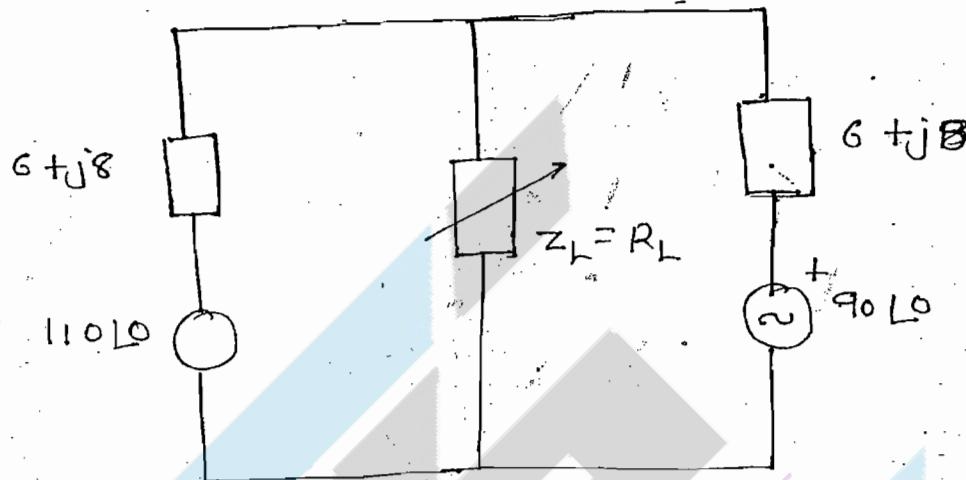
Ans:- Find max power dissipation in load impedance



Soln:- Case-(I) :-  $(V_{th})$

$$\frac{V_{th} - 110 L_0}{6+j8} + \frac{V_{th} - 90 L_0}{6+j8} = 0$$


$$V_{th} = 100 L_0$$

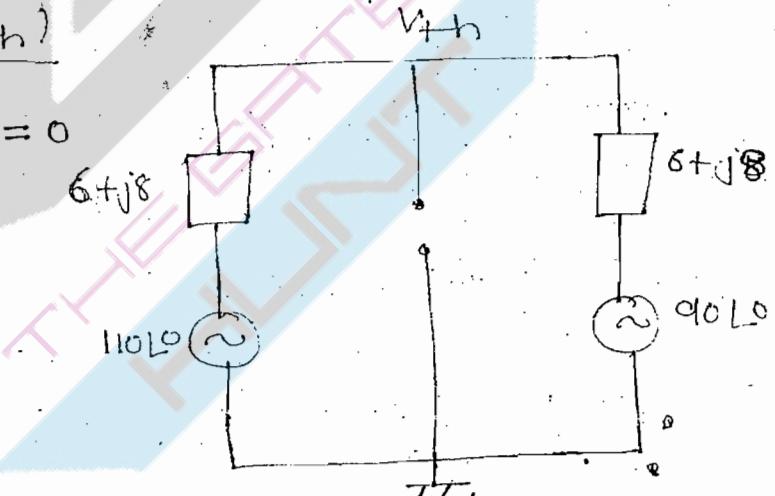

Case-(II)  $(Z_{th})$  :-

$$Z_{th} = \frac{6+j8}{2}$$


$$Z_{th} = 3+j4$$

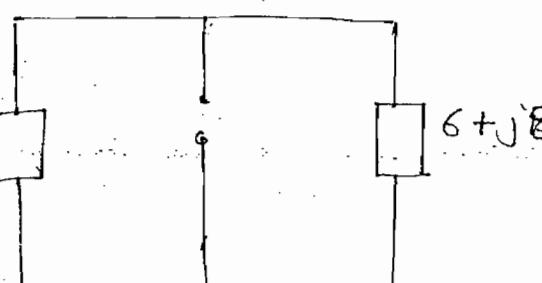


$$R_L = \sqrt{R_{Th}^2 + X_{Th}^2} = \sqrt{3^2 + 4^2} = 5$$

$$i = \frac{100 \angle 0^\circ}{3+j4+5} = \frac{100}{8+j4} = \frac{100}{\sqrt{8^2+4^2}}$$
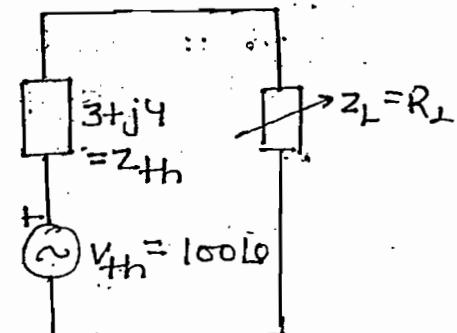
$$P_L = i^2 R_L \Rightarrow P_L = 625 \text{ W}$$



Millman's theorem:

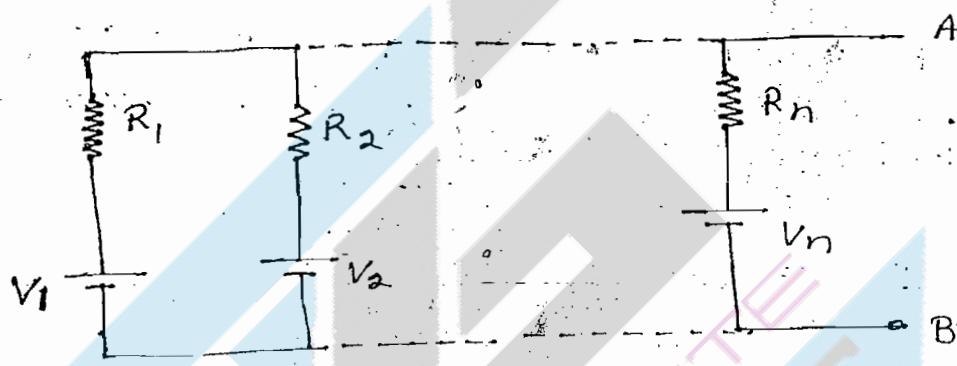


$$R' = R_{Th}$$

$$\frac{1}{R'} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$R' = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$
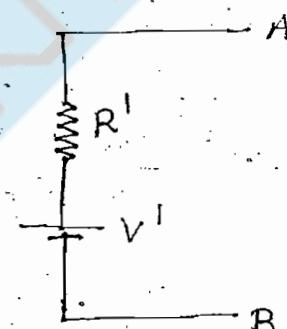
$$R' = \frac{1}{G_1 + G_2 + \dots + G_n}$$




$$V_{Th} = I_{Sc} R_{Th}$$

$$V' = I' R'$$

$$V' = \frac{V_1/R_1 + V_2/R_2 + \dots + V_n/R_n}{G_1 + G_2 + \dots + G_n}$$


PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. 9810000000)
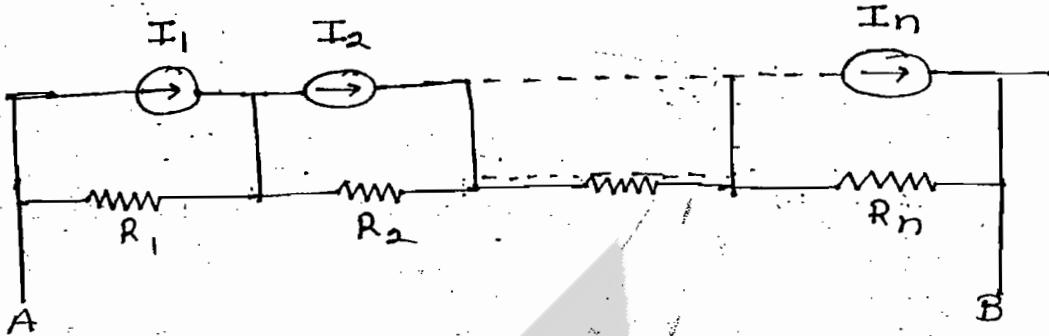
$$V' = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + \dots + G_n}$$



$$R' = R_{th}$$

$$R' = R_1 + R_2 + \dots + R_{th}$$

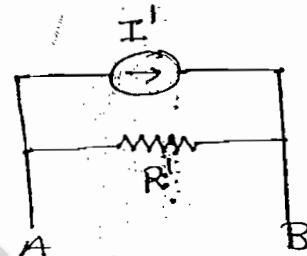



$$I_{sc} = \frac{V_{oc}}{R_{th}}$$

$$I' = \frac{V'}{R'}$$

$$I' = \frac{I_1 R_1 + I_2 R_2 + \dots + I_n R_n}{R_1 + R_2 + \dots + R_n}$$

Ques:- When complex N/w of N is connected to load resistor power dissipation in the load resistor is P Watts.  
When two identical complex N/w of N are connected to same load resistor. Find power dissipation in the load resistor

- (a) P
- (b) 2P
- (c) 4P
- (d) P to 4P

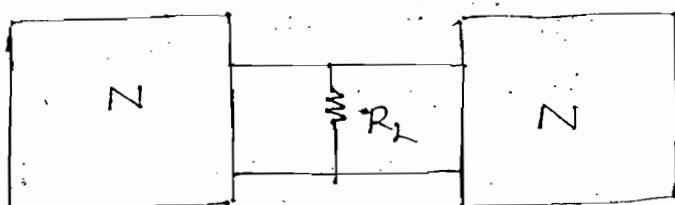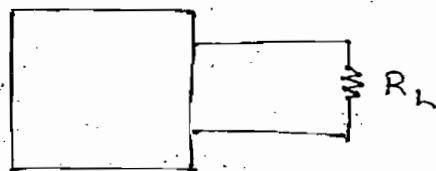

Soln:-

$$I = \frac{V_{th}}{R_L + R_{th}}$$





(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont.-G, 9211010101)

$$P = I^2 R_L$$

$$P = \left( \frac{V_{th}}{R_L + R_{th}} \right)^2 R_L \quad (i)$$

$$V' = \frac{\frac{V_{th}}{R_{th}} + \frac{V_{th}}{R_{th}}}{\frac{1}{R_{th}} + \frac{1}{R_{th}}} = V_{th}$$
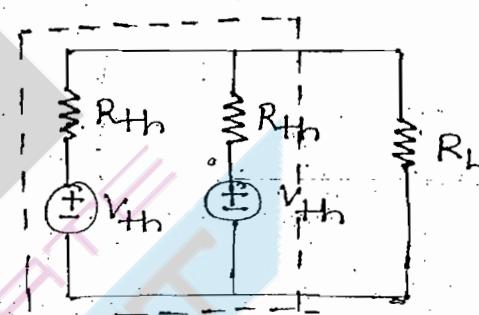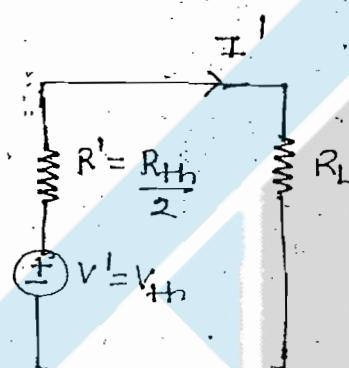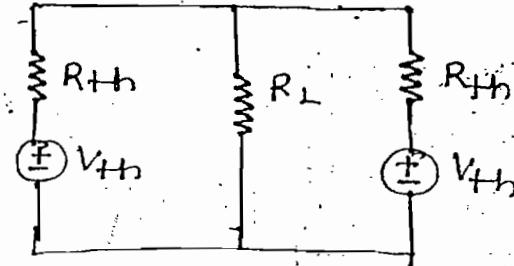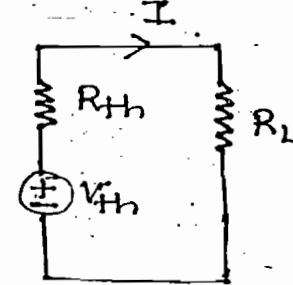
$$R' = \frac{1}{\frac{1}{R_{th}} + \frac{1}{R_{th}}} = \frac{R_{th}}{2}$$




$$I' = \frac{V_{th}}{R_L + \frac{R_{th}}{2}} = \frac{2V_{th}}{2R_L + R_{th}}$$

$$P' = I'^2 R_L = \left( \frac{2V_{th}}{2R_L + R_{th}} \right)^2 R_L \quad (ii)$$

Comparing eq-(i) & (ii) we get option-d

Ques:- Find I of the circuit shown

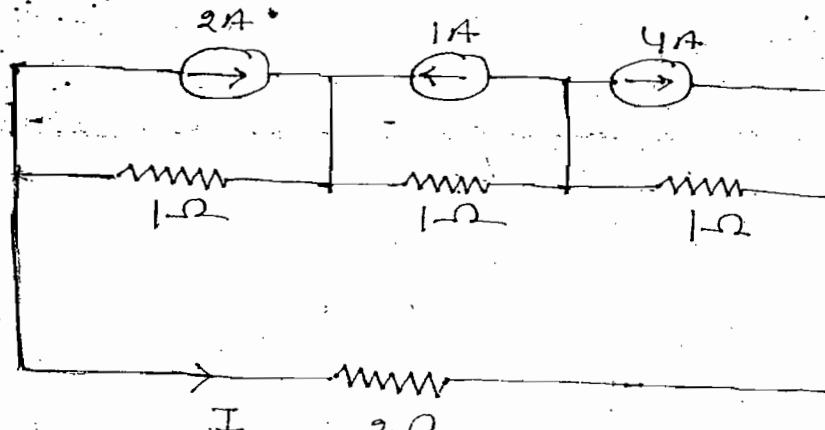


Soln:-

$$I^1 = \frac{(2 \times 1) - (1 \times 1) + (4 \times 1)}{1+1+1} = \frac{5}{3} \quad I^1 = \frac{5}{3} A$$


$$R' = 1+1+1 = 3 \Omega$$
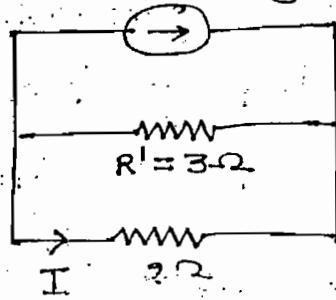
$$I = -\frac{5}{3} \cdot \frac{3}{3+2} = -1 A$$



Tellegen's theorem:-

$$\sum_{k=1}^n V_k i_k = 0$$

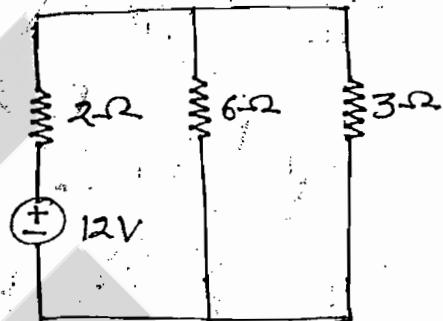

Tellegen's theorem states that algebraic sum of the powers in any circuit at any instant is equal to zero (linear, non-linear, uni-directional, bidirectional, time variant and time invariant elements)

$$R_{eq} = 2 + \frac{6 \times 3}{6+3} = 4$$

$$I_T = \frac{12}{4} = 3 A$$

$$I_6 = 3 \cdot \frac{3}{3+6} = 1 A \quad I_3 = 3-1 = 2 A$$

$$V_2 = I_T \times 2 = 6$$

$$V_6 = V_3 = 2 \times 3 = 6$$


$$V_2 I_T + V_6 I_6 + V_3 I_3 - V_s I_T$$

$$18 + 6 + 12 - 12 \times 3 = 0$$

Note:- Tellegen's theorem is verified by using KCL and KVL equations

→ Tellegen's theorem works based on the principle of law of conservation of energy.


Compensation theorem:-

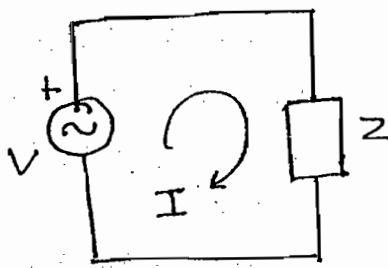

$$I = \frac{V}{Z}$$

$$\Delta I = |I - I'|$$


(Clockwise)

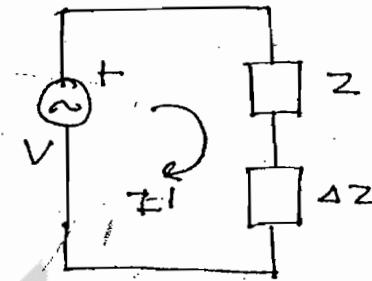

$$I' = \frac{V}{Z + \Delta Z}$$

Modified circuit :-
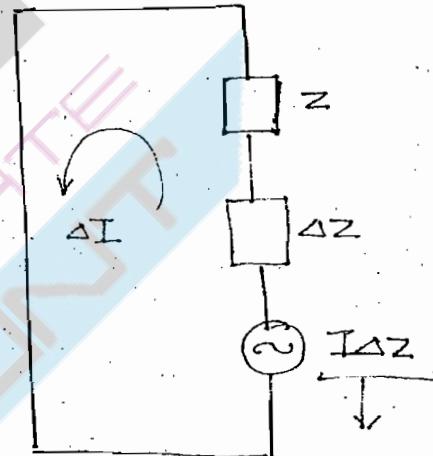
$$\Delta I = -\frac{I \Delta Z}{Z + \Delta Z}$$



Compensation  
emf

or



Opposing emf

PHOTOSTAT  
E-11 Study Material Available  
A-163 Lado Sarai, New Delhi  
Contact No. 9811000000

Ques:- Find change in current in the  $2\Omega$  and  $6\Omega$  resistor when resistance in the variable branch is changed from  $3\Omega$  to  $6\Omega$ .

Soln:- Step-(I) :-

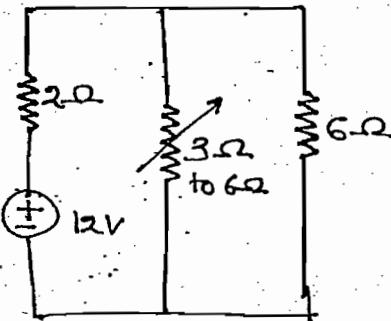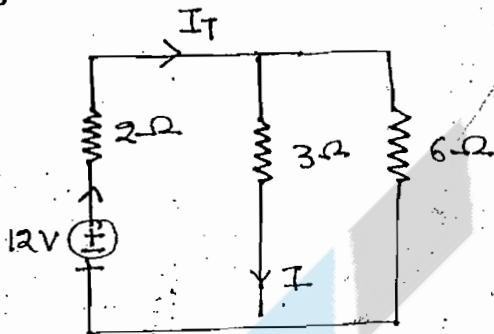Find original current circulating in the variable branch



$$R_{eq} = \frac{2+6}{6+3} = 4$$

$$I_T = \frac{12}{4} = 3A$$

$$I = \frac{6}{6+3} = 2A$$

Step-(II):-

Find compensation emf

$$I \Delta Z = 2(6-3) = 6V$$

Step-(III):-

Develop modified ckt


→ While developing modified circuit deactivate all the original sources and connect the compensation emf in series to variable branch

$$R_{eq} = 6 + \frac{6 \times 2}{6+2}$$

$$I_T = \frac{6}{R_{eq}}$$

$$\Delta I_2 = I_T \cdot \frac{6}{6+2} = 0.6A$$


$$\Delta I_6 = I_T - \Delta I_2 = 0.2A$$

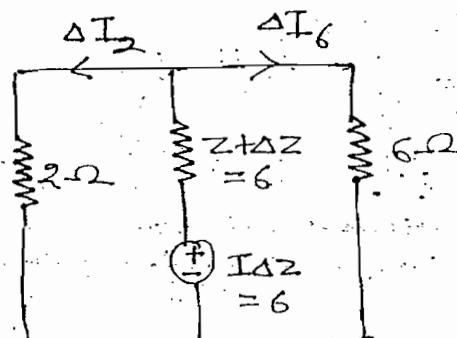




Notes:-

In the bridge circuit by using compensation theory condition for null deflection in the galvanometer is obtained.

## Substitution theorem:

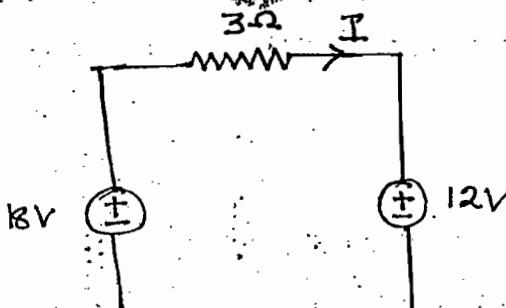

$$I = \frac{18 - 12}{3} = 2$$

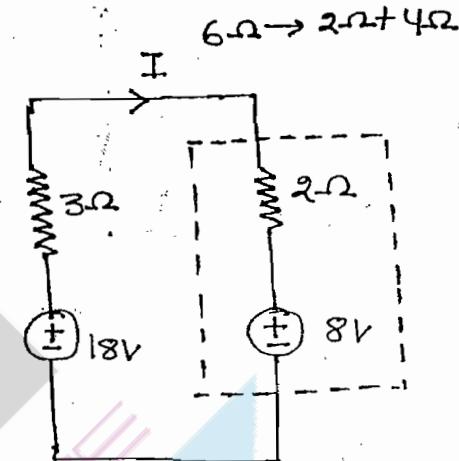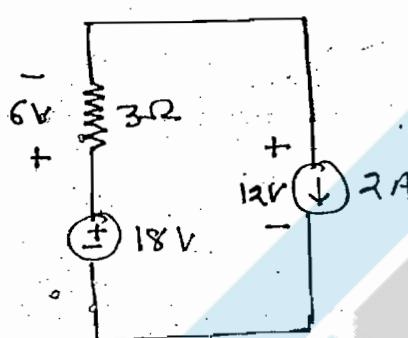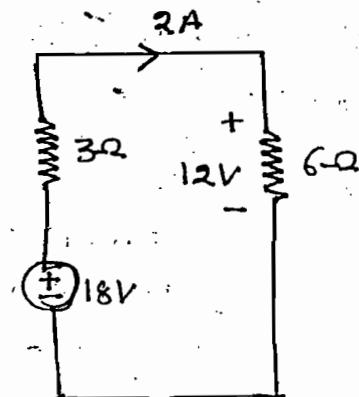

→ All circuits are equivalent.

$$I = \frac{18 - 8}{3 + 2} = 2A$$

Cause:- Find  $R_{th}$  w.r.t. A  
and B



Soln:-

$$\frac{V_A}{8} \text{ to } \frac{V_A - V_X}{4} = 1$$

$$V_X = \frac{V_A}{2}$$

$$V_A = 4V$$

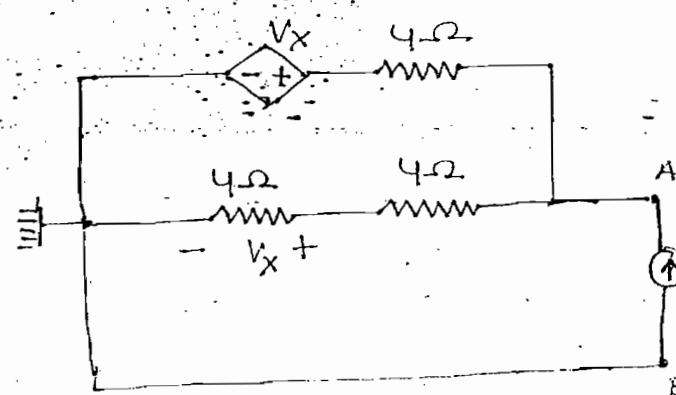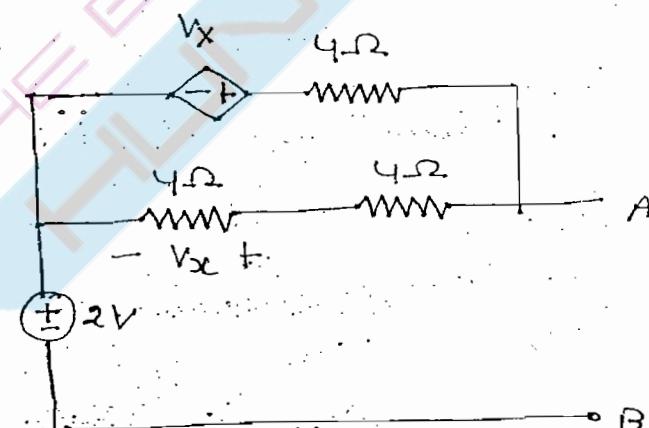
$$R_{th} = \frac{V_A}{I_S} = \frac{4}{1} = 4\Omega$$



Alternate Way:-


By using substitution theorem

$$R_{th} = \frac{8 \times 8}{8+8} = 4$$

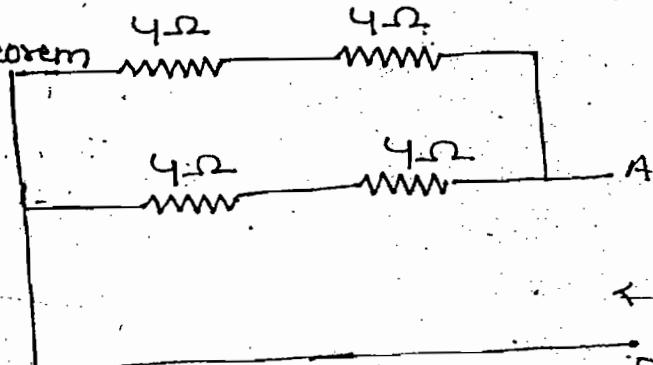

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont-S)

## TRANSIENTS :-

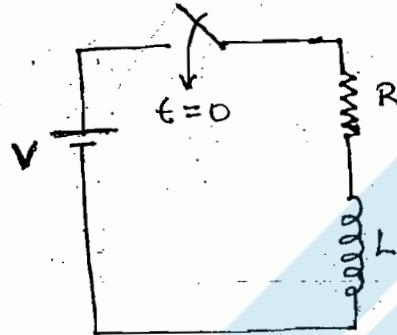

$$t=0^-, i=0$$

$$t=0^+, i=0$$


$\downarrow$   
(O.C.)

$$t=\infty, V_L = L \frac{di}{dt}$$

$$= 0$$

$\downarrow$   
SC

$$i = \frac{V}{R}$$

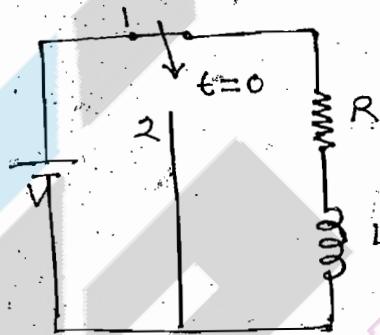


$$t=0^-, i=I_0$$

$$t=0^+, i=I_0$$

Inductor behaves  
as current source

$$t=\infty, i=0$$

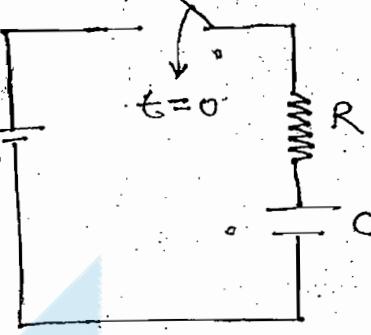

$$t=0^-, V_C = 0$$


$$t=0^+, V_C = 0$$

$\downarrow$   
(S.C.)

$$t=\infty, V_C = V$$

$$i=0$$

$\downarrow$   
(O.C.)

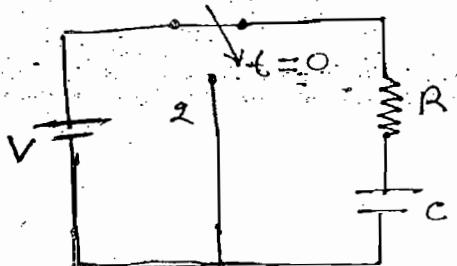


$$t=0^-, V_C = V_0 (V)$$

$$t=0^+, V_C = V_0$$

$\downarrow$   
Acts as voltage source



$$t=\infty, V_C = 0$$

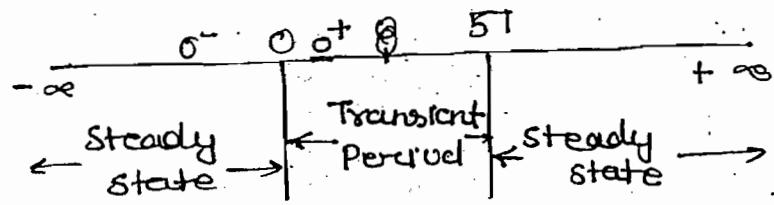

- Transients are present in the circuit when circuit is subjected to any changes either by changing source magnitude or by changing circuit element provided circuit consist of any energy storage element
- When the Ckt is having only resistive element then no transients are present in the N/w since
  - (i) Resistor allows sudden change of current and voltage
  - (ii) Resistor does not store any energy.
- Transients are present in the N/w when the N/w is having any energy storage elements since
  - (i) Inductor does not allow sudden change of current and it stores energy in the form of magnetic field
  - (ii) Capacitor does not allow sudden change of voltage and it stores energy in the form of electric field.
- Due to energy storage property inductor and capacitor are known as dynamic elements (Memory elements)
- $t = 0^-$  indicates immediately before operate the switch
- $t = 0^+$  indicates immediately after operating the switch
- $t = \infty$  indicates steady state condition after operating the switch.

## Source Free RL Circuit:

$t > 0$

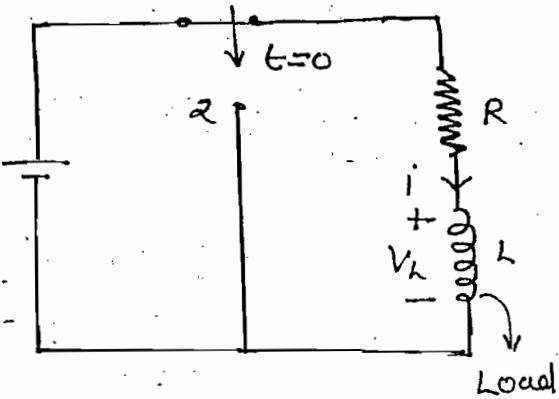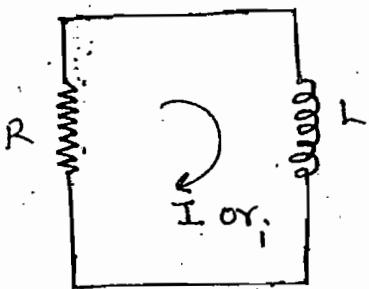


$$iR + L \frac{di}{dt} = 0$$

$$iR = -L \frac{di}{dt}$$


$$\int_0^t -\frac{R}{L} dt = \int_{I_0}^{i(t)} \frac{di}{i}$$
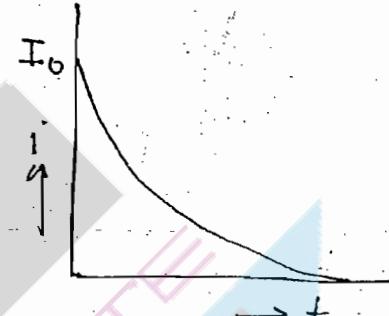
$$\Rightarrow i(t) = I_0 e^{-\frac{Rt}{L}}$$



$$V_R = iR$$

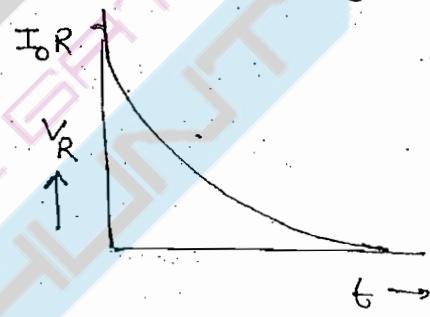
$$\Rightarrow V_R = I_0 R e^{-\frac{Rt}{L}}$$



$$V_L = L \frac{di}{dt}$$

$$V_L = L \frac{d}{dt} (I_0 e^{-\frac{Rt}{L}})$$
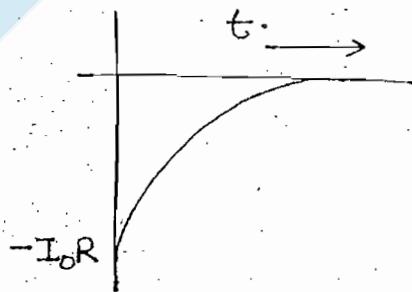
$$\Rightarrow V_L = -I_0 R e^{-\frac{Rt}{L}}$$




$t \rightarrow 0$

$t > 0$

Note:-

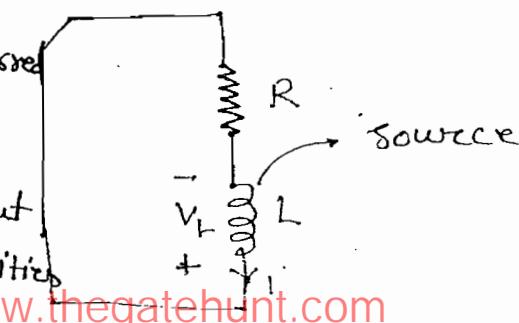When switch is transferred from position 1 to position 2 current direction of the inductor remains same but voltage across inductor polarities are reversed.



## RL Circuit with Source :-


By KVL

$$V = iR + L \frac{di}{dt}$$

Divide whole equation by L

$$\frac{V}{L} = \frac{iR}{L} + \frac{di}{dt}$$
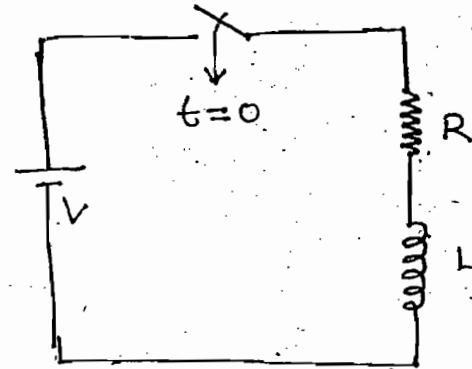
$$\Rightarrow \boxed{\frac{di}{dt} + \frac{R}{L}i = \frac{V}{L}}$$



$$i(t) = C.F + P.I$$

C.F  $\rightarrow$  Transient response or source free response or Natural Response

$$\frac{di}{dt} + \frac{R}{L}i = 0 \Rightarrow i(t) = A e^{\frac{-Rt}{L}}$$

P.I  $\rightarrow$  steady state response or final value or forced response

$$i(t) = C.F + P.I$$

$$i(t) = A e^{\frac{-Rt}{L}} + \frac{V}{R}$$

$$t = 0^- , i = 0$$

$$t = 0^+ , i = 0$$

$$\Rightarrow 0 = A + \frac{V}{R} \Rightarrow A = 0 - \frac{V}{R}$$

$$\Rightarrow \boxed{A = i(0^+) - i(\infty)}$$

PHOTOSTAT  
(All Study Material Available,  
A-163 Lado Sarai, New Delhi  
Cont. 011-3352070

$\rightarrow$  Applicable for RL or RC circuit with source.

$$i(t) = C \cdot F + P I$$

$$i(t) = -\frac{V}{R} e^{-\frac{Rt}{L}} + \frac{V}{R}$$



$$\Rightarrow i(t) = [i(0^+) - i(\infty)] e^{-\frac{Rt}{L}} + i(\infty)$$

→ Valid for RL and RC circuit.

$$i(t) = \frac{V}{R} (1 - e^{-\frac{Rt}{L}}) \rightarrow$$

$$V_R = iR$$
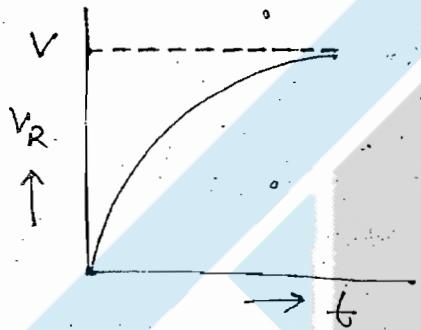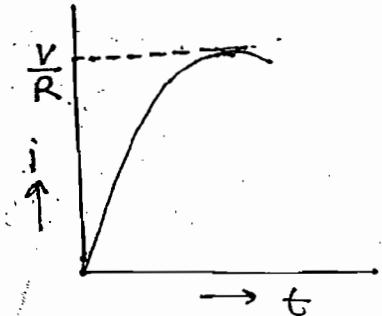
$$\Rightarrow V_R = V (1 - e^{-\frac{Rt}{L}})$$




PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. 2722222222



$$V_L = L \frac{di}{dt}$$

$$V_L = L \frac{d}{dt} \left[ \frac{V}{R} (1 - e^{-\frac{Rt}{L}}) \right]$$

$$V_L = V_0 e^{-\frac{Rt}{L}}$$

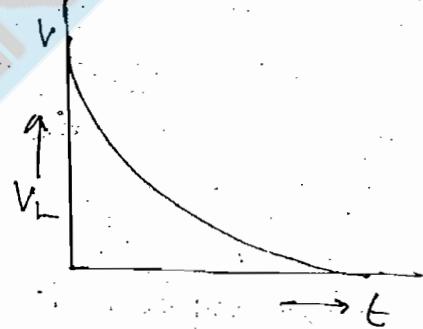

### Source Free RC Circuit

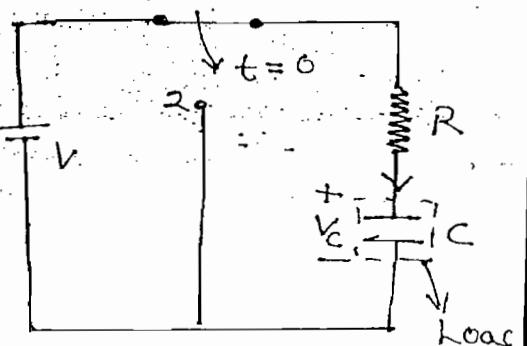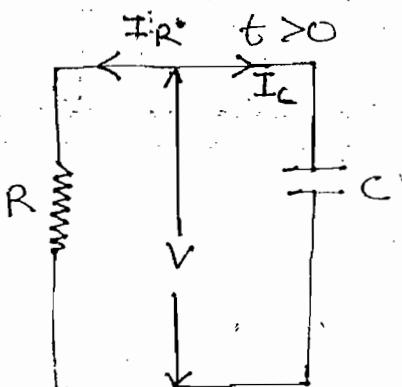

$$t = 0^-, V_C = V_0$$

$$t = 0^+, V_C = V_0$$


$$I_R + I_C = 0$$

$$\Rightarrow \frac{V}{R} + C \frac{dV}{dt} = 0$$

$$\Rightarrow \frac{V}{R} = -C \frac{dV}{dt}$$


$$\Rightarrow \int_{0}^{t} -\frac{1}{RC} dt = \int_{V_0}^{V(t)} \frac{dV}{V}$$

$$\Rightarrow V(t) = V_0 e^{-t/RC}$$

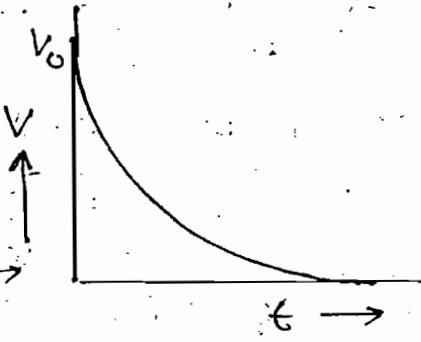

$$I_R = \frac{V}{R}$$

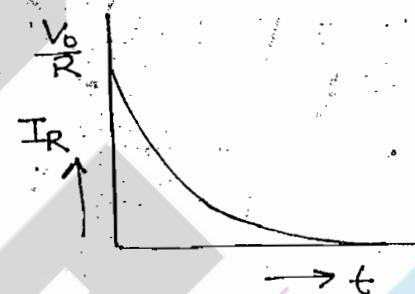
$$\Rightarrow I_R = \frac{V_0}{R} e^{-t/RC}$$



$$I_C = C \frac{dV}{dt}$$

$$I_C = C \frac{d}{dt} (V_0 e^{-t/RC})$$

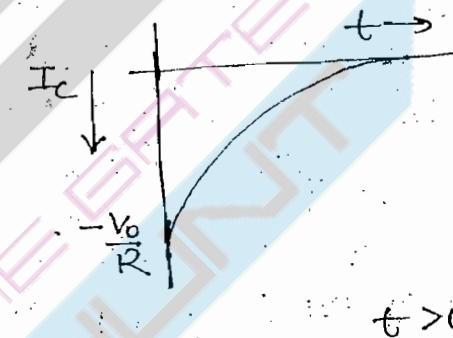
$$\Rightarrow I_C = -\frac{V_0}{R} e^{-t/RC}$$



$t > 0$

Note:-

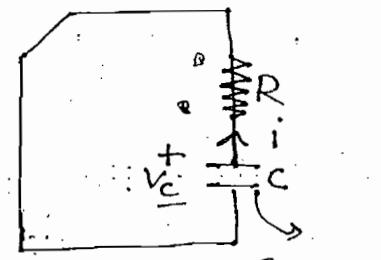When switch is transferred from position 1 to position 2 voltage across the capacitor will remain same but current direction of the capacitor is reversed.



$$I_R = -I_C$$

AT PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contact: 98911 11770

RC Circuit with Source

By KVL

$$V = iR + \frac{1}{C} \int idt$$

Diff. w.r.t. t

$$0 = R \frac{di}{dt} + \frac{i}{C}$$

Divide both sides by R we get

$$\frac{di}{dt} + \frac{i}{RC} = 0$$

$$i(t) = CF + PI$$

CF  $\rightarrow$  Transient Response

$$\frac{di}{dt} + \frac{i}{R} = 0$$

$$i(t) = A e^{-t/RC}$$

PI  $\rightarrow$  steady state responseC  $\rightarrow$  o.c

i = 0

$$i(t) = CF + PI$$

$$i(t) = A C^{-t/RC} + 0$$

$$A = i(0^+) - i(\infty)$$

$$t = 0^+, V_C = 0$$


$$t = 0^+, V_C = 0$$

By KVL

$$t = 0^+, V = V_R + V_C \\ = iR + 0$$

$$at t \rightarrow 0^+ t(0^+) \quad i = \frac{V}{R}$$

$$i(t) = CF + PI$$

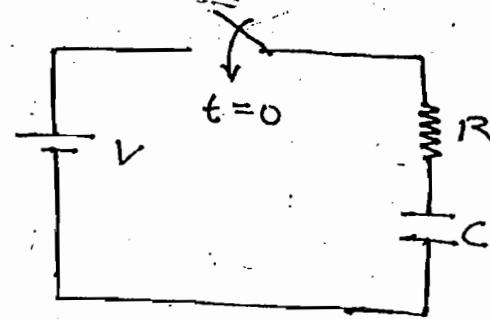


$$A = i(0^+) - i(\infty)$$

$$A = \frac{V}{R} - 0$$


$$i(t) = \frac{V}{R} e^{-t/RC}$$

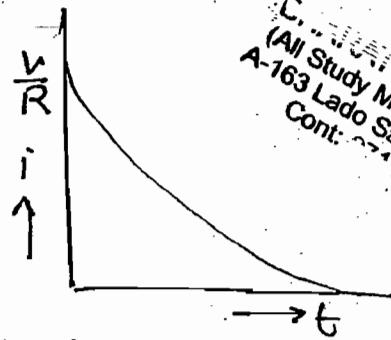C. ... HOTOSTAT  
 All Study Material Available  
 (All Study Material Available)  
 A-163 Lado Sarai, New Delhi  
 Cont: 9810101010



$$V_R = iR$$

$$V_R = V e^{-t/RC}$$

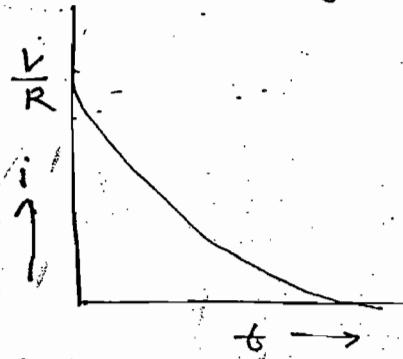


$$V_C = \frac{1}{C} \int_0^t i dt$$

$$V_C = \frac{1}{C} \int_0^t \frac{V}{R} e^{-t/RC} dt$$

$$V_C = -V e^{-t/RC} + V$$


$$V_C(t) = [V_C(0^+) - V_C(\infty)] e^{-t/RC} + V_C(\infty)$$

$$V_C(t) = V(1 - e^{-t/RC})$$

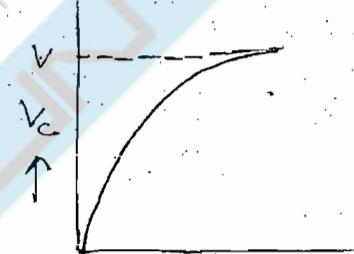


Ques:- Find response of  $V_C$ ,  $I_C$  and  $V_x$  when initial voltage of the capacitor is 3V

Soln:-

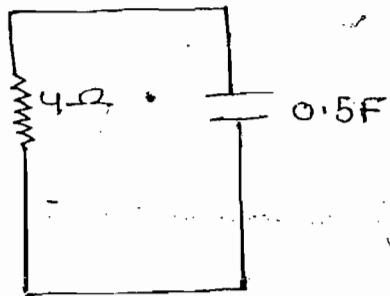

$$V_C = V_0 e^{-t/RC}$$

$$V_C = 3 e^{-t/2}$$

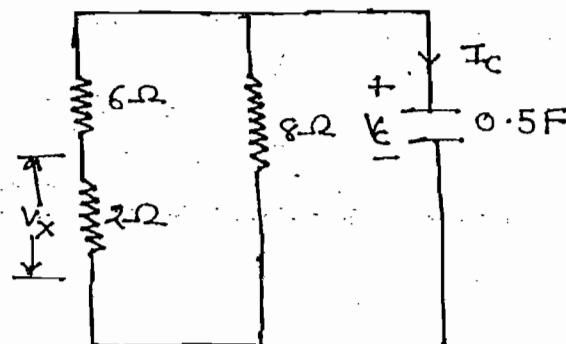

$$V_x = V_c \frac{2}{2+6} \Rightarrow V_x = 3e^{-t/2} / 4$$

$$\Rightarrow V_x = \frac{3}{4} e^{-t/2}$$

$$I_c = C \frac{dV_c}{dt}$$

$$I_c = \frac{1}{2} \frac{d(3e^{-t/2})}{dt} = 3 \left(\frac{1}{2}\right) \left(-\frac{1}{2}\right) e^{-t/2}$$

$$\Rightarrow I_c = -\frac{3}{4} e^{-t/2} \quad \text{Ans}$$

Ques:- Find rate of rise of voltage across the capacitor at  $t = 0^+$

- (a)  $RC$  (b)  $\frac{1}{RC}$  (c)  $0$  (d)  $2RC$

Soln:-

$$V_c = -Ve^{-t/RC} + V$$

$$\frac{dV_c}{dt} = (-V) \left(-\frac{1}{RC}\right) e^{-t/RC} + 0$$

$$\frac{dV_c}{dt} = \frac{V}{RC} e^{-t/RC}$$


$$t = 0^+$$

$$\frac{dV_c}{dt}(0^+) = \frac{V}{RC} = \frac{1}{RC}$$


Ques:- Find  $\frac{di_1}{dt}$  at  $t = 0^+$

Soln:- Step-(1) :-

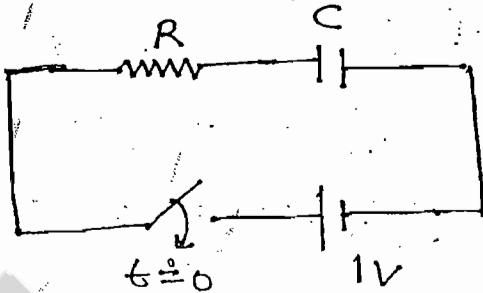Develop eq circuit at  $t = 0^-$  and find initial current of conductor and initial voltage of capacitor



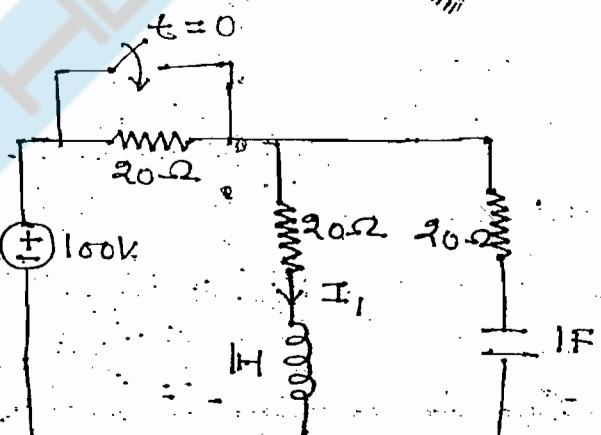PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. 2210111111)



In the above ckt at  $t = 0^-$  for DC source inductor behaves as S.C. and C behaves as O.C

$$i_L(0^-) = \frac{100}{20+20} = 2.5A$$

$$V_C(0^-) = 2.5 \times 20 = 50$$

Step-2:-

Develop eq. ckt at  $t=0^+$  and indicate initial current of the inductor and initial voltage of the capacitor.


$$\therefore t=0^+$$

$$i_L(0^+) = i_L(0^-) = 2.5A$$


$$\therefore V_C(0^+) = V_C(0^-) = 50V$$

$$V_L = L \frac{di}{dt}$$
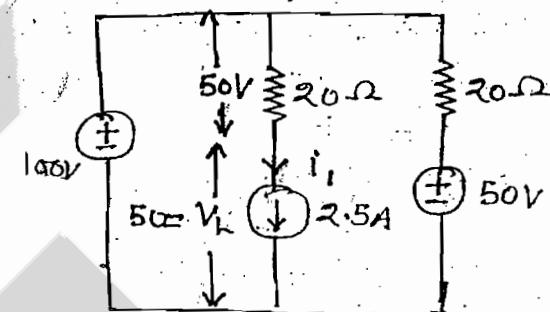
$$\Rightarrow 50 = 1 \frac{di}{dt} \Rightarrow \frac{di}{dt} = 50A/S \text{ ans}$$



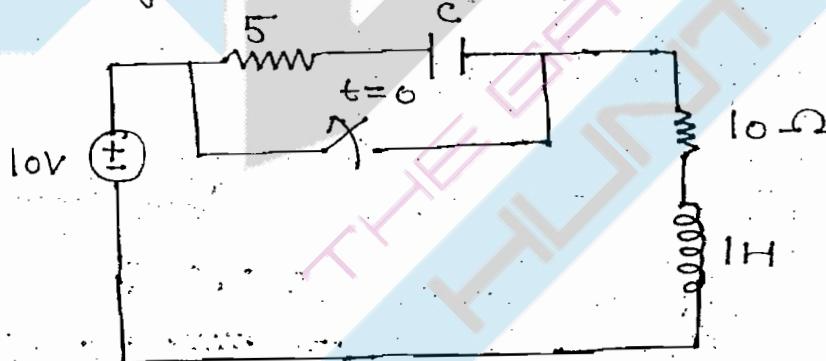Ques:- Find voltage across the switch at  $t=0^+$




Soln:- At  $t=0^-$

→ Develop equivalent circuit at  $t=0^-$

→ In the above ckt. at  $t=0^-$  capacitor is uncharged & for DC source inductor behaves as a S.C
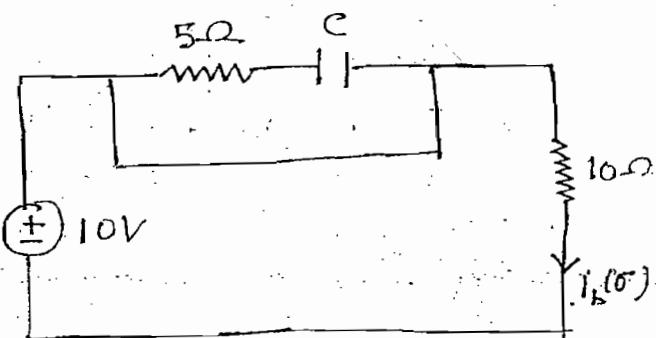
$$i_L(0^-) = \frac{10}{10} = 1A, V_C(0^-) = 0$$




Step-2:-

$$\text{At } t = 0^+$$

$$i_L(0^+) = i_L(0^-) = 1A$$

$$V_C(0^+) = V_C(0^-) = 0$$

$$V(0^+) = 5 \times 1 = 5V$$

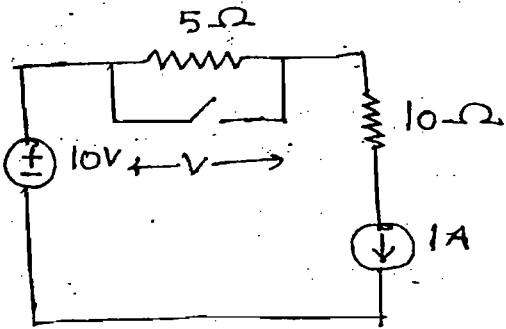


ques:- Find I in capacitor and voltage across inductor

at  $t = 0^+$

Soln:- Step (1) :-

Develop eq. ckt. at  $t = 0^-$

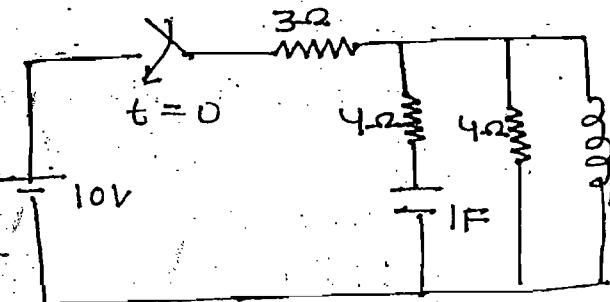

→ In the above ckt. at  $t = 0^-$  capacitor and inductor are uncharged elements.

$$t = 0^-, \quad V_C(0^-) = 0$$

$$i_L(0^-) = 0$$

Step-(II) :-


At  $t = 0^+$

$$i_L(0^+) = i_L(0^-) = 0$$

$$V_C(0^+) = V_C(0^-) = 0$$

$$I_C(0^+) = 1A$$


$$V_L(0^+) = 4 \times 1 = 4V$$

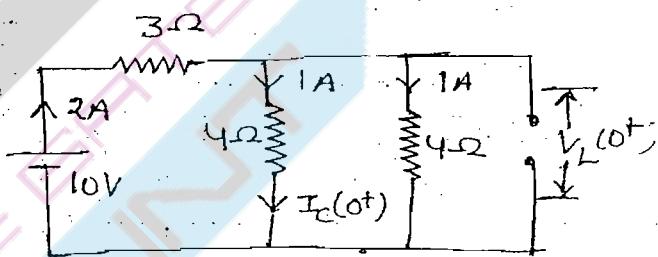

ques:- Find initial voltage and final voltage of the capacitor

Soln:- Step (1) :-

$$t = 0^-$$

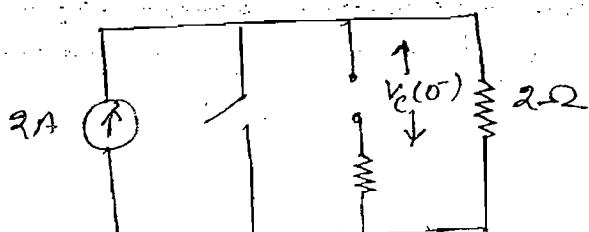


$$V_C(0^-) = 2 \times 2 = 4V$$

Step-(II):-

$$\text{At } t = 0^+.$$

$$V_C(0^+) = V_C(0^-) = 4V$$

$$V_C(\infty) = 0$$

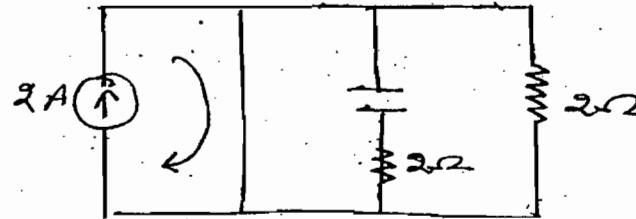


Ques:- Find

(i) Energy of Capacitor at  $t = \infty$

(ii) Current in the capacitor at  $t = 1\text{ sec}$

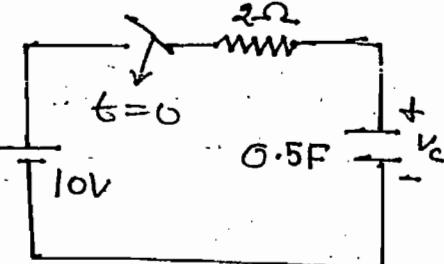(iii) Energy of the resistor from 0 to  $\infty$  interval




When initial charge of the capacitor is 10C


Soln:- At  $t = 0^+$  ( $\therefore Q_{ini} = 10\text{C}$ )

$$V_0 = \frac{Q_0}{C} = \frac{10}{0.5} \Rightarrow V_0 = 20$$

At  $t = \infty$

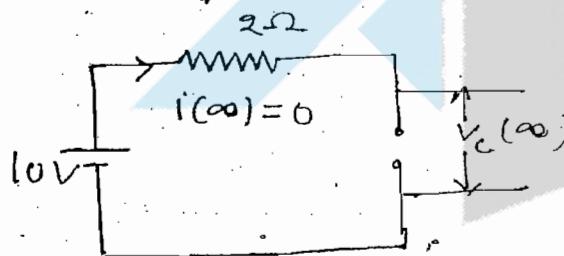

$$V_C(\infty) = 10V$$

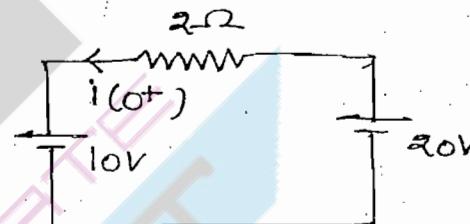

$$W_C(\infty) = \frac{1}{2} C V_C^2(\infty) = \frac{1}{2} \cdot \frac{1}{2} \cdot (10)^2 = 25\text{J}$$

$$(i) i(t) = [i(0^+) + i(\infty)] e^{-t/RC} + i(\infty)$$

$$\Rightarrow i(t) = [-5 - 0] e^{-t/1} + 0$$

$$i(t) = -5 e^{-t}$$

At  $t = 1\text{ sec}$

$$i(1s) = -5 e^{-1} = -\frac{5}{e}$$

$$= -1.84$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont:

$$(iii) W_R = \int_0^{\infty} P_{dt} = \int_0^{\infty} i^2 R dt = \int_0^{\infty} (-5e^{-t})^2 2 dt$$

$$\Rightarrow W_R = 25 J, \text{ Ans.}$$

Time Constant :-

→ Time constant can be defined either w.r.t charging or discharging action of energy storage element.

↔ Time constant is the time taken for response to rise 63.2% of max. value and it is given by

$$T = \frac{L}{R} \text{ sec.}$$

$$T = RC$$

$$V_C(t) = V(1 - e^{-t/T})$$

$$(i) t = T \quad V_C = V(1 - e^{-1}) = 0.632V$$

$$t = 5T \quad V_C = V(1 - e^{-5}) = 0.99V$$


$$R_1 = 10\Omega \quad P_1 = I^2 R_1 \quad t = 1 \text{ sec}$$

$$R_2 = 20\Omega \quad P_2 = I^2 R_2 \quad t = 7 \text{ sec}$$

$$R_3 = 100\Omega \quad P_3 = I^2 R_3 \quad t = 2 \text{ sec}$$

$$\text{Hence } T = \frac{L}{R}$$


RC ckt with source

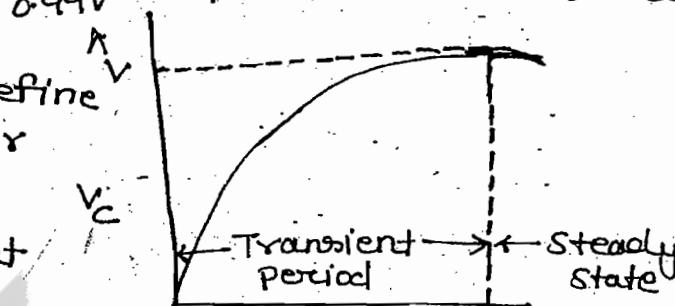

(i)

$t = \frac{5T}{5}$

RC ckt with source

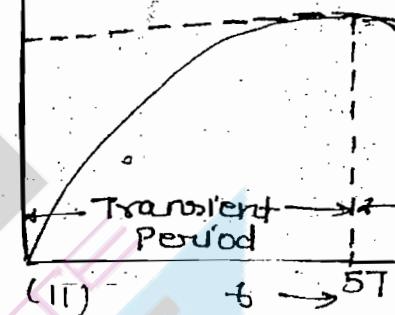


(ii)

$t = \frac{5T}{5}$

$$(i) V_C(t) = V(1 - e^{-t/RC})$$

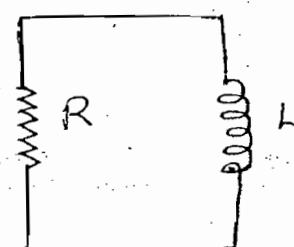
$$(ii) i(t) = \frac{V}{R}(1 - e^{-t/RC})$$



$$R_1 = 10\Omega \quad P_1 = \frac{V^2}{R_1} \quad t = 10\text{sec}$$

$$R_2 = 20\Omega \quad P_2 = \frac{V^2}{R_2} \quad t = 15\text{sec}$$
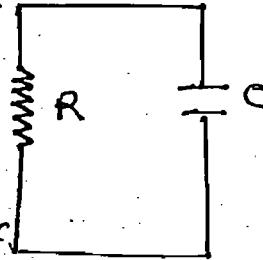
$$R_3 = 100\Omega \quad P_3 = \frac{V^2}{R_3} \quad t = 50\text{sec}$$



$$\text{Hence } T = RC$$

Ques:- Find  $V_o$  response

for  $t > 0$

$$V_{C_1}(0) = 24V$$


$$V_{C_2}(0) = 6V$$

$$(a) 8 + 22e^{-3.75t}$$

$$(b) 8 + 22e^{-t/3.75}$$

$$(c) 8 + 22e^{-t/1.2}$$


$$(d) 8 + 22e^{-1.2t}$$

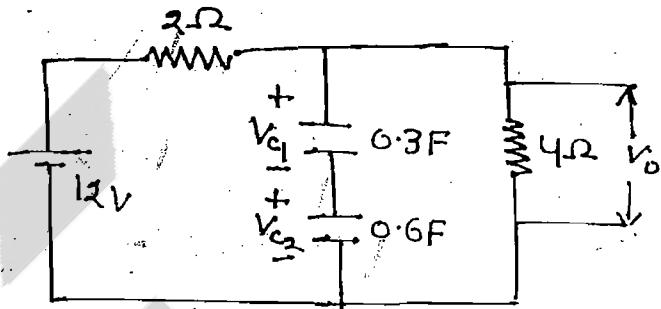

Soln:- For time constant, deactivate all the independent sources

$$R_{eq} = \frac{2 \times 4}{2+4}$$
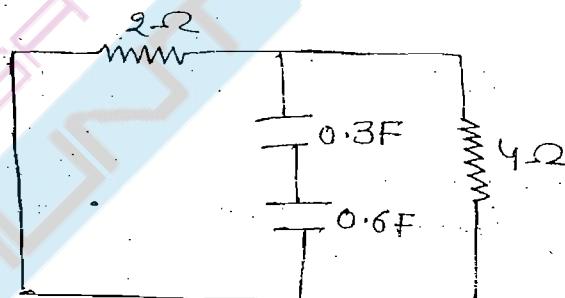
$$C_{eq} = \frac{0.3 \times 0.6}{0.3+0.6}$$



$$T^* = R_{eq}C_{eq} = RC$$

$$V(t) = [V(0^+) - V(\infty)] e^{-t/RC} + V(\infty)$$

$$V_o(t) = [V_o(0^+) - V_o(\infty)] e^{-t/RC} + V_o(\infty)$$

$$V_o = V_{C_1} + V_{C_2}$$

$$t = 0^+$$


$$V_o(0^+) = V_{C_1}(0^+) + V_{C_2}(0^+) = 24 + 6 = 30$$

$$\text{At } t = \infty$$


At  $t = \infty$

$$V_o(\infty) = 2 \times 4 = 8$$
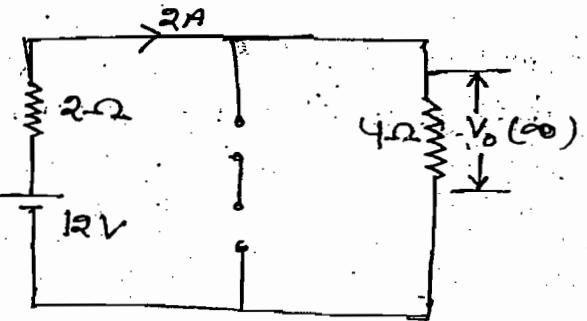
$$\begin{aligned} V_o(t) &= [80 - 8] e^{-3.75t} + 8 \\ &= 8 + 22 e^{-3.75t} \end{aligned}$$




(I)

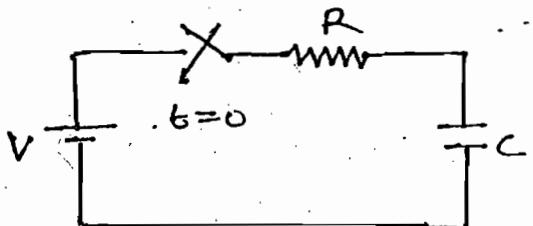


At  $t = 0^+$ ,  $V_C = 0$

$t = 0^+, V_C = 0$

$$T = RC$$

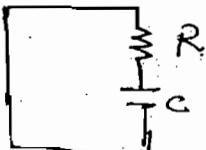


(II)

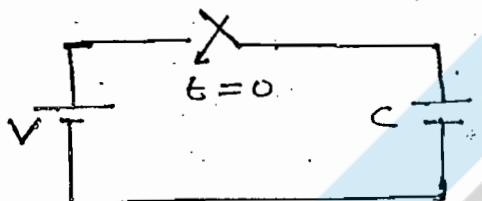


$t = 0^-, V_C = 0$

$t = 0^+, V_C = V$

$$T = RC = 0$$

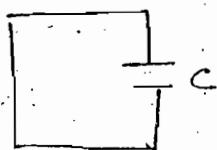


(III)

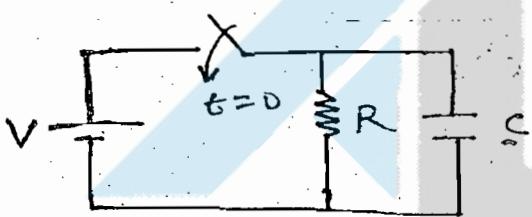


$t = 0^-, V_C = 0$

$t = 0^+, V_C = V$

$$T = RC = 0$$

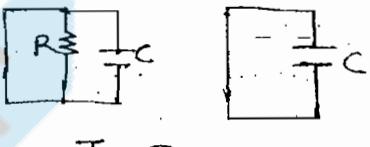


(IV)

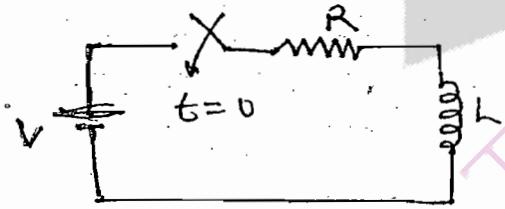


$t = 0^-, i = 0$

$t = 0^+, i = 0$

$$T = R/L$$

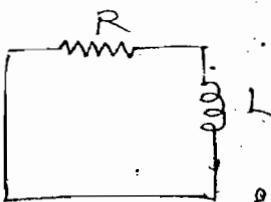

(V)

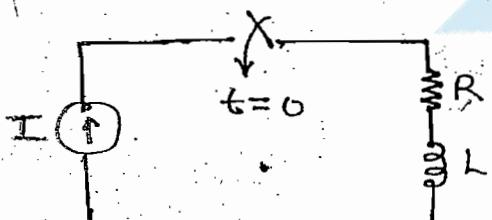


$t = 0^-, i = 0$

$t = 0^+, i = I$

$$R_{eq} = R_{oc} + R = \infty$$

$$T = \frac{L}{R_{eq}} = 0$$

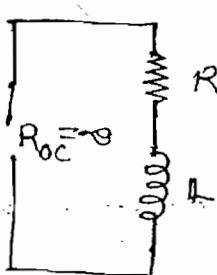

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9713132210




CHART

PHOTOSTAT

Downloaded from www.thegatehunt.com

Ques:- Find time constant of the circuit shown

SOP:-

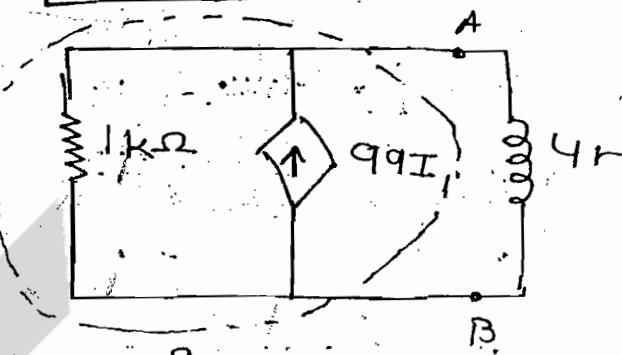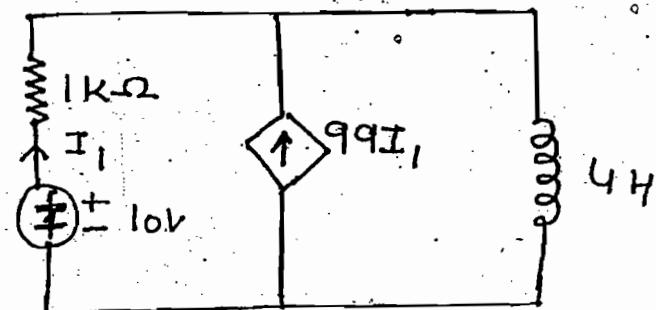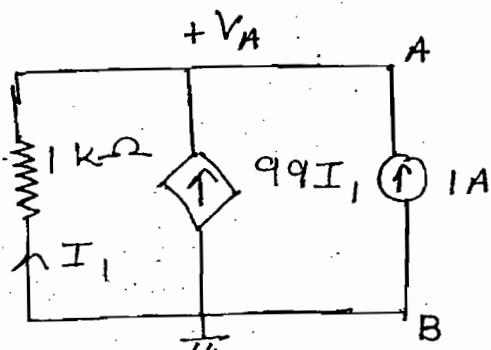

$$\frac{V_A}{1 \times 10^3} = 99I_1 + 1 \quad \text{---(I)}$$

$$I_1 = -\frac{V_A}{1 \times 10^3} \quad \text{---(II)}$$


$$R_{Th} = \frac{V_A}{I_S} = \frac{10}{1} = 10 \Omega$$

$$T = \frac{L}{R_{Th}} = \frac{4}{10}$$

$$R_{Th}$$

From (I) & (II)

$$V_A = 10V$$

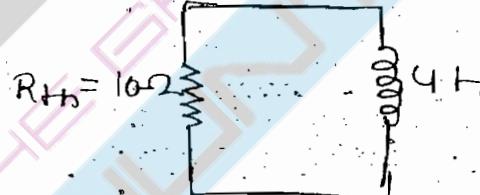


BEST  
PHOTOSTAT

NEWEST PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai New Delhi  
Cont: 011 2656 2659
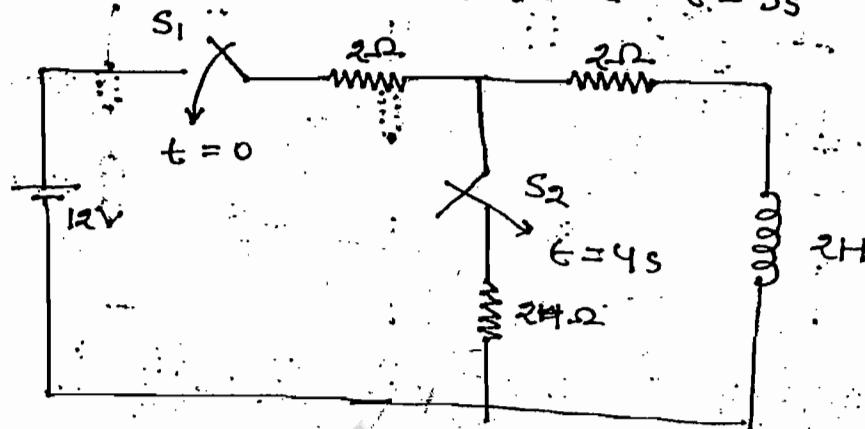
## Lecture - 10

PHOTOSTAT  
Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9718102070

Ques:- Find current in the inductor at  $t = 5s$



Soln:-

$S_1$

$$i(t) = \frac{V}{R} (1 - e^{-\frac{Rt}{L}})$$

$$i(t) = \frac{12}{4} (1 - e^{-2t}) \Rightarrow i(t) = 3(1 - e^{-2t})$$

$t > 4s$ ,  $S_1$  and  $S_2 \rightarrow$  operated

$$i(t) = [i(0^+) - i(\infty)]e^{-\frac{R't}{L}} + i(\infty)$$

$$\Rightarrow i(t) = [i(4) - i(\infty)]e^{-\frac{R'}{L}(t-4)} + i(\infty) - (1)$$

$t = 4$

$$i(4) = 3[1 - e^{-2(4)}] \approx 2.99A$$

$t = \infty$

$$i(\infty) = 2A$$



Time constant for  $t > 4s$

$$R' = 3 \quad -(II)$$


From - (I) & (II)

$$i(t) = [2.99 - 2] e^{-\frac{3}{2}(t-4)} + 2$$

$t = 5 \text{ sec.}$

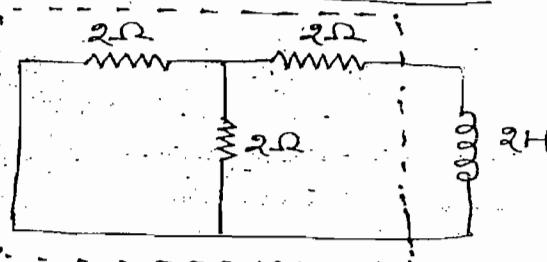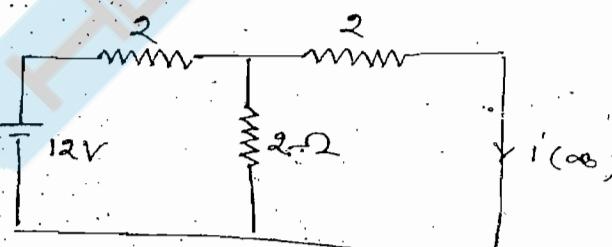

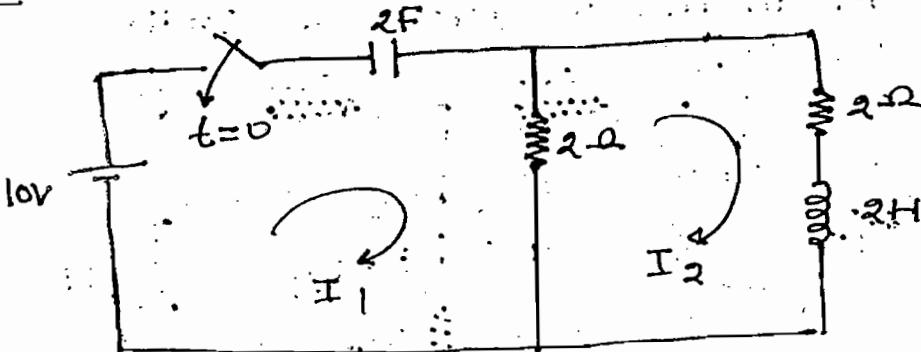PHOTOSTAT  
Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9718102070



Find  $i_1(0^+)$ ,  $i_2(0^+)$ ,  $v_c(0^+)$ ,  $\frac{di_1(0^+)}{dt}$ ,  $\frac{di_2(0^+)}{dt}$ ,  $\frac{d^2i_1(0^+)}{dt^2}$ ,

$$\frac{d^2i_2(0^+)}{dt^2}$$

Soln:-

At  $t = 0^-$

$$i_1(0^-) = 0 \quad i_2(0^-) = 0 \quad v_c(0^-) = 0$$

At  $t = 0^+$

$$i_2(0^+) = 0 \quad v_c(0^+) = 0 \quad i_1(0^+) = \frac{10}{2} = 5A$$

$$(I) \rightarrow 4i_2 + 2\frac{di_2}{dt} - 2i_1 = 0 \quad \rightarrow t = 0^+$$

$$4(0) + 2\frac{di_2}{dt} - 2(5) = 0$$

$$\Rightarrow \frac{di_2}{dt} = 5A/s$$

SHAIKAT PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont.- 98911 22222

$$-10 + \frac{1}{2} \int i_1 dt + 2(i_1 - i_2) = 0$$

Diff. w.r.t. t

$$0 + \frac{i_1}{2} + 2 \left[ \frac{di_1}{dt} - \frac{di_2}{dt} \right] = 0 \quad (II)$$

$$\Rightarrow \frac{5}{2} + 2 \left[ \frac{di_1}{dt} - 5 \right] = 0$$

$$\Rightarrow \frac{5}{2} - 10 + \frac{2di_1}{dt} = 0$$

$$\Rightarrow \frac{di_1}{dt} = \frac{15}{4} = 3.75 A/s$$

Diff eq - (1)  $\omega \cdot r + \frac{d^2 i}{dt^2}$

$$4 \frac{di_2}{dt} + 2 \frac{d^2 i_2}{dt^2} - 2 \frac{di_1}{dt} = 0$$

$$\Rightarrow \frac{d^2 i_2}{dt^2} = -6.25 \text{ A/s}^2$$

Diff eq - (1),  $\omega \cdot r + \frac{d^2 i}{dt^2}$

$$\frac{1}{2} \frac{di_1}{dt} + 2 \left[ \frac{d^2 i_1}{dt^2} - \frac{d^2 i_2}{dt^2} \right] = 0$$

$$\Rightarrow \frac{d^2 i_1}{dt^2} = -7.18 \text{ A/s}^2$$

RLC Series Circuit with AC Excitation :-


By KVL

$$V = IR + L \frac{di}{dt} + \frac{1}{C} \int idt$$

Diff  $\omega \cdot r + \frac{d^2 i}{dt^2}$

$$0 = R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C}$$

Divide both sides by L we get

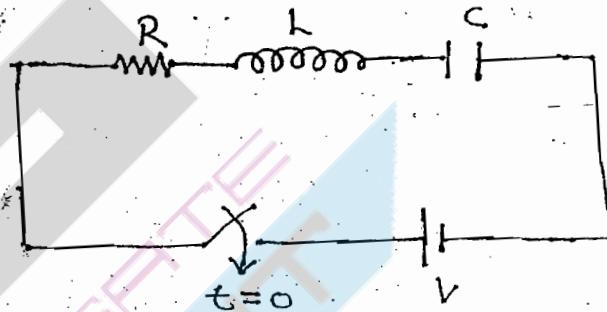

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

$$\left( \omega_0^2 + \frac{R}{L} \omega + \frac{1}{LC} \right) i = 0 \quad \left( \because \frac{d}{dt} = \omega \right)$$

$$\omega_1, \omega_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}$$

$$\omega_1, \omega_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9810182333

Case-(I) :-

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

Overdamping

$$\alpha = \frac{-R}{2L}$$

$$\beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)}$$

$$i(t) = C_1 e^{(\alpha-\beta)t} + C_2 e^{(\alpha+\beta)t}$$

Case-(II) :-

$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$$

→ Critical damping

$$i(t) = (C_1 + C_2 t) e^{\alpha t}$$

Case-(III) :-

$$\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$$

→ Underdamping

$$\alpha = \frac{R}{2L}$$

$$\beta = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$i(t) = (C_1 \cos \beta t + C_2 \sin \beta t) e^{\alpha t}$$

$$\text{Damping coefficient} = \frac{R}{2L}$$

$$\text{Time constant} = \frac{1}{\text{Damping Coefficient}} = \frac{2L}{R}$$

Case-(IV) :-

$$R=0 \rightarrow \text{Underdamping}$$

$$\alpha = 0, \quad \beta = \frac{1}{\sqrt{LC}}$$

$$i(t) = C_1 \cos \beta t + C_2 \sin \beta t$$

RLC Parallel Circuit with AC Excitation:-

$$I = \frac{V}{R} + C \frac{dV}{dt} + \frac{1}{L} \int V dt$$

Diffr. w.r.t. t

$$0 = \frac{1}{R} \frac{dV}{dt} + C \frac{d^2V}{dt^2} + \frac{V}{L}$$

Divide the whole equation by C, we get

$$\frac{d^2V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{V}{LC} = 0$$

$$(D^2 + \frac{1}{RC} D + \frac{1}{LC})V = 0. \quad (\because D = \frac{d}{dt})$$

$$\omega_1, \omega_2 = \frac{-\frac{1}{RC}}{2} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}$$

$$\alpha_1, \alpha_2 = \frac{-\frac{1}{2RC}}{2} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

Case-(I):-

$$\left(\frac{1}{2RC}\right)^2 > \frac{1}{LC} \rightarrow \text{over damping}$$

$$\alpha = -\frac{1}{2RC}$$


$$\beta = \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$V(t) = C_1 e^{(\alpha-\beta)t} + C_2 e^{(\alpha+\beta)t}$$

Case-(II):-

$$\left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} \rightarrow \text{critical damping}$$

$$r(t) = (C_1 + C_2 t) e^{\alpha t}$$

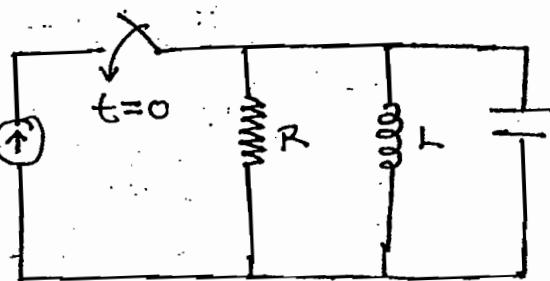

Case-(III) :-

$$\left(\frac{1}{2RC}\right)^2 < \frac{1}{LC} \rightarrow \text{Under damping}$$

$$\alpha = -\frac{1}{2RC}, \quad \beta = \sqrt{\frac{1}{LC} - \left(\frac{1}{2RC}\right)^2}$$

$$V(t) = (c_1 \cos \beta t + c_2 \sin \beta t) e^{\alpha t}$$

$$\text{Damping coefficient} = \frac{1}{2RC}$$

$$\text{Time constant} = \frac{1}{\text{Damping coefficient}} = 2RC$$

Case-(IV) :-

$$G_1 = 0, \quad \frac{1}{R} = 0 \Rightarrow R = \infty$$

→ Underdamping

$$\alpha = 0, \quad \beta = \frac{1}{\sqrt{LC}}$$

$$V(t) = c_1 \cos \beta t + c_2 \sin \beta t$$

Note:-

1. steady state current response of RLC series circuit with DC excitation = 0

2. At  $t = \infty$ ,

L → Uncharged ( $I = 0$ )

C → Charged ( $V_C = V$ )

3.

$$\zeta = \frac{R}{2} \sqrt{\frac{C}{L}}$$

→ Series :

$\zeta > 1 \rightarrow \text{overdamping}$

$\zeta < 1 \rightarrow \text{Underdamping}$

$\zeta = 1 \rightarrow \text{Critical damping}$

$\zeta = 0 \rightarrow \text{Undamping}$

$$\zeta = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

$\rightarrow$  Parallel

4. For over and critical damping system no oscillations are present




$$\frac{1}{2R} \sqrt{\frac{L}{C}} \geq 1 \rightarrow \text{Parallel}$$

$$\frac{R}{2} \sqrt{\frac{C}{L}} \geq 1 \rightarrow \text{Series}$$

$$\zeta \geq 1.$$

- $\rightarrow$  In the underdamping system more than 1 oscillation are present

$$\zeta < 1$$

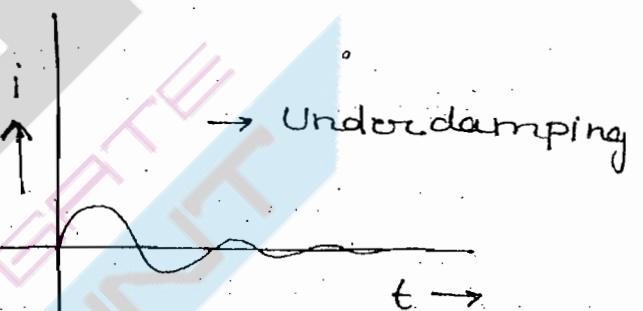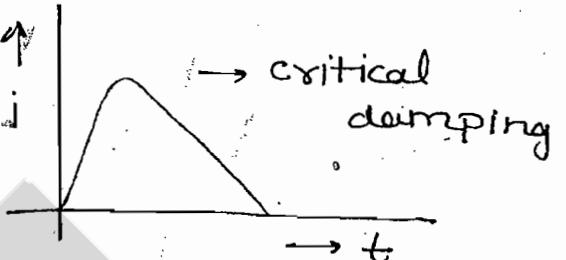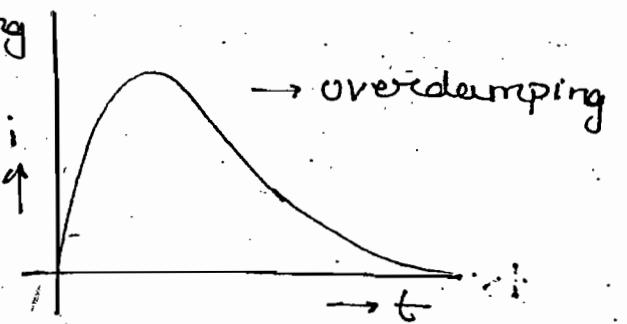


5. At  $t = \infty$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contact: 98910 22220

$L \rightarrow$  Charged ( $I_L = I$ )

$C \rightarrow$  Uncharged ( $V_C = 0$ )

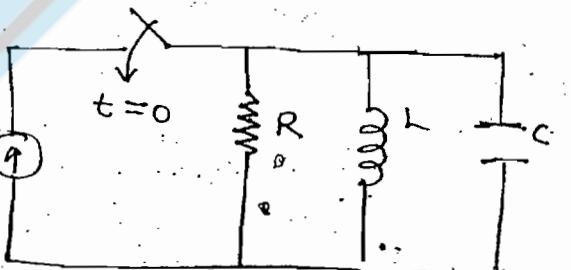


6.  $t = \infty$

$C_1 \rightarrow$  charged ( $V_{C_1} = V$ )



$C_2 \rightarrow$  uncharged ( $V_{C_2} = 0$ )

$L \rightarrow$  uncharged ( $I_L = 0$ )

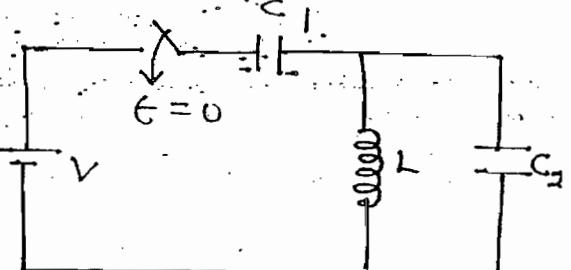
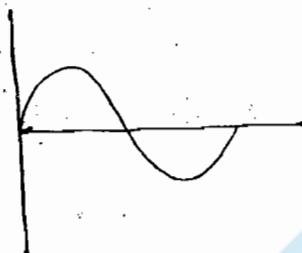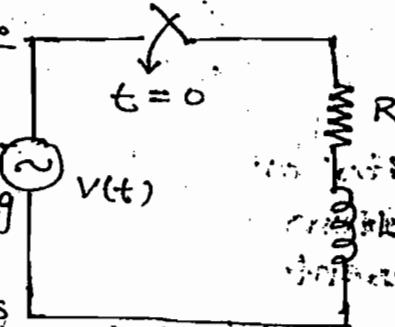
## A.C Transients :-

- DC transients intensity is more than intensity of AC transients
- Based on selection of operating frequency and switching operation and circuit elements it is possible to obtain transient free response. But in DC circuit it is not possible to obtain transient free response



By KVL

$$V = iR + L \frac{di}{dt}$$

Divide both sides by L, we get

$$\frac{di}{dt} + \frac{R}{L}i = \frac{V}{L}$$

$$i(t) = C.F + P.I$$

↓  
Transient Response

C.F:-

$$\frac{di}{dt} + \frac{R}{L}i = 0$$

$$\Rightarrow i(t) = A e^{-\frac{Rt}{L}}$$

P.I → Steady state response

$$i = \frac{V}{Z_{\text{Lc}}} = \frac{V L}{Z}$$

$$i(t) = \frac{V_m}{Z} \sin(\omega t + \theta - \alpha)$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9811111111

$$X_L = WL$$

$$\alpha = \tan^{-1}\left(\frac{WL}{R}\right)$$

$$i(t) = C.F + P.I$$

$$i(t) = A e^{-\frac{R}{L}t} + \frac{V_m}{Z} \sin(\omega t + \theta - \alpha)$$

$$t=0^-, i=0$$

$$t=0^+, i=0$$

$$0 = A + \frac{V_m}{Z} \sin(\theta - \alpha)$$

$$\Rightarrow A = -\frac{V_m}{Z} \sin(\theta - \alpha)$$

$$i(t) = -\frac{V_m}{Z} \sin(\theta - \alpha) e^{-\frac{R}{L}t} + \frac{V_m}{Z} \sin(\omega t + \theta - \alpha)$$

T.R.

S.R.

### Case - (I) :-

$$v(t) = V_m \sin(\omega t + \theta), t=0$$

$$\theta - \alpha = 0$$

$$\theta = \alpha \Rightarrow$$

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

→ Condition for transient free response

### Case - (II) :-

$$v(t) = V_m \cos(\omega t + \theta), t=0$$


$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right) + \frac{\pi}{2}$$

→ condition for transient free response

### Case - (III) :-

$$t=t_0^-, i=0$$

$$t=t_0^+, i=0$$

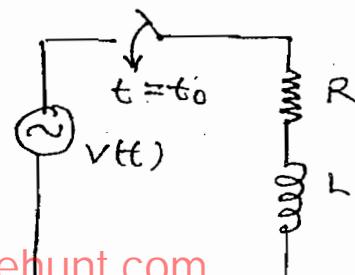

$$0 = A + \frac{V_m}{Z} \sin(\omega t_0 + \theta - \alpha)$$

$$\Rightarrow A = -\frac{V_m}{Z} \sin(\omega t_0 + \theta - \alpha)$$

$$i(t) = \frac{-\frac{V_m}{Z} \sin(\omega t_0 + \theta - \alpha)}{e^{-Rt/L}(t-t_0)} \xrightarrow{T.R} + \frac{\frac{V_m}{Z} \sin(\omega t + \theta - \alpha)}{e^{-Rt/L}} \xrightarrow{S.R}$$

condition for transient free response for

Case - (III)

$$V(t) = V_m \sin(\omega t + \theta), \quad t = t_0$$

$$\omega t_0 + \theta - \alpha = 0$$

$$\Rightarrow \omega t_0 = \alpha - \theta$$

$$\Rightarrow \omega t_0 = \tan^{-1}\left(\frac{wL}{R}\right) - \theta$$

Case - (IV) :-

$$V(t) = V_m \cos(\omega t + \theta), \quad t = t_0$$

$$\omega t_0 = \tan^{-1}\left(\frac{wL}{R}\right) - \theta + \frac{\pi}{2}$$

RL

$$(i) V(t) = V_m \sin(\omega t + \theta)$$

$$t = t_0$$

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$\theta = \tan^{-1}(\omega C)$$

] RC

$$\theta = \tan^{-1}(i\omega R)$$

$$(ii) V(t) = V_m \cos(\omega t + \theta)$$

$$t = 0$$

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right) + \frac{\pi}{2}$$

$$\theta = \tan^{-1}(\omega C) + \frac{\pi}{2}$$

$$\theta = \tan^{-1}(i\omega R) + \frac{\pi}{2}$$

$$(iii) V(t) = V_m \sin(\omega t + \theta)$$

$$t = t_0$$

$$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta$$

$$\omega t_0 = \tan^{-1}(\omega C) - \theta$$

$$\omega t_0 = \tan^{-1}(i\omega R) - \theta$$

$$(iv) V(t) = V_m \cos(\omega t + \theta)$$

$$t = t_0$$

$$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta$$


$$\omega t_0 = \tan^{-1}(\omega C) - \theta + \frac{\pi}{2}$$

$$\omega t_0 = \tan^{-1}(i\omega R) - \theta + \frac{\pi}{2}$$

→ The above condition for series circuit for transient free response and also for parallel circuit.

→ In the RLC circuit it is not possible to obtain transient free response since circuit is having two energy storage element (simultaneously both charging and discharging action are present).

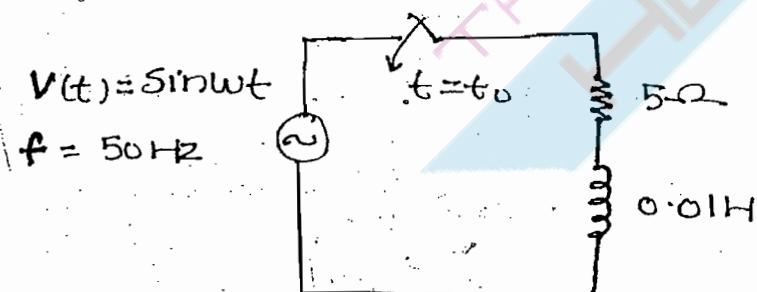Ques:- Find  $t_0$  to obtain transient free response.



Soln:-

$$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta$$

$$t_0 = \frac{\tan^{-1}\left(\frac{\omega L}{R}\right)}{\omega} \rightarrow \text{rad}$$

$$= \frac{\tan^{-1}\left(\frac{\omega L}{R}\right)}{\omega} \rightarrow \text{rad/s}$$

$$t_0 = \frac{32.1 \times \pi / 180}{100\pi} = 1.78 \text{ ms, Ans}$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contd.)


Ques:- Find  $t_0$  to obtain transient free response

Soln:-  $\omega t_0 = \tan^{-1}(\omega RC) - \theta + \frac{\pi}{2}$

$$\Rightarrow t_0 = \frac{\tan^{-1}(1) + \frac{\pi}{2}}{\omega}$$

$$\Rightarrow t_0 = \frac{\frac{\pi}{4} + \frac{\pi}{2}}{\omega} = \frac{3\pi}{4\omega} \quad (\omega^2 = 22/7)$$
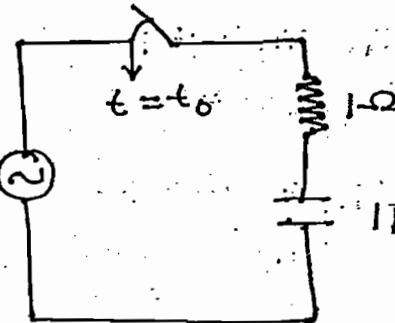
$$\Rightarrow t_0 = 7.35 \text{ s} \quad \text{Ans}$$



Laplace :-

$$A \rightarrow \frac{1}{s}$$

$$e^{at} \rightarrow \frac{1}{s-a}$$

$$\sin \omega t \rightarrow \frac{\omega}{s^2 + \omega^2}$$

$$\cos \omega t \rightarrow \frac{s}{s^2 + \omega^2}$$

$$e^{at} \sin \omega t \rightarrow \frac{\omega}{(s-a)^2 + \omega^2}$$

$$e^{-at} \sin \omega t \rightarrow \frac{\omega}{(s-a)^2 + \omega^2}$$

$$e^{-at} \cos \omega t \rightarrow \frac{s+a}{(s+a)^2 + \omega^2}$$

$$\frac{df}{dt} \Rightarrow SF(s) - f(0)$$

$$u(t) \rightarrow \frac{1}{s}$$

$$\delta(t) \rightarrow 1$$

$$f(0^+) = \lim_{s \rightarrow \infty} SF(s) = \lim_{t \rightarrow 0} f(t)$$

→ Initial value theorem

Ques:- Find initial value of the following functions! -

$$F(s) = \frac{(s+1)(s+3)}{s(2s+2)(s+4)}$$

Soln:-  $f(0^+) = \lim_{s \rightarrow \infty} sF(s)$

$$= \lim_{s \rightarrow \infty} s \cdot \frac{s \cdot s^2 \left(1 + \frac{1}{s}\right) \left(3 + \frac{3}{s}\right)}{s \cdot s^2 \left(2 + \frac{2}{s}\right) \left(1 + \frac{4}{s}\right)} = \frac{1}{2}$$

Ques:- Find initial value of the following function

$$f(t) = 3 + 8t$$

Soln:-  $F(s) = \frac{3}{s} + 1$

Note:-

For the above function initial value theorem can't be applied since to apply the initial value theorem denominator power should be greater than Numerator power.

Final Value Theorem:-

$$f(\infty) = \lim_{s \rightarrow 0} sF(s) = \lim_{t \rightarrow \infty} f(t)$$

Ques:- Find final value of the following function

(i)  $F(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)}$

(ii)  $f(t) = 3 + e^{2t}$

Soln:- (i)  $f(\infty) = \lim_{s \rightarrow 0} sF(s)$

$$= \lim_{s \rightarrow 0} s \cdot \frac{s(s+1)(s+3)}{s(s+2)(s+4)} = \frac{3}{8}$$

(ii)  $f(t) = 3 + e^{2t}$

$$F(s) = \frac{3}{s} + \frac{1}{s-2}$$

$$V_C(t) = \frac{1}{C} \int_{-\infty}^t i dt$$

$$\Rightarrow V_C(t) = \frac{1}{C} \int_{-\infty}^{0^-} i dt + \frac{1}{C} \int_{0^-}^t i dt$$

$$\Rightarrow V_C(t) = V_C(0^-) + \frac{1}{C} \int_{0^-}^t i dt$$

At  $t=0^+$

$$V_C(0^+) = V_C(0^-) + \frac{1}{C} \int_{0^+}^{0^+} i dt = 0$$

$$V_C(0^+) = V_C(0^-) \quad \text{--- (I)}$$

$$V_C(0^+) = V_C(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i dt$$

$$V_C(0^+) = V_C(0^-) + \frac{1}{C} \int_{0^-}^{0^+} \delta(t) dt$$

$$V_C(0^+) = \frac{1}{C}$$

--- (II)

$$w_C(0^+) = \frac{1}{2} C V_C^2(0^+) = \frac{1}{2} C \left(\frac{1}{C}\right)^2$$

$$w_C(0^+) = \frac{1}{2C}$$



--- (III)

### Note:-

- From eq-(I) it is concluded that capacitor does not allow instantaneous changes for given i/p.
- From eq-(II) & (III) it is concluded that capacitor allows instantaneous changes for current impulse function.

$$V(t) = i(t)R$$



$$V(s) = I(s)R$$

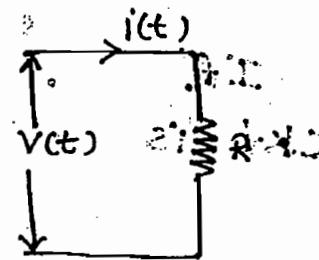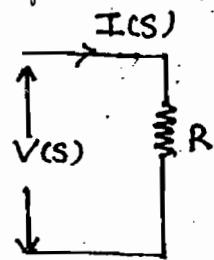

$$V = L \frac{di}{dt} \quad s = j\omega$$

$$V(s) = L [sI(s) - i(0^+)]$$
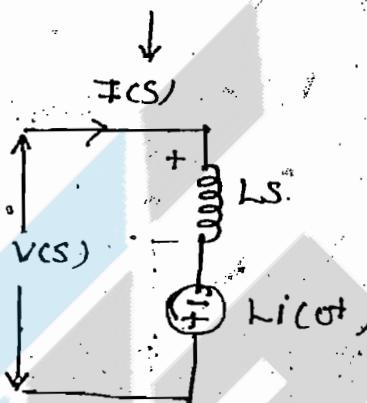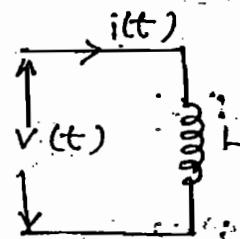
$$V(s) = LS I(s) - L i(0^+) \rightarrow KVL$$




$$Z(s) = \frac{V(s)}{I(s)}$$

$$\Rightarrow Z(s) = LS - \frac{L i(0^+)}{I(s)}$$

$$LS I(s) = V(s) + L i(0^+)$$
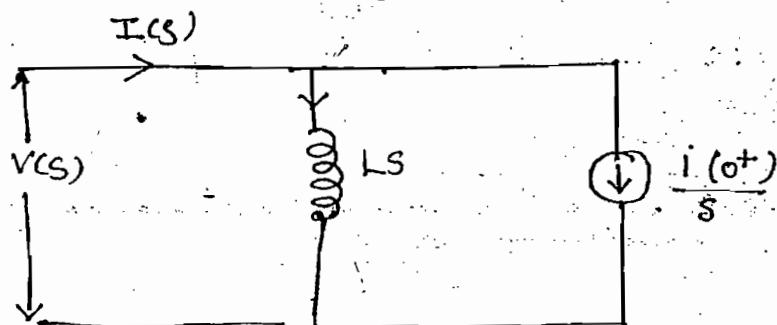
$$I(s) = \frac{V(s)}{LS} + \frac{L i(0^+)}{LS} \rightarrow KCL$$



$$Y(s) = \frac{I(s)}{V(s)}$$


$$Y(s) = \frac{1}{LS} + \frac{i(0^+)}{SV(s)}$$

CHART PHOTOSTAT  
(All Study Material Available  
4-163 Lado Sarai, New Delhi  
Cont.-C, 110001)

Note

NN

If  $i(0^+) = 0$  then eq.  
Ckt is

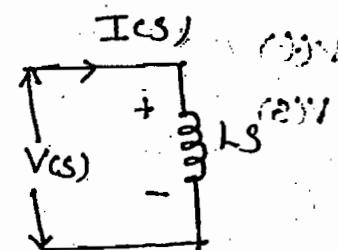


$$r = C \frac{dV}{dt}$$

$$I(s) = C [sV(s) - V(0^+)]$$

$$\Rightarrow I(s) = \frac{V(s)}{\frac{1}{Cs}} - CV(0^+) \quad \rightarrow KCL$$

$$s = j\omega$$


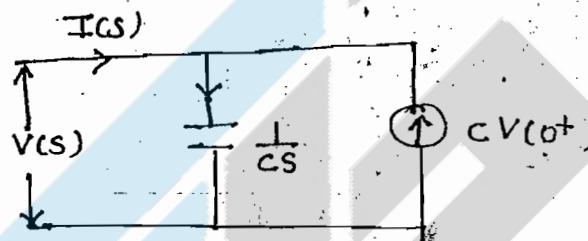


$$Y(s) = \frac{I(s)}{V(s)}$$

$$Y(s) = Cs - \frac{CV(0^+)}{V(s)}$$

$$\frac{V(s)}{Y(s)} = I(s) + CV(0^+)$$

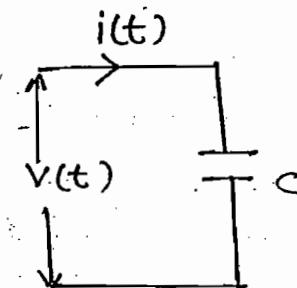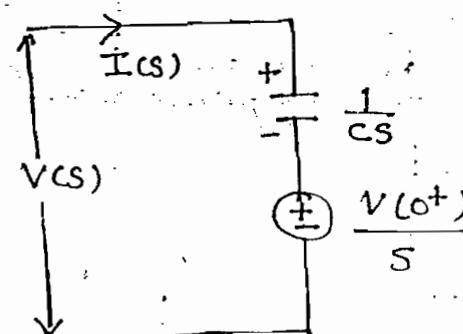
$$\Rightarrow V(s) = \frac{1}{Cs} I(s) + \frac{CV(0^+)}{Cs} \quad \rightarrow KVL$$




"MOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. No. 9810000000

$$Z(s) = \frac{V(s)}{I(s)} = \frac{1}{cs} + \frac{V(0^+)}{sI(s)}$$


$$V(0^+) = 0 \rightarrow$$

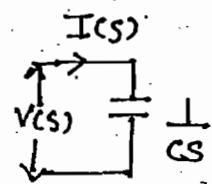

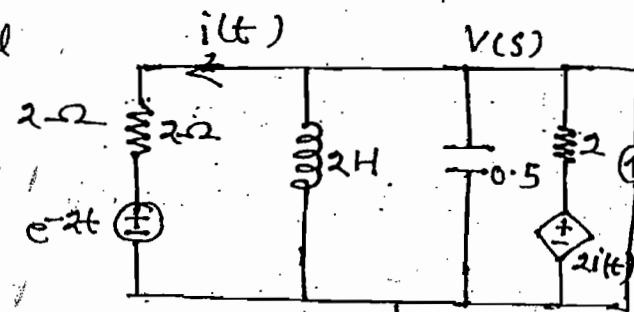ques:- Find  $V(s)$  when initial current of the inductor is  $2A$  and initial voltage of the capacitor is  $3V$



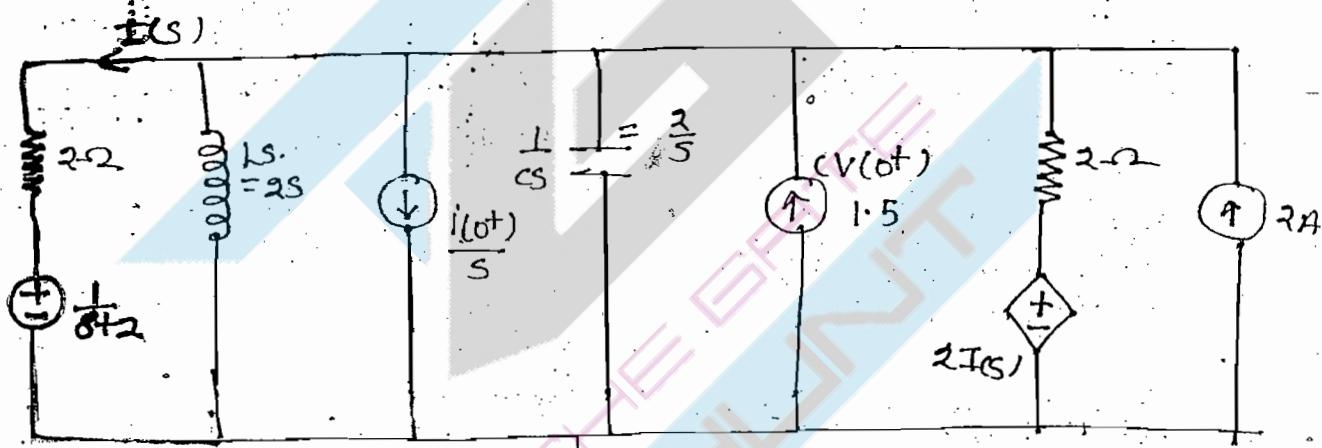
Soln:- When elements are in parallel then for simple calculation convert elements into current sources.



$$\frac{V(s)}{s+2} + \frac{V(s)}{2s} + \frac{2}{5} + \frac{V(s)}{\frac{1}{cs}} + \frac{V(s) - 2I(s)}{2} = 1.5 + 2 \quad \rightarrow (1)$$

$$I(s) = \frac{V(s) - \frac{1}{s+2}}{2}$$

Ques:- Find  $i(t)$  for  $t > 0$

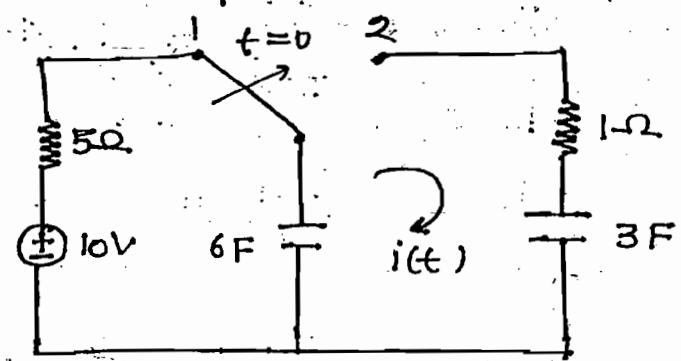

Soln:-

At  $t = 0^-$

$$V_{C_6}(0^-) = 10V$$



$$V_{C_3}(0^-) = 0V$$

At  $t > 0$

$$I(s) = \frac{10/s}{\frac{1}{6s} + \frac{1}{as} + 1}$$

$$i(t) = L^{-1} I(s)$$


$$\Rightarrow i(t) = 10 e^{-t/2}$$

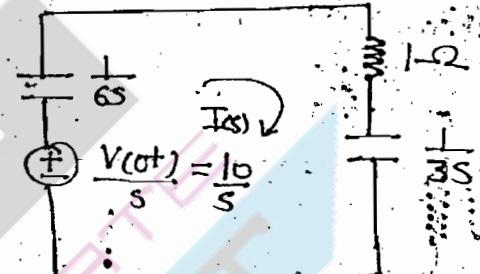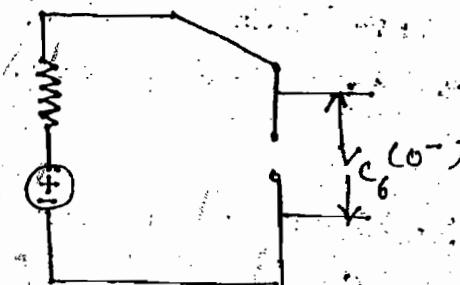


Verification :-  $\rightarrow$  Method for MCA

$$i(t) = \frac{V_0}{R} e^{-t/RC}$$

$$i(t) = \frac{10}{1} e^{-t/2}$$

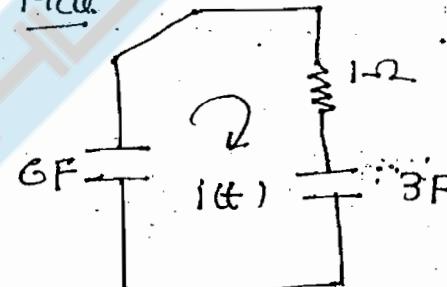

Ques:- Find  $i(t)$  for  $t > 0$

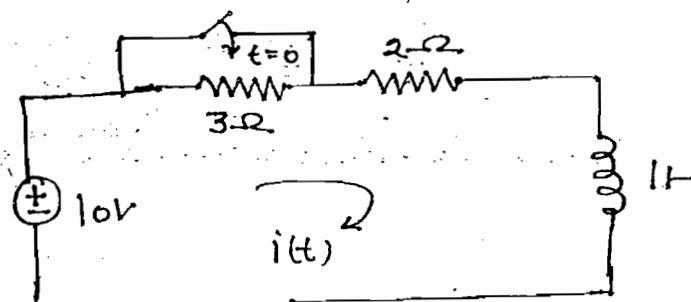


**PHOTOSTAT**  
 (All Study Material Available)  
 A-163 Lado Sarai, New Delhi  
 Cont: 91-91022040

Soln:-

At  $t = 0^-$

$$i(0^-) = \frac{10}{3+2} = 2A$$

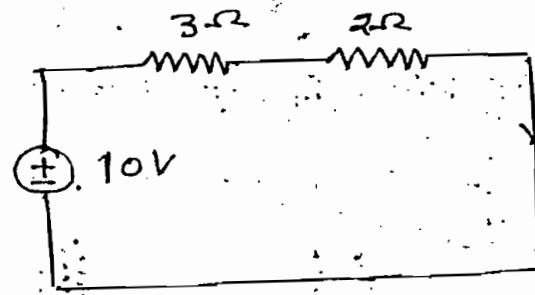


For  $t > 0$

$$I(s) = \frac{10 + 2}{\frac{1}{s} + 3 + 2}$$

$$i(t) = L^{-1} I(s)$$

$$i(t) = 5 - 3e^{-2t}$$

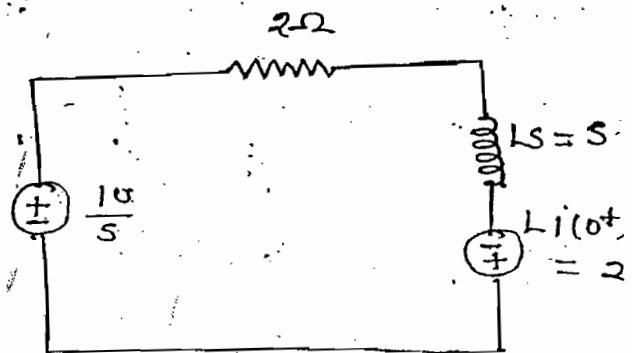


Alternate way:-

$$i(t) = [i(0^+) - i(\infty)] e^{-Rt} + i(\infty)$$

$$i(0^+) = i(0^-) = 2$$

$$i(t) = [2 - 5] e^{-2t} + 5$$

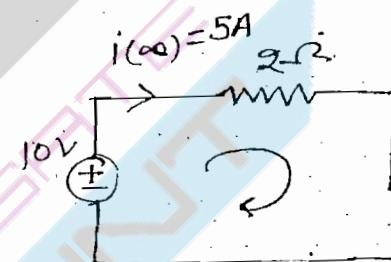


PHOTOSTAT  
All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. -

Q-SOFT  
PHOTOSTAT  
GATE 2017
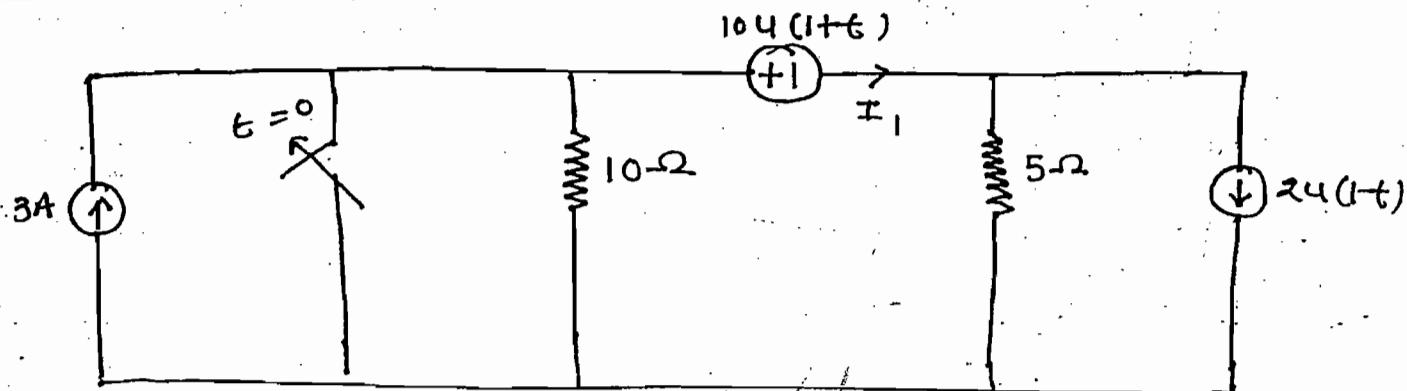
# Lecture - 11

PHOTOSTAT  
All Study Material Available  
A-163 Lajpat Sarai, New Delhi  
Cont: 0712 122270

Ques:- Find  $I_1$  at  $t = -2$  seconds:



Soln:-

$$DC \rightarrow -\infty \text{ to } \infty$$

$$u(t) \rightarrow 0 \text{ to } \infty$$


$$u(-t) \rightarrow -\infty \text{ to } 0$$

$$u(1+t)$$

$$-1 \text{ to } \infty$$


$$u(1-t)$$

$$-\infty \text{ to } 1$$

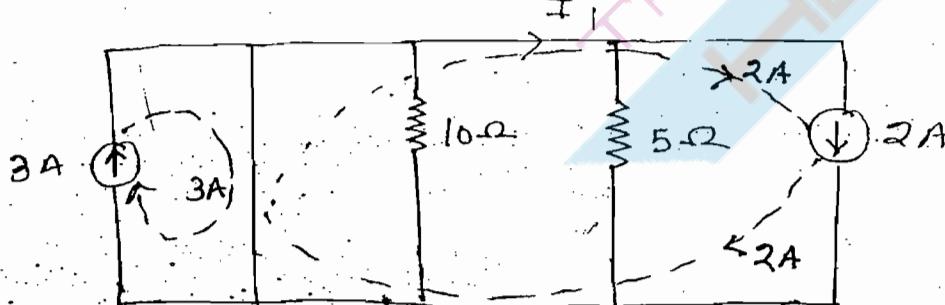

$$I_1 = 2A$$


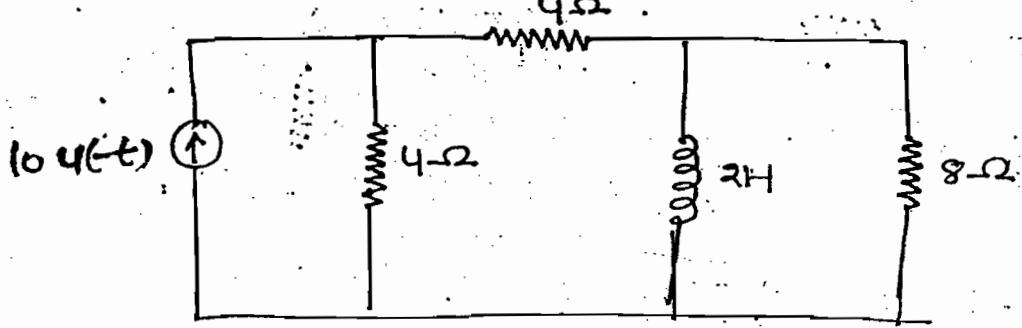
Ques:- Find current response in the inductor for  $t > 0$




Soln:-

$$t = 0^-$$
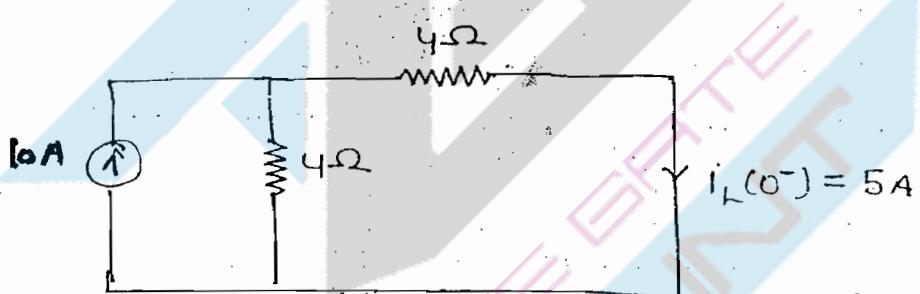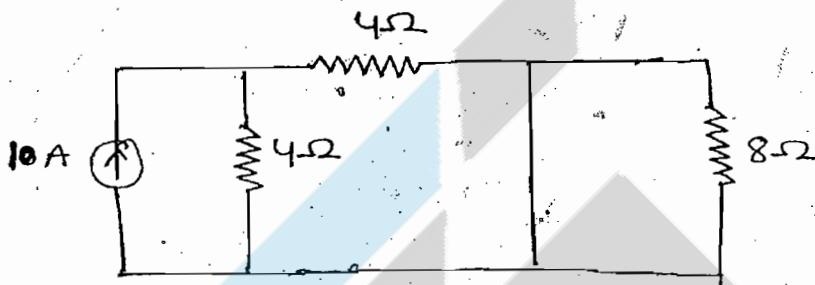
$$u(-t) \rightarrow -\infty \text{ to } 0$$




$$t > 0$$

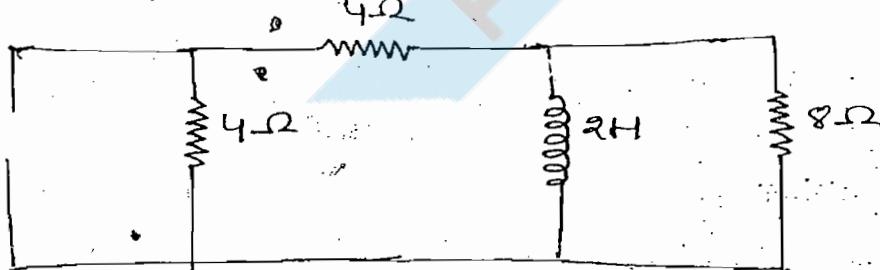


$$i(t) = I_0 e^{-R_L t}$$

$$i(t) = 5 e^{-2t}, \text{ Ans}$$

$$I_0 = i_L(0^-) = 5A$$

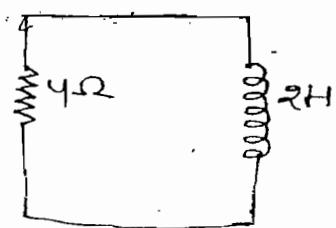

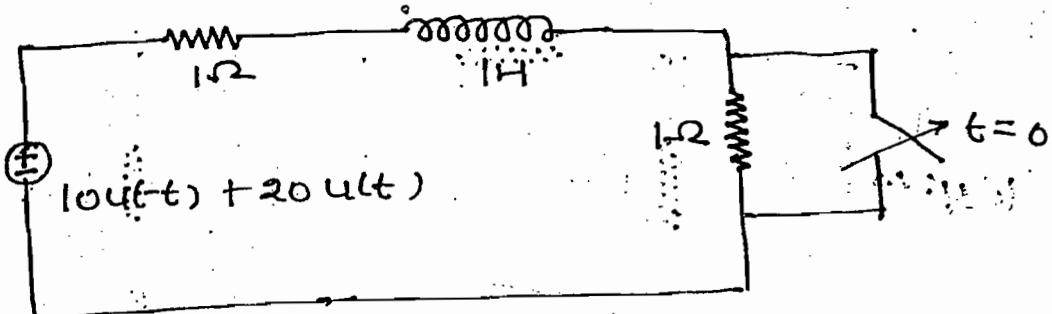
ques:- Find current in the inductor for  $t > 0$




Soln:-  $i(t) = [i(0^+) - i(\infty)] e^{-\frac{R}{L}t} + i(\infty)$

$t = 0^-$

$$i(0^+) = i(0^-) = 10A$$

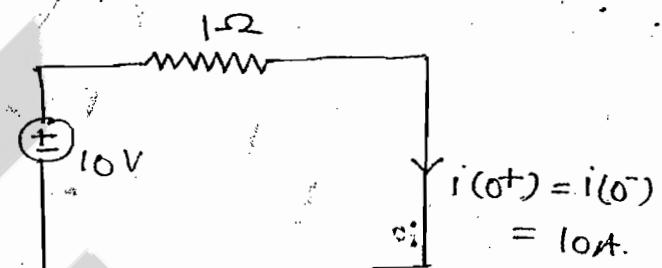

$t = \infty$

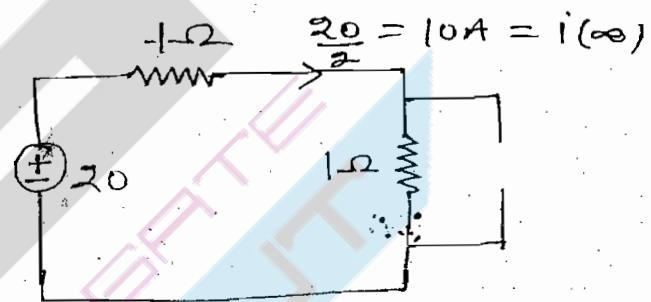


$$i(t) = [10 - 10] e^{-\frac{R}{L}t} + 10 = 10 \text{ Ans.}$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont.
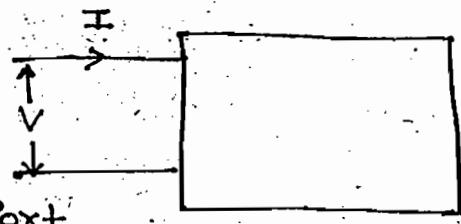
## TWO PORT NETWORK

BHARAT PHOTOSTAT 918102070


→ A pair of terminals at which signal may enter or leave from the N/w is called as port.




→ When the N/w is having one pair of terminals then the N/w is called as single port + N/w

eg:- Motor, Generator

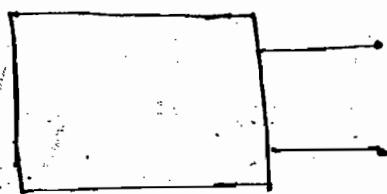Single Port  
A pair of terminals, eg:- Motor



eg:- Generator

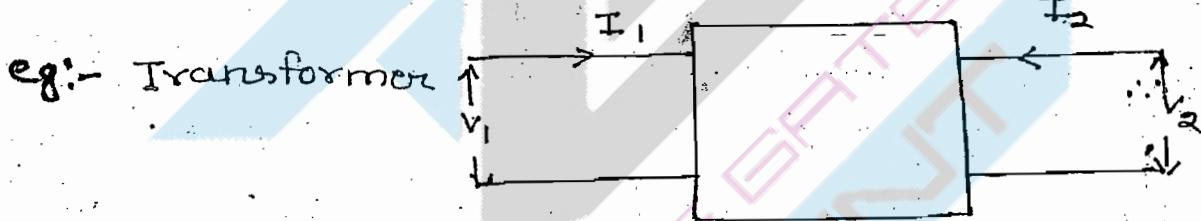

### Classification of Parameters:-

- (I) Z - Parameter (O.C Parameter)
- (II) Y - Parameter (S.C Parameter)
- (III) h - Parameter (Hybrid Parameter)
- (IV) g - Parameter (Inverse hybrid Parameter)
- (V) ABCD - Parameter (Transmission line parameter)
- (VI) abc'd - Parameter (Inverse transmission line parameter)

BHARAT PHOTOSTAT  
Full Study Material Available  
A-163 Lado Sarai, New Delhi


- (I) Z-Parameters:-
- $$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad (I) \rightarrow \text{KVL}$$
- $$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad (II) \rightarrow \text{KVL}$$
- $V_1, V_2 \rightarrow$  Dependent Variables  
Sources  $\rightarrow I_1, I_2 \rightarrow$  Independent Variables

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

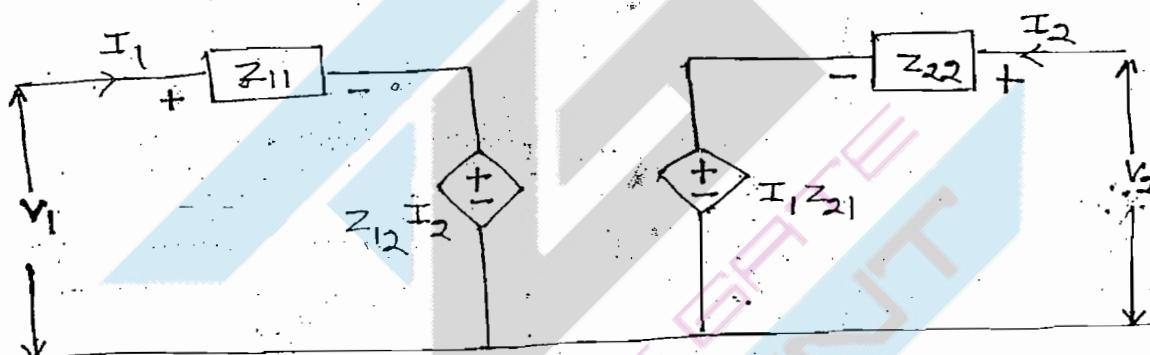

$Z_{11}$  = Open ckt i/p impedance / Driving point i/p impedance

$Z_{21}$  = Forward transfer impedance

$Z_{12}$  = Reverse transfer impedance

$Z_{22}$  = Open ckt o/p impedance / Driving point o/p impedance

- (II) Y-Parameters:-

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad (I) \rightarrow \text{KCL}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad (II) \rightarrow \text{KCL}$$


$I_1, I_2 \rightarrow$  Dependent Variables  
 $V_1, V_2 \rightarrow$  Independent Variables  
 (source)

$$X_1 = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

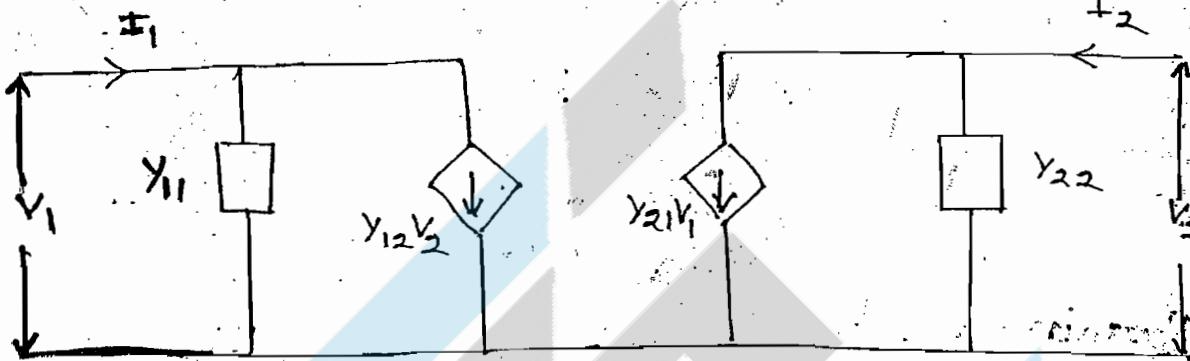

$Y_{11}$  = s.c i/p admittance / driving point i/p admittan.

$Y_{21}$  = forward transfer admittance

$Y_{12}$  = Reverse transfer admittance

$Y_{22}$  = s.c o/p admittance / driving point o/p admittan

h-Parameters:-

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad (1) \rightarrow \text{KVL}$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad (II) \rightarrow \text{KCL}$$


$$(1) \quad h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \quad \left( h_{11} \neq Z_{11}, h_{11} = \frac{1}{Y_{11}} \right)$$

$$(2) \quad h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} \quad \left( h_{21} = \frac{Y_{21}}{Y_{11}} = \frac{I_2/V_1}{I_1/V_1} \right)$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_2=0} \quad ( h_{12} = \frac{z_{12}}{z_{22}} )$$

Unitless

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} \quad ( h_{22} \neq y_{22}, h_{22} = \frac{1}{z_{22}} )$$

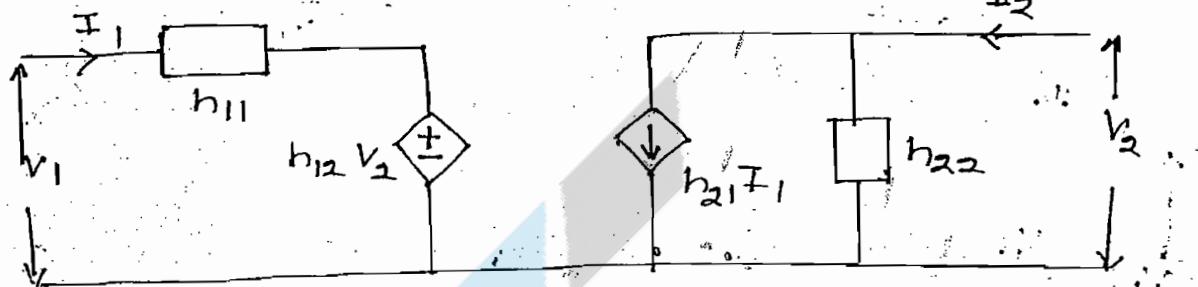

g-Parameters:

$$I_1 = g_{11} V_1 + g_{12} I_2 \rightarrow (1)$$

$$V_2 = g_{21} V_1 + g_{22} I_2 \rightarrow (1)$$

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0}$$

$$( g_{11} \neq y_{11}, g_{11} = \frac{1}{z_{11}} )$$

$$g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0}$$

$$( g_{21} = \frac{z_{21}}{z_{11}} )$$

Unitless

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0}$$


$$( g_{12} = \frac{y_{12}}{y_{22}} )$$

(unitless)

$$g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

$$( g_{22} \neq z_{22}, g_{22} = \frac{1}{y_{22}} )$$

(unitless)

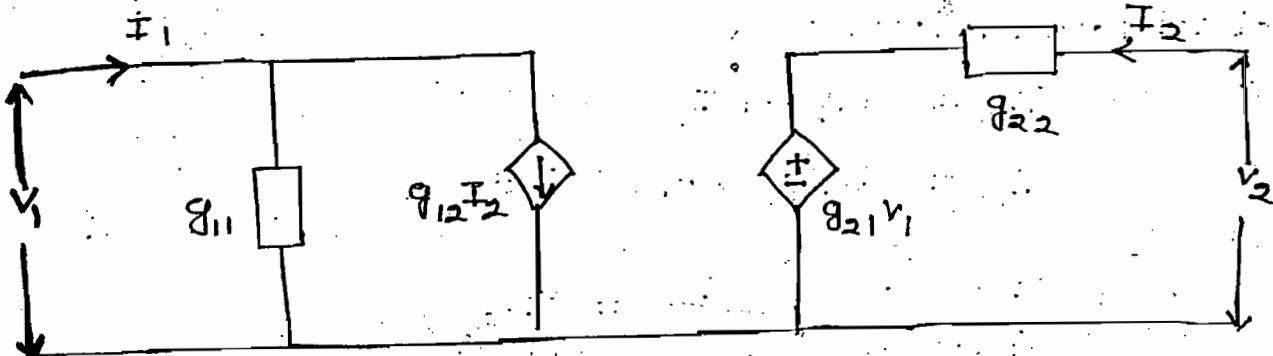

ABC<sub>12</sub> Parameters:-

$$V_1 = AV_2 - BI_2 \quad (I)$$

$$I_1 = CV_2 - DI_2 \quad (II)$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad \left( A = \frac{Z_{11}}{Z_{21}} \right)$$

Unitless

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad \left( C = \frac{1}{Z_{21}} \right)$$

mho

$$B = \left. \frac{-V_1}{I_2} \right|_{V_2=0} \quad \left( B = -\frac{1}{Y_{21}} \right)$$

$$D = \left. \frac{-I_1}{I_2} \right|_{V_2=0} \quad \left( D = -\frac{Y_{11}}{Y_{21}} \right)$$

Unitless

By using eq-(I) & (II) it is not possible to develop eq ckt since both equations are developed w.r.t i/p

abcd Parameters:-

$$V_2 = aV_1 - bI_1 \quad (1)$$

$$I_2 = cV_1 - dI_1 \quad (2)$$

$$\therefore a = \frac{V_2}{V_1} \Big|_{I_1=0} \quad (a = \frac{Z_{22}}{Z_{12}})$$

Unitless


$$c = \frac{I_2}{V_1} \Big|_{I_1=0} \quad (c = \frac{1}{Z_{12}})$$

mho


$$b = \frac{-V_2}{I_1} \Big|_{V_1=0} \quad (b = -\frac{1}{Y_{12}})$$

$$d = -\frac{I_2}{I_1} \Big|_{V_1=0} \quad (d = -\frac{Y_{22}}{Y_{12}})$$

No units

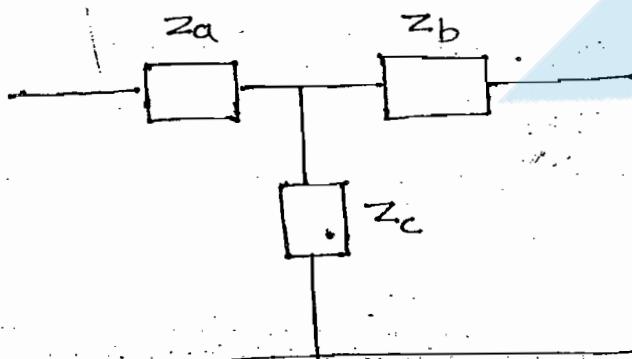


→ Unsymmetrical T-N/w

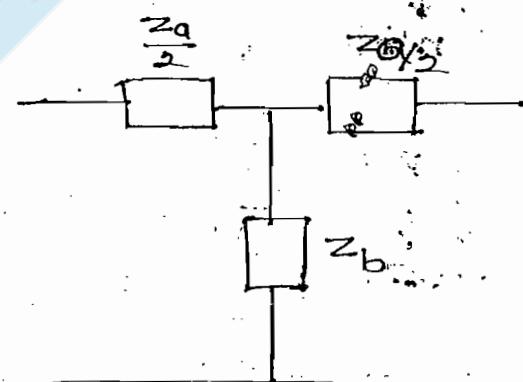


→ Symmetrical T-N/w

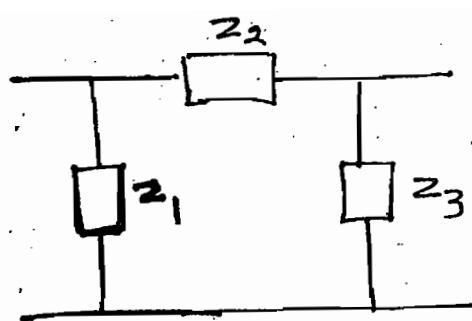
PHOTOSTAT  
 (AM Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont-97



→ Unsymmetrical  
T N/w

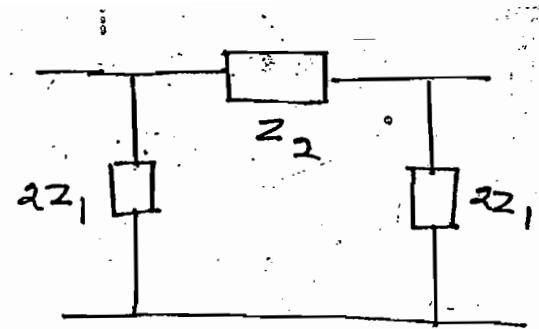

→ Symmetrical - T N/w

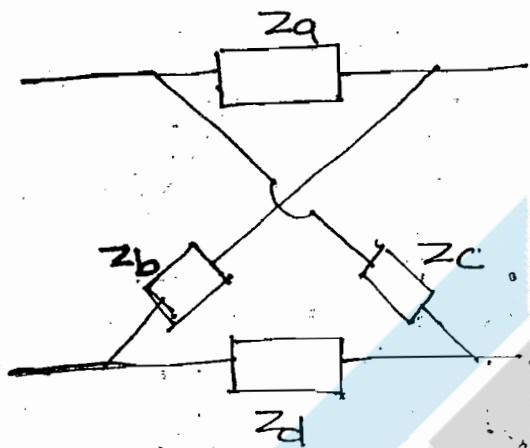

$z_a = z_d$       → Symmetrical  
 $z_b = z_c$       Lattice  
N/w

$z_a \neq z_d$       ]  
 $z_b \neq z_c$       → Unsymmet-  
-rical  
Lattice N/w

Symmetrical	Reciprocal
$z_{11} = z_{22}$	$z_{12} = z_{21}$
$y_{11} = y_{22}$	$y_{12} = y_{21}$
$h_{11}h_{22} - h_{12}h_{21} = 1$	$h_{12} = -h_{21}$
$A = B$	$AB - BC = 1$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont.


Z-Parameter  $\rightarrow$  Use - T - N/w

$$V_1 = (z_a + z_b)I_1 + z_b I_2 \quad (I)$$

$$V_1 = z_{11}I_1 + z_{12}I_2 \quad (II)$$

$$z_{11} = z_a + z_b$$

$$z_{12} = z_b$$

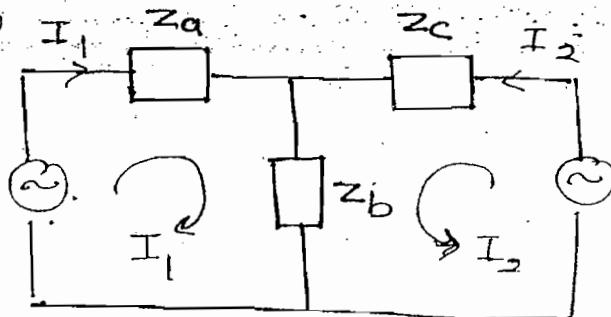

$$V_2 = Z_b I_1 + (Z_b + Z_c) I_2 \quad \text{--- (III)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (IV)}$$

$$Z_{21} = Z_b \quad \& \quad Z_{22} = Z_b + Z_c$$

\*\*

$$Z_{11} = Z_a + Z_b$$

$$Z_{11} = Z_a + Z_{12}$$


$$Z_a = Z_{11} - Z_{12}$$

$$Z_c = Z_{22} - Z_{12}$$

$$Z_b = Z_{12} = Z_{21}$$

For Y-Parameter  $\rightarrow$  Convert complex N/w into T-N/w

$$I_1 = V_1 Y_a + (V_1 - V_2) Y_b$$

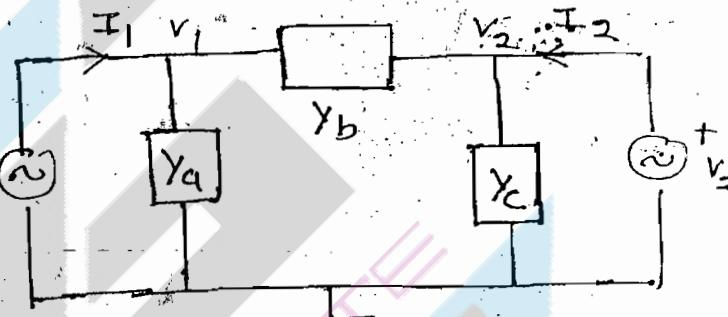

$$I_1 = (Y_a + Y_b)V_1 - Y_b V_2 + V_1 \quad \text{--- (I)}$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (II)}$$

$$Y_{11} = Y_a + Y_b$$

$$Y_{12} = -Y_b$$

$$I_2 = V_2 Y_c + (V_2 - V_1) Y_b$$

$$\Rightarrow I_2 = -V_1 Y_b + (Y_b + Y_c) V_2 \quad \text{--- (III)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (IV)}$$

$$Y_{21} = -Y_b \quad \& \quad Y_{22} = Y_b + Y_c$$

\*\*

$Y_a = Y_{11} + Y_{12}$
$Y_c = Y_{22} + Y_{12}$
$Y_b = -Y_{12} = -Y_{21}$

PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai New Delhi  
Cont: 9810000000

$$z_a = z_d, z_b = z_c$$

→ Symmetrical lattice N/W

$$z_{11} = z_{22} = \frac{z_b + z_a}{2}$$

$$z_{12} = z_{21} = \frac{z_b - z_a}{2}$$

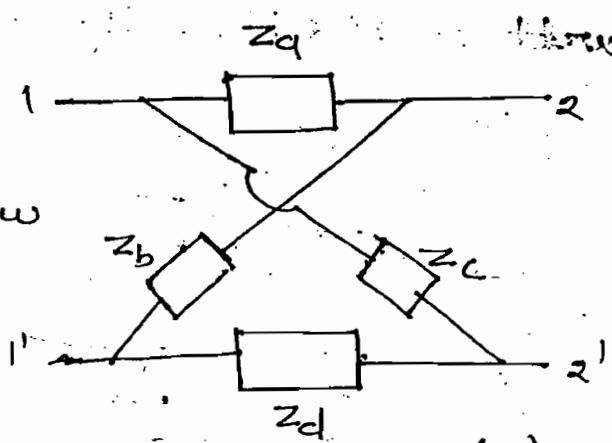


Fig - (1)

$$z_b = z_{11} + z_{12}$$


$$z_a = z_{11} - z_{12}$$

$$y_a = y_d, y_b = y_c$$

→ Symmetrical lattice N/W

$$y_{11} = y_{22} = \frac{y_b + y_a}{2}$$
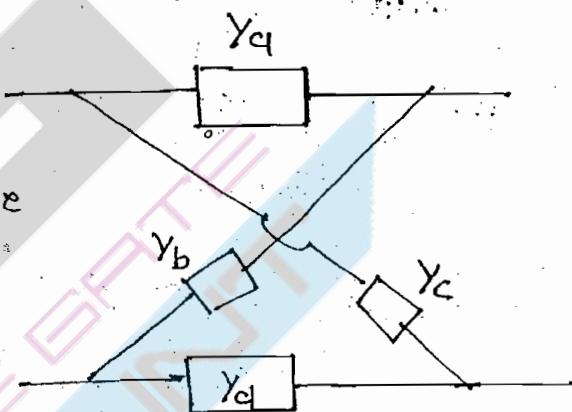
$$y_{12} = y_{21} = \frac{y_b - y_a}{2}$$




**EFEST PHOTOSTAT**  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9810000070

$$y_b = y_{11} + y_{12}$$

$$y_a = y_{11} - y_{12}$$


→ Fig-(1) & (ii) are same.

Fig - (ii)

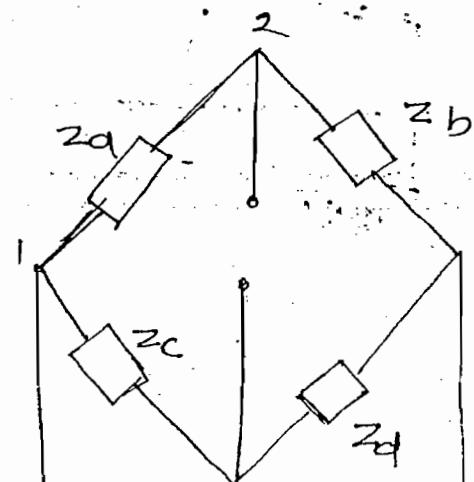

## Bartlett's Bi-section theorem:-

Cy! - Filters



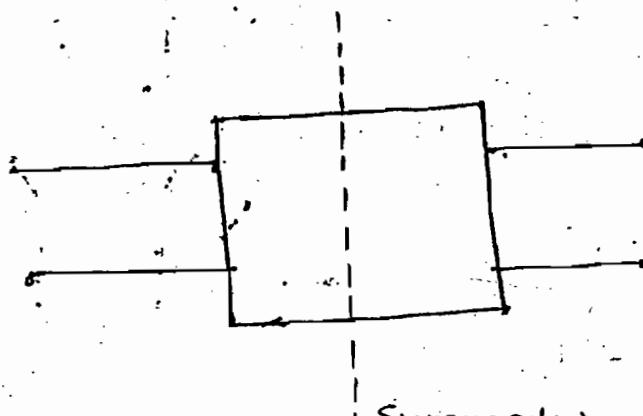


PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Cont.- 8710000000


Symmetrical

$$Z_{11} = Z_{22} = \frac{Z_{OCH} + Z_{SCH}}{2}$$
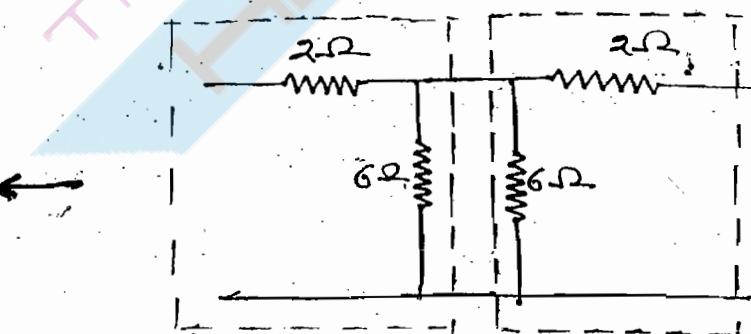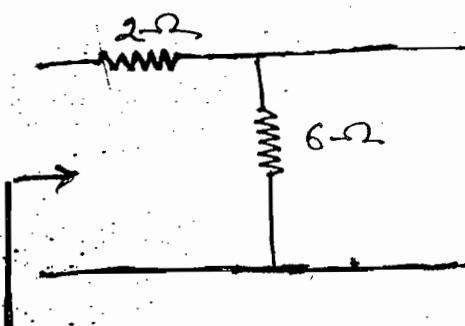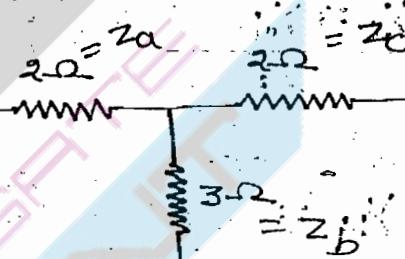
$$Z_{12} = Z_{21} = \frac{Z_{OCH} - Z_{SCH}}{2}$$



$$Z_{OCH} = 2 + 6 = 8$$

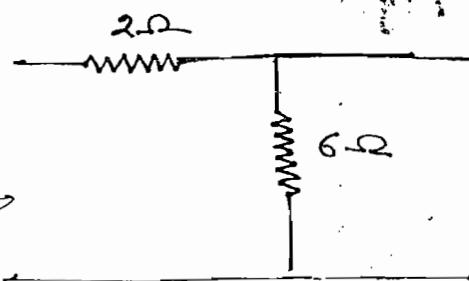

$$Z_{11} = Z_{22} = \frac{Z_{OCH} + Z_{SCH}}{2} = \frac{8+2}{2} = 5$$

$$Z_{12} = Z_{21} = \frac{Z_{OCH} - Z_{SCH}}{2} = \frac{8-2}{2} = 3$$

Alternate Way:-


$$Z_{11} = Z_a + Z_b = 5$$

$$Z_{22} = Z_b + Z_c = 5$$


$$Z_{12} = Z_{21} = Z_b = 3$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 97110100170

Series combination:-

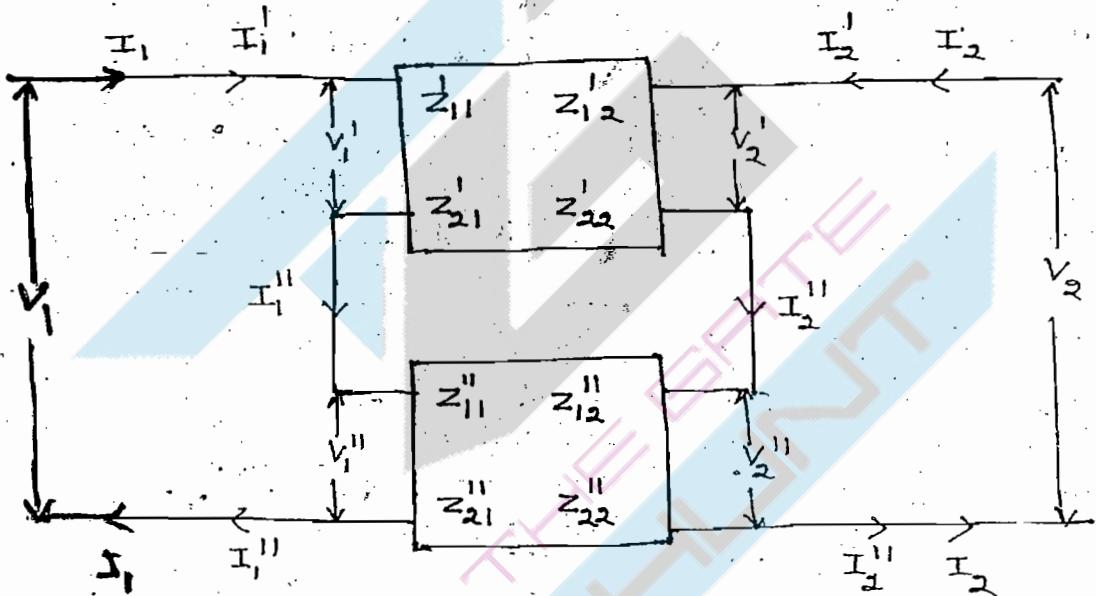

Parallel combination:-

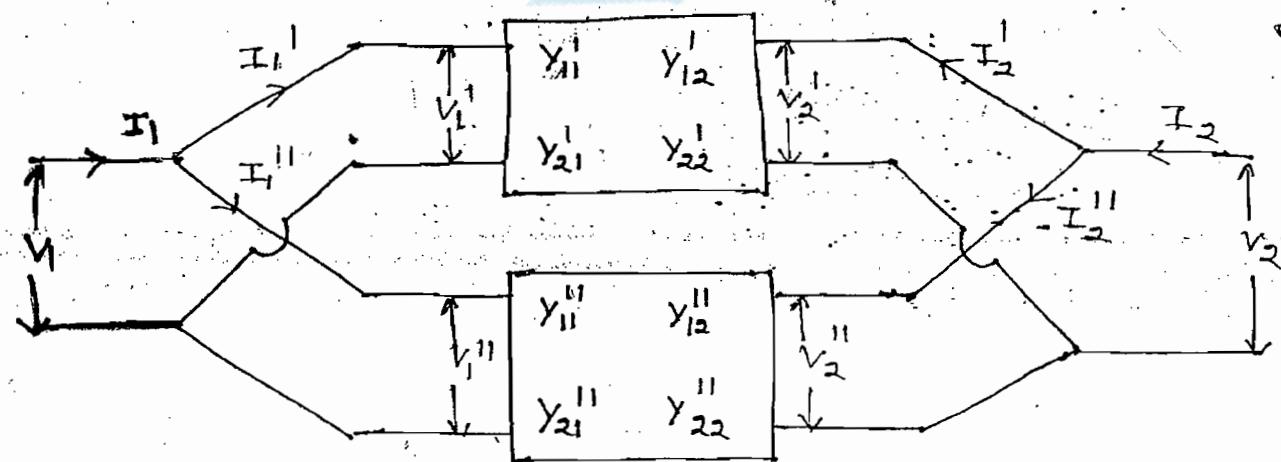

For Series combination: —

$$V_1 = V_1' + V_1''$$

$$I_1 = I_1' = I_1''$$

$$V_2 = V_2' + V_2''$$

$$I_2 = I_2' = I_2''$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_{11}' & Z_{12}' \\ Z_{21}' & Z_{22}' \end{bmatrix} + \begin{bmatrix} Z_{11}'' & Z_{12}'' \\ Z_{21}'' & Z_{22}'' \end{bmatrix}$$

For Parallel combination: —


$$V_1 = V_1' = V_1''$$

$$I_1 = I_1' + I_1''$$

$$V_2 = V_2' = V_2''$$

$$I_2 = I_2' + I_2''$$
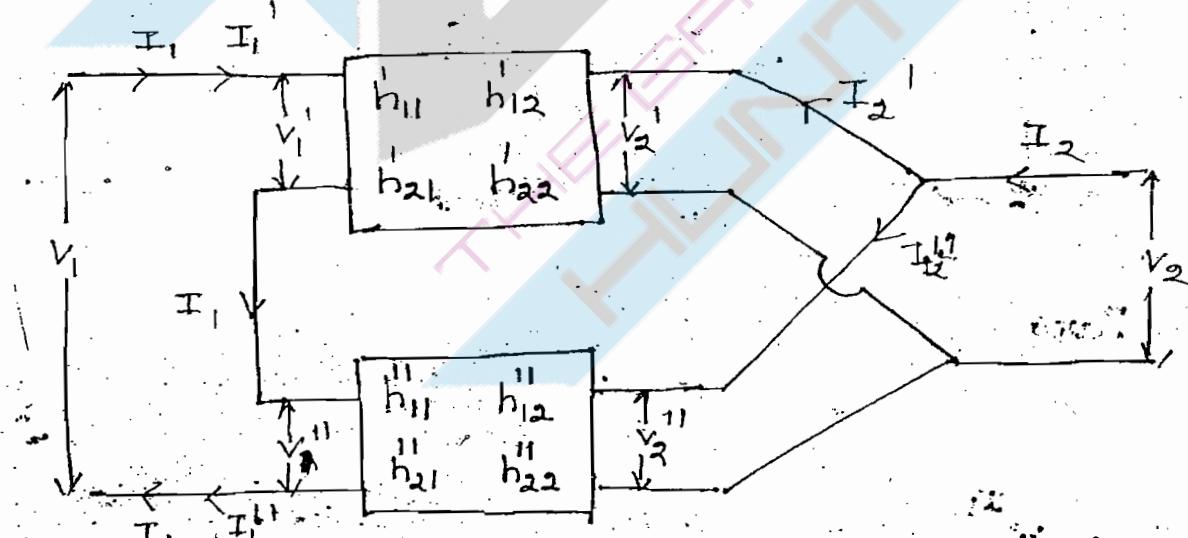
$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Y_{11}' & Y_{12}' \\ Y_{21}' & Y_{22}' \end{bmatrix} + \begin{bmatrix} Y_{11}'' & Y_{12}'' \\ Y_{21}'' & Y_{22}'' \end{bmatrix}$$



$$V_1 = V_1' + V_1''$$


$$I_1 = I_1' = I_1''$$

$$V_2 = V_2' = V_2''$$

$$I_2 = I_2' + I_2''$$


$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} h_{11}' & h_{12}' \\ h_{21}' & h_{22}' \end{bmatrix} + \begin{bmatrix} h_{11}'' & h_{12}'' \\ h_{21}'' & h_{22}'' \end{bmatrix}$$

## Cascade or Tandem Connection:-

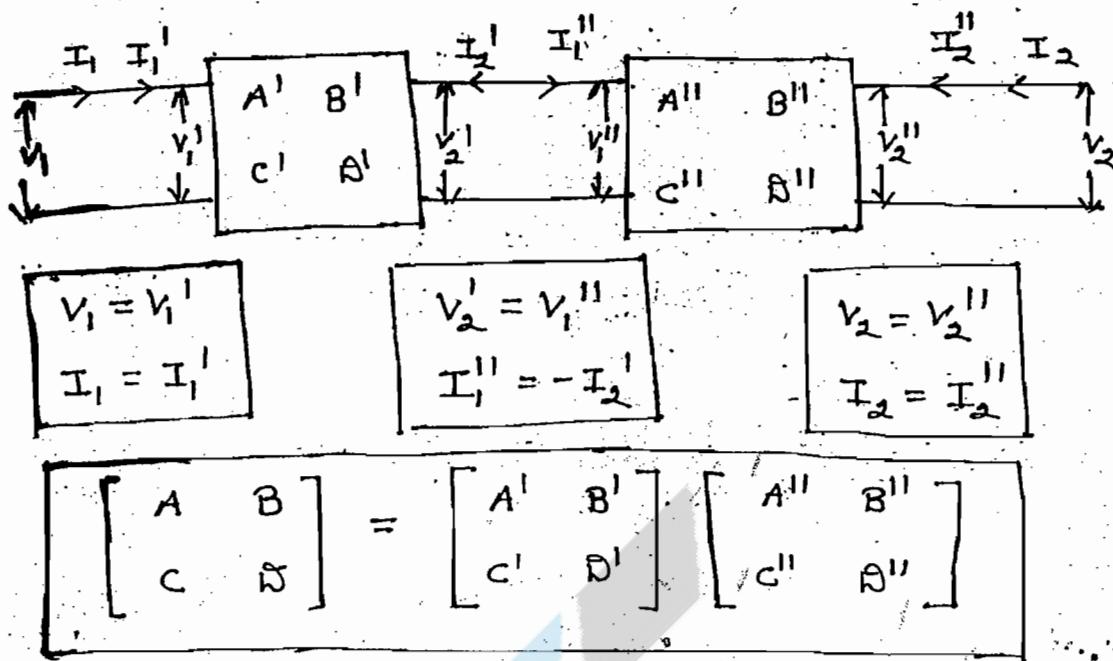

Ques:- Find  $Z$ ,  $Y$ ,  $ABCD$  parameters of the N/W shown:-

Ideal t/f

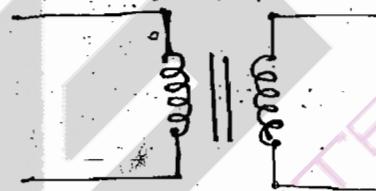

Soln:-

$$A = \frac{V_1}{V_2} = n$$

$$D = -\frac{I_1}{I_2} = +\frac{1}{n}$$

$$\frac{I_2}{I_1} = \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{n}{n} = 1$$

-ve is due to current direction

PHOTOSTAT  
A-163 Lado Sarai, New Delhi  
Cont-c  
CAH Study Material Available

Note:-


In ideal t/f it is not possible to find impedance and admittance values since self and mutual inductance of ideal transformer are  $\infty$

Ques:- Find O.C & S.C

impedance w.r.t

(I) 1-1'

(II) 2-2'

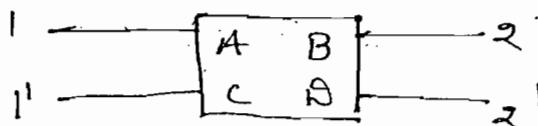

Soln:- (1)

$$Z_{i/p} = \frac{V_1}{I_1} = \frac{AV_2 - BI_2}{CV_2 - DI_2}$$

$$(Z_{i/p})_{o.c} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{A}{C} \Omega$$

$$(Z_{i/p})_{s.c} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{B}{D} \Omega$$

(II) 2-2 :-

$$(Z_{o/p})_{o.c} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$I_1 = CV_2 - DI_2 = 0$$

$$\Rightarrow \frac{V_2}{I_2} = \frac{D}{C}$$

$$(Z_{o/p})_{o.c} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{D}{C} \Omega$$

$$(Z_{o/p})_{s.c} = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

$$V_1 = AV_2 - BI_2$$

$$\Rightarrow 0 = AV_2 - BI_2$$

$$\Rightarrow \frac{V_2}{I_2} = \frac{B}{A}$$


$$(Z_{o/p})_{s.c} = \frac{B}{A} \Omega, \text{ Ans.}$$

PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Cont: 011-26511222

$$B = -\frac{V_1}{I_2} \Rightarrow \frac{2s+1}{s^2} \Rightarrow \frac{eq-(1)}{eq-(4)}$$

$$\Rightarrow Z(s) = \frac{1}{s} \quad \text{Ans}$$

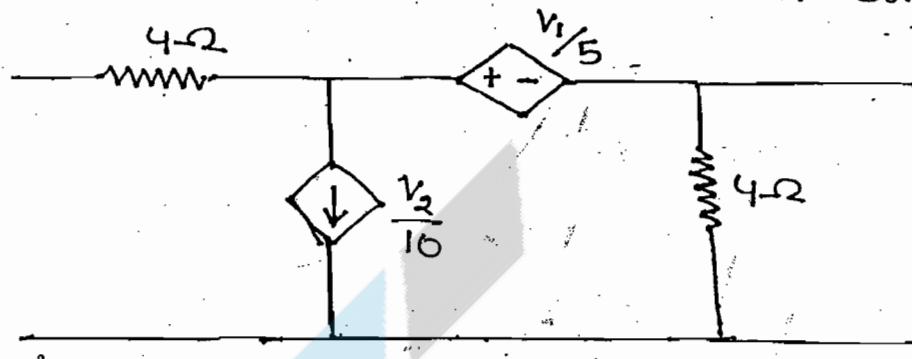ques:- Find B and  $\beta$  of the circuit shown



Soln:-

$$B = -\frac{V_1}{I_2} \Big|_{V_2=0}$$

$$\beta = -\frac{I_1}{I_2} \Big|_{V_2=0}$$

$$= -\frac{(-I_2)}{I_2} = 1$$

$$I_1 = -I_2$$

$$I_1 = V_1 - \frac{V_1}{5}$$

$$-I_2 = \frac{4V_1}{5}$$



$$\Rightarrow B = -\frac{V_1}{I_2} = 5$$

Ans
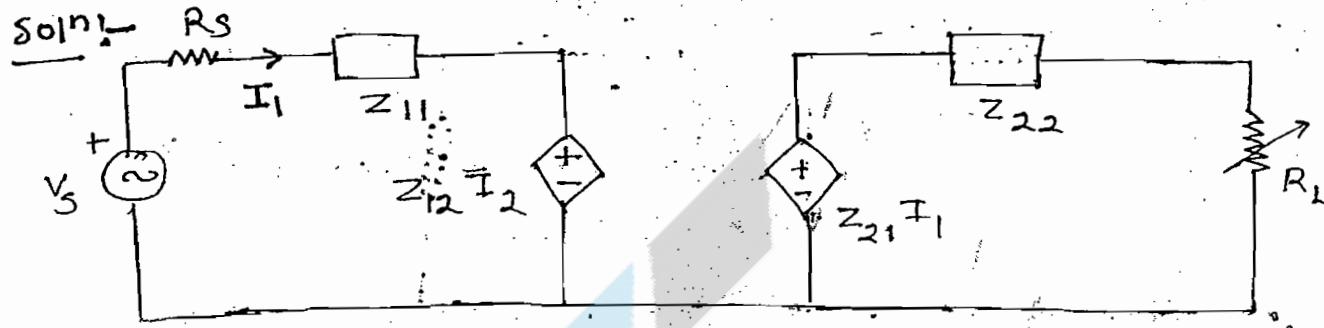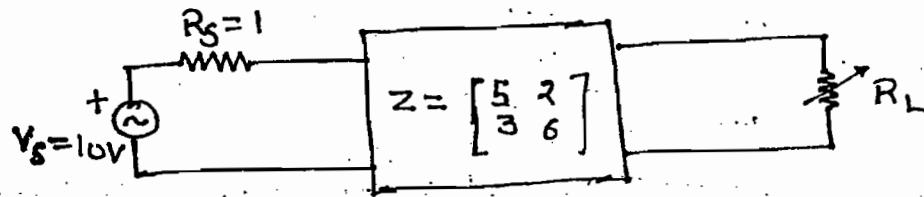
## Lecture - 12


**PHOTOSTAT**  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont: 9716162670

Ques:- Find max. power dissipation in load resistor



Case-(I) :-  $V_{th}$

Disconnect local resistor

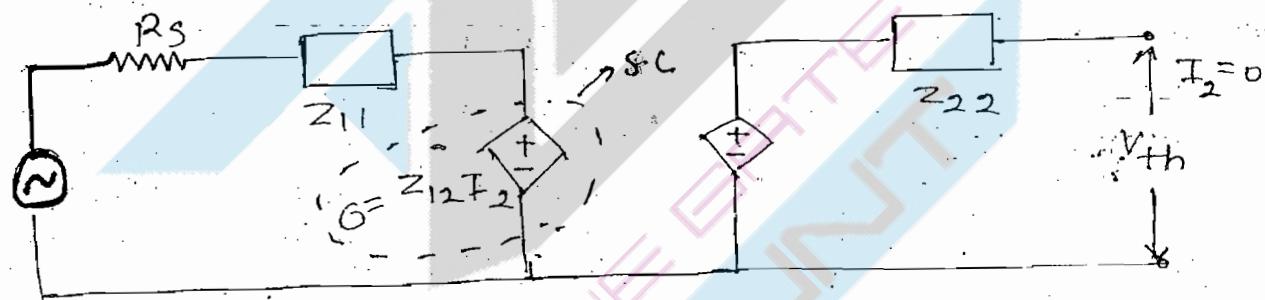

$$I_1 = \frac{V_s}{R_s + Z_{11}} \quad (I)$$

$$V_{th} = z_{21} I_1 \quad (II)$$


Substitute eq-(I) in eq-(II)

$$V_{th} = z_{21} \frac{V_s}{R_s + Z_{11}}$$

$$V_{th} = \frac{3 \times 10}{1+5} = 5$$

**PHOTOSTAT**  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont: 9716162670

Case-(ii) ( $R_{Th}$ ) :-

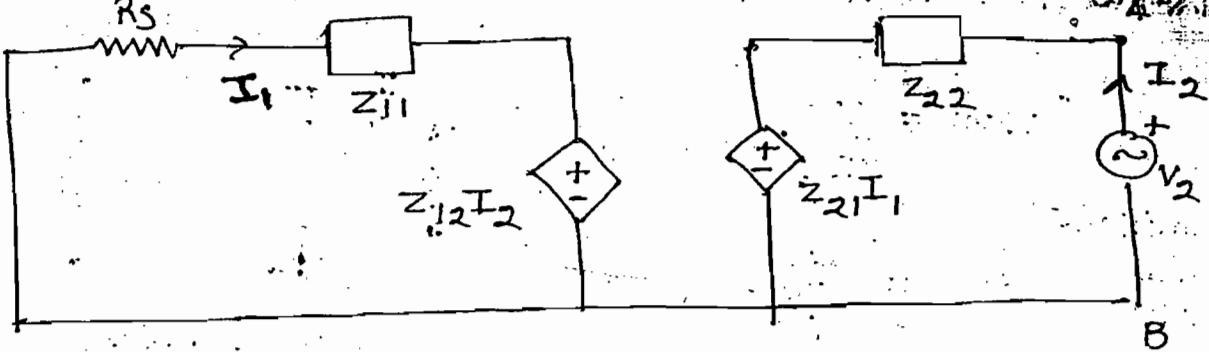

$$Z_{Th} = \frac{V_2}{I_2}$$

$$I_2 = \frac{V_2 - z_{21}I_1}{z_{22}}$$

$$I_1 = -\frac{z_{12}I_2}{R_s + z_{11}} \quad \text{--- (i)}$$

$$I_2 z_{22} = V_2 - z_{21}I_1$$

$$V_2 = I_2 z_{22} + z_{21}I_1 \quad \text{--- (ii)}$$

Substitute eq-(i) in eq-(ii).

$$V_2 = I_2 z_{22} - \frac{z_{12}z_{21}I_2}{R_s + z_{11}}$$


$$Z_{Th} = \frac{V_2}{I_2} = z_{22} - \frac{z_{12}z_{21}}{R_s + z_{11}}$$

$$= 6 - \frac{2 \times 3}{1+5} \Rightarrow Z_{Th} = 5$$

$$R_f = R_{Th} = 5 \Omega$$

$$P_{max} = \frac{V_{Th}^2}{4R_L}$$

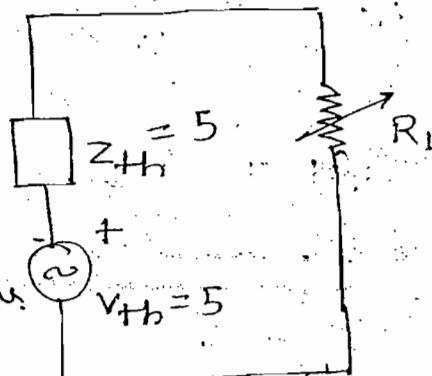
$$= \frac{25 \times 5}{4 \times 8} = 1.25 W, \text{ Ans.}$$


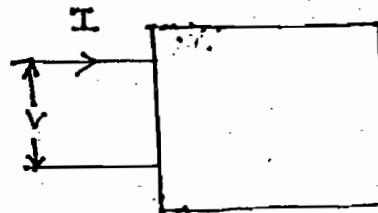
## Network Functions :-


PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Contd...

$$\left[ \begin{array}{l} Z(s) = \frac{V(s)}{I(s)} \\ Y(s) = \frac{I(s)}{V(s)} \\ \text{Immittance} \\ \text{Common Name} \end{array} \right]$$



Single Port

## Two Port :-

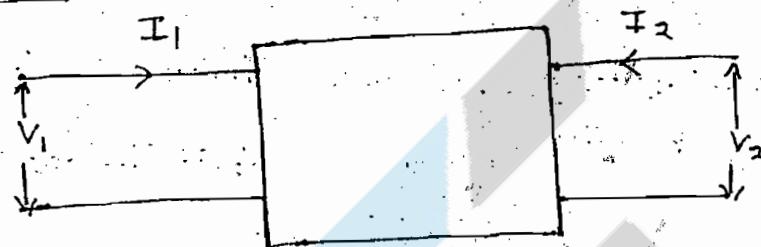

Driving Point I/p impedance

$$(I) \quad Z_{11}(s) = \frac{V_1(s)}{I_1(s)}$$

$$Z_{22}(s) = \frac{V_2(s)}{I_2(s)}$$

$$(II) \quad Y_{11}(s) = \frac{I_1(s)}{V_1(s)}$$

$$Y_{22}(s) = \frac{I_2(s)}{V_2(s)} \rightarrow \text{Driving pt admittance function}$$

$$(III) \quad Z_{12}(s) = \frac{V_1(s)}{I_2(s)}$$

$$Z_{21}(s) = \frac{V_2(s)}{I_1(s)} \rightarrow \text{Transfer impedance ratio}$$

$$(IV) \quad Y_{12}(s) = \frac{I_1(s)}{V_2(s)}$$

$$Y_{21}(s) = \frac{I_2(s)}{V_1(s)} \rightarrow \text{Transfer admittance ratio}$$

$$(V) \quad G_{12} = \frac{V_1(s)}{V_2(s)}$$

$$G_{21} = \frac{V_2(s)}{V_1(s)} \rightarrow \text{Transfer voltage ratio}$$

$$(VI) \quad \alpha_{12} = \frac{I_1(s)}{I_2(s)}$$

$$\alpha_{21} = \frac{I_2(s)}{I_1(s)} \rightarrow \text{Transfer current ratio}$$

- N/w parameter is calculated at pre-defined condition (either o.c or s.c)
- eg:-  $Z_{11} = \frac{V_1}{I_1} \quad | \quad Y_{11} = \frac{I_1}{V_1} \quad |$   
 $I_2 = 0 \rightarrow \text{o.c.} \quad V_2 = 0 \rightarrow \text{s.c.}$
- To find the N/w function, no pre-defined condition is required
- To represent the N/w simultaneously four parameter are required  
 eg:- To develop T-N/w  $Z_{11}, Z_{12}, Z_{21}, Z_{22}$  are required.
- By using only one N/w function it is possible to represent the N/w.

### Network Synthesis

- In the N/w analysis for a given N/w it is possible to find either voltage response or current response or impedance function or admittance function
- In a N/w synthesis, for a given function N/w is designed (It is reverse procedure of N/w analysis)
- In a N/w synthesis it is possible to design the N/w for the following functions


- Single port  $\rightarrow [1. Z(s) \quad 2. Y(s)] \rightarrow$  Immittance  
 $\qquad\qquad\qquad$  Driving Point Immittance
- Two port  $\rightarrow [1. Z_{11}(s), Z_{22}(s), Y_{11}(s), Y_{22}(s)] \rightarrow$  func  
 $\qquad\qquad\qquad$  2.  $Z_{12}(s), Z_{21}(s), Y_{12}(s), Y_{21}(s), G_{12}, G_{21}, X_{12}, X_{21} \rightarrow$  Transfer func

- In the N/w synthesis for given function it is possible to design the following N/w
- (I) Series      (II) Parallel      (III) Ladder

(I) Series  $\rightarrow$  Foster - I form

Partial fraction  
of expansion

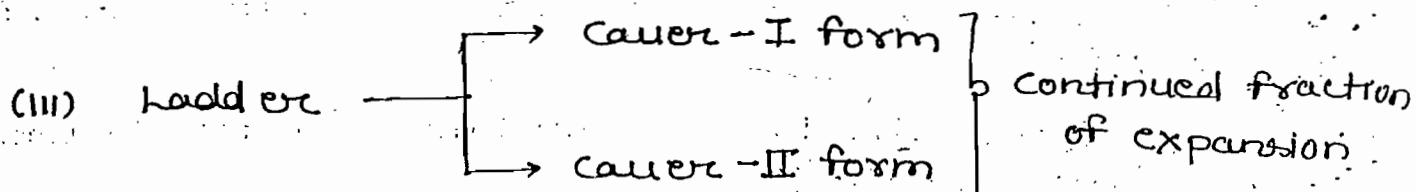(II) Parallel  $\rightarrow$  Foster - II form



Necessary condition to design a N/w:-

(I)  $F(s)$  should be ~~primarily~~ <sup>positive</sup> real function (PRF).

$$\begin{array}{l} R \geq 0 \\ L \geq 0 \\ C \geq 0 \end{array} \rightarrow \text{Positive Real}$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont-  
C

(II) If  $F(s)$  is PRF then  $\frac{1}{F(s)}$  also PRF

(III) If  $F_1(s)$  and  $F_2(s)$  are PRF then

$$F(s) = F_1(s) + F_2(s) \text{ are always PRF}$$

(IV) All the poles of the function should be present in the left half of the plane

(V) Imaginary poles and zeroes should be conjugate pairs

(VI) In the partial fraction of expansion residue should be positive real

(VII) Numerator and denominator polynomials should satisfy Hurwitz.


(VIII) The highest power of Numerator and denominator of polynomial should be differ at ~~by~~ <sup>at most</sup> unity. This condition prohibits multiple pole and zero at infinity.

→ The lowest power of Numerator and Denominator should be differ by almost unity. This conditions prohibits multiple poles and zeroes at origin.

→ Total No. of poles of a function should be equal to total no. of zeroes.

$$Z(s) = Z_1(s) + Z_2(s)$$


$$\Rightarrow Z_2(s) = Z(s) - Z_1(s)$$

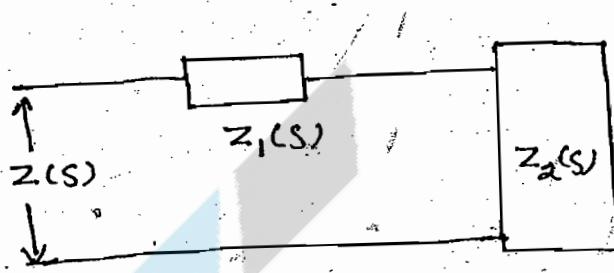

$$Y(s) = Y_1(s) + Y_2(s)$$

$$\Rightarrow Y_2(s) = Y(s) - Y_1(s)$$

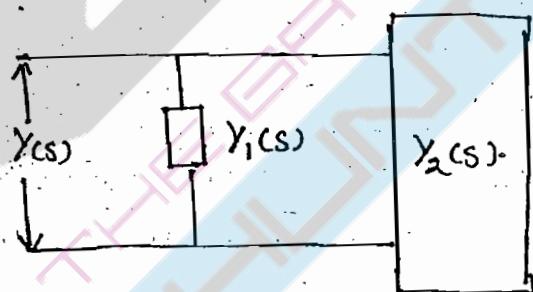**PHOTOSTAT**  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Contd. a-1102000



Removal of Pole at  $\infty$  :-

$$Z(s) = \frac{b_{n+1}s^{n+1} + b_ns^n + \dots + b_0}{a_ns^n + a_{n-1}s^{n-1} + \dots + a_0}$$

Numerator Power > Denominator power  
 → pole exist at  $\infty$ .

By long division


$$Z(s) = \frac{b_{n+1}s^{n+1}}{a_n s^n} + z_2(s)$$

$$\left( H = \frac{b_{n+1}}{a_n} \right)$$

$$Z(s) = HS + Z_2(s)$$

$$X_L = HS$$

$$Z_2(s) = Z(s) - HS$$

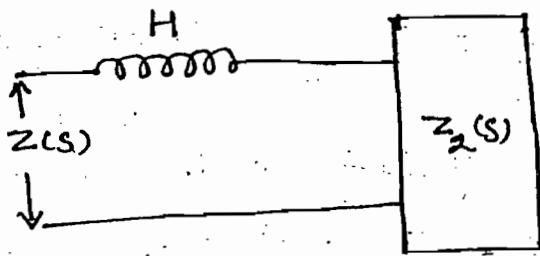

$$Y(s) = \frac{HS + Y_2(s)}{1}$$

$$B_C = SC$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9717122070

$$Y_2(s) = Y(s) - HS$$



Removal of pole at origin :-

$$Z(s) = \frac{b_0 + \dots + b_{n-1}s^{n-1} + b_n s^n}{s(a_0 + \dots + a_{n-1}s^{n-1} + a_n s^n)}$$


By long division,

$$Z(s) = \frac{b_0}{sa_0} + Z_2(s) \quad (k_0 = \frac{b_0}{a_0})$$

$$Z(s) = \frac{k_0}{s} + Z_2(s)$$

$$\Rightarrow Z_2(s) = Z(s) - \frac{k_0}{s}$$


$$X_C = \frac{1}{Cs}$$

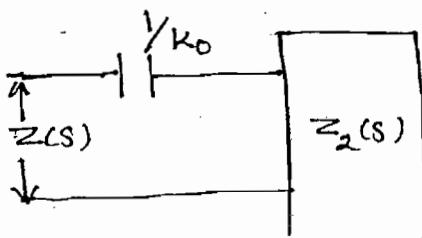

$$Y(s) = \frac{k_0}{s} + Y_2(s)$$

$$Y_2(s) = Y(s) - \frac{k_0}{s}$$

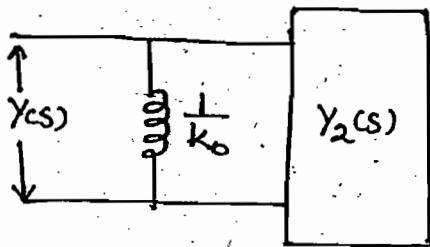PHOTOSTAT  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont.-S)



### Removal of conjugate Pair of Poles:

$$Z(s) = Z_1(s) + Z_2(s)$$

$$Z_2(s) = Z(s) - Z_1(s)$$

$$Z_1(s) \xrightarrow{\text{Poles}} \pm j\omega$$

$$Z_1(s) = \frac{k_1}{s+j\omega} + \frac{k_2}{s-j\omega} \quad (k_1 = k_2 = k)$$


$$Z_1(s) = \frac{k}{s+j\omega} + \frac{k}{s-j\omega}$$

$$Z_1(s) = \frac{2ks}{s^2 + \omega^2}$$

$$Z_1(s) = \frac{1}{\frac{s^2}{2k} + \frac{\omega^2}{2k}} = \frac{1}{Y_a + Y_b}$$

$B_C = SC$

$B_L = \frac{1}{Ls}$

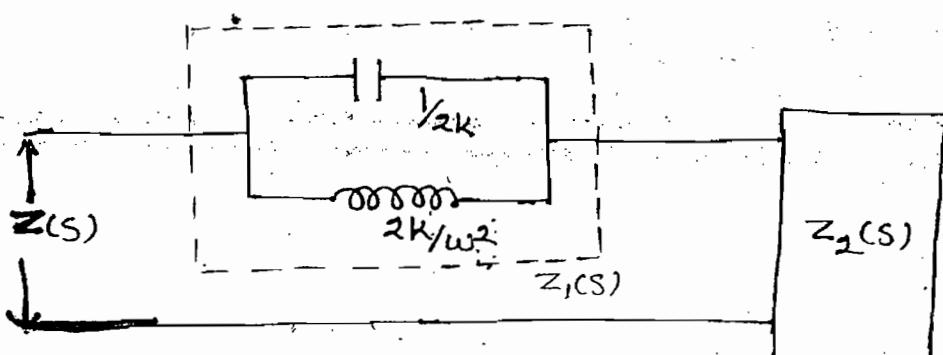

$$Y(s) = Y_1(s) + Y_2(s)$$


$$Y_2(s) = Y(s) - Y_1(s)$$

$$Y_1(s) = \frac{1}{\frac{s + \omega^2}{2K} + \frac{1}{2Ks}} = \frac{1}{Z_a + Z_b}$$

$X_L = s$

$$X_C = \frac{1}{Cs}$$

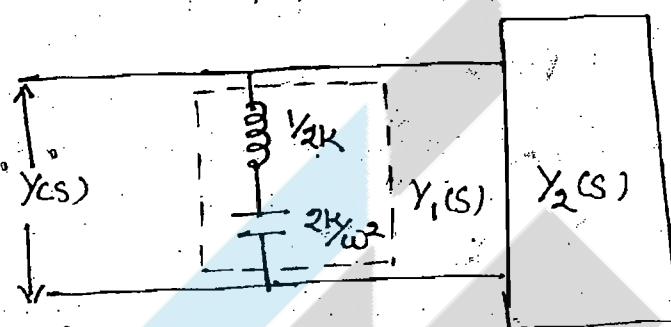
PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont.-o)



Removal of constant:


$$Z(s) = K + Z_2(s)$$

$$Z_2(s) = Z(s) - K$$

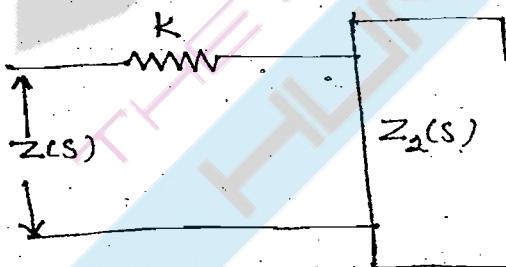

$$Y(s) = K + \frac{1}{2}(s)$$

$$Y_2(s) = Y(s) - K$$

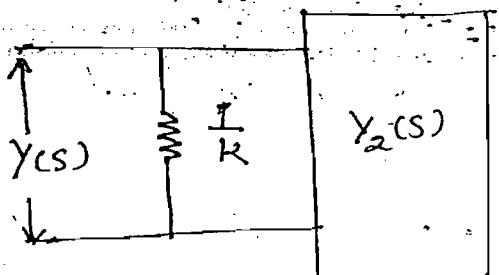


PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont.-o)

## LC N/W Foster - I form :- (Series)

$$Z(s) = \frac{k_0}{s} + \sum_{i=1}^n \frac{2k_i s}{s^2 + \omega_i^2} + HS \quad (X_L = LS)$$

$$X_C = \frac{1}{CS}$$

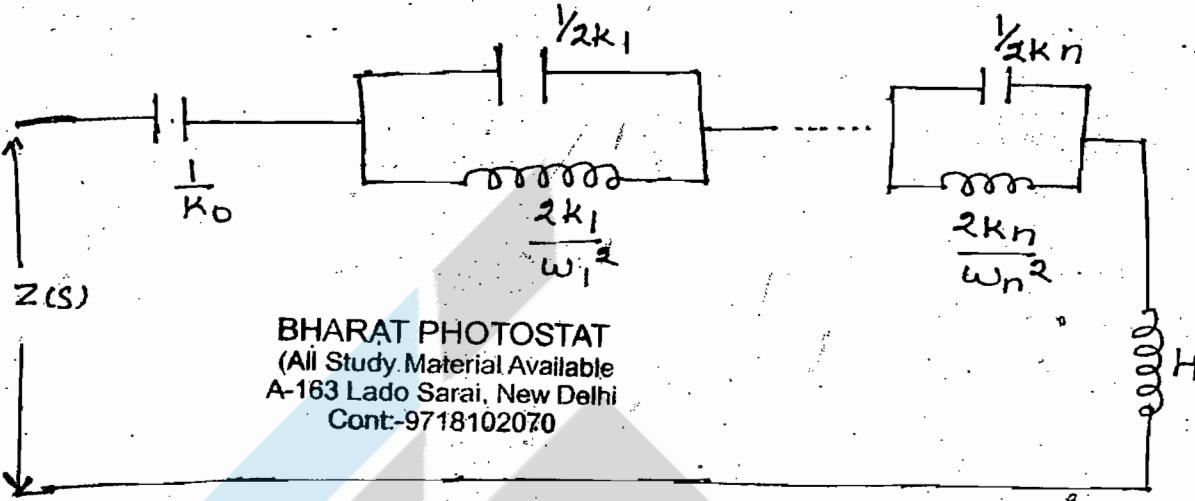


BHARAT PHOTOSTAT  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont-9718102070

## Lecture - 13

## LC N/W Foster - II form :- (Parallel)

$$Y(s) = \frac{k_0}{s} + \sum_{i=1}^n \frac{2k_i s}{s^2 + \omega_i^2} + HS \quad B_C = SC$$

$$B_L = \frac{1}{LS}$$

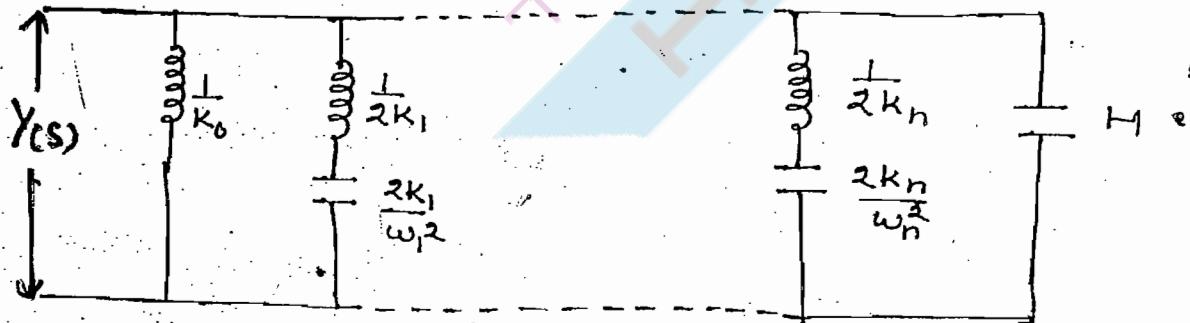

Ques:- Obtain foster - I & II from  $Z(s)$

$$Z(s) = \frac{(s^2 + 2)(s^2 + 4)}{s(s^2 + 3)}$$

Soln:-

Foster - I :-

Pole  $\rightarrow \infty \rightarrow HS$

Pole  $\rightarrow$  origin  $\rightarrow k_0/s$

Pole  $\rightarrow$  conjugate  $\rightarrow \frac{2ks}{s^2 + \omega^2}$

$$Z(s) = \frac{k_0}{s} + \frac{2ks}{s^2 + \omega^2} + HS$$


$$\frac{(s^2+2)(s^2+4)}{s(s^2+3)} = \frac{k_0}{s} + \frac{2ks}{s^2+3} + HS \quad (\text{Partial Fraction})$$

$$k_0 = \frac{8}{3} \quad 2k \rightarrow \frac{1}{3} \quad H \rightarrow 1$$

$$Z(s) = \frac{8/3}{s} + \frac{s/3}{s^2+3} + s$$

$$\Rightarrow Z(s) = \frac{1}{\frac{3}{8}s} + \frac{\frac{1}{3}}{\frac{s^2}{3} + \frac{3}{3}} + s$$
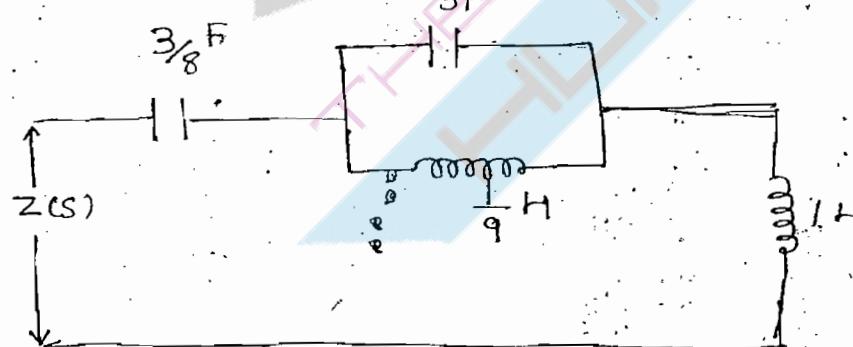
$$\Rightarrow Z(s) = \frac{1}{\frac{3}{8}s} + \frac{\frac{1}{3}}{\frac{3s^2 + 9}{3}} + s$$
  
$$X_C = \frac{1}{Cs}$$
  
$$B_C = sc$$
  
$$B_L = \frac{1}{Ls}$$



CHIAT STAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 97

Foster - II :-

Note :- If  $F(s)$  is given by using same function foster - I and II form are obtained.

- If  $Z(s)$  is given by using  $\frac{1}{Z(s)}$  function foster-II form is obtained
- If  $Y(s)$  is given by using  $\frac{1}{Y(s)}$  function foster-I form is obtained.

$$Y(s) = \frac{s(s^2+3)}{(s^2+2)(s^2+4)}$$

$P \rightarrow \infty$  X

$P \rightarrow \text{origin}$  X

$P \rightarrow \text{conjugate pair}$

$$Y(s) = \frac{2k_1 s}{s^2 + \omega_1^2} + \frac{2k_2 s}{s^2 + \omega_2^2}$$

$$\frac{s(s^2+3)}{(s^2+2)(s^2+4)} = \frac{2k_1 s}{s^2+2} + \frac{2k_2 s}{s^2+4}$$

$$2k_1 \rightarrow \frac{1}{2} \quad \& \quad 2k_2 \rightarrow \frac{1}{2}$$


$$Y(s) = \frac{s/2}{s^2+2} + \frac{s/2}{s^2+4}$$

$$\Rightarrow Y(s) = \frac{1}{\frac{s^2}{s/2} + \frac{2}{s/2}} + \frac{1}{\frac{s^2}{s/2} + \frac{4}{s/2}}$$

$$\Rightarrow Y(s) = \frac{1}{2s + \frac{4}{s}} + \frac{1}{2s + \frac{8}{s}}$$

$$\left( x_L = Ls \quad x_C = Cs \right)$$
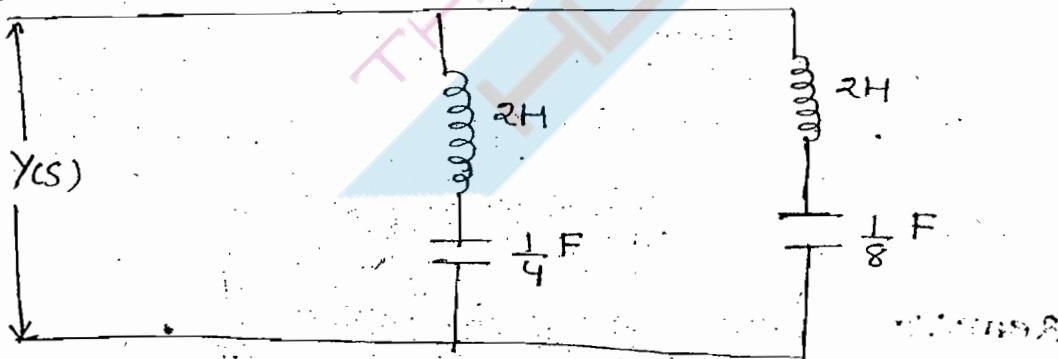
$$\frac{1}{z_a + z_b} \quad \frac{1}{z_c + z_d}$$



PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contd...)

LC N/W Cauer-I form :-

→ Laddler

(i) Removal of Pole at  $\infty$  :-

$$Z_2(s) = Z(s) - H_1 s \quad (X_L = 1s)$$

$$Y_2(s) = \frac{1}{Z_2(s)}$$

$$Y_3(s) = Y_2(s) - H_2 s \quad (B_C = sC)$$


$$Z_3(s) = \frac{1}{Y_3(s)}$$

$$Z_4(s) = Z_3(s) - H_3 s$$

$$Y_4(s) = \frac{1}{Z_4(s)}$$

$$Y_5(s) = Y_4(s) - H_4 s$$

$$Y_4(s) = Y_5(s) + H_4 s$$

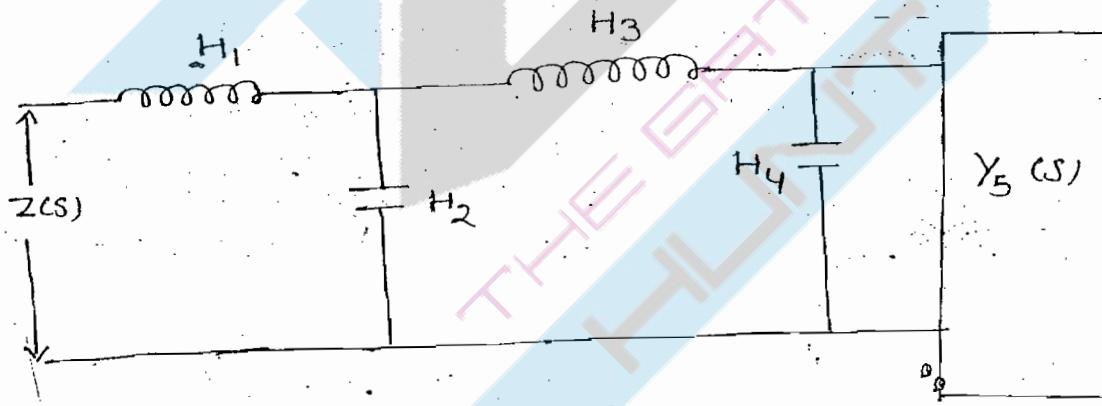

PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai New Delhi  
Contd.

LC N/W Cauer-II form :-


Removal of Pole at origin :-

$$Z_2(s) = Z(s) - \frac{k_{01}}{s}$$

$$Y_2(s) = \frac{1}{Z_2(s)} \quad \left( X_C = \frac{1}{Cs} \right)$$

$$Y_3(s) = Y_2(s) - \frac{k_{02}}{s}$$
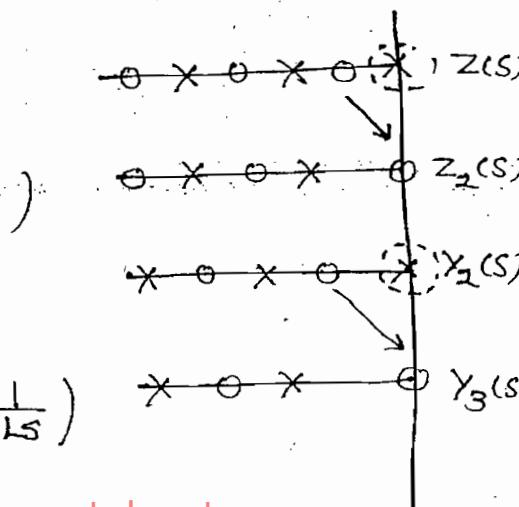
$$Z_3(s) = \frac{1}{Y_3(s)} \quad (B_L = \frac{1}{Ls})$$




$$z_4(s) = z_3(s) - \frac{k_{03}}{s}$$

$$y_4(s) = \frac{1}{z_4(s)}$$

$$y_5(s) = y_4(s) - \frac{k_{04}}{s}$$

$$y_4(s) = y_5(s) + \frac{k_{04}}{s}$$

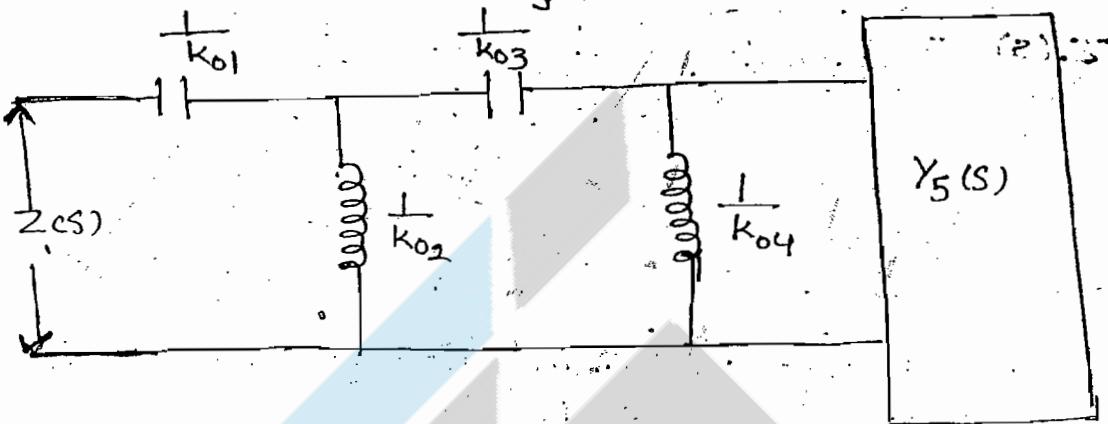

ques:- Obtain Cauer - I and II form

$$z(s) = \frac{s^3 + 2s}{s^4 + 5s^2 + 4}$$

Soln:-

Cauer - I

Pole at  $\infty \rightarrow$  not present

then reciprocal


$$y(s) = \frac{s^4 + 5s^2 + 4}{s^3 + 2s}$$

$$\begin{array}{r} s^3 + 2s \\ \sqrt{s^4 + 5s^2 + 4} \\ \hline s^4 + 2s^2 \end{array} \quad \begin{array}{l} s^3 \rightarrow B_C = SC \\ \hline s \rightarrow Y \end{array}$$

$$\begin{array}{r} 3s^2 + 4 \\ \sqrt{s^4 + 5s^2 + 4} \\ \hline s^3 + 2s \end{array} \quad \begin{array}{l} s \rightarrow Z \\ \hline \frac{s}{3} \rightarrow X_L = LS \end{array}$$

$$\begin{array}{r} s^3 + \frac{4s}{3} \\ \sqrt{\frac{2s}{3}} \int 3s^2 + 4 \\ \hline \frac{2s}{3} \end{array} \quad \begin{array}{l} \frac{9}{2}s \rightarrow Y \\ \hline 4 \int \frac{2s}{3} \left( \frac{s}{6} \right) \rightarrow Z \\ \hline \frac{2s}{3} \end{array}$$

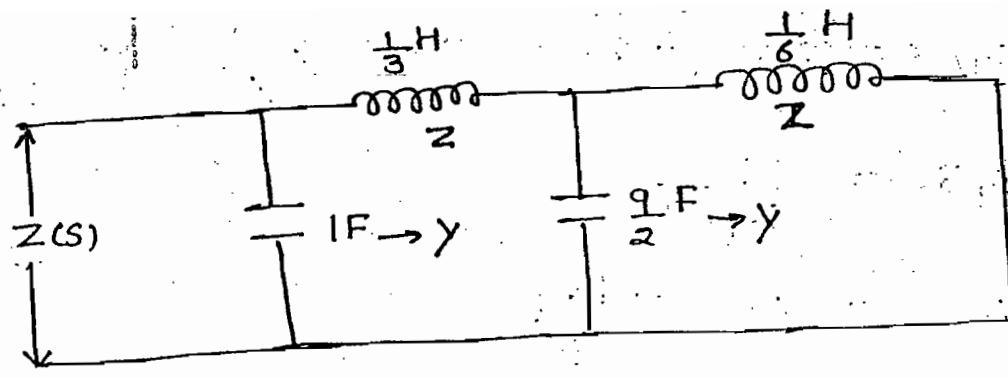PHOTOSTAT  
All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. 071 277 2770



$$Z(s) = s + \frac{1}{\frac{s}{3} + \frac{1}{\frac{9s}{2} + \frac{1}{\frac{s}{6}}}}$$

**PHOTOSTAT**  
 (All Study Material Available)  
 A-163 Lado Sarai, New Delhi  
 Cont:

Cause-II Form:-

Pole → origin not present then take reciprocal

$$Z(s) = \frac{s(s^2+2)}{s^4+5s^2+4}$$

$$Y(s) = \frac{s^4+5s^2+4}{s^3+2s}$$

$$2s+s^3 \overline{) s^4+5s^2+4} \left( \frac{2}{s} \right) \rightarrow Y \quad B_L = \frac{1}{1s}$$

$$\frac{2s^2+4}{3s^2+s^4} \overline{) 2s+s^3} \left( \frac{2}{3s} \right) \rightarrow Z \quad X_C = \frac{1}{cs}$$

$$2s+\frac{2s^3}{3} \overline{) } \frac{s^3}{3} \left( \frac{9}{s} \right) \rightarrow Y$$

$$\frac{9}{s} \overline{) } \frac{s^3}{3} \left( \frac{1}{3s} \right) \rightarrow Z$$

$$\frac{s^3}{3} \overline{) }$$

$$\frac{5}{3} \overline{) }$$


$$\frac{5}{3} \overline{) }$$

$$\frac{X}{3} \overline{) }$$

**PHOTOSTAT**

**PHOTOSTAT**

20/12/2070

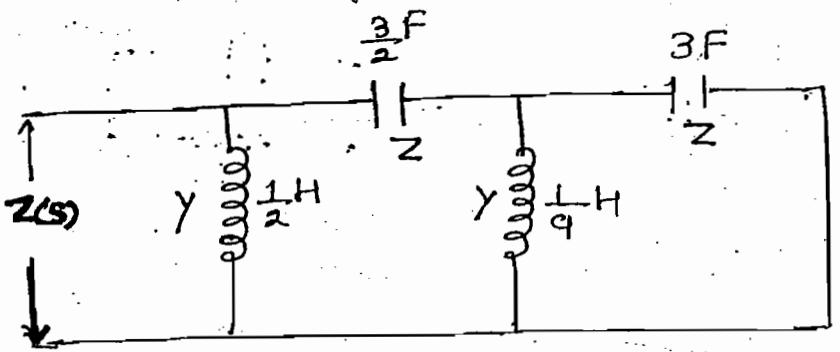




$$Z(s) = \frac{2}{s^2} + \frac{1}{\frac{2}{3s} + \frac{1}{\frac{9}{s} + \frac{1}{\frac{1}{3s}}}}$$

RC N/W Foster-I form :-

$$\frac{Z(s)}{R_C} = \frac{k_0}{s} + \sum_{i=1}^n \frac{2k_i s}{s^2 + \omega_i^2} + Hs$$

$$\frac{Z(s)}{R_C} = \frac{k_0}{s} + \sum_{i=1}^n \frac{k_i}{s + \omega_i} + k_\theta s$$

$$x_c = \frac{1}{cs}$$

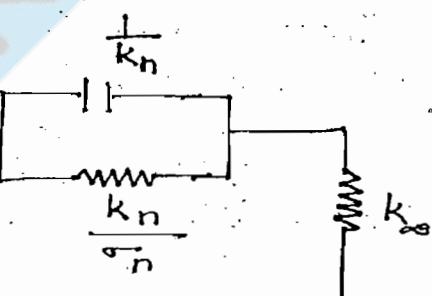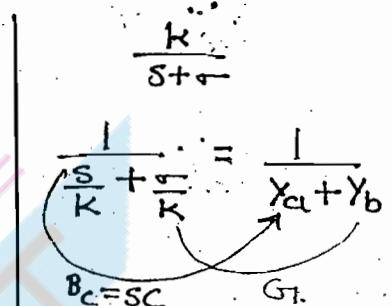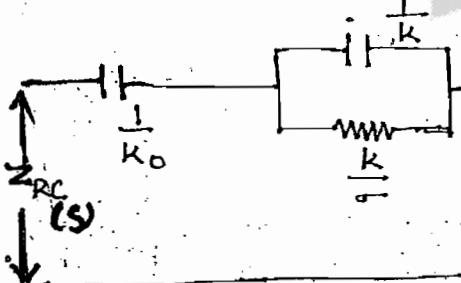


→ Series N/W is obtained

RC N/W Foster-II form :-

$$\frac{Z(s)}{R_C} = \frac{k_0}{s} + \sum_{i=1}^n \frac{k_i}{s + \omega_i}$$

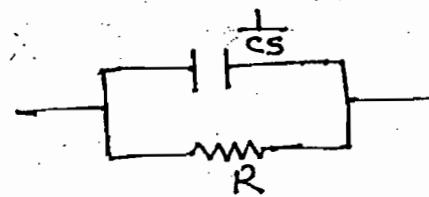
$$\rightarrow Z_{RC}(s) = \frac{R \frac{1}{cs}}{R + \frac{1}{cs}}$$



$$Z_{RC}(s) = \frac{R}{Rcs + 1}$$

$$Z_{RC}(s) = \frac{R}{RC(s + \frac{1}{RC})}$$
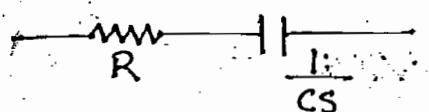
$$\rightarrow Y_{RC}(s) = \frac{1}{R + \frac{1}{cs}}$$



$$Y_{RC}(s) = \frac{cs}{Rcs + 1}$$

$$Y_{RC}(s) = \frac{cs}{RC(s + \frac{1}{RC})}$$

$$\frac{Y_{RC}(s)}{s} = \frac{1}{R(s + \frac{1}{RC})}$$


PHOTOSTAT  
 (All Study Material Available)  
 A-163 Lado Sarai, New Delhi  
 Cont: 9101010101

Note:-



→ Pole-zero pattern of  $Z_{RC}$  and  $Y_{RC}(s)$  are identical  
 Thereby both functions can be represented by same mathematical equation.

$$\frac{Y_{RC}(s)}{s} = \frac{k_0}{s} + \sum_{i=1}^n \frac{k_i s}{s + \omega_i} + k_\infty$$
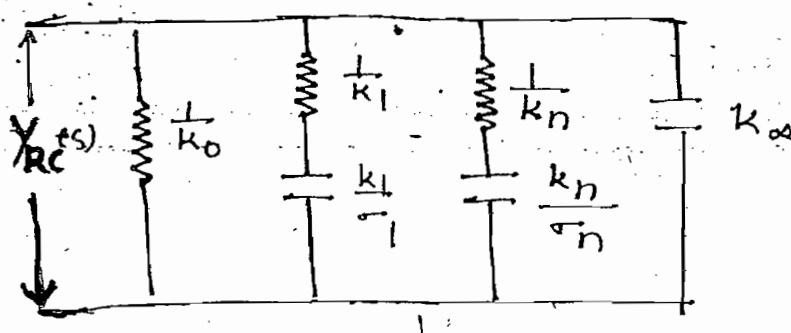
$$Y_{RC}(s) = k_0 + \sum_{i=1}^n \frac{k_i s}{s + \omega_i} + k_\infty s$$



Dotted upto n

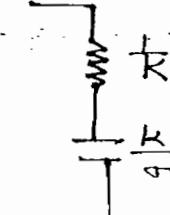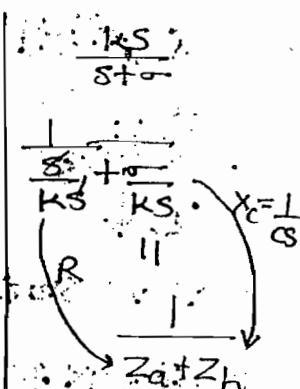

RC N/W Cauer-I form:-

$$LC \rightarrow z_2(s) = z(s) - H_1 s \quad Y_2(s) = \frac{1}{z_2(s)} \quad (X_L = LS)$$

$$Y_3(s) = H_2 s$$

RC  $\rightarrow$  Step-I :-

Removal of constant from  $Z(s)$

$$z_2(s) = z(s) - k_1$$

$$Y_2(s) = \frac{1}{z_2(s)}$$

Step-II :-

Removal of Pole at  $\infty$  from  $Y(s)$

$$Y_3(s) = Y_2(s) - H_1 s$$


$$Z_3(s) = \frac{1}{Y_3(s)}$$

$$Z_4(s) = Z_3(s) - k_2$$

$$Y_4(s) = \frac{1}{Z_4(s)}$$

$$Y_5(s) = Y_4(s) - H_2 s$$

$$Y_4(s) = Y_5(s) + H_2 s$$

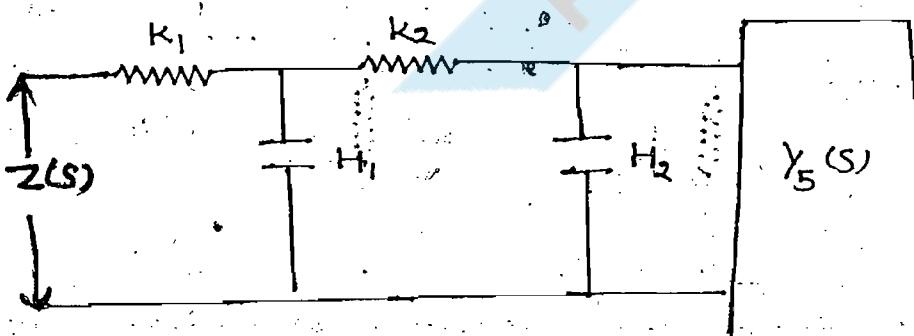

→ Ladder N/W is obtained

Notes -

Step-I and Step-II are alternatively repeated until the total function is realised

RC N/W Cauer-II form! -

$$LC \rightarrow Z_2(s) = Z(s) - \frac{k_{01}}{s} \quad Y_2(s) = \frac{1}{Z_2(s)}, \quad Y_3(s) = \frac{k_{02}}{s} \quad (B_L = \frac{1}{Ls})$$

$(X_C = \frac{1}{Cs})$

RC  $\rightarrow$  Step-I:

Removal of pole at origin from  $Z(s)$

$$Z_2(s) = Z(s) - \frac{k_{01}}{s}$$

$$Y_2(s) = \frac{1}{Z_2(s)}$$

Step-II:

Removal of constant from  $Y(s)$

$$Y_3(s) = Y_2(s) - k_1$$

$$Z_3(s) = \frac{1}{Y_3(s)}$$


$$Z_4(s) = Z_3(s) - \frac{k_{03}}{s}$$

$$Y_4(s) = \frac{1}{Z_4(s)}$$

$$Y_5(s) = Y_4(s) - k_2$$

$$Y_4(s) = Y_5(s) + k_2$$

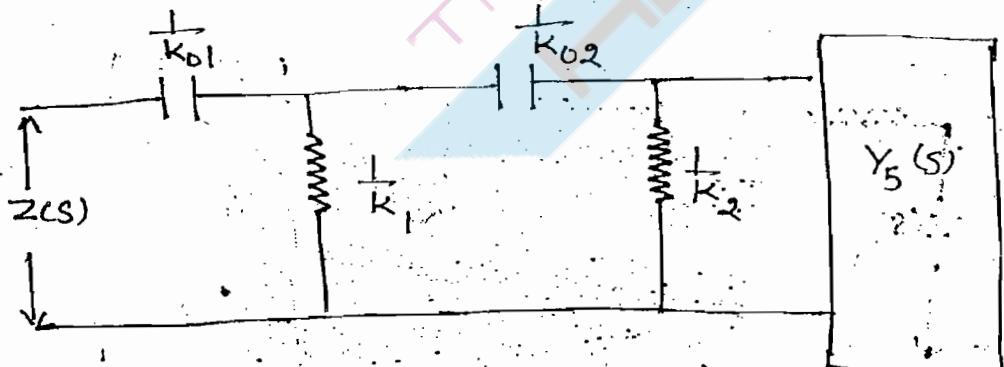Digitized by PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont.



$\rightarrow$  Ladder N/W is obtained

Note! -

Step-I and II are alternatively repeated until the total function is realised.

Filters:-

W.r.t to components present in the N/W filters are classified as

(I) Active Filter

→ Active filter consist of op-amp and capacitor

→ In the active filter it is possible to inc. the gain of the system

→ Generally inductor is not preferred in the active filter since its size is bulky and cost is high

→ Passive filter consist of LC series and parallel sections (Reactive N/W)

→ Based on the operating frequency filters are classified as

(I) LPF

(II) HPF


(III) BPF

(IV) BRF (Band stop)

(V) All pass

LPF:-

First order

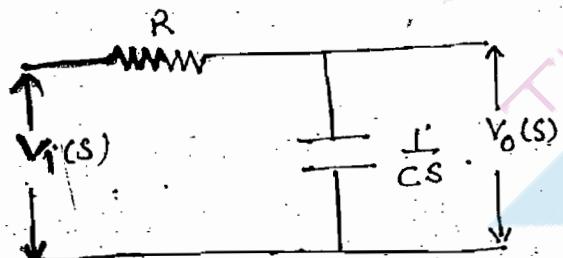


$$V_o(s) = V_i(s) \frac{1}{\frac{R}{C} + sL}$$


$$\Rightarrow \frac{V_o(s)}{V_i(s)} = \frac{1}{1 + RCs}$$

$$\boxed{\frac{V_o(s)}{V_i(s)} = \frac{1}{1 + RCs}}$$


Second order

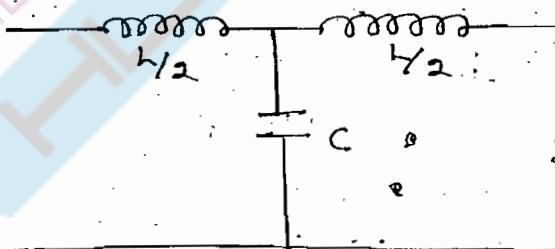
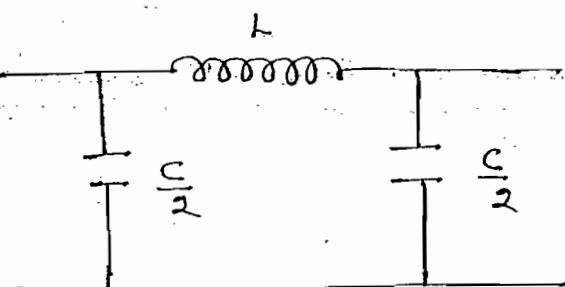
$$Z_L = 2\pi f L, \quad Z_C = \frac{1}{2\pi f C}$$



Sym-IT

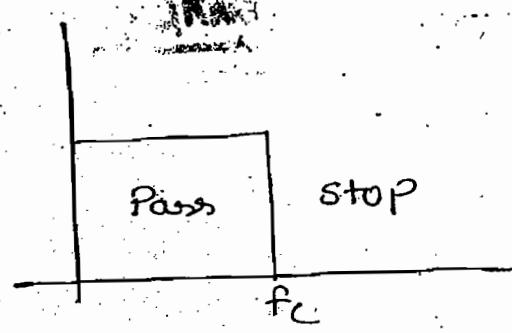


→ Inductor provide low resistance path and capacitor bypass higher frequency

$L \rightarrow$

HPF :-

→ For lower freq. capacitor provides high impedance




First order

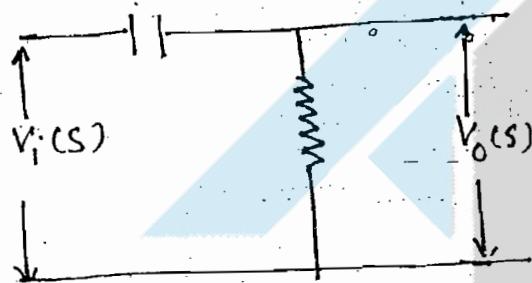


$$V_o(s) = V_i(s) \frac{R}{R + \frac{1}{Cs}}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{Rcs}{Rcs + 1}$$

Second order

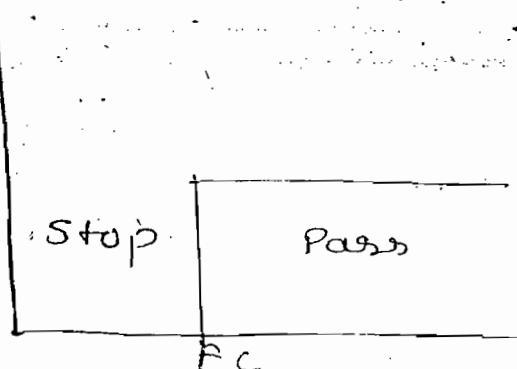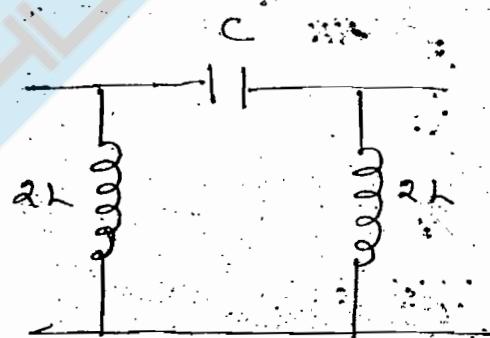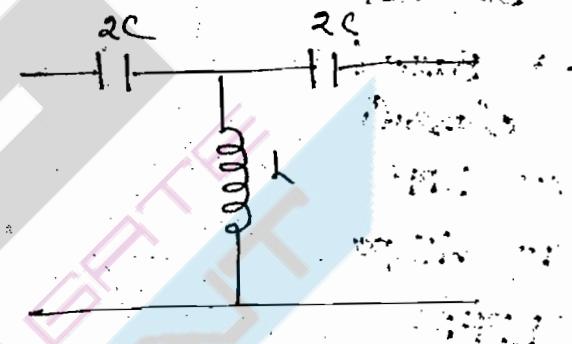


BPF:-

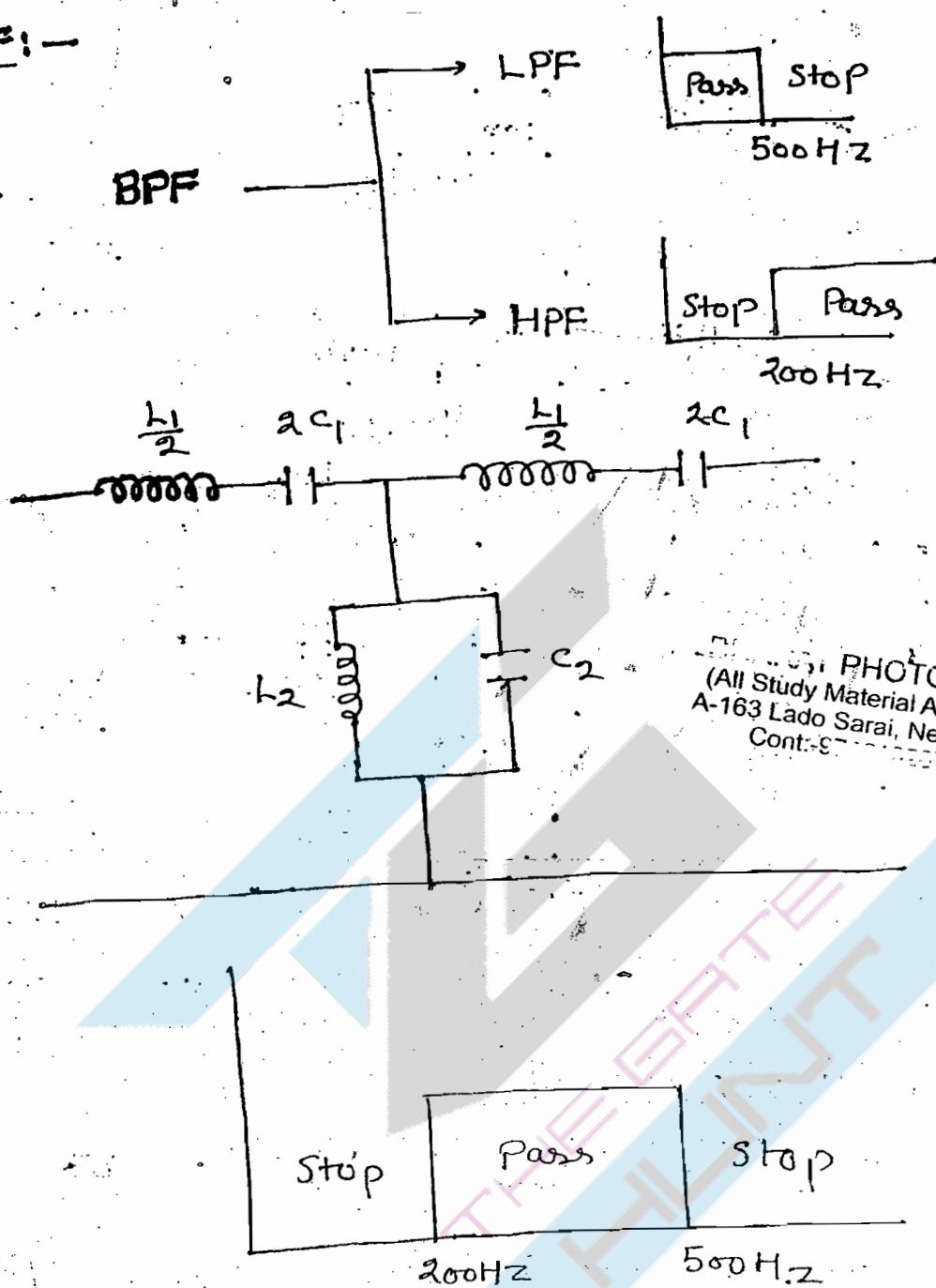

- BPF is obtained with a combination of LPF & HPF and cut-off freq of LPF should be greater than cut-off freq of HPF
- In the BPF first cut-off frequency is calculate w.r.t series resonance and second cut-off freq is calculated w.r.t parallel resonance


BEF !

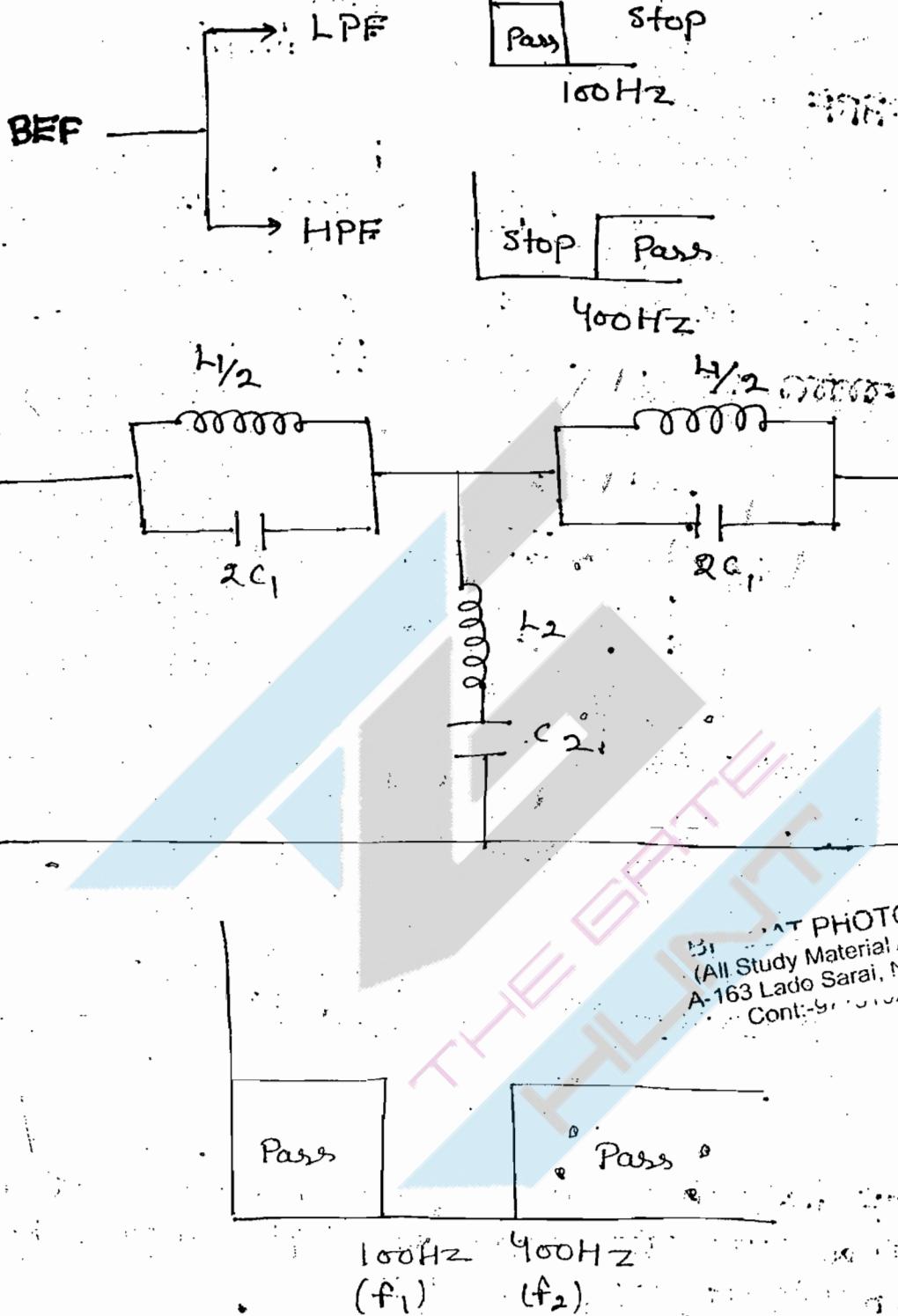

B1 PHOTOSTAT  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Contd...)


→ BEF is obtained with a combination of LPF and HPF and cut-off frequency of high pass filter should be greater than cut-off freq. of low pass filter.
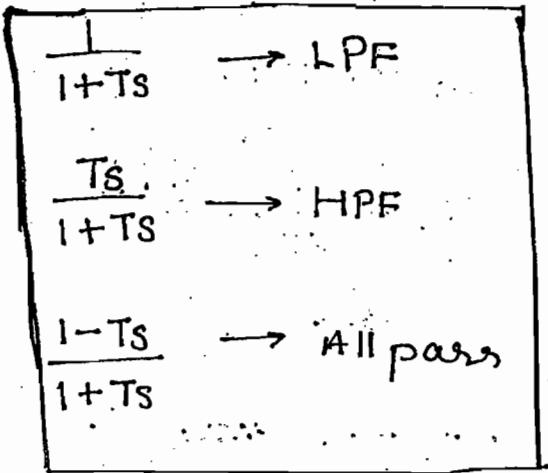
## Transfer Function of first order filter:-



Note! - In all pass filter zero's are present in the right half of plane and poles are present in left half of plane

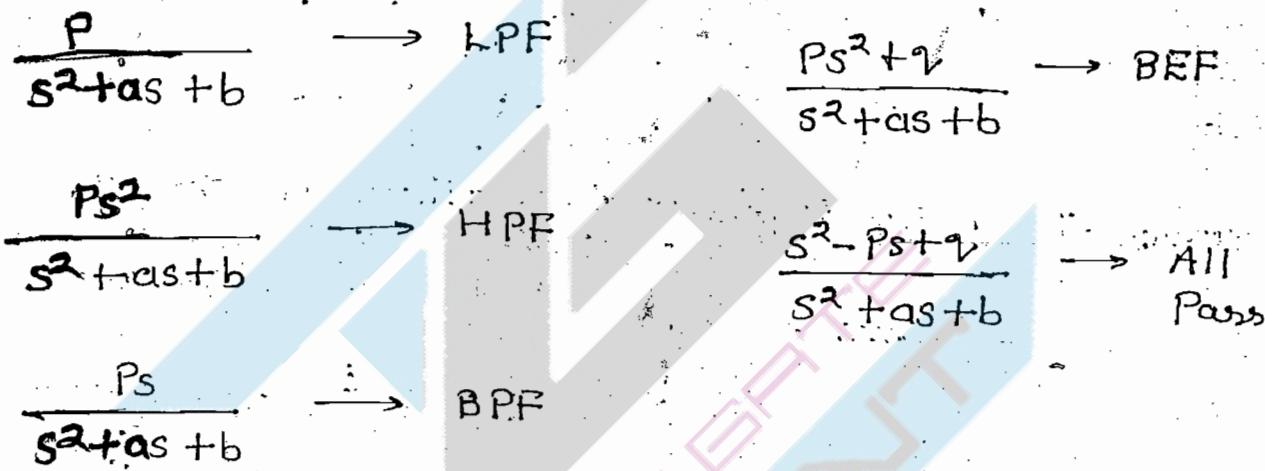
## Transfer Function of second order filter:-


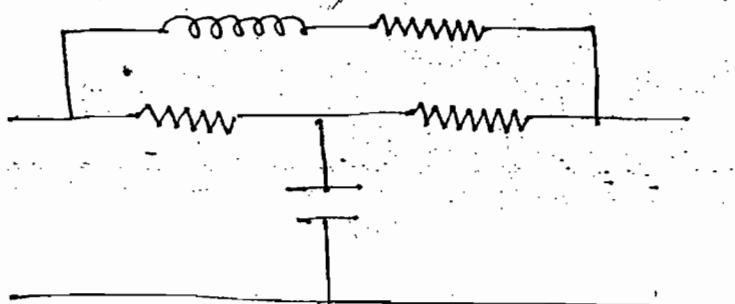
### Note! -

Poles and zeroes are unsymmetrical about  $jw$ -ax  
(All pass)

Ques! Identify type of the filter of the ckt shown



Soln:-

Soln:


$$f = 0$$

$$X_L = 2\pi f L = 0$$

$L \rightarrow S.C$

$$X_C = \frac{1}{2\pi f C} = \infty$$

$C \rightarrow O.C$

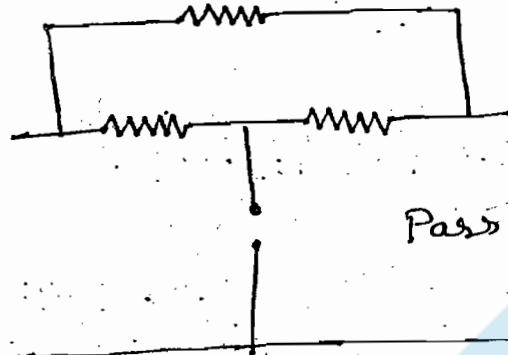


$$f = \infty$$

$$X_L = 2\pi f L = \infty$$


$L \rightarrow O.C$

$$X_C = \frac{1}{2\pi f C} = 0$$

$C \rightarrow S.C$

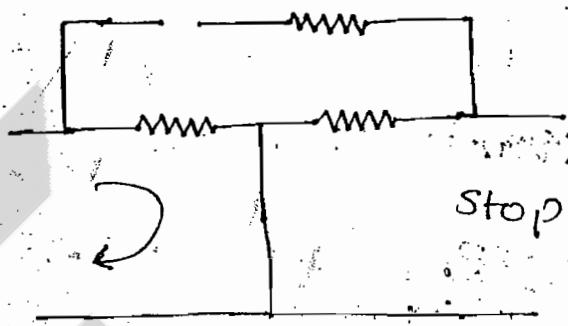

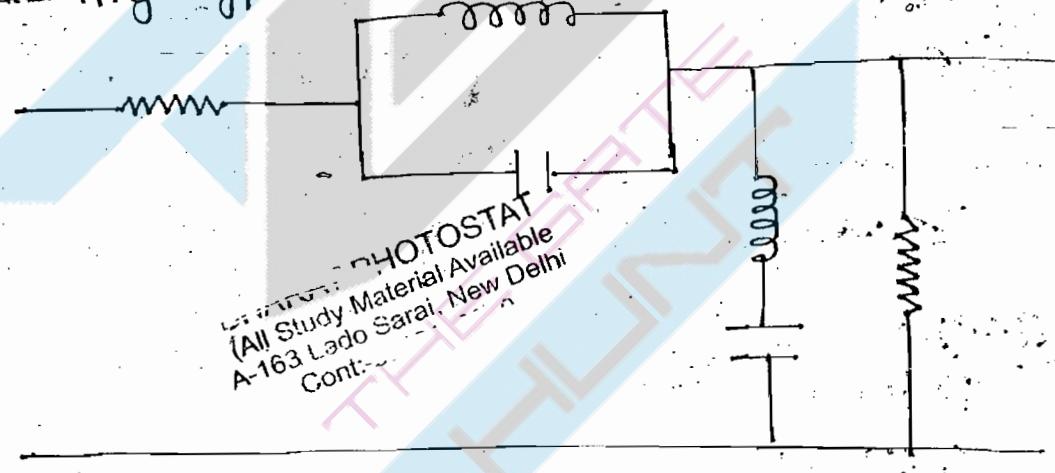Ques: Identify type of the filter of ckt. shown.



Soln:


$$f = 0$$

$$X_L = 2\pi f L = 0$$

$L \rightarrow S.C$

$$X_C = \frac{1}{2\pi f C} = \infty$$

$C \rightarrow O.C$

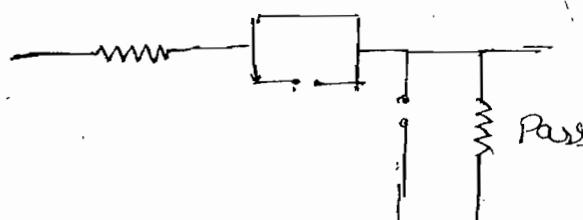


$$f = \infty$$

$$X_L = 2\pi f L = \infty$$

$L \rightarrow O.C$



$$X_C = \frac{1}{2\pi f C} = 0$$

$C \rightarrow S.C$

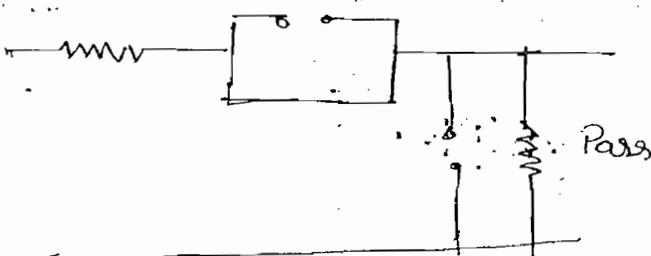

For BEF & All pass filter draw eq. ckt at resonant freq.

$$f = f_0$$

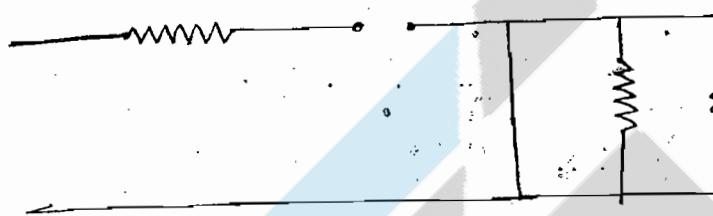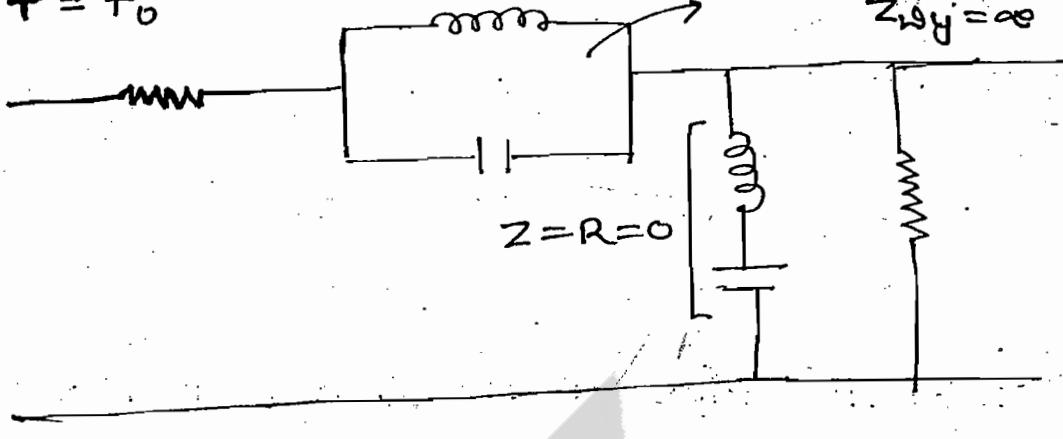

→ BEF Ans

PRINTED PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont: 9899999999

### Note:-

When BEF eliminates only few frequency then it is also called as Notch filter.

Ques:- Identify type of the filter of the ckt shown





Soln:-  $f = 0$

$$X_L = 2\pi f L = 0$$

$\rightarrow S.C$

$$X_C = \frac{1}{2\pi f C} = 0$$

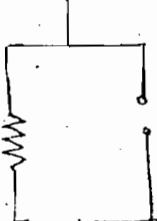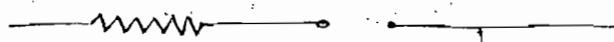

Stop

$$f = \infty$$

$$X_L = 2\pi f L = \infty$$


L  $\rightarrow$  0.C

$$X_C = \frac{1}{2\pi f C} = 0$$

C  $\rightarrow$  S.C

$\rightarrow$  BPF

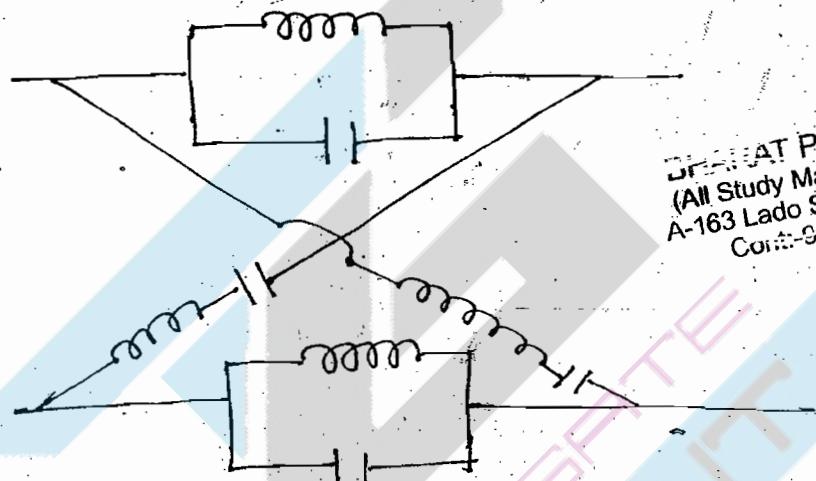Ques!:- Identify type of the filter of the ckt shown




DRAVAT PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contt: 91 9899673

Ans!- All pass ( $f = 0, f = \infty, f = f_0$ )

Magnetic Coupled circuits!-

Case-(I) :-

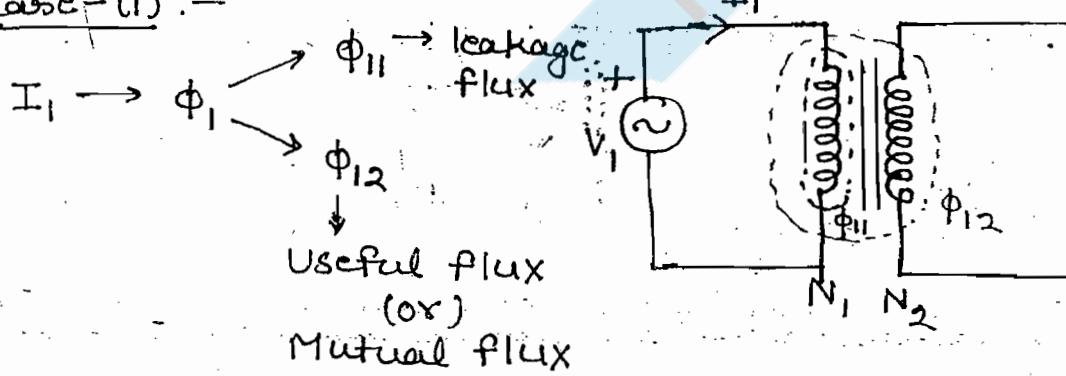

$$e_1 \propto \frac{d\phi_1}{dt}$$

$$e_1 = -N_1 \frac{d\phi_1}{dt}$$

$$e_1 = -N_1 \frac{d\phi_1}{di_1} \cdot \frac{di}{dt} \quad (L = \frac{N\phi}{i})$$

$$e_1 = -L_1 \frac{di_1}{dt}$$

Self induced emf

$$e_2 \propto \frac{d\phi_{12}}{dt}$$

$$e_2 = -N_2 \frac{d\phi_{12}}{dt}$$



$$e_2 = -N_2 \frac{d\phi_{12}}{di_1} \frac{di_1}{dt} \quad (M_{21} = \frac{N_2 \phi_{12}}{i_1})$$

$$e_2 = -M_{21} \frac{di_1}{dt}$$

Mutual Induced emf

Mutual inductance  
of second inductor  
w.r.t. 1

Case-(II):-

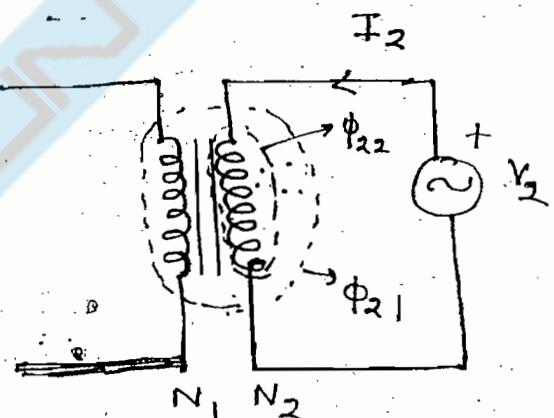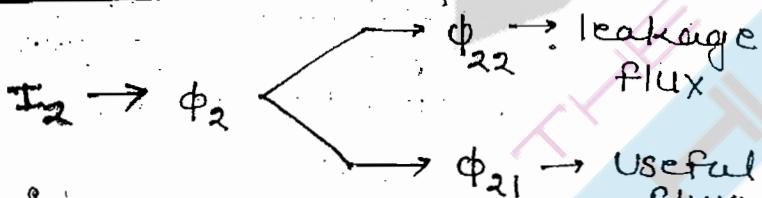

$$e_2 \propto \frac{d\phi_2}{dt}$$

$$e_2 = -N_2 \frac{d\phi_2}{dt}$$

$$e_2 = -N_2 \frac{d\phi_2}{di_2} \frac{di_2}{dt} \quad (L = \frac{N\phi}{i})$$

$$e_2 = -L_2 \frac{di_2}{dt}$$

self induced emf

$$e_1 \propto \frac{d\phi_{21}}{dt}$$

$$e_1 = -N_1 \frac{d\phi_{21}}{dt}$$

$$e_1 = -N_1 \frac{d\phi_{21}}{di_2} \cdot \frac{di_2}{dt}$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont.-9716100000


$$(M_{12} = \frac{N_1 \phi_{21}}{i_2})$$

$$e_1 = -M_{12} \frac{di_2}{dt}$$

Mutual induced emf


If current is flowing in any one of inductor then the sign of self & mutually induced voltage is same

Note!:-

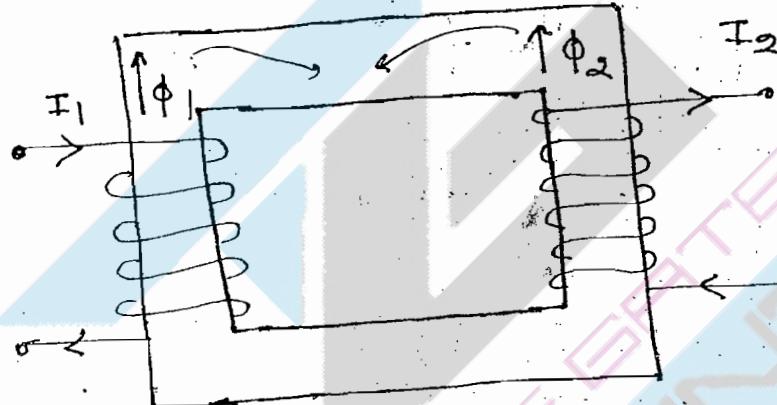


In above figure flux of the two inductors are completely closed path in opposite direction. Hence sign of mutually induced voltage is opposite to sign of self induced voltage


Dot convention:-

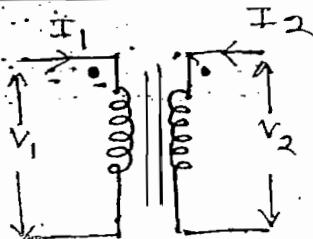

(1)

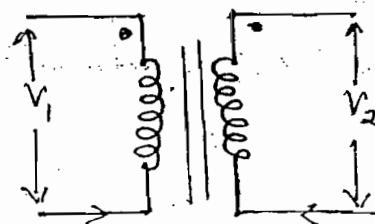

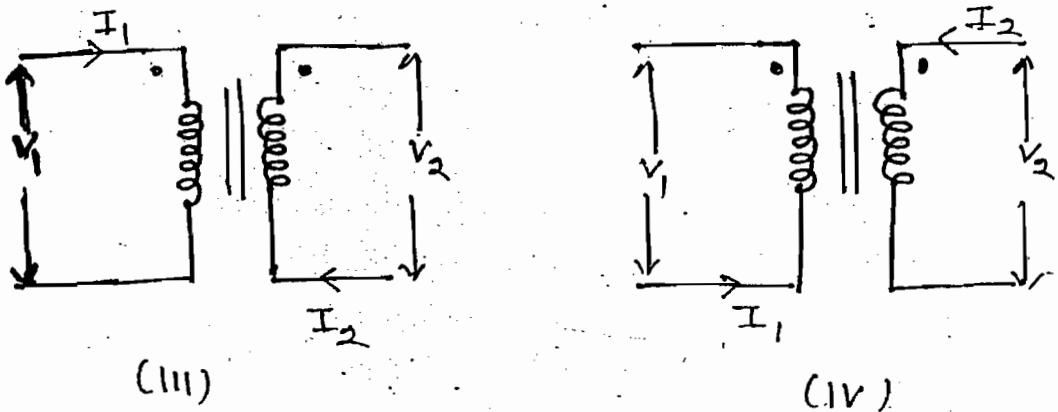Contra (II), i.e.,  $V_1 < 0$ ,  $V_2 > 0$



$$V_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

$$M_{12} = M_{21} = M$$

Valid for (I) & (II)

$$V_2 = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

$$V_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

Valid for (III) & (IV)

$$V_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

### Note:-

→ When either both currents are entering or both are leaving at dotted terminal sign of mutually induced voltage is same as the sign of self induced voltage.


→ When one current is entering and other current is leaving at dotted terminal sign of the mutually induced voltage is opposite to sign of self induced voltage.

### Coefficient of Coupling / Coupling Factor :-

$$K = \frac{\text{Useful flux}}{\text{Total flux}} \rightarrow K_1 = K_2 \rightarrow \text{condition}$$

$$\phi_1 \begin{matrix} \nearrow \\ \searrow \end{matrix} \phi_{12}$$

$$K_1 = \frac{\phi_{12}}{\phi_1}$$

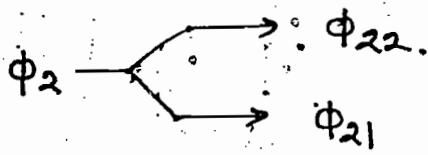

$$k_2 = \frac{\phi_{21}}{\phi_2}$$

$$K = \sqrt{k_1 k_2}$$

For ideal system  $k=1$  and for practical system  
the range of  $K$  is 0 to 1

$$M_{21} = \frac{N_2 \phi_{12}}{i_1}$$

$$M_{12} = \frac{N_1 \phi_{21}}{i_2}$$

$$M_{12} = M_{21} = M$$

$$M^2 = M_{12} M_{21}$$

$$\Rightarrow M^2 = \frac{N_1 \phi_{12}}{i_1} \cdot \frac{N_2 \phi_{12}}{i_1} \quad (1)$$

$$\phi_{12} = k_1 \phi_1 \quad (III)$$

$$\phi_{21} = k_2 \phi_2 \quad (IV)$$

Substitute eq-(III) & (IV) in eq-(1)

$$M^2 = k_1 k_2 \frac{N_1 \phi_1}{i_1} \cdot \frac{N_2 \phi_2}{i_2}$$

$$M^2 = K^2 L_1 L_2$$


$$\Rightarrow M = K \sqrt{L_1 L_2}$$

$$V = L_1 \frac{di}{dt} + M \frac{di}{dt} + L_2 \frac{di}{dt} + M \frac{di}{dt}$$

$$L_{eq} \frac{di}{dt} = (L_1 + L_2 + 2M) \frac{di}{dt}$$


$$L_{eq} = L_1 + L_2 + 2M$$

→ Series Aiding

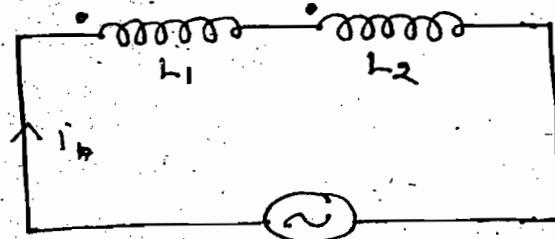


→ Series Opposing:-

$$L_{eq} = L_1 + L_2 - 2M$$

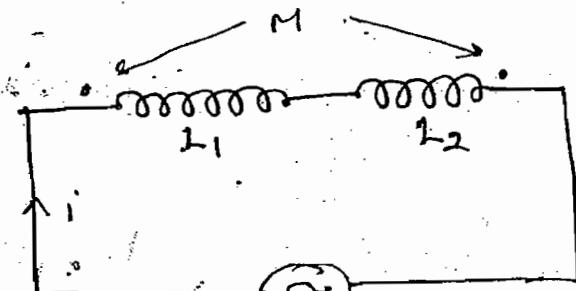


→ Parallel Aiding:-
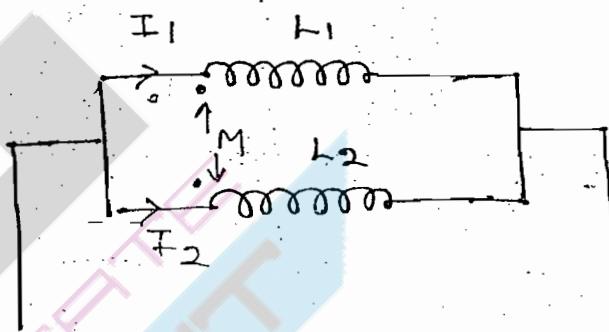
$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$




→ Parallel Opposing:-
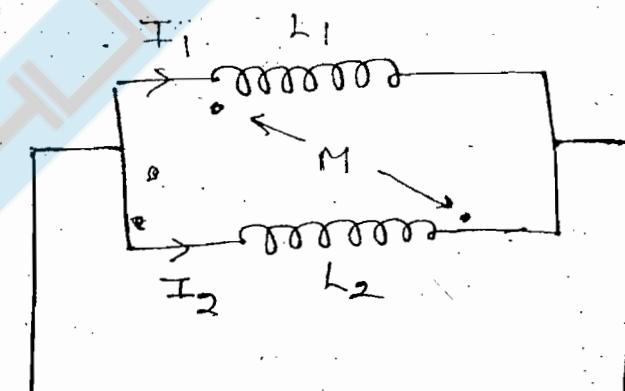
$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$



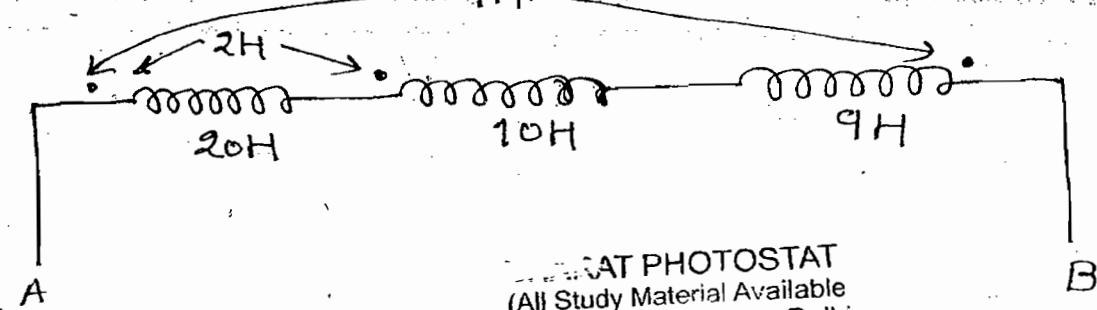
Ques: Find equivalent inductance w.r.t A and B.



Soln:-  $L_{eq} = L_1 + L_2 + L_3 \pm 2M_1 \pm 2M_2 \pm 2M_3$

$$\Rightarrow L_{eq} = 20 + 10 + 9 + 2(2) + 0 - 2(1)$$

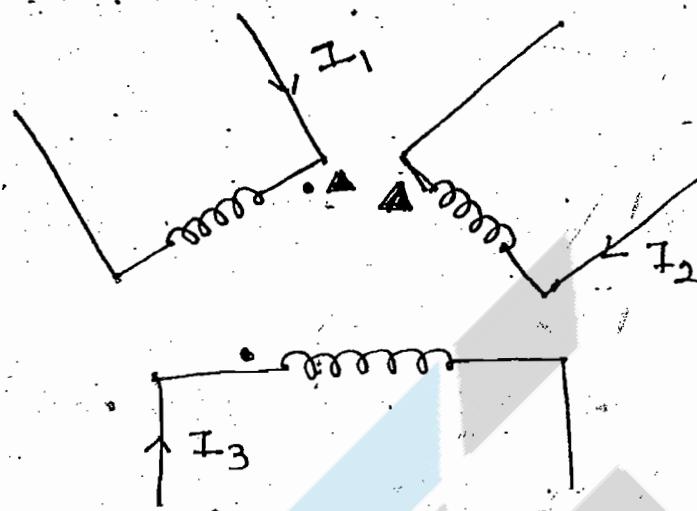ques:- Develop inductance matrix of the figure shown




Soln:- Diagonal points denotes self inductance

$$L = \begin{bmatrix} L_{11} & L_{12} & L_{13} \\ L_{21} & L_{22} & L_{23} \\ L_{31} & L_{32} & L_{33} \end{bmatrix}$$

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Contd.

$$L = \begin{bmatrix} 15 & -2 & 1 \\ -2 & 20 & 0 \\ 1 & 0 & 10 \end{bmatrix}$$

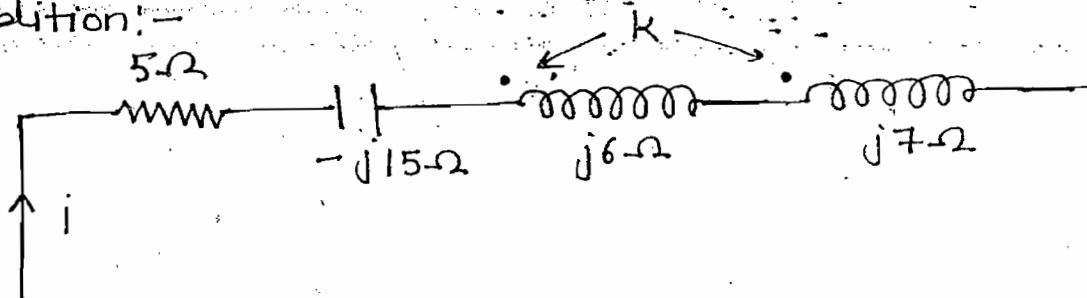ques:- Find the value of  $K$  under resonance condition:-



Soln:-

$$2\pi f \quad (L_{eq} = L_1 + L_2 + 2M)$$

$$M = k \sqrt{L_1 L_2}$$

$$\Rightarrow 2\pi f M = 2\pi f k \sqrt{L_1 L_2}$$

$$X_M = k \sqrt{X_1 X_2}$$



$$X_{eq} = X_1 + X_2 + 2X_M$$

$$\Rightarrow X_{eq} = X_1 + X_2 + 2k \sqrt{X_1 X_2}$$

$$\Rightarrow 15 = 6 + 7 + 2k \sqrt{6 \times 7}$$

$$\Rightarrow k = \frac{1}{\sqrt{42}}$$

Ans

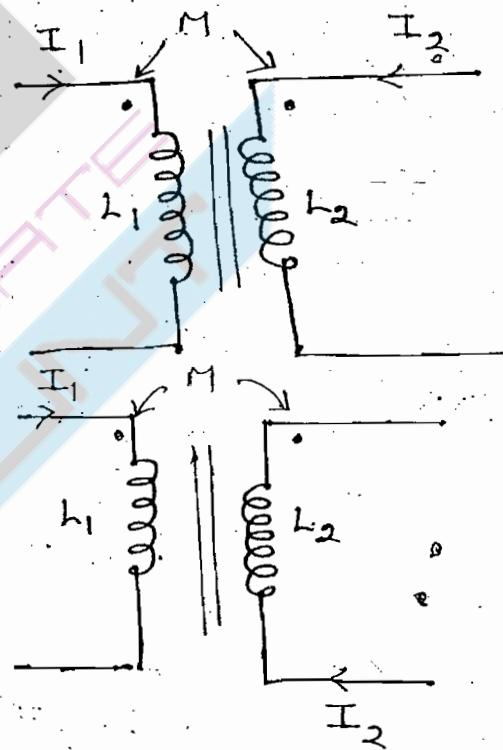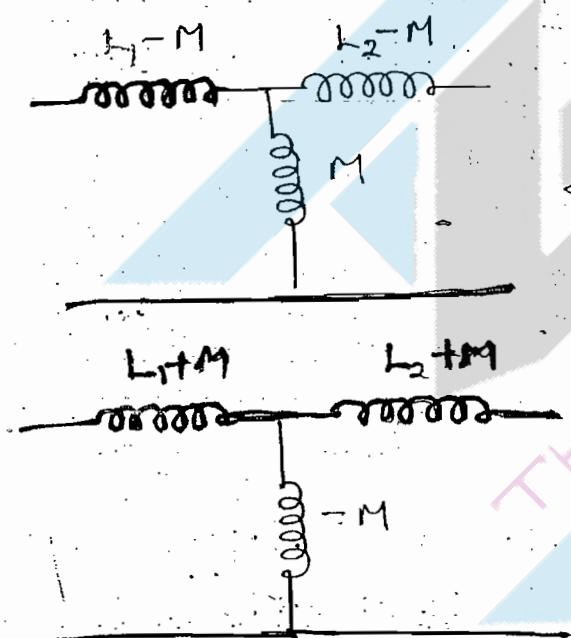


$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 \pm M I_1 I_2$$

+ → fig-(I) -ve → fig(II)

Energy stored in the coupled coils.


DIAFRAGM PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont.-9715220010

Ques:- Find  $L_{eq}$  w.r.t A and B

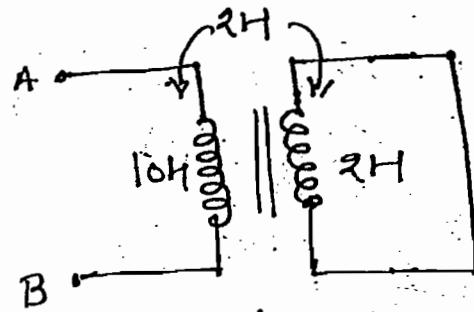


PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont-9)

Soln:-

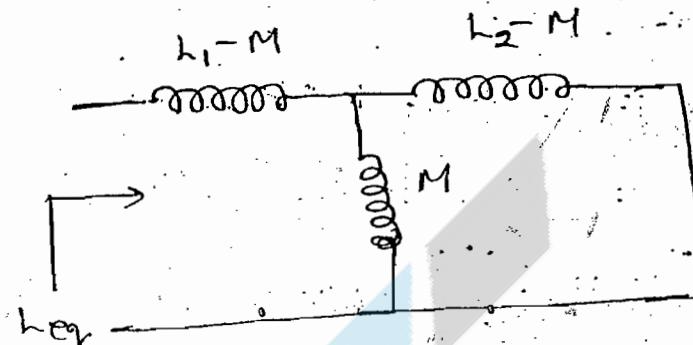
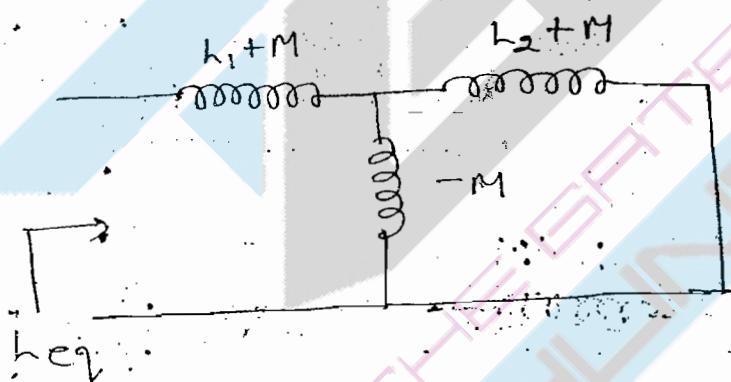
$$L_{eq} = L_1 - M + \frac{M(L_2 - M)}{L_2 - M + M} = L_1 - \frac{M^2}{L_2}$$





$$L_{eq} = (L_1 + M) + (-M)(L_2 + M) / L_2 + M - M$$

$$L_{eq} = L_1 - \frac{M^2}{L_2}$$

$$\Rightarrow L_{eq} = 10 - \frac{2^2}{2} = 8H, \text{ itns}$$

Ans

## Graph Theory :-

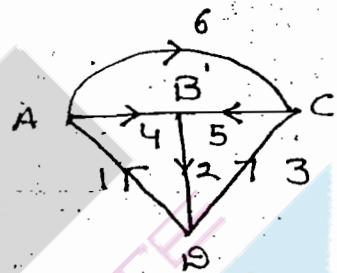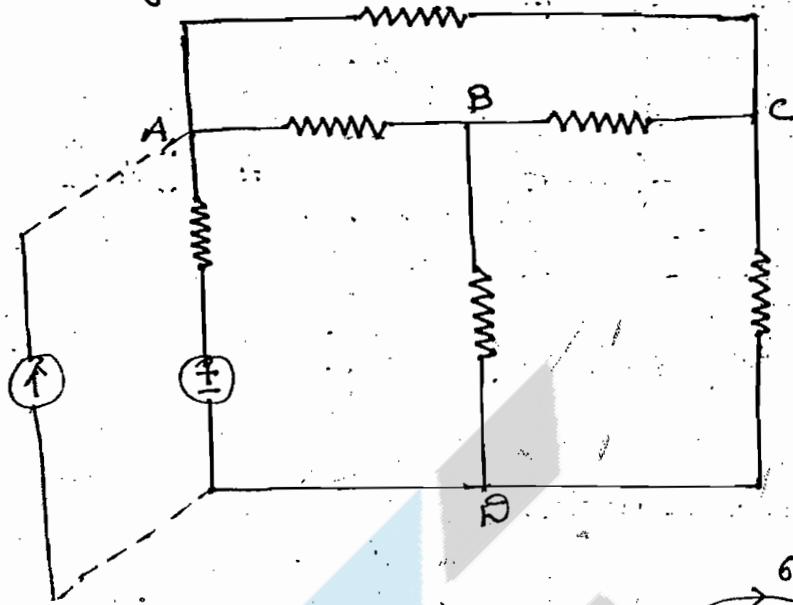

- N/w topology is the study of the N/w properties by investigating interconnection b/w branches and nodes, it mainly concentrate on the geometry of the N/w
- In the N/w topology any N/w is replace by graph. To develop graph of each element is replace by either straight line or arc of the semi-circle, Voltage source is replace by s.c and current source is replace by o.c and graph retains all the nodes of original N/w
- $\text{No. of branches} \geq \text{No. of branch of N/w}$

## Augmented Incidence Matrix :-

	1	2	3	4	5	6
A	-1			+1		+1
B		+1		-1	-1	
C			-1		+1	-1
D	+1	-1	+1			

$$= [A_a]$$

## Reduced Incidence Matrix :-

SURESH PHOTOSTAT  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont: 37155575

	1	2	3	4	5	6
A	-1			+1		+1
B		+1		-1	-1	
C		-1		+1	-1	
D	X	X	X	X	X	X

$$= [A]$$


D → Ref - Node or Datum Node


→ All the information regarding the graph can be represent mathematically in concise form is called as Augmented incidence matrix

→ For a given graph Augmented incidence matrix is unique

Type:-

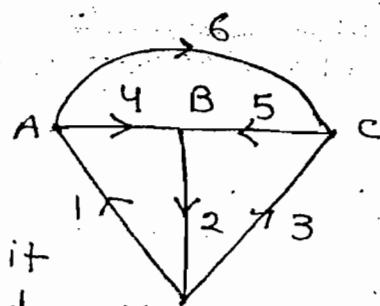→ Tree is a connected sub-graph. It connects the all the nodes of the N/w but it doesn't consist of any closed path



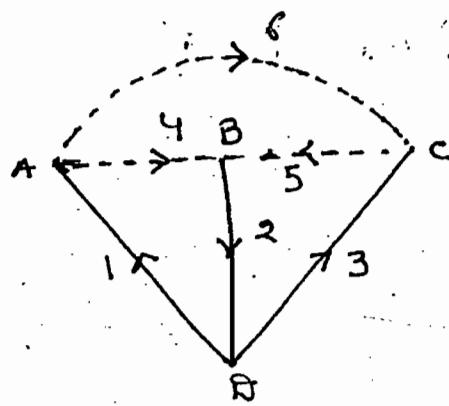

Tree  $\{1, 2, 3\}$

$$\begin{aligned}\text{Total Tree Branches} &= N-1 \\ &= 4-1 = 3\end{aligned}$$

→ The set of branches which are disconnected to form a tree is called as co-tree or complementary tree

Co-Tree  $\{4, 5, 6\}$

→ The branch which form a tree is called as tree branch (twig)

→ Total no. of tree branches =  $N-1$

→ The branch which is disconnected to form a tree is called as link (chord)

→ Total no. of links ( $l$ ) =  $b - (N-1)$

where  $b$  = total no. of branches of the N/w

→ Tree is not unique.



$$\text{Total no. of tree} \approx N^{N-2} = 4^{4-2} = 16$$

$$\rightarrow \text{Total No. of possible tree} \approx N^{N-2}$$

### Notes:-

→ The above formula can be applied

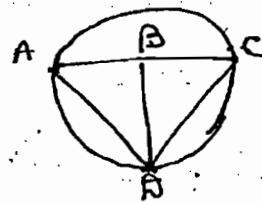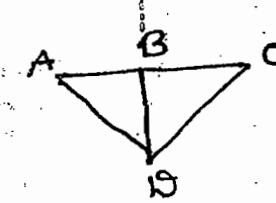- (a) When connection is present b/w all the node
- (b) When no repeated branch is present b/w the node



→ Total no. of possible tree for any graph  
 $= \text{det}(AAT)$

where  $A =$  Reduced incidence matrix

Node Pair Voltages! —


Total no. of node pair voltages  $= \frac{N(N-1)}{2}$

e.g.:  $V_{AB}, V_{AC}, V_{BC}, V_{BS}, V_{CS}$ ,

Edges = Branches

→ Total no. of edges (branches)  $= \frac{N(N-1)}{2} = \frac{4 \times 3}{2} = 6$

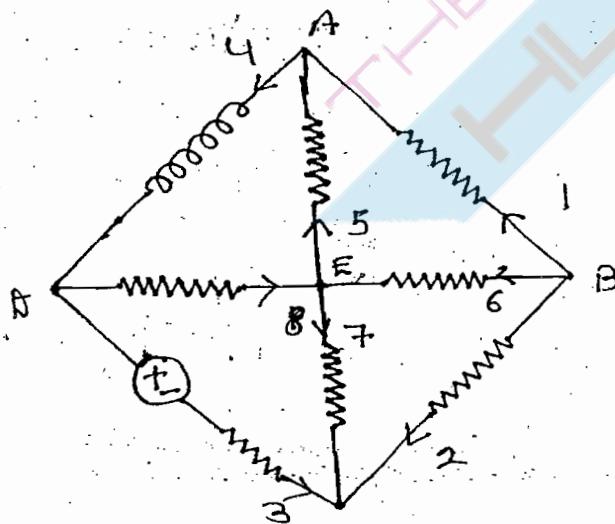
ques! — Develop Tie-set matrix of the N/w shown



PHOTOSTAT  
 (All Study Material Available)  
 A-163 Lado Sarai, New Delhi  
 Cont: 9711111111


Step-1! —

Develop the graph for the given N/w

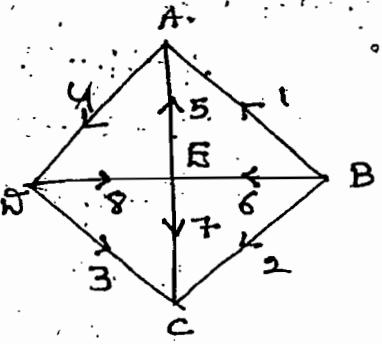

Step-(II):-

Develop a tree for the graph

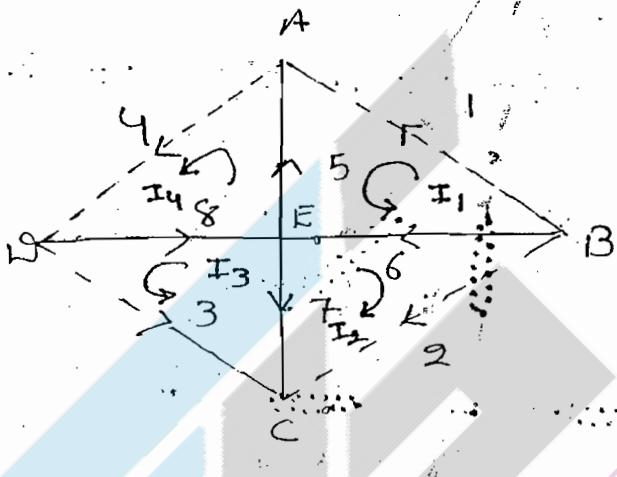

Step-(III):-

Identify total no. of basic loop / fundamental loop (f-loop) or independent loops

- Basic loop should consist of only one link
- Total no. of basic loop = total no. of links

$$\text{i.e. } l = b - (N-1)$$

- Basic loop direction is same as link current direction

	$v_1$	$v_2$	$v_3$	$v_4$	$v_5$	$v_6$	$v_7$	$v_8$	$c_b$
$I_1$	+1				-1	-1	-1		
$I_2$		+1				-1	-1		
$I_3$			+1				-1	-1	
$I_4$				+1	+1				+1

= [C]

KVL Equations:-

$$V_1 - V_5 - V_6 = 0$$


$$V_2 - V_6 - V_7 = 0$$

$$V_3 - V_7 - V_8 = 0$$

$$V_4 + V_5 + V_8 = 0$$

$$\boxed{[C] = [U : C_b]}$$

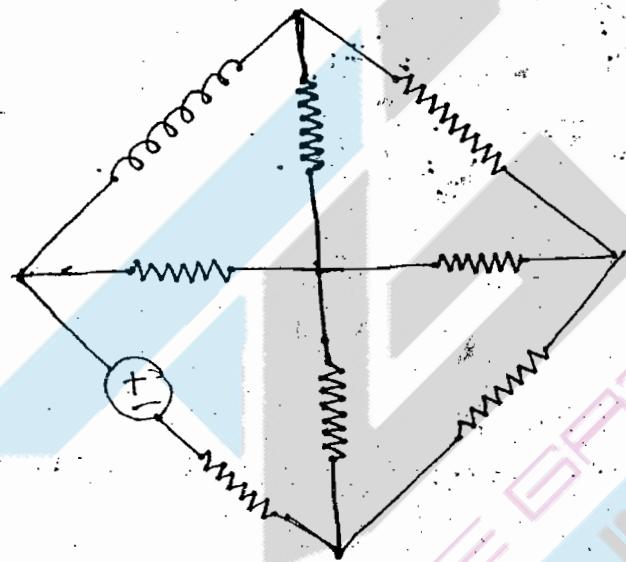
ques:- Develop cut-set matrix of the N/w shown



PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont:-


Step-(I) :-

Develop a graph for the given N/w

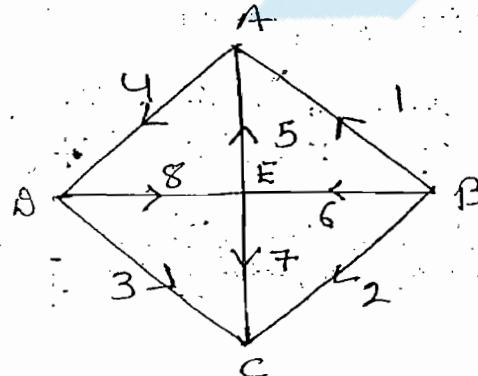

Step-(II) :-

Develop a tree for a graph

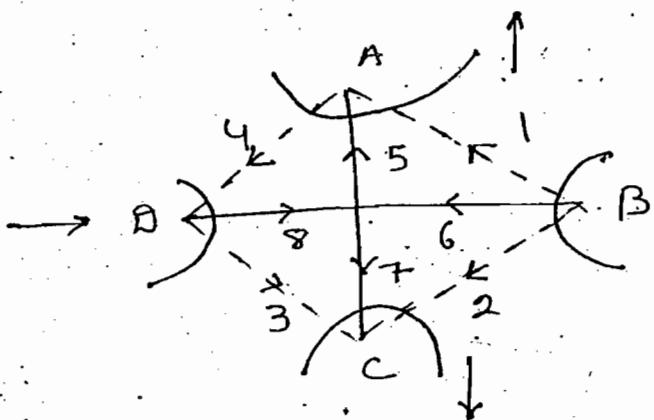

PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Cont. 011-33651070

### Step-(III):—

Identify total no. of basic cut-sets or fundamental cut-sets / f-cut-sets

→ Basic cut-sets should consist of only one tree branch

→ Total No. of basic cut-sets = total No. of tree branches

$$i.e. = N-1$$

→ Basic cut-set direction can be same as a tree branch current direction

	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$	$I_6$	$I_7$	$I_8$
$A$	+1			-1	+1			
$B$	+1	+1				+1		
$C$		+1	+1				+1	
$D$			+1	-1				+1

$$= [B]$$

### KCL Equations:-

$$I_1 - I_4 + I_5 = 0$$

$$I_1 + I_2 + I_6 = 0$$

$$I_2 + I_3 + I_7 = 0$$

$$I_3 - I_4 + I_8 = 0$$

$$[B] = [B_{el}] \cup T$$

$$[C] = [U : C_b]$$

↓  
Tie-set


$$[B] = [B_d : U]$$

↓  
cut-set

$$[C_b] = -[B_d]^T$$

$$[B_d] = -[C_b]^T$$

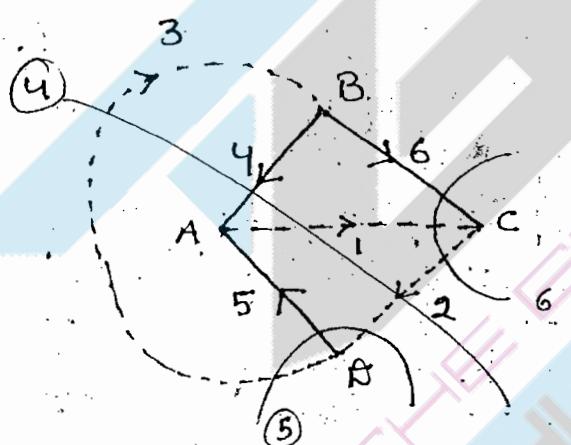ques:- Develop cut-set matrix of the graph shown




PHOTOSTAT  
(All Study Material Available  
A-163 Lado Sarai, New Delhi  
Corr. 51)

Soln:-

	1	2	3	4	5	6
** 4	-1	+1	-1	+1	..	
5	.	-1	+1	.	+1	
6	+1	-1				+1

ques:- Identify total no. of cut-sets of the graph shown

- (a) 3      (b) 4
- (c) 5      (d) 6


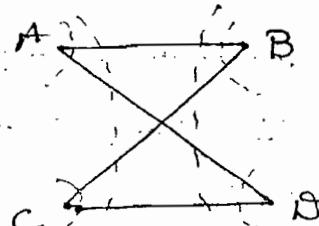


### Note:-

- cut-sets may consist of one tree branch or more than one tree branch
- Basic cut-sets consist of only one tree branch
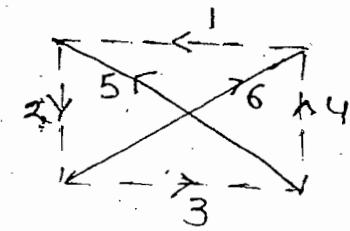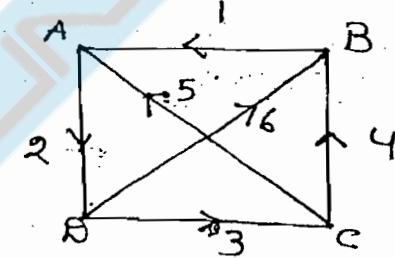
### Conclusion:-

- Total no. of possible tree =  $N^{N-2}$
- Tie-set matrix is not unique, total no. of possible tie-set matrix =  $N^{N-2}$
- cut-set matrix is not unique, Total no. of possible cut-set matrix =  $N^{N-2}$
- Rank of Tie-set matrix = total no. of links  
i.e.  $d = b - (N-1)$
- Rank of cut-set matrix = total no. of tree branches  
 $= N-1$
- Rank of Incidence Matrix =  $N-1$
- The given figure is invalid tree. Since no connection is present b/w tree branches



### Duality:-

$$R \longleftrightarrow G_1$$

$$L \longleftrightarrow C$$

$$V \longleftrightarrow I$$

$$\text{Series} \longleftrightarrow \text{Parallel}$$

$$O.C \longleftrightarrow S.C$$

$$KVL \longleftrightarrow KCL$$

LTHGATE PHOTOSTAT  
 (All Study Material Available  
 A-163 Lado Sarai, New Delhi  
 Cont: 9891111111

Loop  $\longleftrightarrow$  Node  
(Mesh)


Tie-set  $\longleftrightarrow$  Cut-set

Thevenin's  $\longleftrightarrow$  Norton's


Foster-I form  $\longleftrightarrow$  Foster-II form  
(Series)  $\qquad\qquad$  (Parallel)

$$\frac{dV}{dt} \longleftrightarrow \frac{dI}{dt}$$
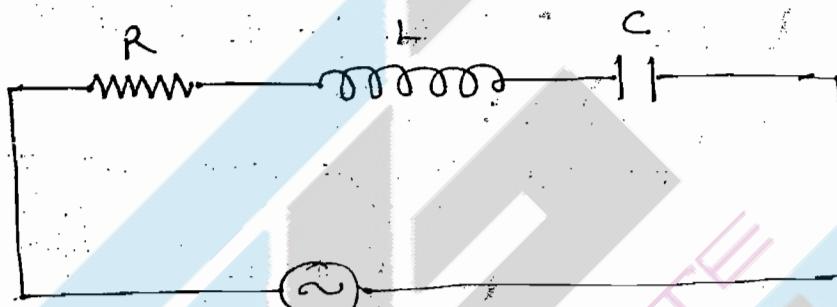
$$\int V dt \longleftrightarrow \int i dt$$



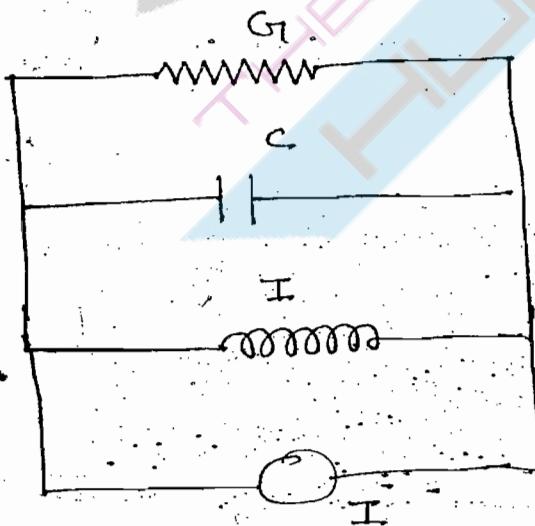
$$V = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt \rightarrow KVL$$



$$I = V G_I + C \frac{dv}{dt} + \frac{1}{L} \int v dt \rightarrow KCL$$


Equality does not mean the equivalence but it means that mathematical representation of both N/w are identical.

Ques:- Develop dual of the N/w shown

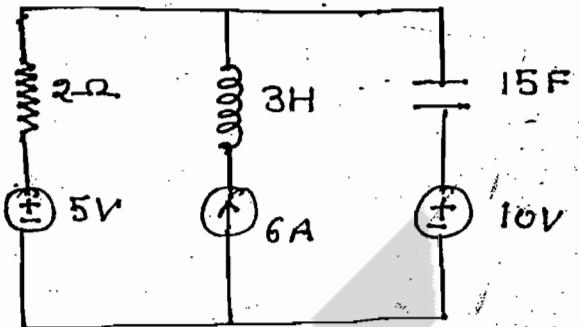

Soln:-

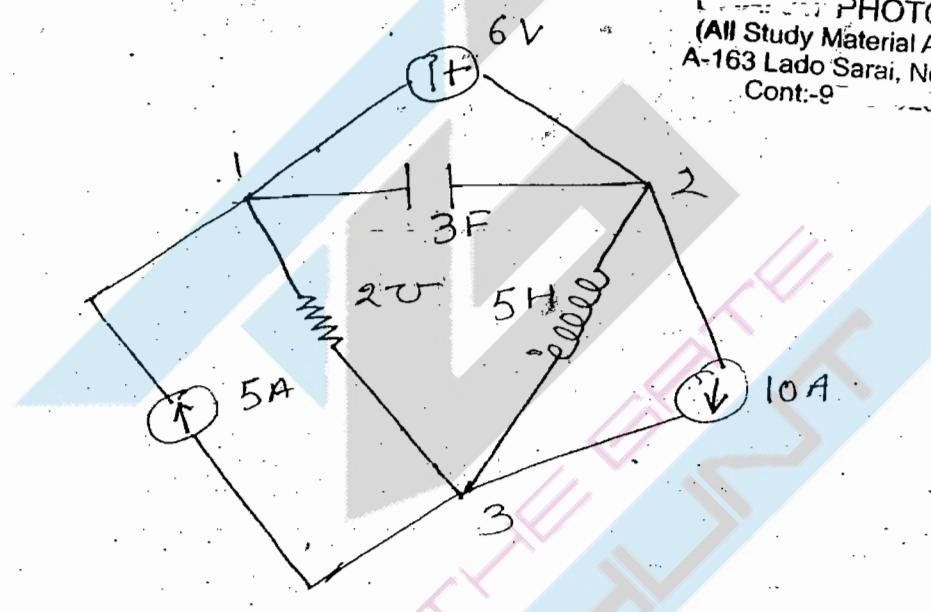PHOTOSTAT  
(All Study Material Available)  
A-163 Lado Sarai, New Delhi  
Cont.-9810000000



Note! -

- When voltage source circulate a current in clockwise direction arrowmark of the current source is indicated towards respective node
- When current source circulate a current in clockwise direction the sign is assign to respective node

PHOTOSTAT - Mob - 9810000000